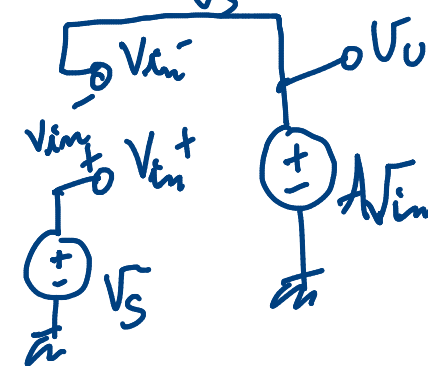



$$A_V = \frac{V_U}{V_{in}}$$



$$V_U = A V_{in}$$

$$V_{in} = V_S - V_U$$


$$V_U = A V_S - A V_U$$

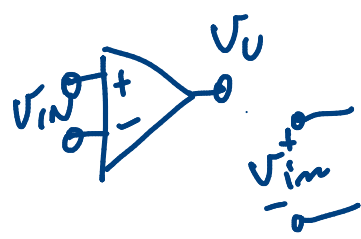


$$V_U = A V_{in} \quad (1+A)V_U = A V_S$$


$$A_V = \frac{V_U}{V_S} = \frac{A}{1+A}$$
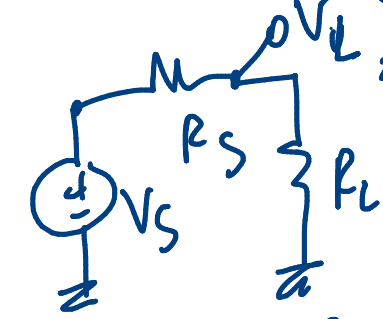
$$A \rightarrow +\infty \Rightarrow A_V \rightarrow 1$$




$$V_L = \frac{R_L}{R_L + R_S} V_S$$

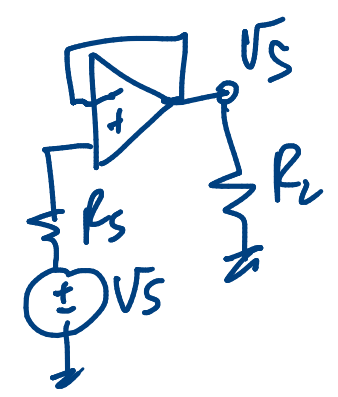

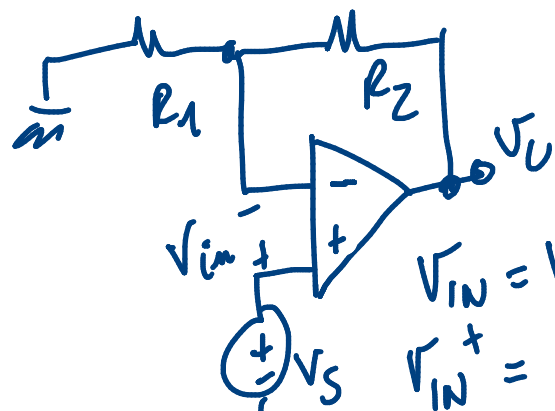

$$V_{IN} = V_{IN}^+ - V_{IN}^-$$

$$V_{IN}^+ = V_S$$

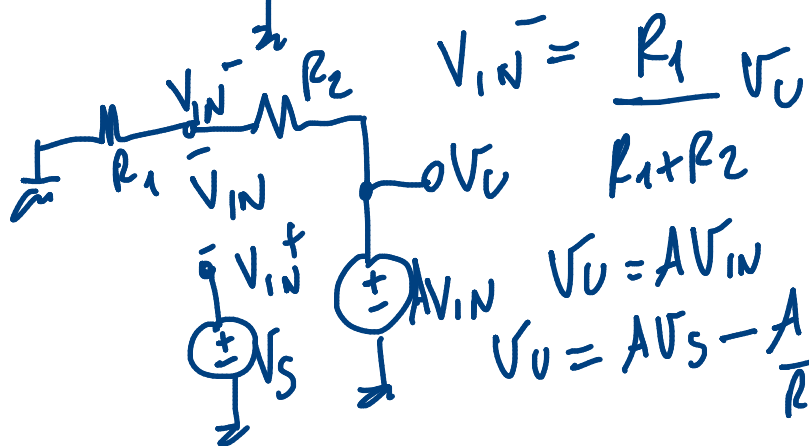


$$V_{IN}^- = \frac{R_1}{R_1 + R_2} V_O$$

$$V_O = AV_{IN}$$

$$V_O = AV_S - \frac{AR_1}{R_1 + R_2} V_O$$

$$V_O \left[1 + \frac{AR_1}{R_1 + R_2} \right] = AV_S \quad A_V = \frac{V_O}{V_S} = \frac{A}{1 + \frac{AR_1}{R_1 + R_2}}$$
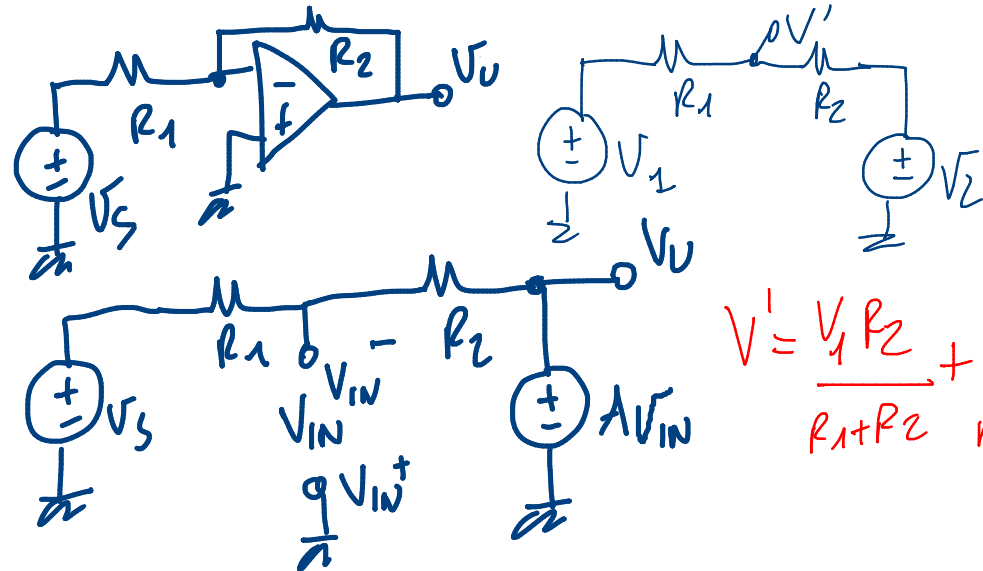
$$A \rightarrow +\infty \quad A_V \rightarrow \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$



$$V' = \frac{V_1 R_2}{R_1 + R_2} + \frac{V_2 R_1}{R_1 + R_2}$$


$$V_U = A V_{IN} \quad V_{IN} = V_{IN}^+ - V_{IN}^-$$


$$V_{IN}^+ = 0 \quad V_{IN}^- = V_S \frac{R_2}{R_1 + R_2} + V_U \frac{R_1}{R_1 + R_2}$$

$$V_U = -A \left[\frac{V_S R_2}{R_1 + R_2} + \frac{V_U R_1}{R_1 + R_2} \right]$$

$$V_U \left[1 + \frac{A R_1}{R_1 + R_2} \right] = - \frac{A R_2}{R_1 + R_2} V_S$$
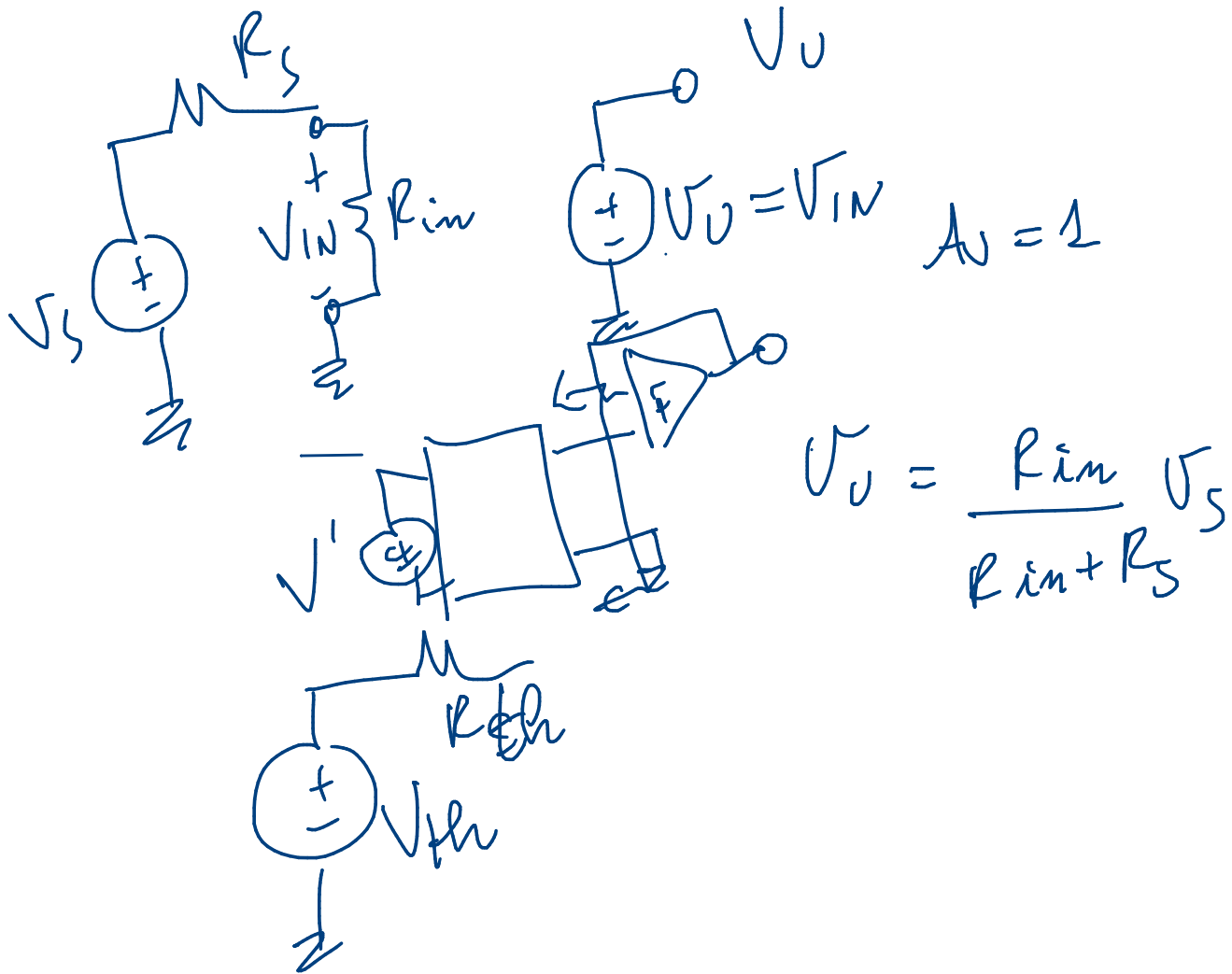
$$A \frac{V_U}{V_S} = - \frac{A R_2}{R_1 + R_2} \cdot \left[1 + \frac{A R_1}{R_1 + R_2} \right]^{-1} \xrightarrow{A \rightarrow \infty} A_U \rightarrow - \frac{R_2}{R_1}$$



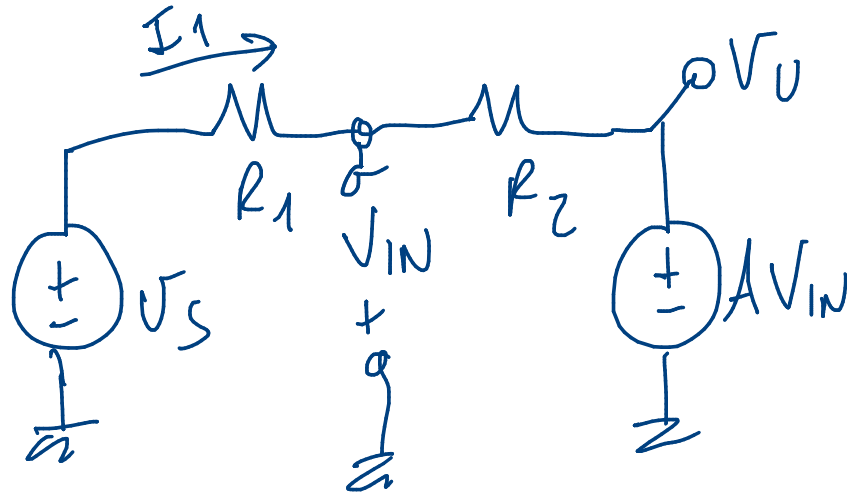


$$V_U = -\frac{R_2}{R_1} V_S$$

$$R_{IN} = \frac{V_S}{I_1}$$

$$I_1 = \frac{V_S - V_U}{R_1 + R_2}$$

$$I_1 = \frac{V_S + \frac{R_2}{R_1} V_S}{R_1 + R_2} = \frac{\frac{R_1 + R_2}{R_1} V_S}{R_1 + R_2} \Rightarrow I_1 = \frac{V_S}{R_1}$$

$R_{IN} = R_1$

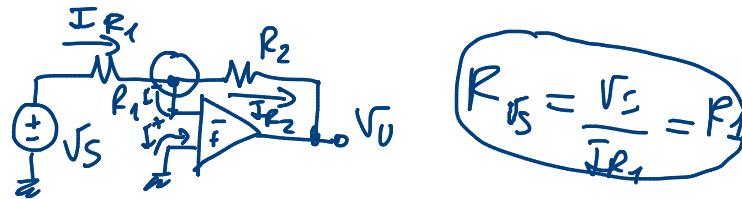



Reitl CV: $V_{IN}^+ \approx V_{IN}^- \wedge I^+ \approx 0 ; I^- \approx 0$

$$I_{R1} = \frac{V_S}{R_1} \quad I_{R2} = I_{R1} - I^- \approx I_{R1}$$

$$V_U = -R_2 I_{R2}$$

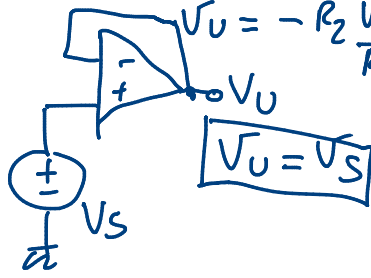
$$V_U = -R_2 \frac{V_S}{R_1} \quad A_V = \frac{V_U}{V_S} = -\frac{R_2}{R_1}$$



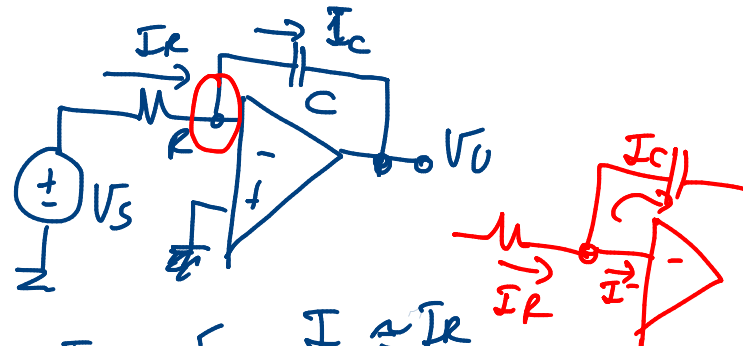

$$I_R = \frac{V_S}{R}$$


$$I_C \approx I_R$$

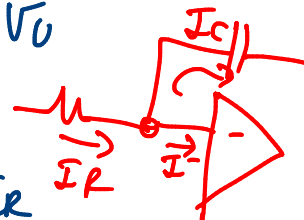


$$I_C = I_R - I^-$$

$$V_U = -\frac{1}{C} \int i_C(t) dt \quad I^- \approx 0 \quad I_C \approx I_R$$

$$V_U = -\frac{1}{RC} \int V_S(t) dt$$

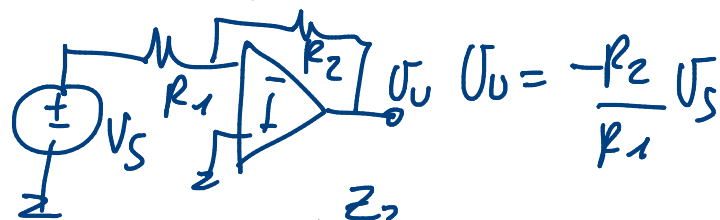


$$V_U = -\frac{R_2}{R_1} V_S$$

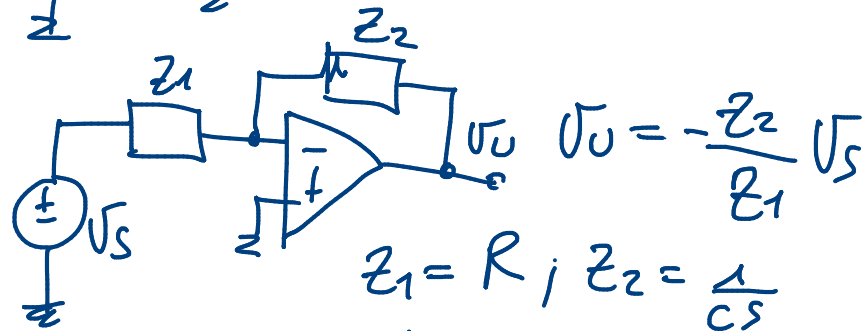

$$V_U = -\frac{Z_2}{Z_1} V_S$$


$$Z_1 = R, \quad Z_2 = \frac{1}{Cs}$$

$$V_U = -\frac{1}{RCs} V_S$$

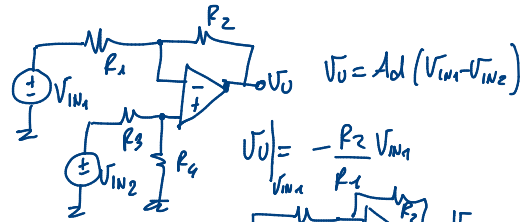

$$V_U = Ad(V_{IN1} - V_{IN2})$$

$$V_U = -\frac{R_2}{R_1} V_{IN1}$$

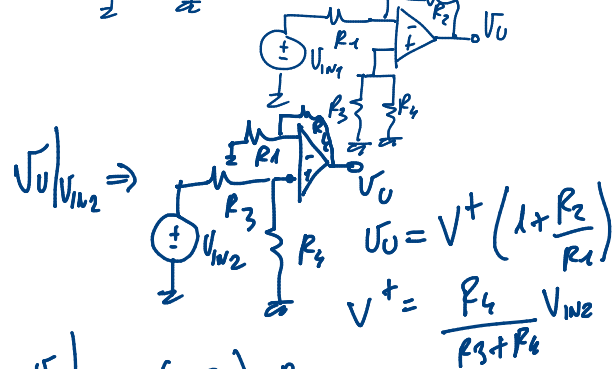

$$V_U = V^+ \left(1 + \frac{R_2}{R_1}\right)$$

$$V^+ = \frac{R_4}{R_3 + R_4} V_{IN2}$$

$$V_U |_{V_{IN1}} = \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3 + R_4} V_{IN2}$$

$$V_U = -\frac{R_2}{R_1} V_{IN1} + \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3 + R_4} V_{IN2} =$$

$$= -\frac{R_2}{R_1} V_{IN1} + \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3} V_{IN2}$$

$$\text{Se } \frac{R_2}{R_1} = \frac{R_4}{R_3} \Rightarrow$$

$$V_U = -\frac{R_2}{R_1} V_{IN1} + \frac{R_4}{R_3} V_{IN2} = -\frac{R_2}{R_1} (V_{IN1} - V_{IN2})$$

$$V_U = Ad(V_{IN1} - V_{IN2})$$

$$Ad = -\frac{R_2}{R_1}$$