

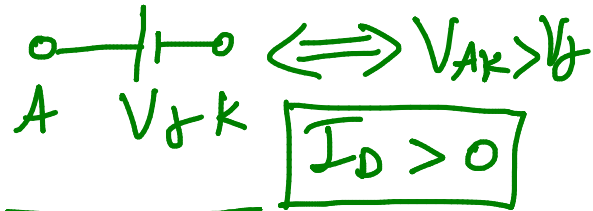
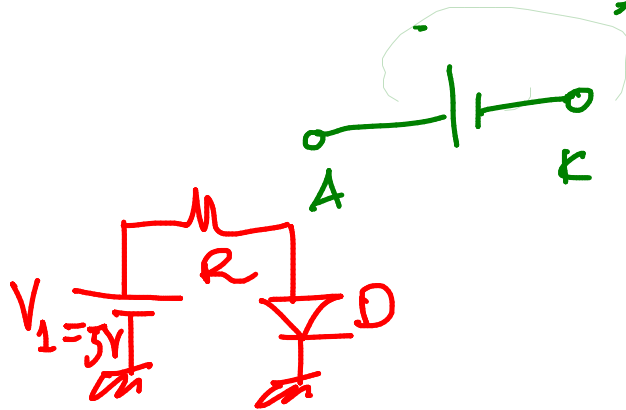



D : ON \Rightarrow



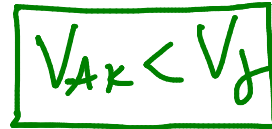


OFF \Rightarrow

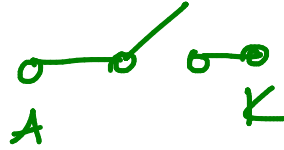


D : OFF:



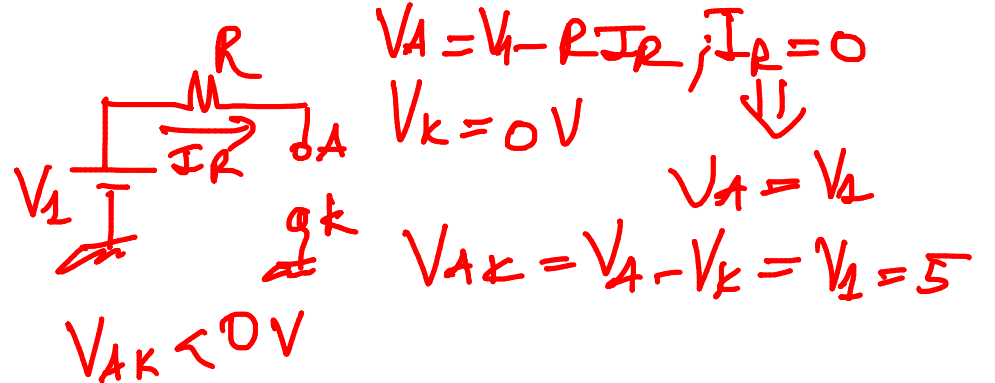


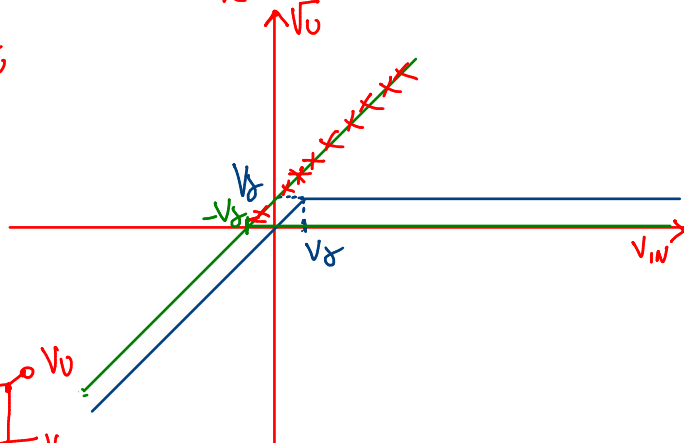
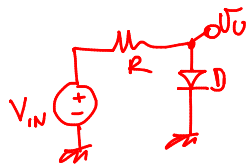
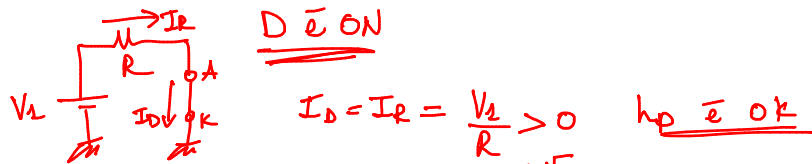


$V_{IN} \gg 1$

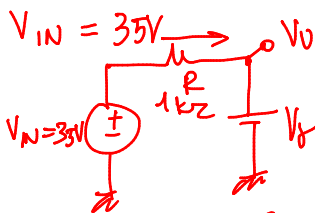

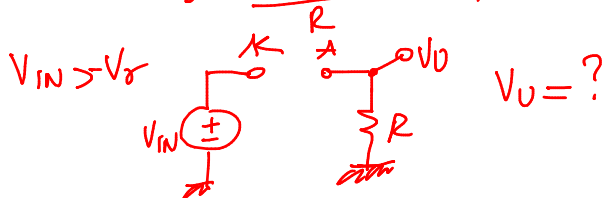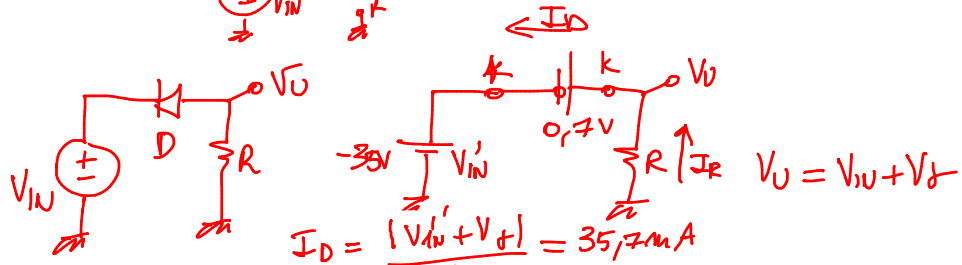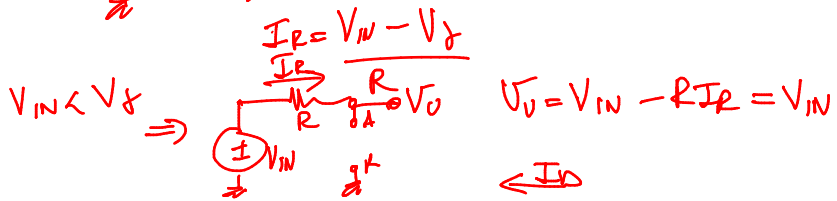$I_R > 0 \Rightarrow V_O = V_D \quad V_{IN} > V_D \Rightarrow D: ON$



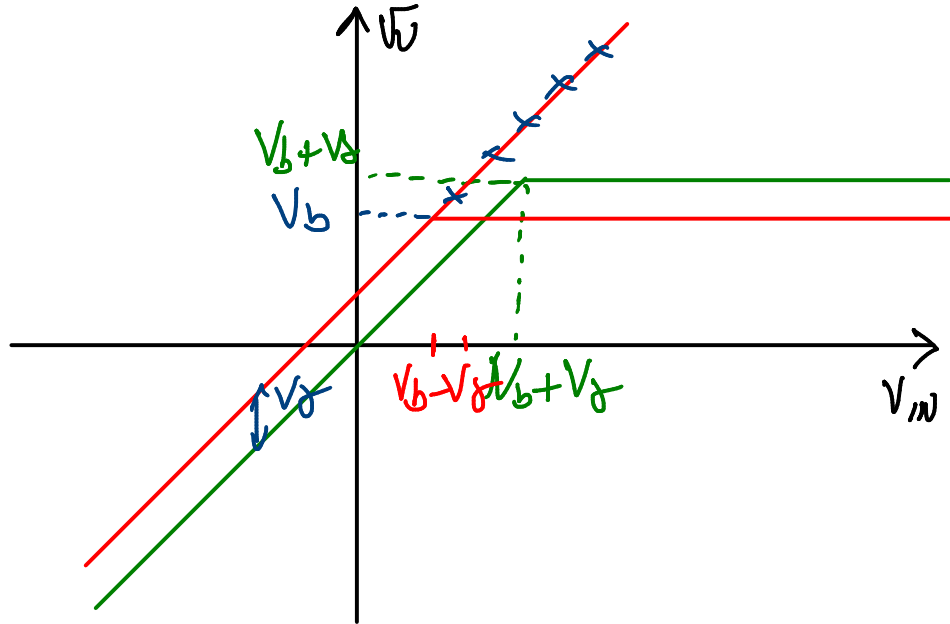
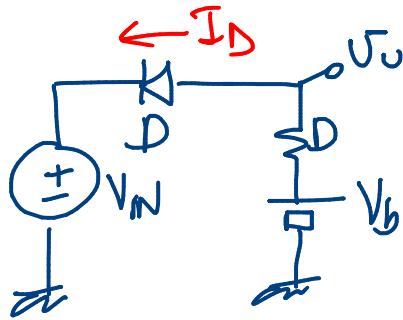
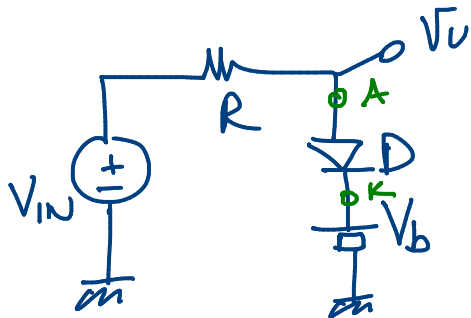






$$V_U = V_{IN} + V_s$$


$$I_D = \frac{V_b - V_s - V_{IN}}{R} > 0$$

$$V_{IN} = V_b - V_s$$


Tagliatori in basso

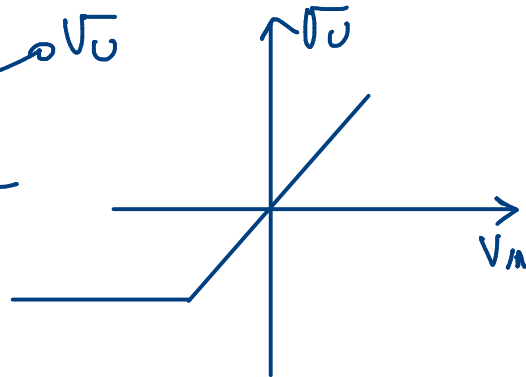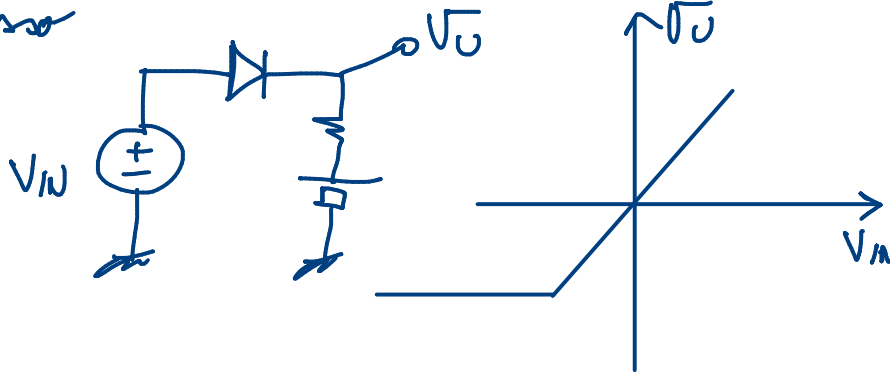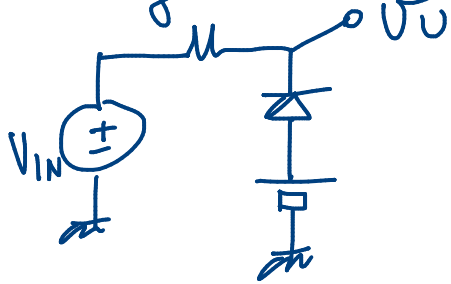

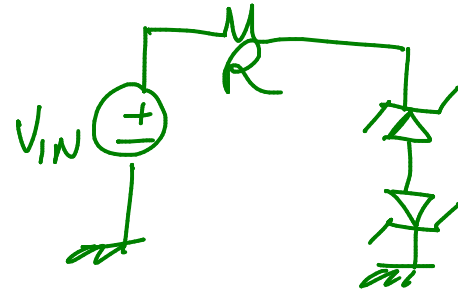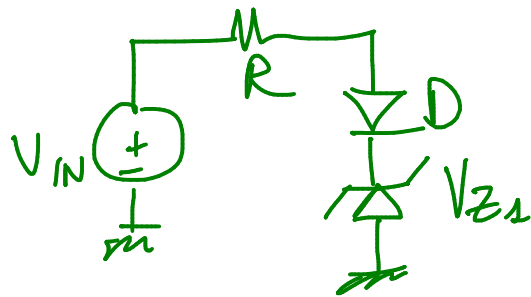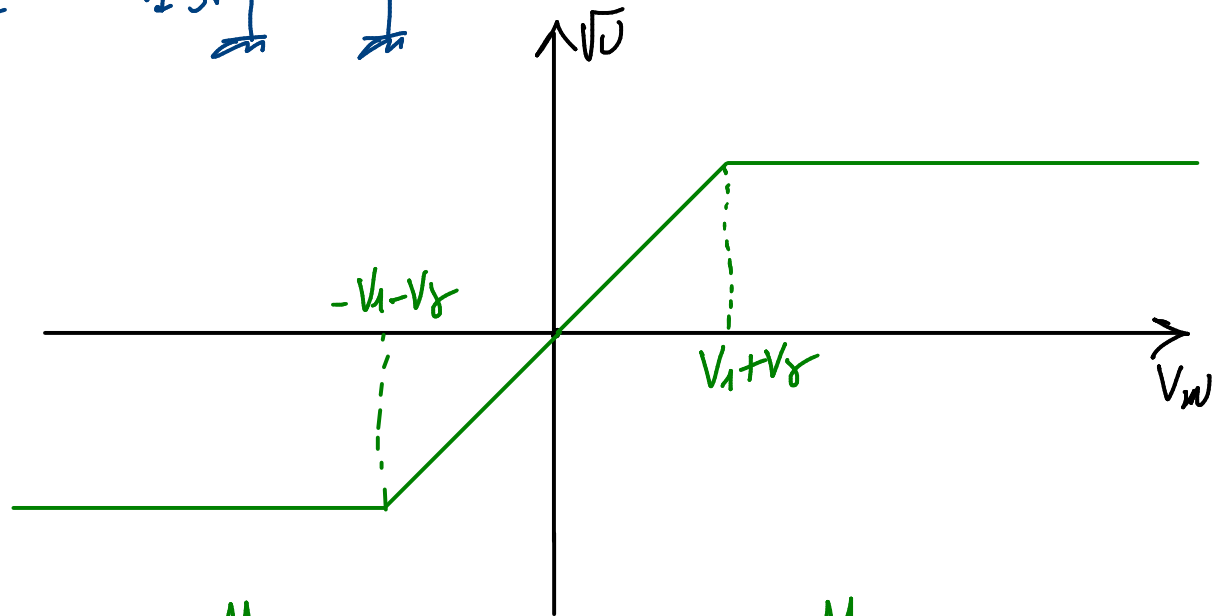
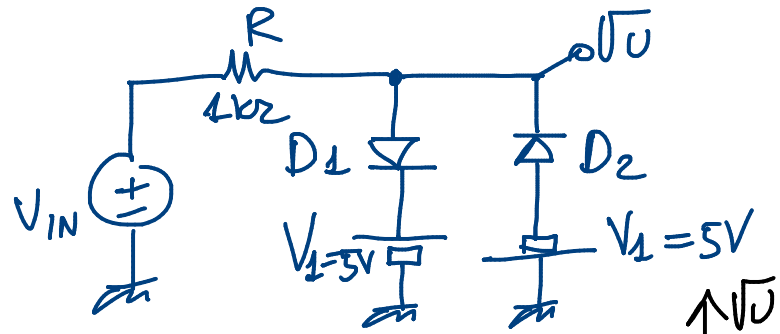


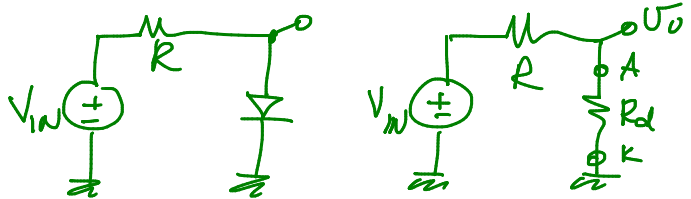

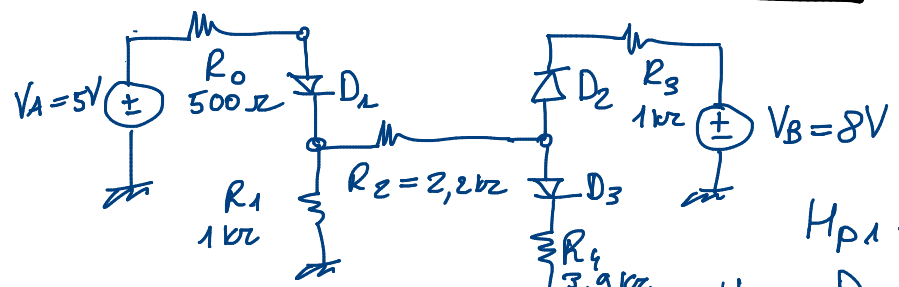$U_0 \neq 0 \quad U_0 = \frac{R_d}{R+R_d} V_{IN}$



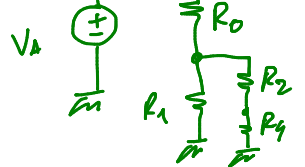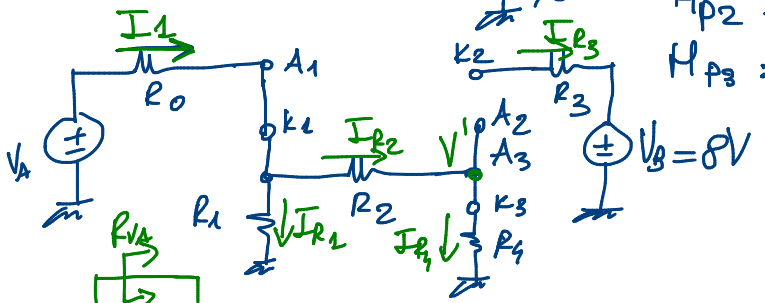- M_{P1}: D₂ OFF
- M_{P2}: D₁ ON
- M_{P3}: D₃ ON




$R_{VA} = R_0 + R_1 \parallel (R_2 + R_4)$
 $R_p = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$

$R_1 \parallel R_2 \parallel R_3 = (R_1 \parallel R_2) \parallel R_3 = R_1 \parallel (R_2 \parallel R_3)$

$$I_2 = \frac{V_A}{R_{VA}} = \frac{V_A}{R_0 + R_1 \parallel (R_2 + R_4)} = \underline{\underline{3,68 \text{ mA}}}$$

Verifica Hp2

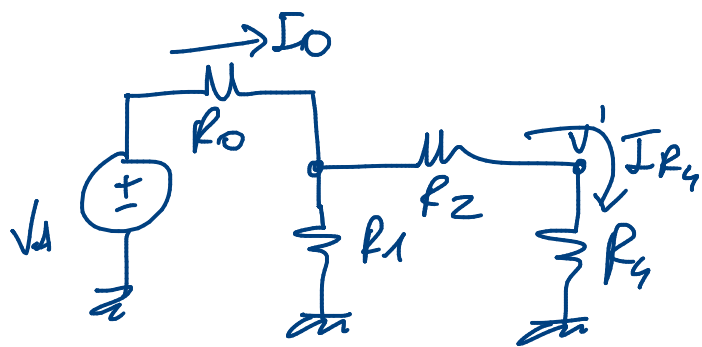

$$I_{R_4} = ?$$

$$I_{R_4} = \frac{I_0 R_1}{R_1 + R_2 + R_4} = \underline{\underline{0,518 \text{ mA}}}$$


Verifica Hp3

$$V' = R_4 I_{R_4} = 2,02 \text{ V} = V_{A2}$$

$$V_{K2} = V_B = 8 \text{ V}$$

$$V_{AK2} = V_{A2} - V_{K2} = \underline{\underline{-5,98 \text{ V}}}$$

Verifica Hp2

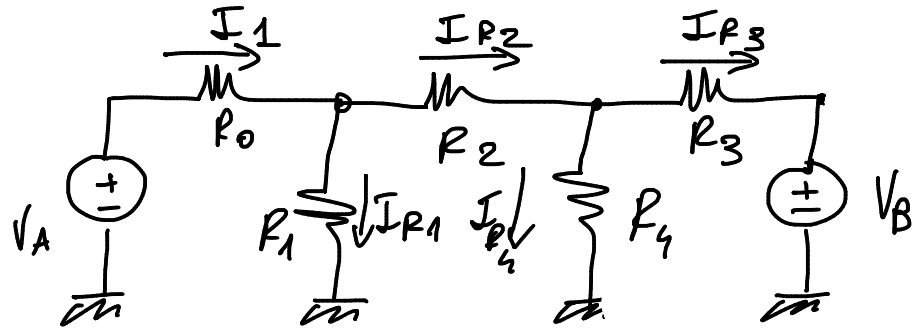

$H_p: D_1 \wedge D_2 \wedge D_3$ ON

Disattivo B

$$I_1^{(A)} = \frac{V_A}{R_{VA}} ;$$

$$R_{VA} = R_0 + R_1 \parallel [R_2 + R_3 \parallel R_4] = 1,25 \text{ k}\Omega$$

$$I_1^{(A)} \approx 4 \text{ mA} ; I_{R2}^{(A)} = \frac{I_1^{(A)} R_1}{R_1 + R_2 + R_3 \parallel R_4} \approx 1 \text{ mA}$$


$$I_{R3}^{(A)} = \frac{I_{R2}^{(A)} R_4}{R_4 + R_3} = 0,797 \text{ mA}$$

$$I_{R4}^{(A)} = \frac{I_{R2}^{(A)} R_3}{R_3 + R_4} = 0,203 \text{ mA}$$

Disattivato A

$$I_{R_3}^{(B)} = - \frac{V_B}{R_{VB}}$$

$$R_{VB} = ?$$

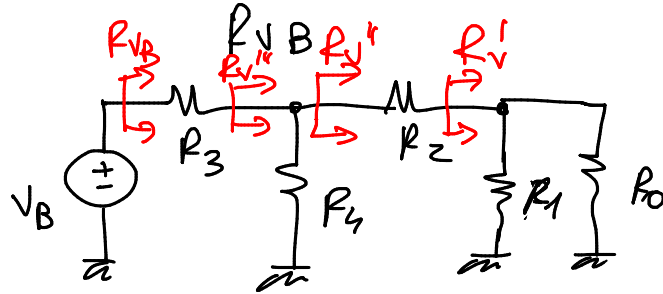

$$R_V' = R_1 \parallel R_0$$

$$R_V'' = R_2 + R_V'$$

$$R_V''' = R_4 \parallel R_V''$$

$$R_{VB} = R_3 + R_V'''$$

$$R_{VB} = R_3 + R_4 \parallel [R_2 + R_1 \parallel R_0] = 2,54 \text{ k}\Omega$$

$$I_{R_3}^{(B)} \approx - 3,15 \text{ mA}$$

$$I_{R_2}^{(B)} = I_{R_3}^{(B)} \frac{R_4}{R_4 + R_2 + R_1 \parallel R_0} \approx - 1,913 \text{ mA}$$

$$I_{R_4}^{(B)} = I_{R_2}^{(B)} - I_{R_3}^{(B)} = 1,2423 \text{ mA}$$

$$I_1^{(B)} = I_{R_2}^{(B)} \frac{R_1}{R_1 + R_0} = - 1,27503 \text{ mA}$$

$$I_1 = I_{D1} = I_1^{(A)} + I_1^{(B)} = 2,7258 \text{ mA} \quad \underline{\underline{D_1 \bar{e} ON}}$$

$$I_2 = I_{R_3} = I_{R_3}^{(A)} + I_{R_3}^{(B)} = - 2,3580 \text{ mA} \quad \underline{\underline{D_2 \bar{e} OFF}}$$

$$I_3 = I_{R_4} = I_{R_4}^{(A)} + I_{R_4}^{(B)} = 1,4466 \text{ mA} \quad \underline{\underline{D_3 \bar{e} ON}}$$