

$$v_U(t) = \bar{v}_U + v_U(t) = \bar{v}_U + r(t)$$


$$\bar{v}_U = \frac{1}{T} \int_0^T v_U(t) dt$$

$$v_{Ueff} = \sqrt{\frac{1}{T} \int_0^T v_U^2(t) dt}$$

$$v_{Ueff}^2 = \frac{1}{T} \int_0^T [\bar{v}_U + r(t)]^2 dt = \bar{v}_U^2 + \frac{1}{T} \int_0^T r^2(t) dt = \bar{v}_U^2 + R_{eff}^2$$

$$RF = \frac{R_{eff}}{\bar{v}_U} = \frac{\sqrt{v_{Ueff}^2 - \bar{v}_U^2}}{\bar{v}_U}$$
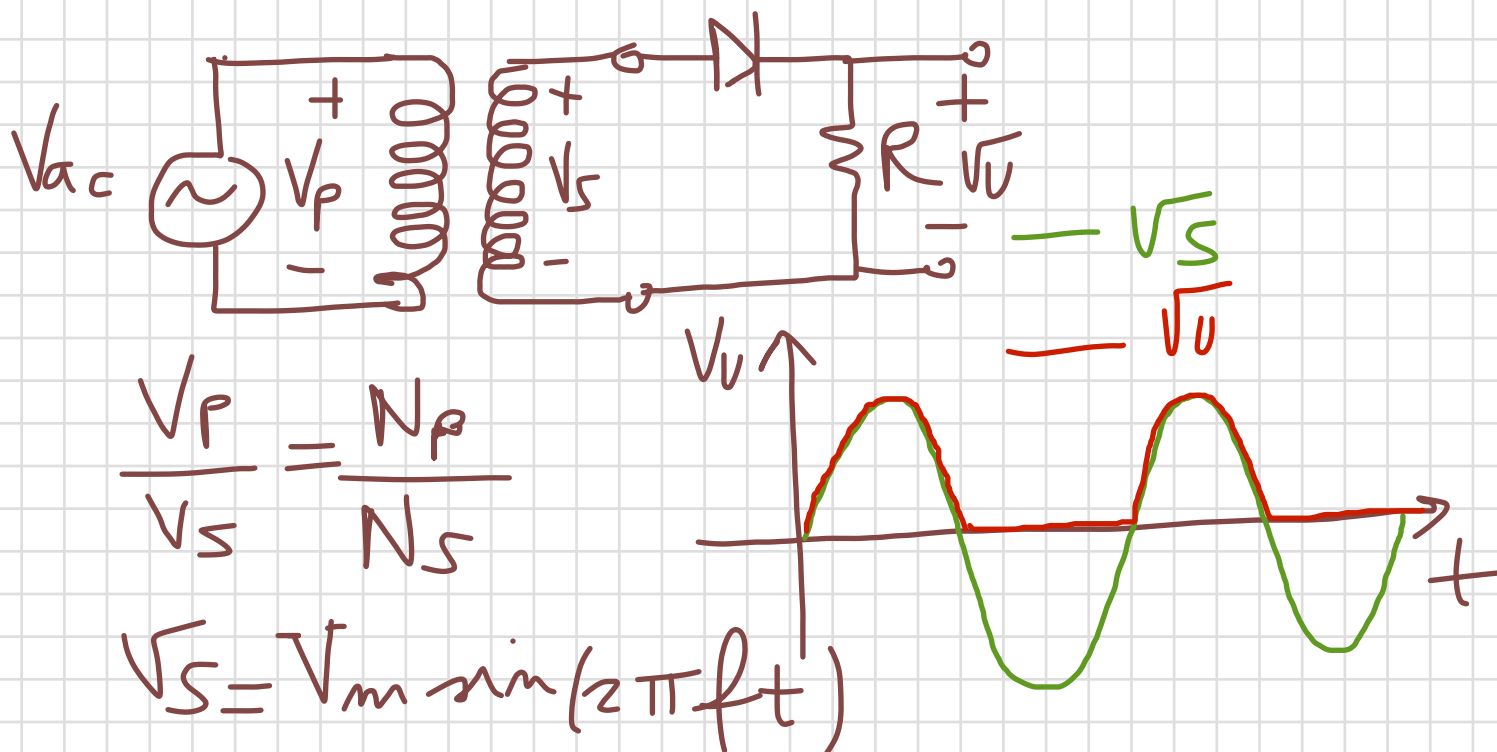
$$\eta_R = \frac{\frac{v_U^2}{R}}{\frac{v_{Ueff}^2}{R}} = \frac{v_U^2}{v_{Ueff}^2}$$



$$\frac{v_p}{v_s} = \frac{N_p}{N_s}$$

$$v_s = v_m \sin(2\pi ft)$$

$$V_U = \frac{V_m}{T} \int_0^{\frac{T}{2}} \sin(\omega t) dt = \frac{V_m}{\pi} = 0,32 V_m$$

$$V_{\text{eff}} = \sqrt{V_m \sqrt{\frac{1}{T} \int_0^{\frac{T}{2}} \sin^2(\omega t) dt}} =$$



$$= \sqrt{V_m \sqrt{\frac{1}{2T} \int_0^{\frac{T}{2}} [1 - \cos(2\omega t)] dt}} =$$

$$= \frac{V_m}{2}$$

$$\omega = 2\pi f$$

$$RF = \frac{\sqrt{V_{\text{eff}}^2 - V_U^2}}{V_U} = \sqrt{\frac{\pi^2}{4} - 1} = 1,211$$
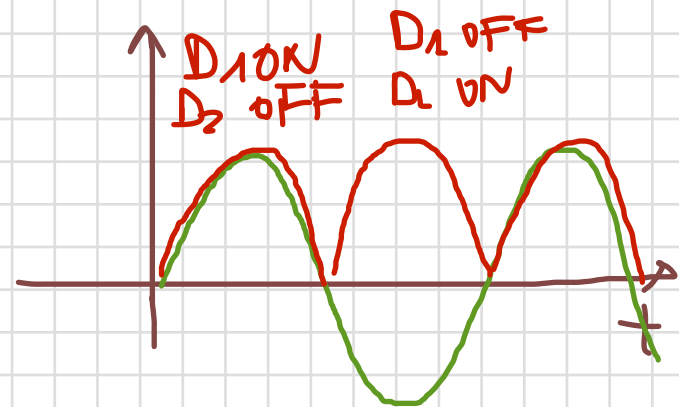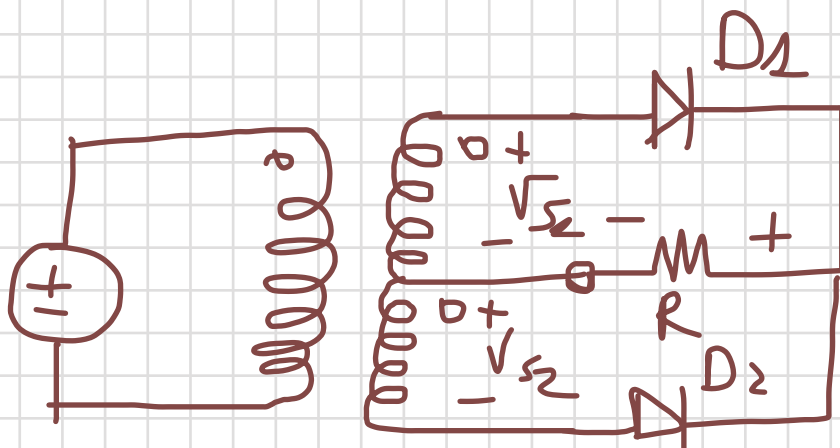
$$\eta_R = \frac{V_U^2}{V_{\text{eff}}^2} = \frac{4}{\pi^2} = 0,4053$$




$$V_s = V_m \sin(\omega t)$$

$$V_U = V_m |\sin(\omega t)|$$

$$V_U = 0,637 V_m ; V_{eff} = 0,7101 V_m = \frac{V_m}{\sqrt{2}}$$



$$RF = 0,4834 ; \eta_R = \frac{8}{\pi^2} = 0,8106$$

PANTE DI GRABETZ

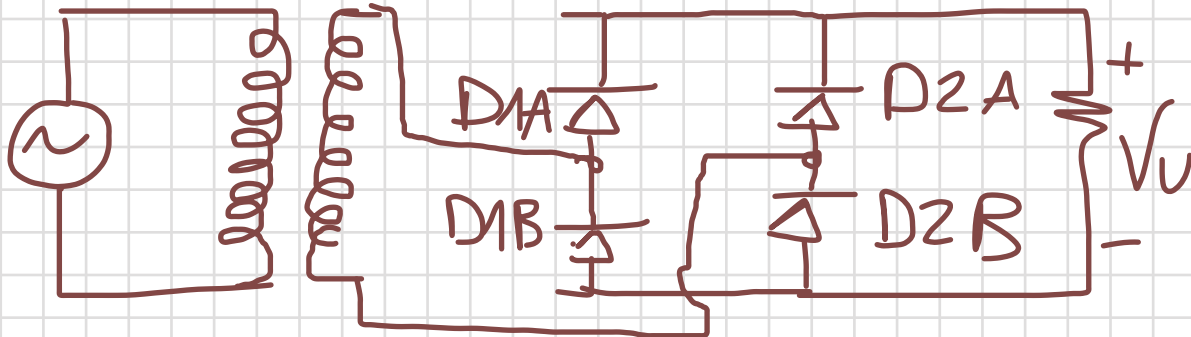

$$V_U = V_m |\sin(\omega t)|$$

Raddrizzatore esafase

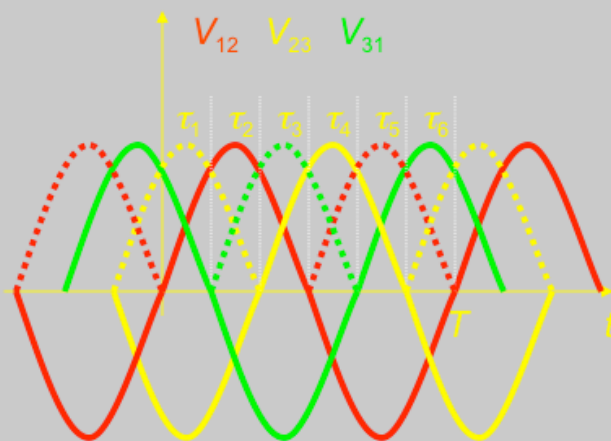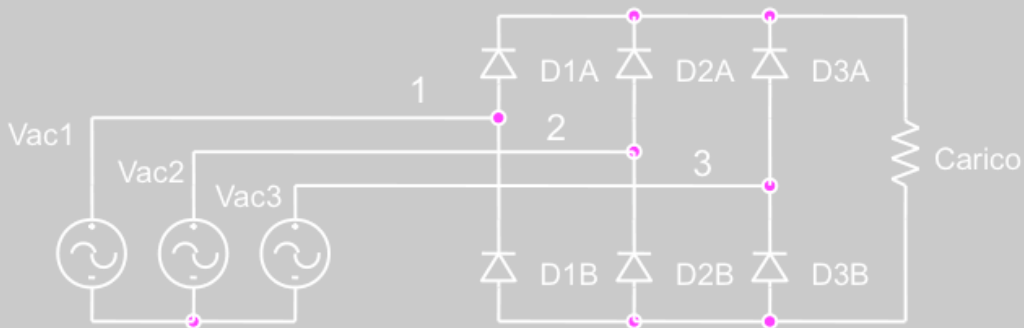

τ_1	D3A, D2B
τ_2	D1A, D2B
τ_3	D1A, D3B
τ_4	D2A, D3B
τ_5	D2A, D1B
τ_6	D3A, D1B



$$V_u = \frac{6V_M}{T} \int_{\frac{2T}{12}}^{\frac{4T}{12}} \sin(\omega t) dt = \frac{3V_M}{\pi} \left(\cos\left(\frac{\pi}{3}\right) - \cos\left(\frac{2\pi}{3}\right) \right) = \frac{3V_M}{\pi} = 0.9549 \cdot V_M$$

$$V_{Ueff} = V_M \sqrt{\frac{6}{T} \int_{\frac{2T}{12}}^{\frac{4T}{12}} \sin^2(\omega t) dt} = V_M \sqrt{\frac{3}{T} \int_{\frac{2T}{12}}^{\frac{4T}{12}} (1 - \cos(2\omega t)) dt} =$$

$$= V_M \sqrt{\frac{3}{T} \left(\frac{T}{6} + \frac{\sqrt{3}}{2\omega} \right)} = V_M \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{4\pi}} = 0.9958 \cdot V_M$$

$$RF = \frac{\sqrt{V_{Ueff}^2 - V_u^2}}{V_u} = 0.04197$$


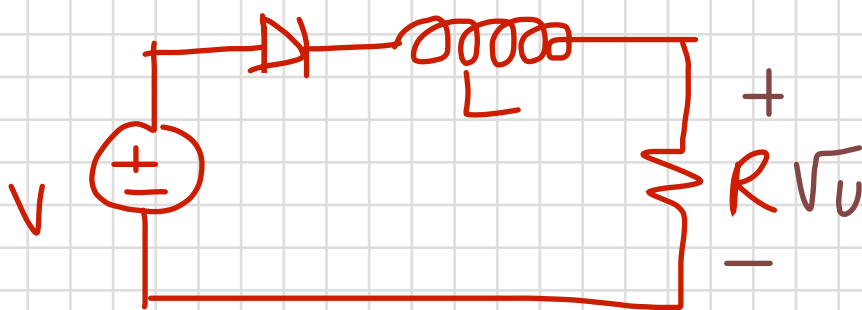
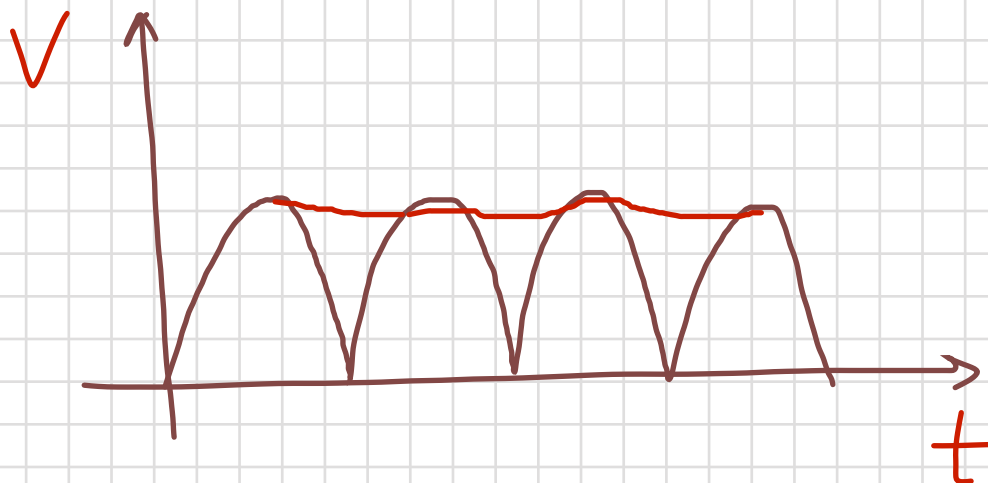
$$\eta_R = \frac{V_u^2}{V_{Ueff}^2} = 0.9982$$



$$V = V_u + L \frac{dV_u}{R dt}$$


$$V_u(j\omega) = \frac{V(j\omega) R}{R + j\omega L}$$

$$H(j\omega) = \frac{R}{R + j\omega L}$$

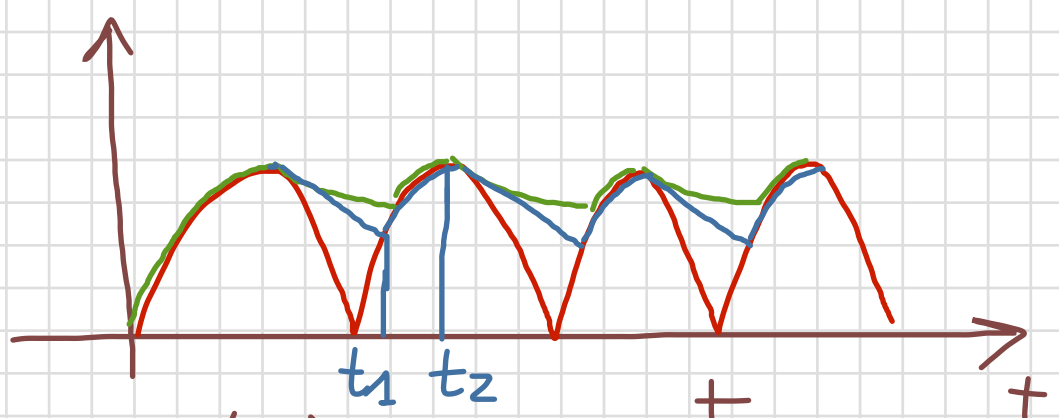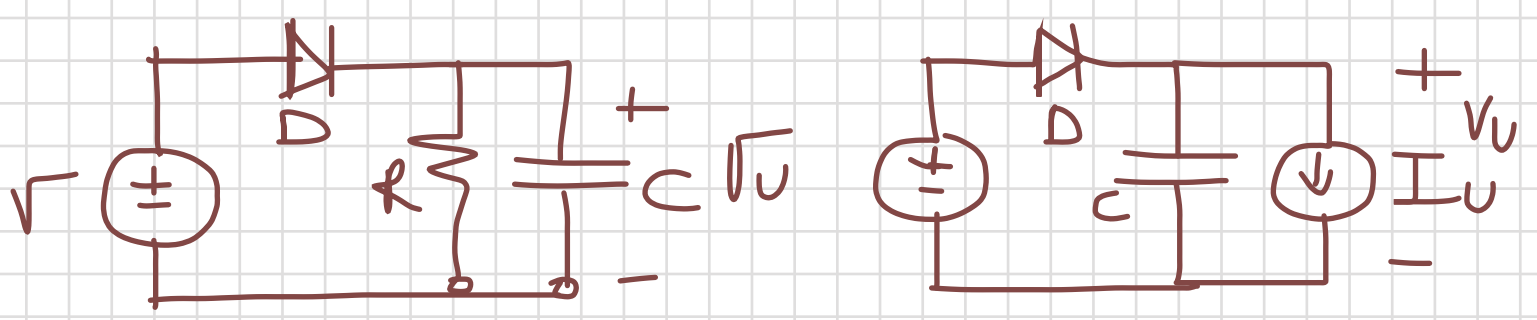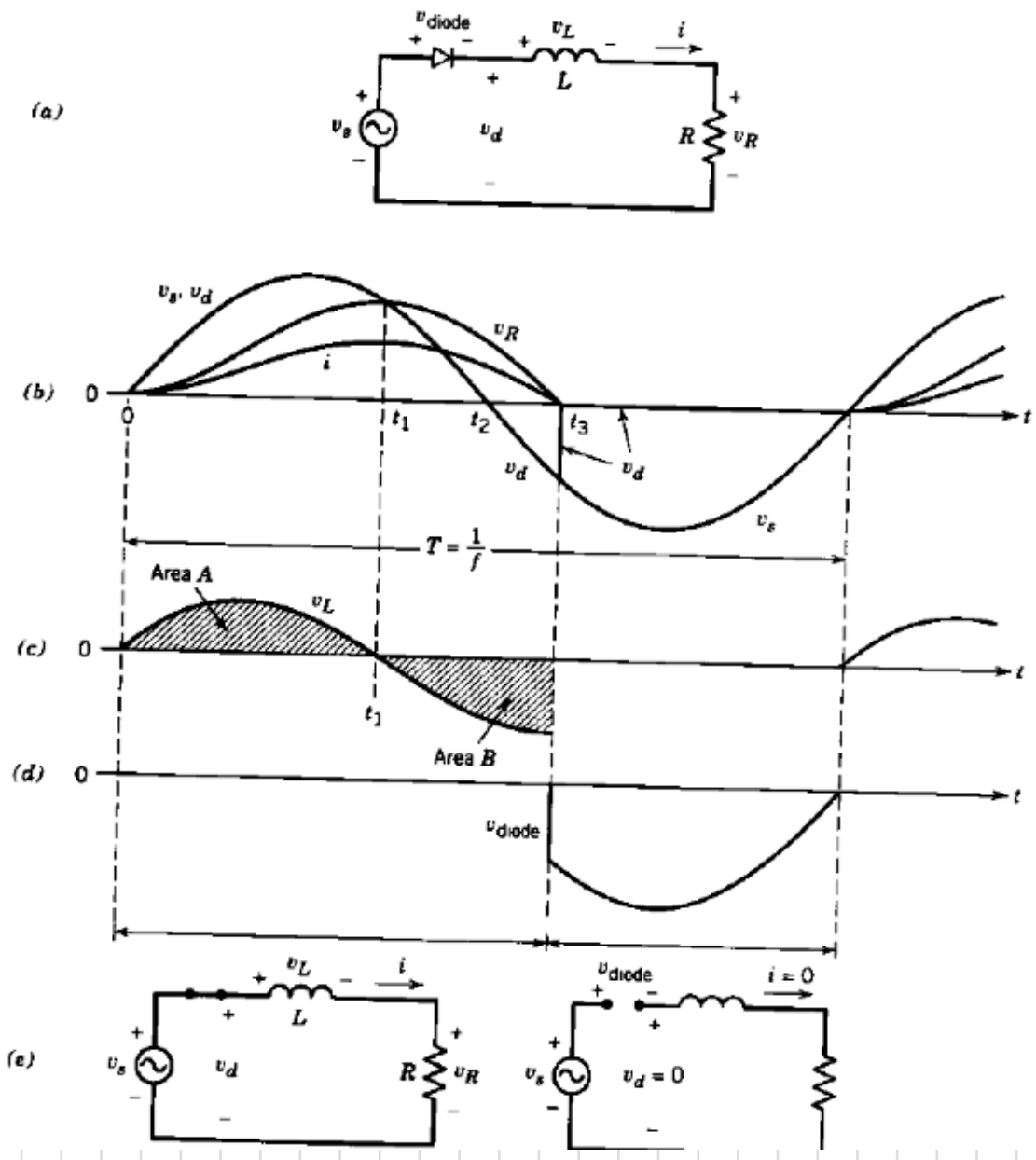

R: $v_U(t) = V_m e^{-\frac{t}{\tau}}$


$$t_2 - t_1 \ll \frac{T}{2}$$

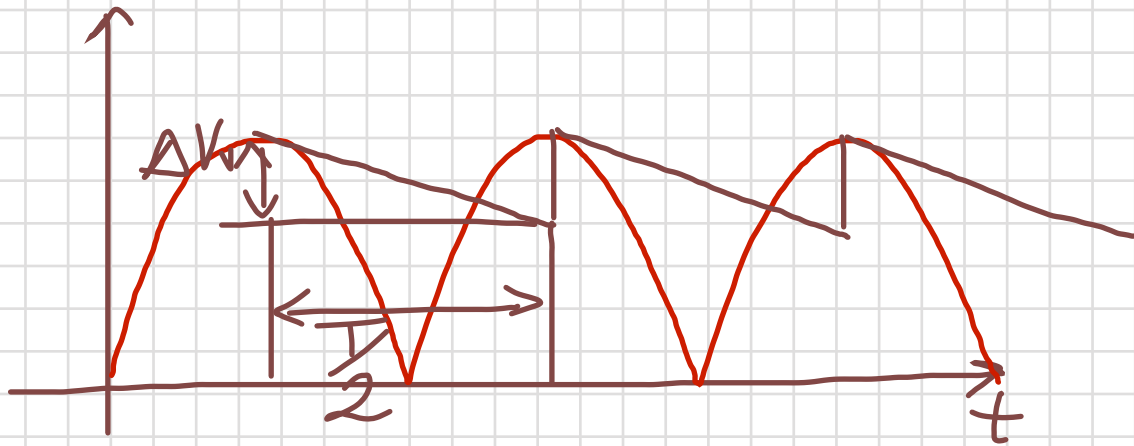

$$\Delta V_U = \frac{I_U T}{C 2}$$

$$\Delta V_U = V_m \left(1 - e^{-\frac{T}{2RC}} \right)$$

$$\hat{C} = RC$$


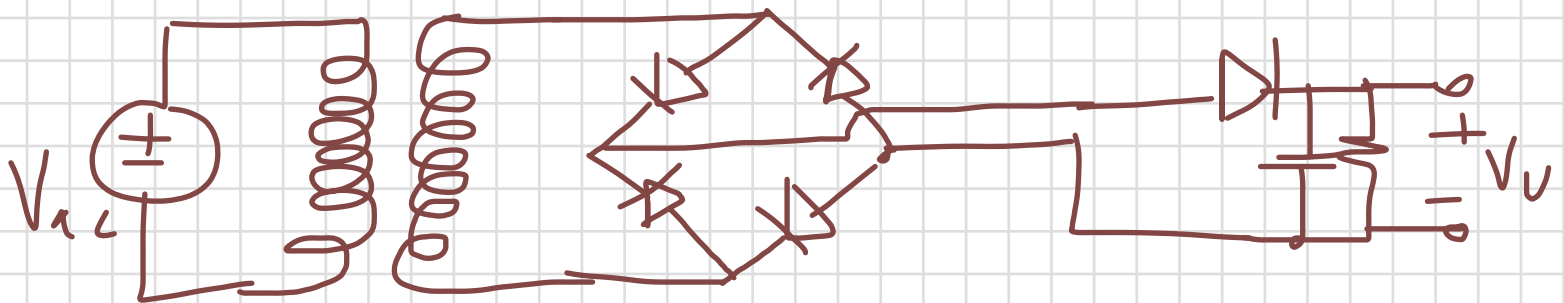


$$V_U = V_m - \frac{\Delta V_U}{2} = V_m - \left(\frac{T}{4C} \right) I_U = V_m - R_R I_U$$

$$V_{\text{ueff}} = \sqrt{\frac{2}{T} \int_0^{T/2} \left(V_m - \frac{I_U t}{C} \right)^2 dt} = \sqrt{\frac{2}{T} \int_0^{T/2} \left(V_m^2 - 2V_m \frac{I_U t}{C} + \frac{I_U^2 t^2}{C^2} \right) dt} =$$

$$= \sqrt{V_m^2 - 2V_m R_R I_U + \frac{4}{3} (R_R I_U)^2}$$

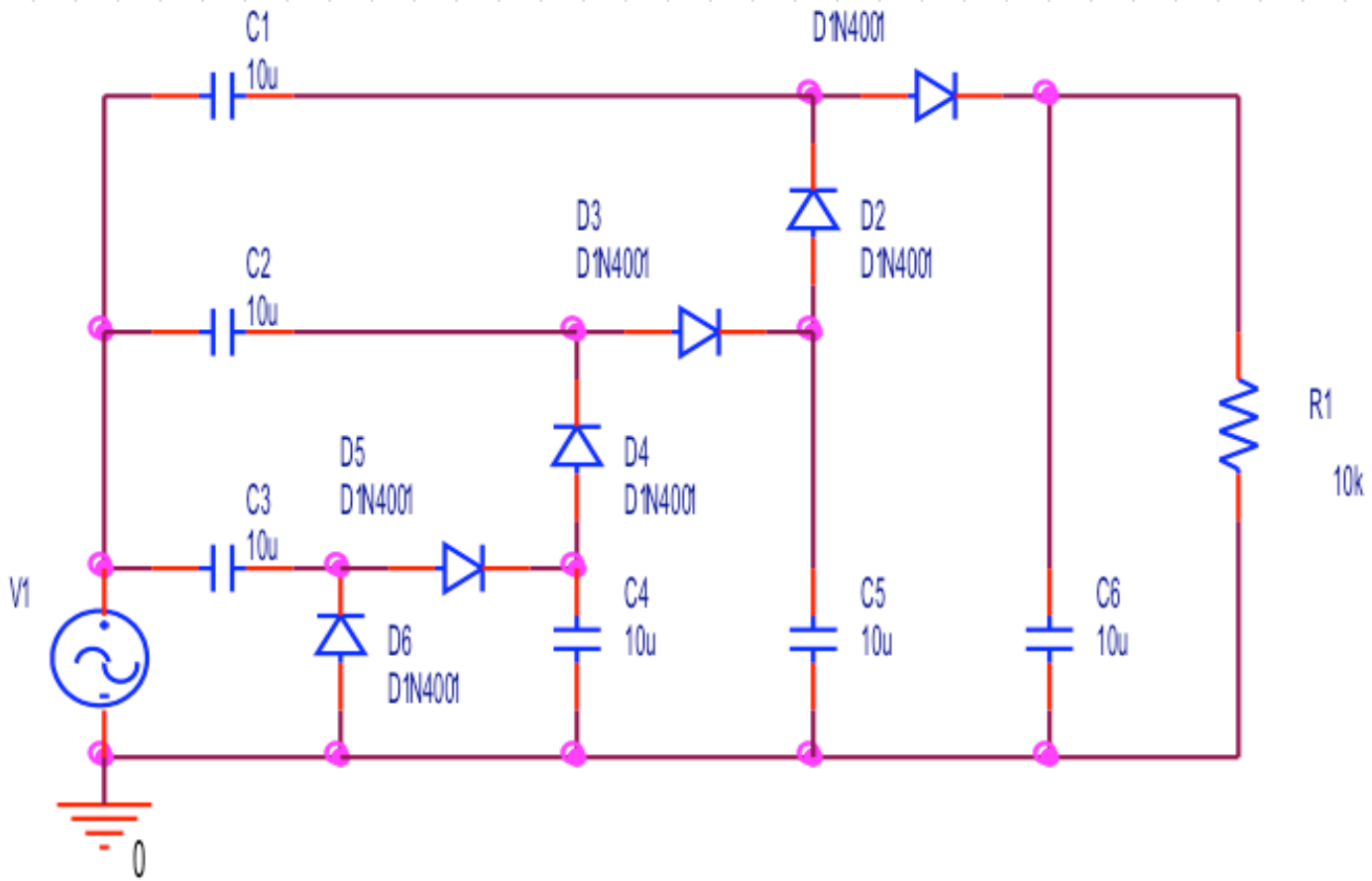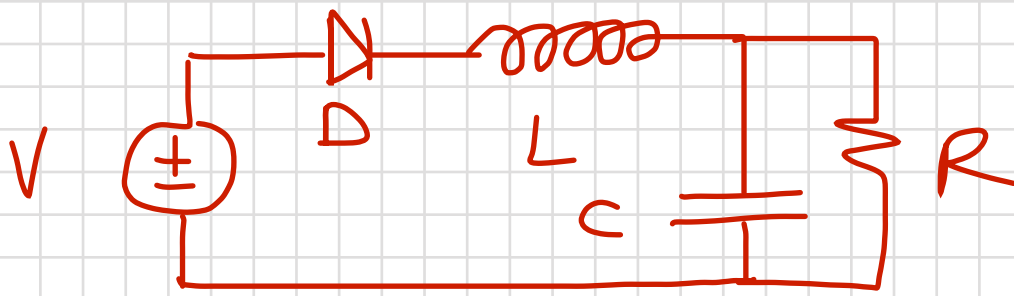
$$RF = \frac{\sqrt{V_{\text{ueff}}^2 - V_U^2}}{V_U} = \frac{R_R I_U}{\sqrt{3} (V_m - R_R I_U)}$$





$$S_v = \left| \frac{dV_U}{dV_{IN}} \right|$$

$$r_u = \left| \frac{dV_U}{dI_U} \right|$$

$$S_T = \left| \frac{dV_U}{dT} \right|$$

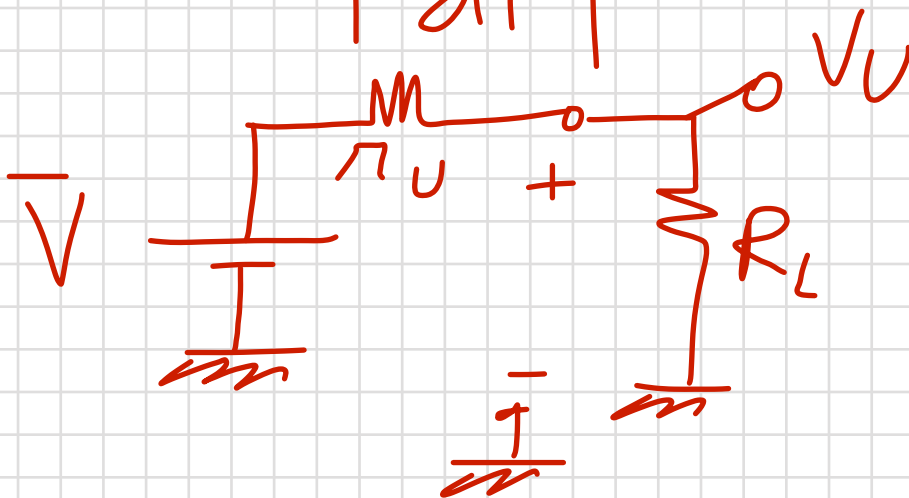

$$V_U = \frac{R_L}{R_L + r_u} V$$

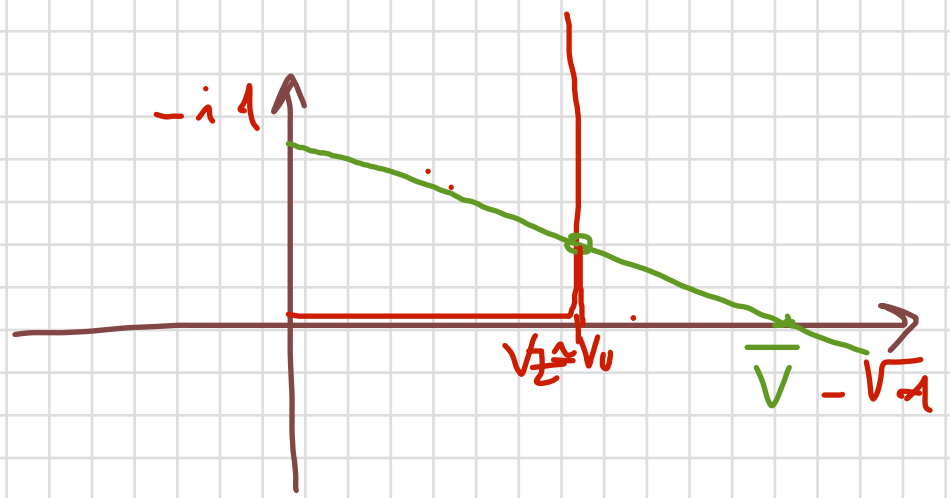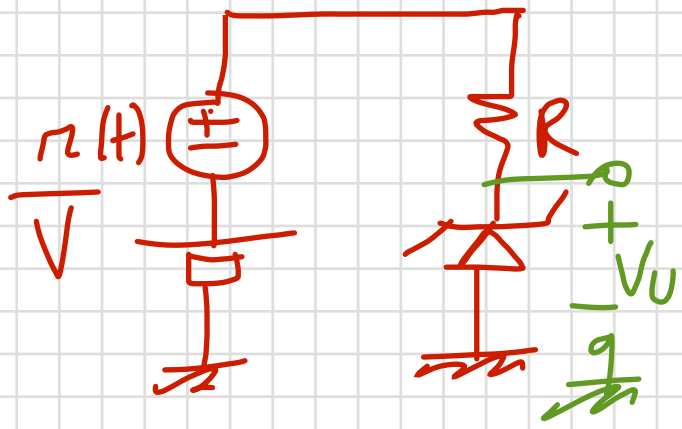

r_z è la resistenza dello Zener

$$S_V = \frac{r_z}{R + r_z}$$

$$r_U = R // r_z$$