

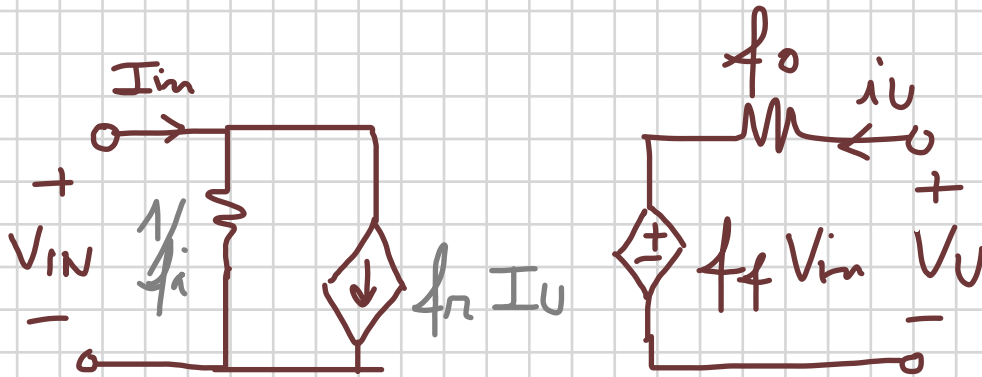
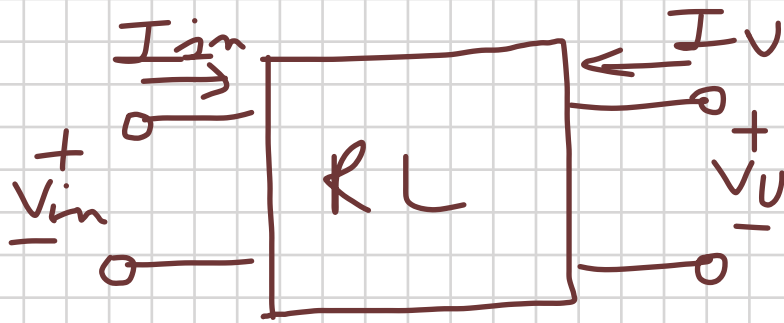


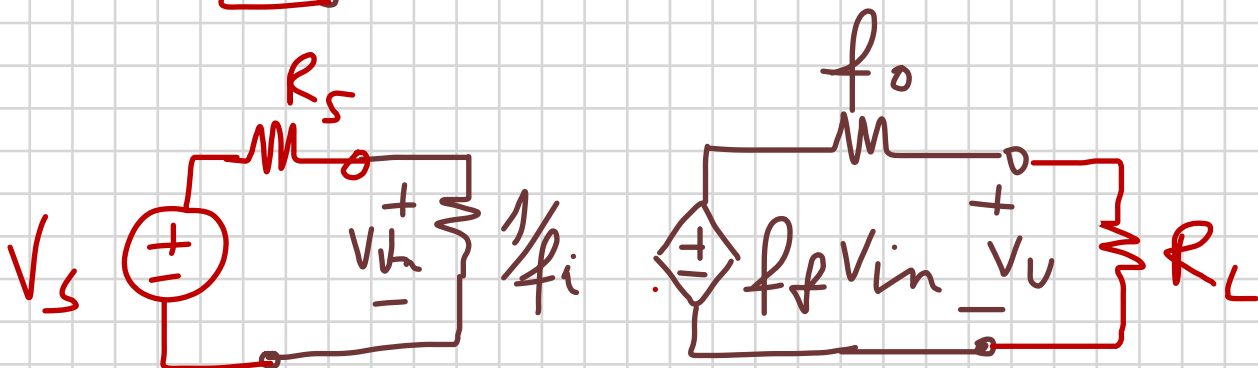
- Tensione $V_U = A_V V_{in}$
- Corrente $I_U = A_I I_{in}$
- Tramconduttivi $I_U = G V_{in}$
- Tramresistivi $V_U = R I_{in}$



Se $f_r = 0$
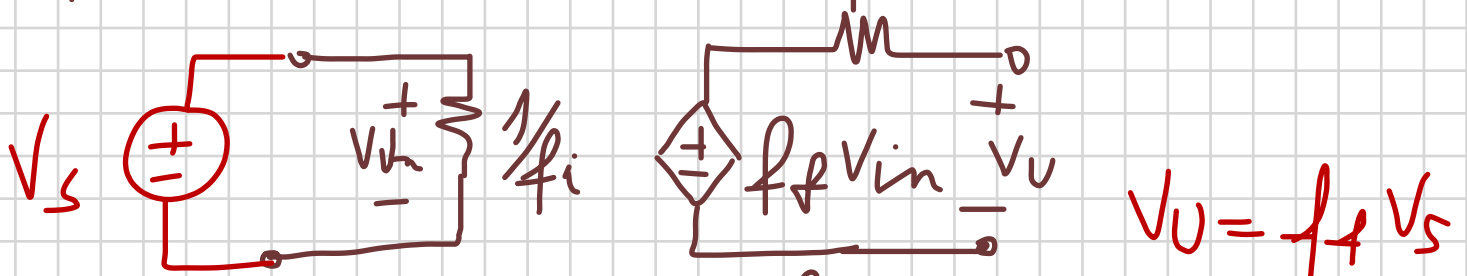
$$\begin{cases} V_U = f_f V_{in} + f_o i_U \\ I_{in} = f_v V_{in} + f_r I_U \end{cases}$$





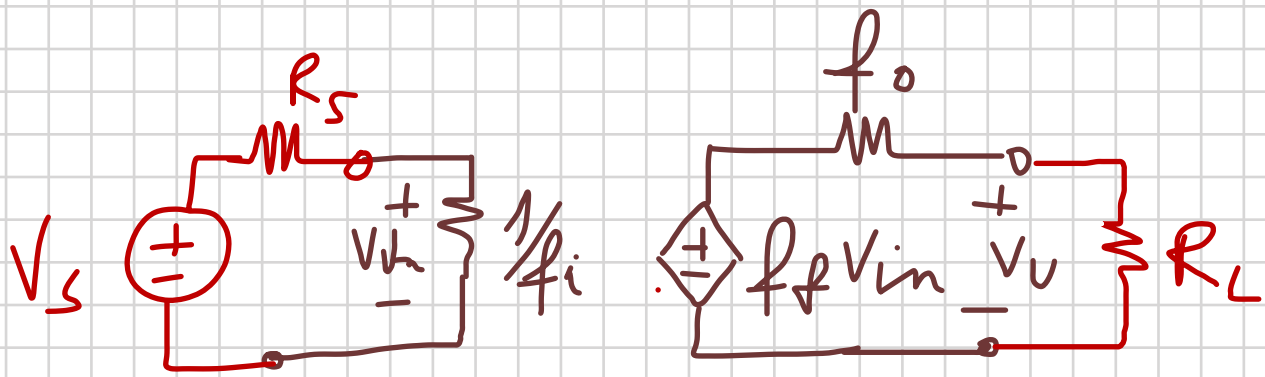


$$V_{in} = \frac{\frac{1}{f_i}}{\frac{1}{f_i} + R_s} V_s ; \quad V_U = \frac{R_L}{R_L + f_o} f_f V_{in}$$

$$V_U = \underbrace{\frac{R_L}{R_L + f_o} f_f}_{A_v} \frac{\frac{1}{f_i}}{\frac{1}{f_i} + R_s} V_s$$
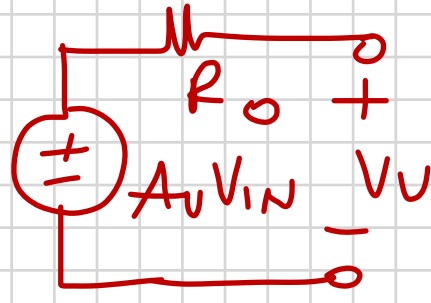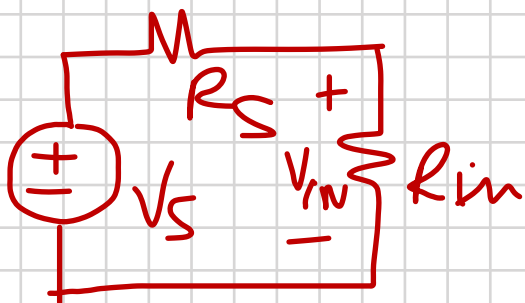
$$\begin{aligned} \frac{1}{f_i} \gg R_s &\Rightarrow \frac{\frac{1}{f_i}}{\frac{1}{f_i} + R_s} \approx 1 \\ f_o \ll R_L &\Rightarrow \frac{R_L}{R_L + f_o} \approx 1 \end{aligned} \Rightarrow \boxed{V_U = f_f V_s}$$





$$R_V = \frac{V_p}{I_p}$$

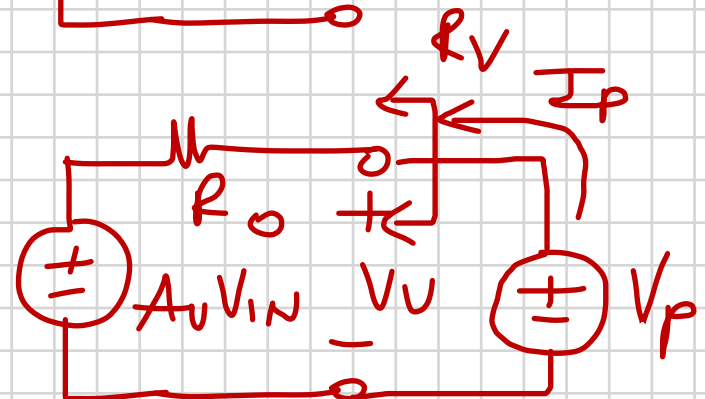

$$V_p = R_o I_p + A_v V_{in}$$

$$V_{in} = 0 \Rightarrow V_p = R_o I_p \Rightarrow \frac{V_p}{I_p} = R_v = R_o$$
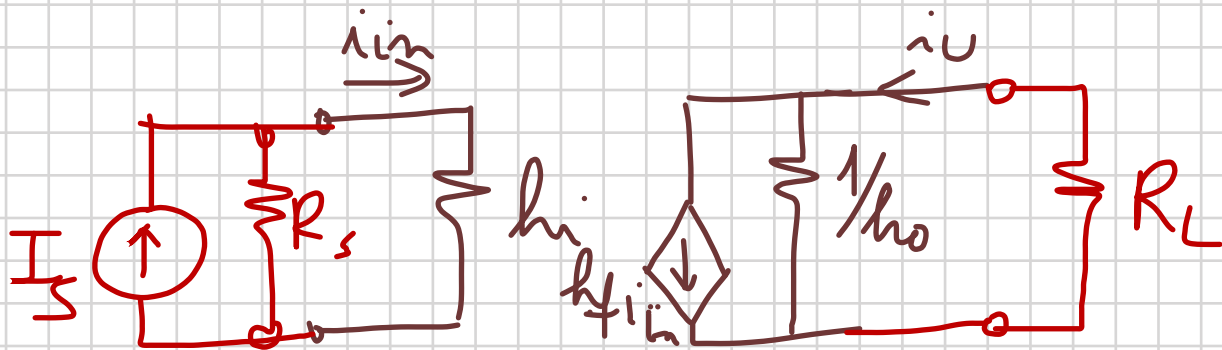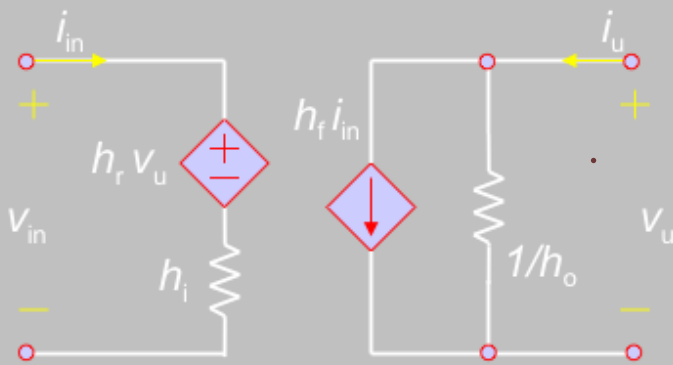
$$\begin{cases} i_u = h_f i_{in} + h_o v_u \\ v_{in} = h_i i_{in} + h_r v_u \end{cases}$$



$$i_{in} = \frac{R_S}{R_S + h_i} I_S \quad R_S \gg h_i \Rightarrow i_{in} = I_S$$

$$i_u = h_f i_{in} \frac{1/h_o}{1/h_o + R_L}$$


$$\frac{1/h_o}{1/h_o + R_L} \gg R_L \Rightarrow i_u \approx h_f i_{in} \approx h_f I_S$$

Amplificatore transconduttivo

Equazioni

$$\begin{cases} i_u = g_f v_{in} + g_o v_u \\ i_{in} = g_i v_{in} + g_r v_u \end{cases}$$

Modello

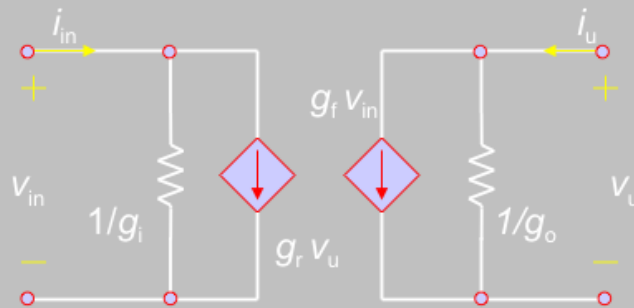


Amplificatore transresistivo

Equazioni

$$\begin{cases} v_u = r_f i_{in} + r_o i_u \\ v_{in} = r_i i_{in} + r_r i_u \end{cases}$$

Modello

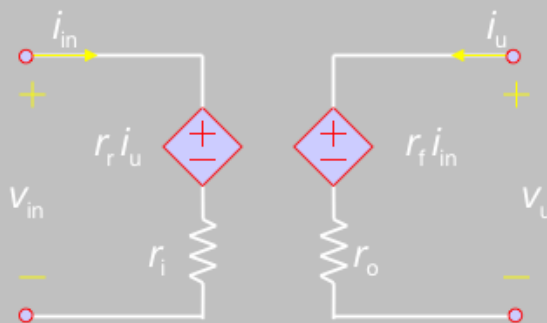

$$\begin{cases} \underline{v_u = f_f v_{in} + f_o i_u} \\ i_{in} = f_i v_{in} + f_r i_u \end{cases}$$


$$f_f = \frac{V_u}{V_s} \Big|_{I_u=0} \Rightarrow \text{USCITA APERTA}$$

$$f_o = \frac{V_u}{I_u} \Big|_{V_{in}=0} \Rightarrow \text{INGRESSO IN C.C.}$$

$$f_i = \frac{i_{in}}{V_{in}} \Big|_{i_u=0}$$

$$f_r = \frac{i_{in}}{i_u} \Big|_{V_{in}=0}$$

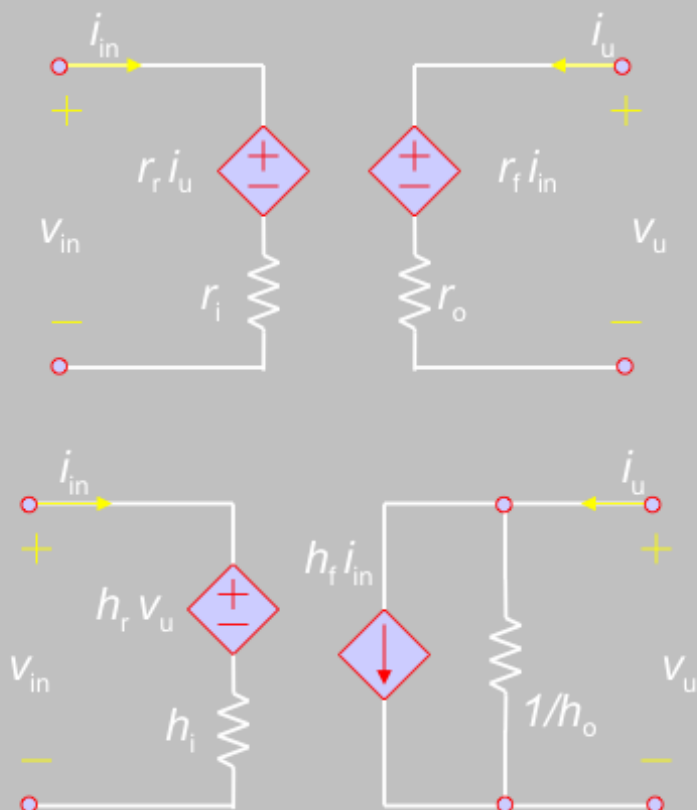Da transresistivo ad amplificatore di corrente




$$h_f = \frac{i_u}{i_{in}} \Big|_{V_u=0} = -\frac{r_f}{r_o}$$


$$h_o = \frac{i_u}{V_u} \Big|_{i_{in}=0} = \frac{1}{r_o}$$

$$h_i = \frac{V_{in}}{i_{in}} \Big|_{V_u=0} = r_i - r_r \frac{r_f}{r_o}$$

$$h_r = \frac{V_{in}}{V_u} \Big|_{i_{in}=0} = \frac{r_r}{r_o}$$

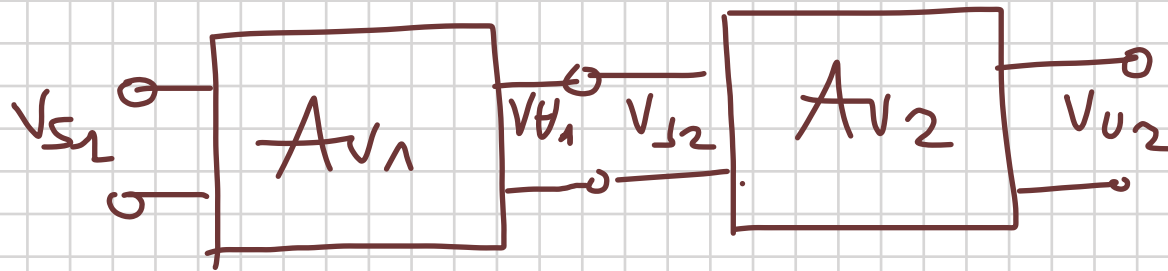

$$V_{U2} = AV_2 AV_1 V_S$$

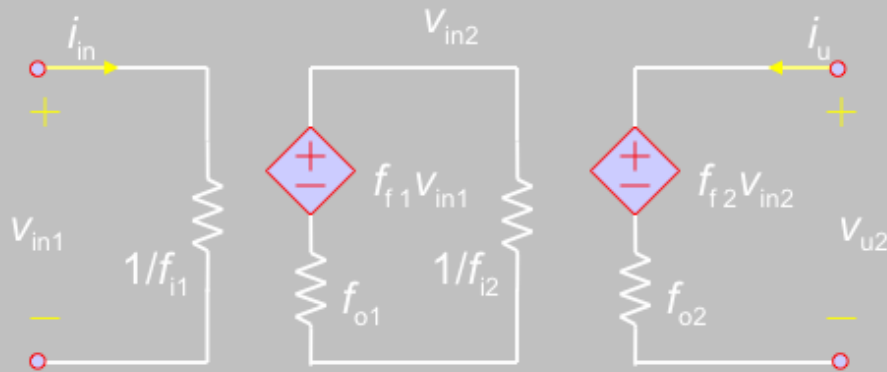

$$V_{u2} = \frac{f_{f2} f_{f1}}{1 + f_{i2} f_{o1}} V_{in1} + f_{o2} i_{u2}$$

$$i_{in1} = f_{i1} V_{in1}$$