


$$R_{vB} = \frac{V_p}{I_p} \quad V_p = h_{ie} i_b + R_E (h_{fe} + 1) i_b$$

$$i_b = I_p$$


$$V_p = h_{ie} I_p + R_E (h_{fe} + 1) I_p$$

$$\frac{V_p}{I_p} = h_{ie} + R_E (h_{fe} + 1) = R_{vB} \quad 10 \div 100 \text{ k}\Omega$$

$R_{VE}$

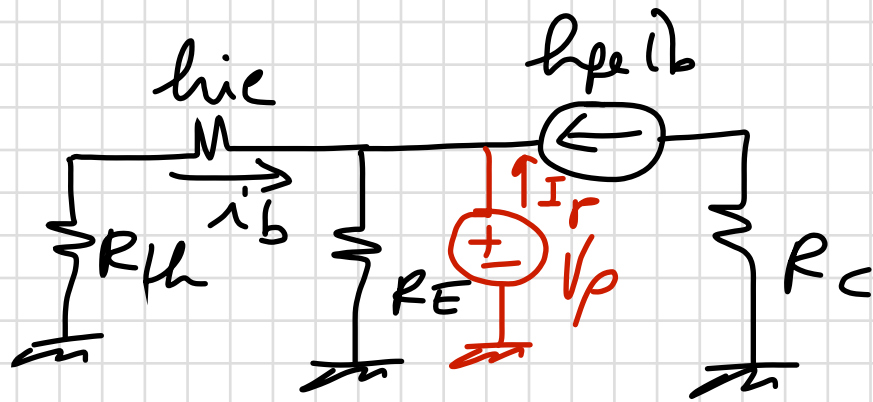

$$R_{VE} = R_E // R'_{VE}$$

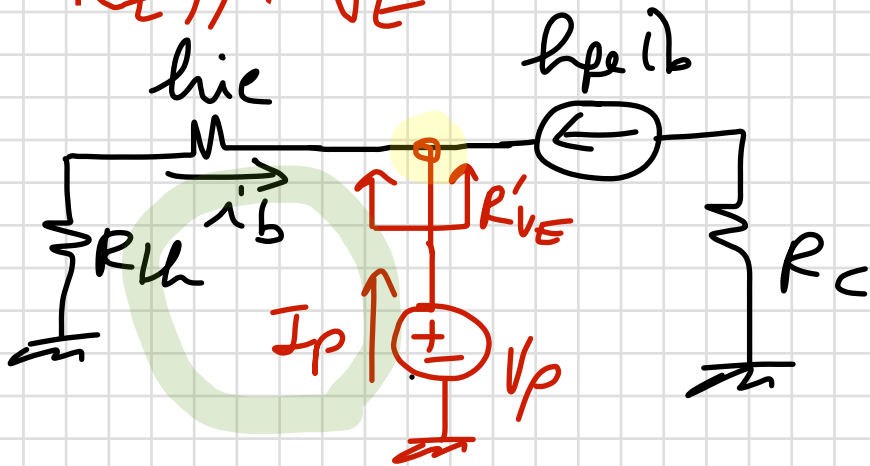


$$\begin{cases} (h_{fe} + 1) i_b = -I_p \Rightarrow i_b = -\frac{I_p}{h_{fe} + 1} \\ (R_{th} + h_{ie}) i_b = -V_p \end{cases}$$


$$V_p = \frac{R_{th} + h_{ie}}{h_{fe} + 1} I_p \Rightarrow R'_{VE} = \frac{R_{th} + h_{ie}}{h_{fe} + 1}$$

$$R_{VE} = R_E // \left[ \frac{R_{th} + h_{ie}}{h_{fe} + 1} \right] \approx 10 \div 100 \Omega$$

$R_{VC}$

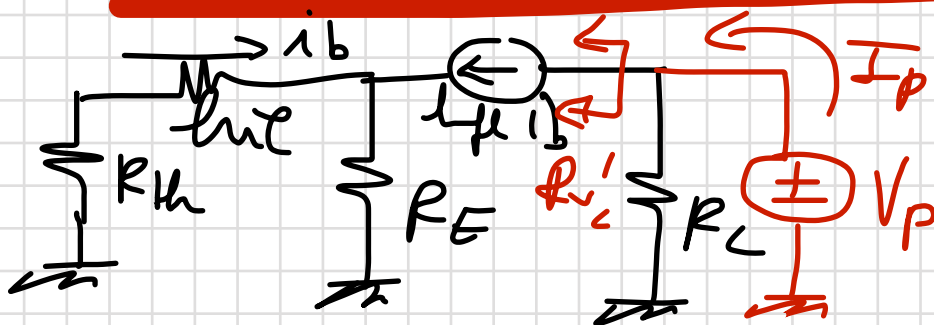

$$R_{VC} = R_C // R'_{VC}$$

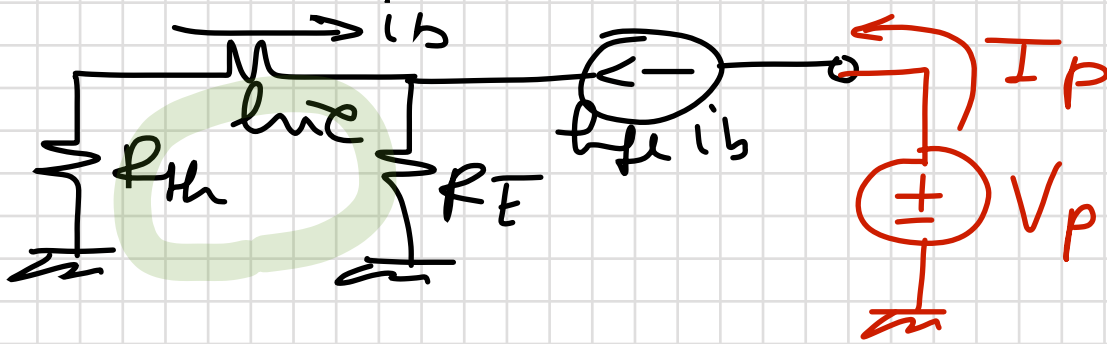


$$+(R_{th} + h_{ie}) i_b + R_E (h_{fe} + 1) i_b = 0$$


$$i_b = 0 \Rightarrow h_{fe} i_b = 0 = I_P$$

$$R_{V_C}' \rightarrow +\infty$$

$$R_{V_C} = R_C$$

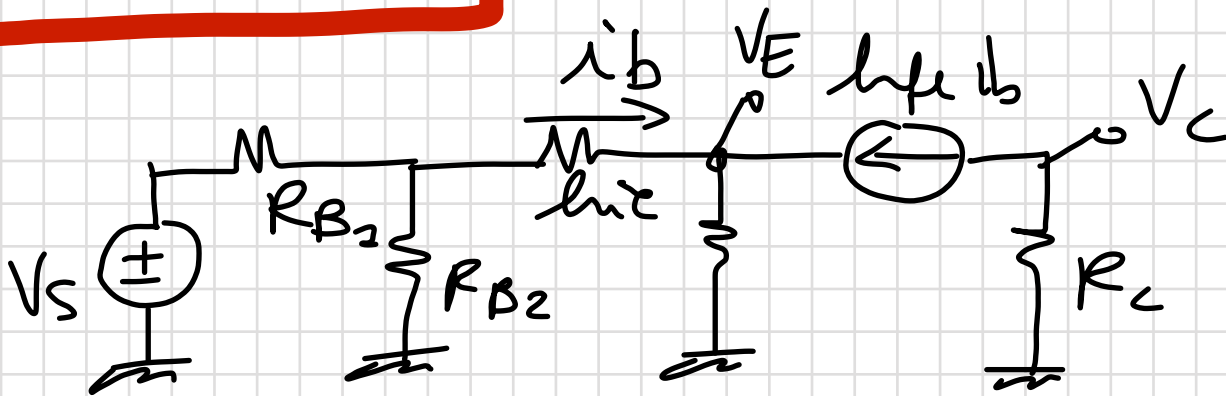
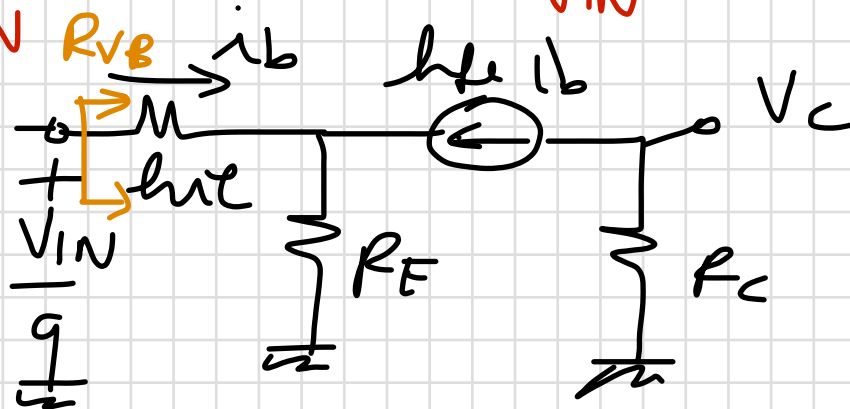
$$A_{V_C} = \frac{V_C}{V_{IN}} ; A_{V_E} = \frac{V_E}{V_{IN}}$$



$$V_C = -R_C h_{fe} i_b$$

$$i_b = \frac{V_{IN}}{R_{VB}} = \frac{V_{IN}}{h_{ie} + R_E (h_{fe} + 1)}$$

$$V_c = - \frac{h_{fe} R_c V_{in}}{h_{ie} + R_E (h_{fe} + 1)}$$

$$A_{Vc} = \frac{V_c}{V_{in}} = - \frac{h_{fe} R_c}{h_{ie} + R_E (h_{fe} + 1)}$$

$$R_E (h_{fe} + 1) \gg h_{ie} \Rightarrow$$

$$A_{Vc} \approx - \frac{h_{fe} R_c}{R_E (h_{fe} + 1)} \approx - \frac{R_c}{R_E}$$

$A_{VE}$

$$V_E = R_E (h_{fe} + 1) i_b$$


$$i_b = \frac{V_{in}}{h_{ie} + R_E (h_{fe} + 1)}$$

$$V_E = \frac{R_E (h_{fe} + 1) V_{in}}{h_{ie} + R_E (h_{fe} + 1)} \Rightarrow A_{VE} = \frac{R_E (h_{fe} + 1)}{R_E (h_{fe} + 1) + h_{ie}}$$

$$h_{ie} \ll R_E (h_{fe} + 1)$$

$\Downarrow$

$$A_{VE} \approx 1$$

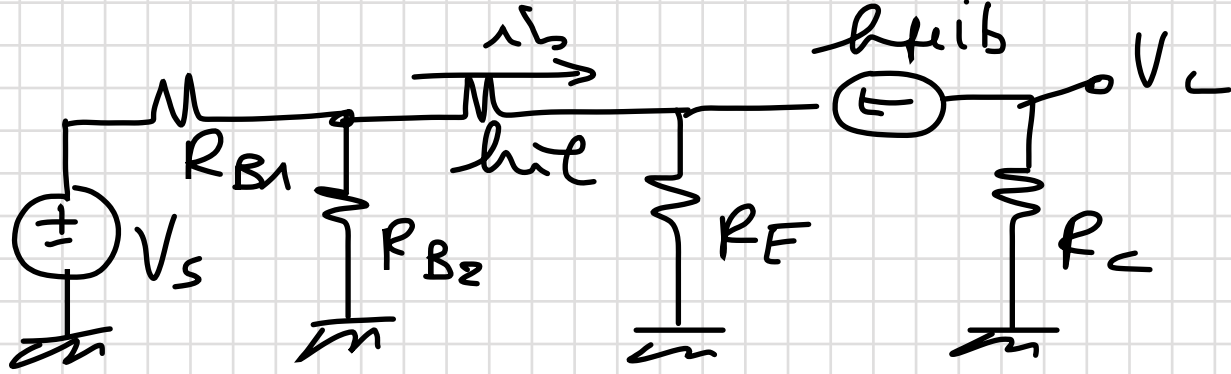


$$V_C = -R_C h_{fe} i_b$$


$$i_b = \frac{V_{th}}{R_{th} + h_{ie} + R_E (h_{fe} + 1)}$$

$$A_{V_C} = \frac{V_C}{V_S} = \frac{R_C h_{fe}}{R_{th} + h_{ie} + R_E (h_{fe} + 1)} \frac{R_{B2}}{R_{B1} + R_{B2}}$$

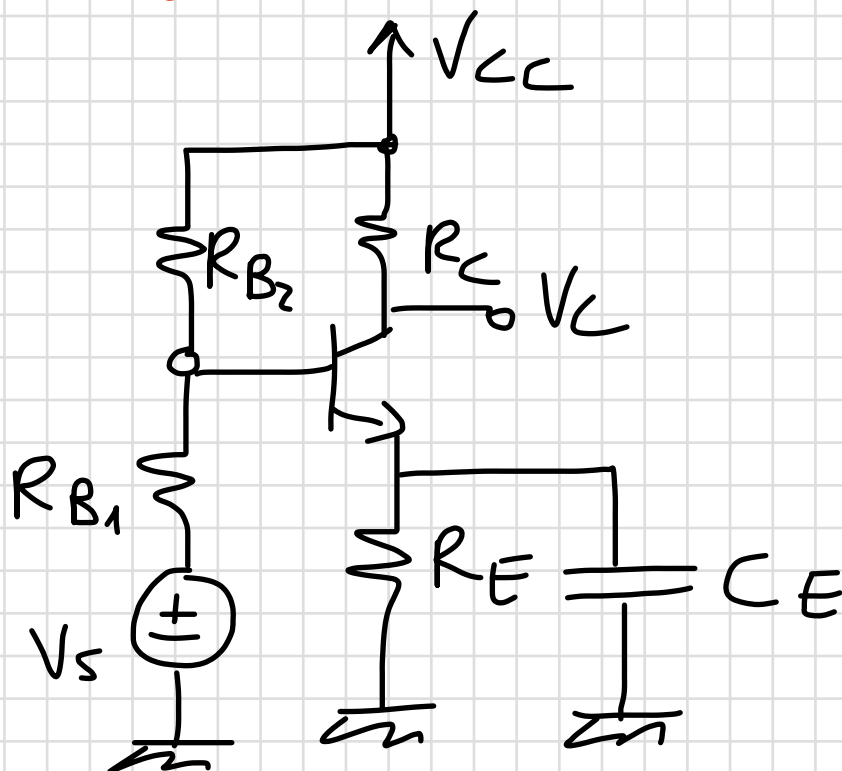
$$A_{V_E} = \frac{V_E}{V_S} = \frac{R_E (h_{fe} + 1)}{R_{th} + h_{ie} + R_E (h_{fe} + 1)} \frac{R_{B2}}{R_{B1} + R_{B2}}$$


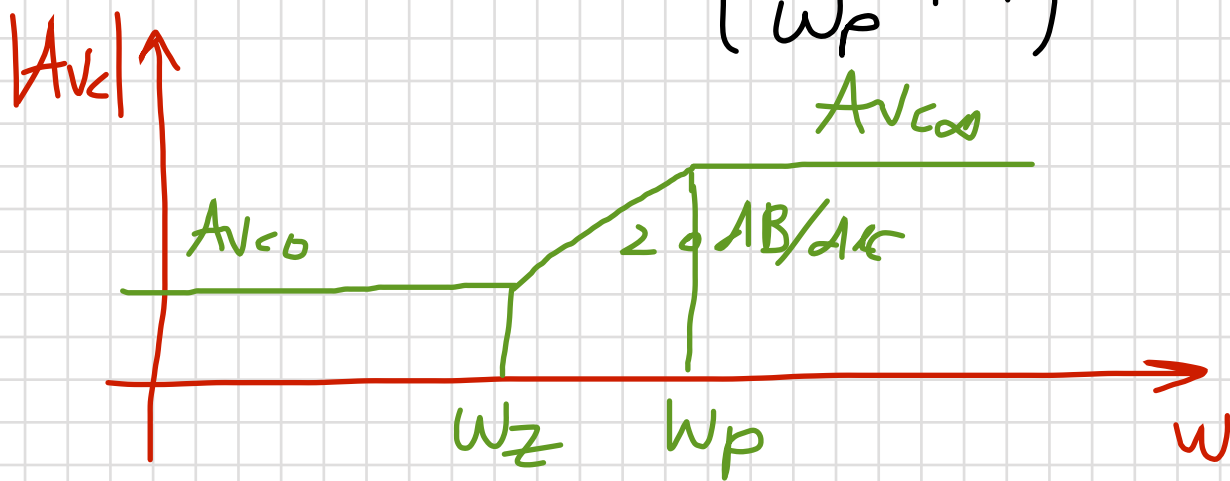
$$A_{vC}(s) = A_{vC0} \frac{\left(\frac{s}{\omega_z} + 1\right)}{\left(\frac{s}{\omega_p} + 1\right)}$$



$$\omega_p = \frac{1}{C R_{VCE}}$$

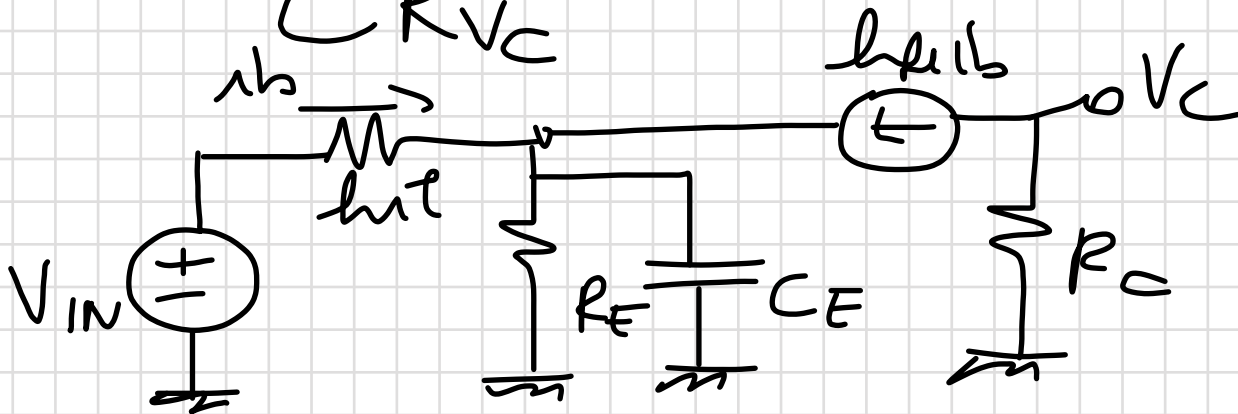

$$A_{vC}(s) = \frac{A_{vC0} \left(\frac{s}{\omega_0} + 1\right)}{\left(\frac{s}{\omega_p} + 1\right)}$$


$$A_{vC0} = - \frac{R_C h_{FE}}{h_{ie} + R_E (h_{FE} + 1)}$$

$$A_{vC\infty} = - \frac{R_C h_{FE}}{h_{ie}} = - g_m R_C \quad g_m = \frac{h_{FE}}{h_{ie}}$$


$$\omega_p = \frac{1}{C_E R_{VCE}} \quad R_{VCE} = R_E \parallel \left( \frac{h_{ie}}{h_{FE} + 1} \right)$$

$$\lim_{S \rightarrow \infty} A_V(S) = A_{V\infty} = A_{Vc0} \frac{\omega_p}{\omega_0}$$
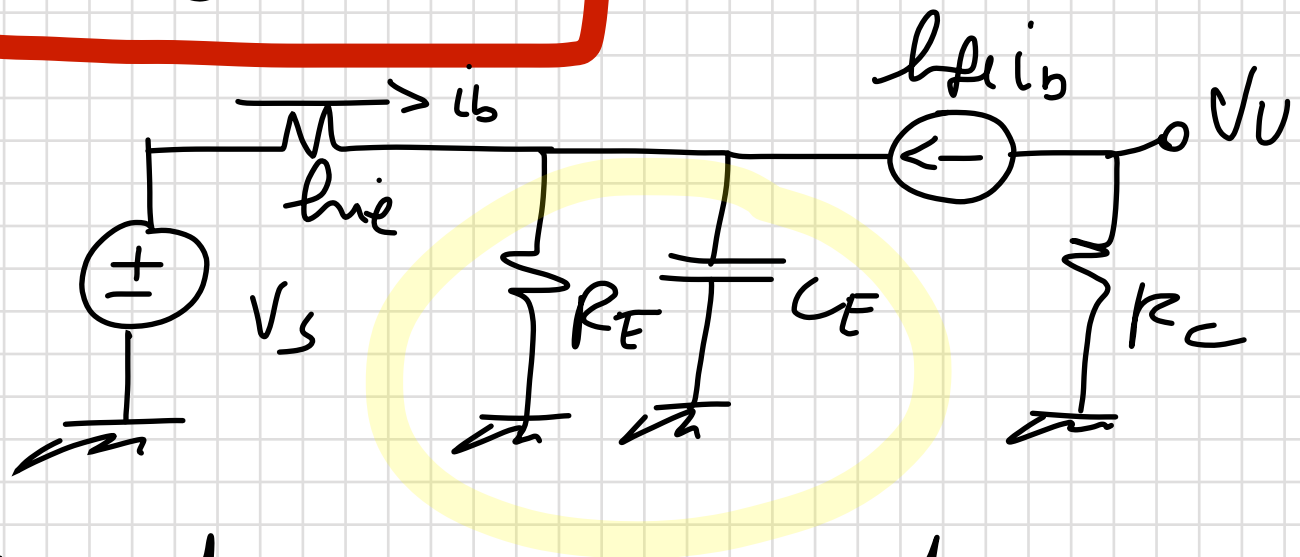
$$\omega_0 = \frac{A_{Vc0}}{A_{V\infty}} \omega_p$$


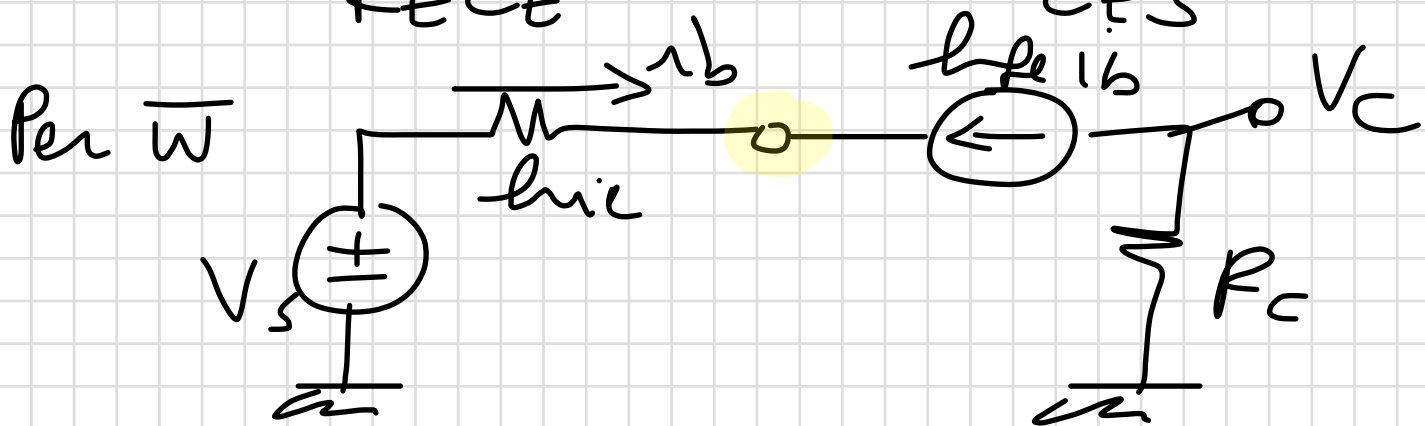
$$\bar{\omega} = \frac{1}{R_E C_E} \Rightarrow R_E // \frac{1}{C_E S} \rightarrow +\infty$$



$$i_b = -h_{fe} i_b \Rightarrow i_b = 0$$

$$\Rightarrow V_C = 0 \Rightarrow \bar{\omega} = \omega_0$$

$$A_{VCE} = \frac{A_{VE}}{\left(1 + \frac{S}{\omega_p}\right)}$$

