


$$V_o = R_o A_I I_{Em} =$$

$$= R_o A_I I_s$$

$$I_{Em} = I_s - I_f$$

$$I_{sc} = \frac{A I_s}{1 + \beta A}$$
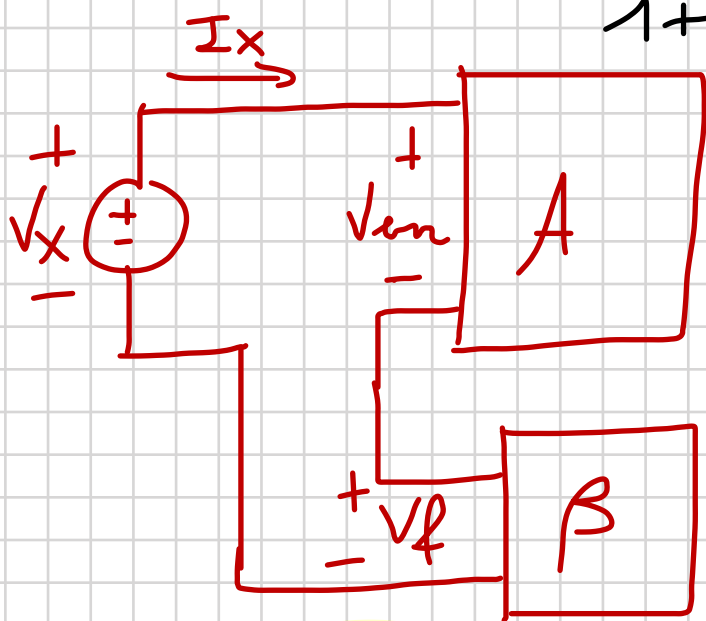
$$R_v = \frac{V_o}{I_{sc}} = \frac{R_o A_I I_s}{\frac{A_I I_s}{1 + \beta A}} = R_o (1 + \beta A)$$



$$R_{in} = \frac{V_x}{I_x} \Rightarrow$$


$$I_x = \frac{V_o}{Z_{AIN}}$$

$$V_o = A V_{em}$$

$$V_o = \frac{A}{1 + \beta A} V_x$$

$$V_{em} = \frac{V_x}{1 + \beta A}$$
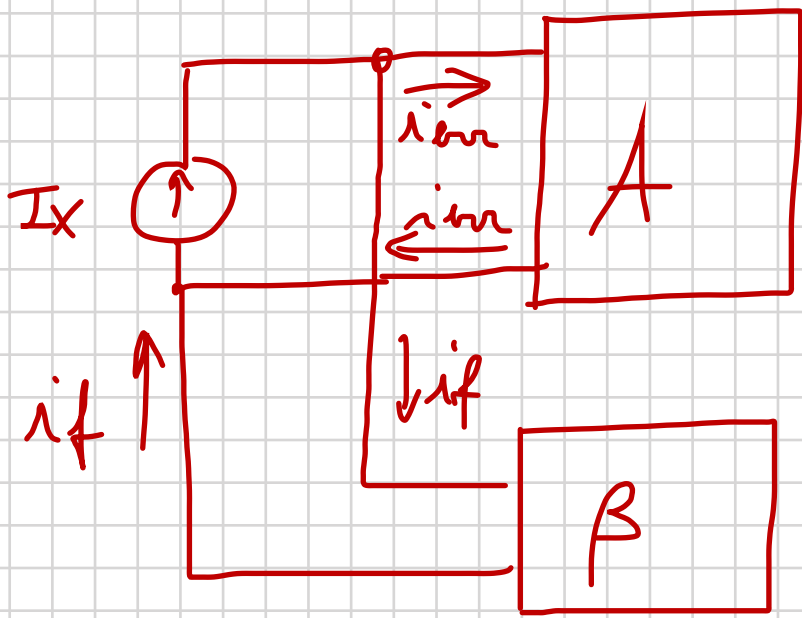
$$I_x = \frac{V_x}{Z_{AIN} (1 + \beta A)} \Rightarrow R_{in} = Z_{AIN} (1 + \beta A)$$



$$V_x = Z_{AN} i_{ov} =$$

$$= \frac{Z_{AN} I_x}{1 + \beta A}$$

$$Z_N = \frac{V_x}{I_x} = \frac{Z_{AN}}{1 + \beta A}$$

$$A_f = \frac{A}{1 + \beta A}$$

$$A = \frac{A_0}{1 + \frac{s}{\omega_p}}$$

$$\beta = \beta_0$$

$$A_f = \frac{A_0}{\left(1 + \frac{s}{\omega_p}\right)} = \frac{A_0}{1 + \frac{s}{\omega_p} + \beta_0 A_0} =$$

$$\frac{1 + \beta_0 A_0}{\left(1 + \frac{s}{\omega_p}\right)}$$

$$= \frac{A_0}{(1 + \beta_0 A_0) \left[1 + \frac{s}{\omega_p (1 + \beta_0 A_0)}\right]} = \frac{A_{f0}}{1 + \frac{s}{\omega_p'}}$$



$$A_{f0} = \frac{A_0}{1 + \beta_0 A_0} ; \omega_p' = \omega_p (1 + \beta_0 A_0)$$

$$P_{FB} = A \omega_p$$

$$A_0 \omega_p$$

$$\frac{A_0}{(1 + \beta_0 A_0)} \cdot \omega_p (1 + \beta_0 A_0)$$

$$(P_{FB})_{RNR} \geq (P_{FB})_{RR}$$

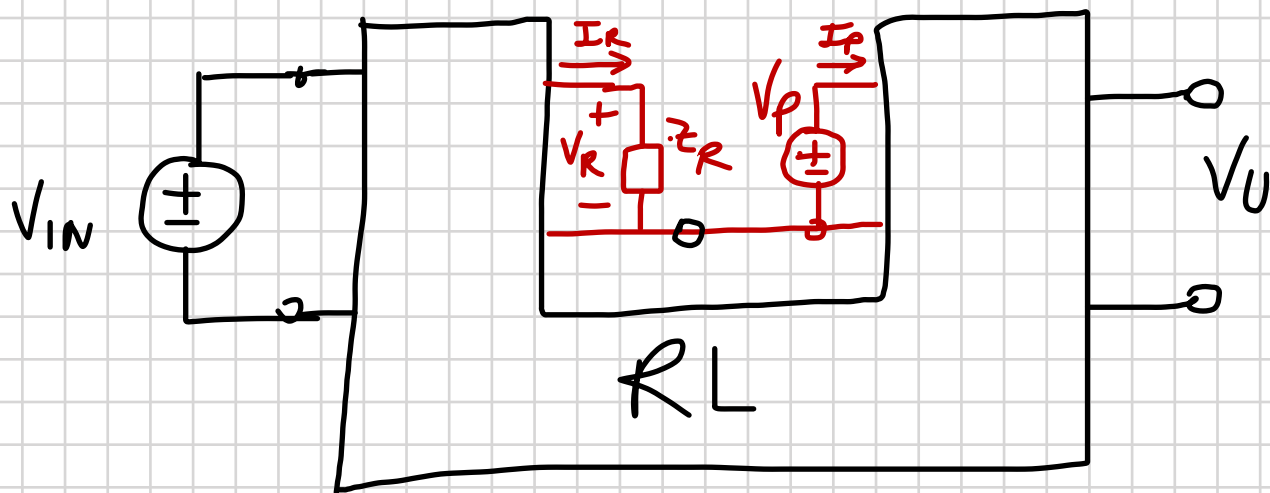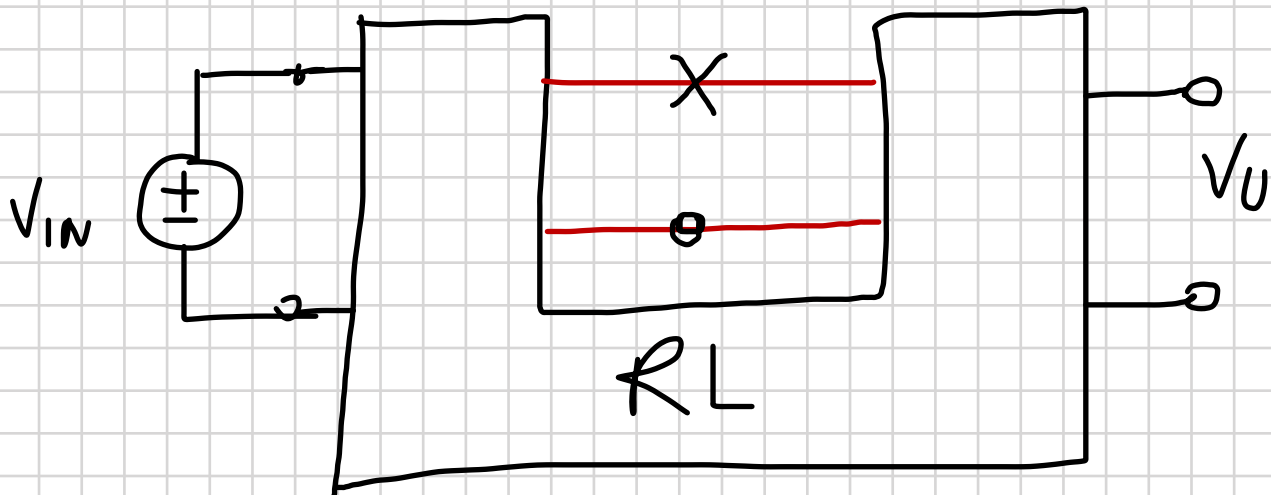

$$A = \left. \frac{V_u}{V_p} \right|_{V_s=0} \quad \beta = \left. \frac{V_r}{V_u} \right|_{V_s=0}$$


$$Z_p = \left. \frac{V_p}{I_p} \right|_{V_s=0} \quad \alpha = \left. \frac{V_r}{V_s} \right|_{V_p=0}$$




$$\gamma = \left. \frac{V_u}{V_s} \right|_{V_p=0} \quad \rho = \left. \frac{I_p}{V_r} \right|_{V_p=0}$$

$$\frac{1}{Z_n} = \frac{1}{Z_p} + \rho(1 - \beta A)$$


$$V_p = V_s \frac{\alpha}{1 - \beta A}$$
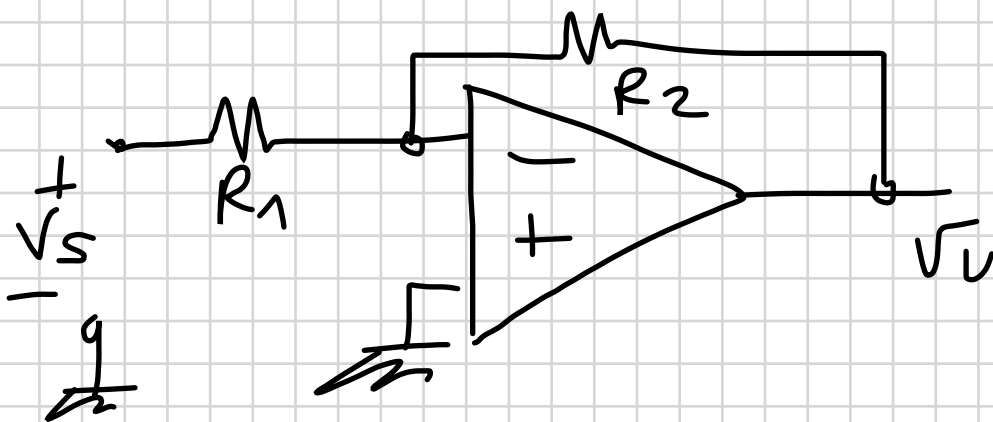
$$A_f = \frac{\alpha A}{1 - \beta A} + \gamma$$



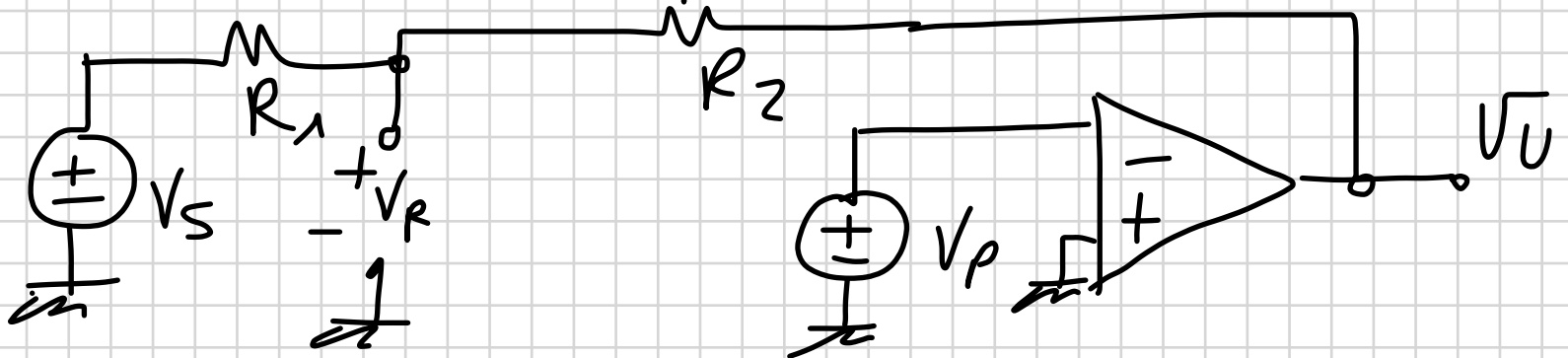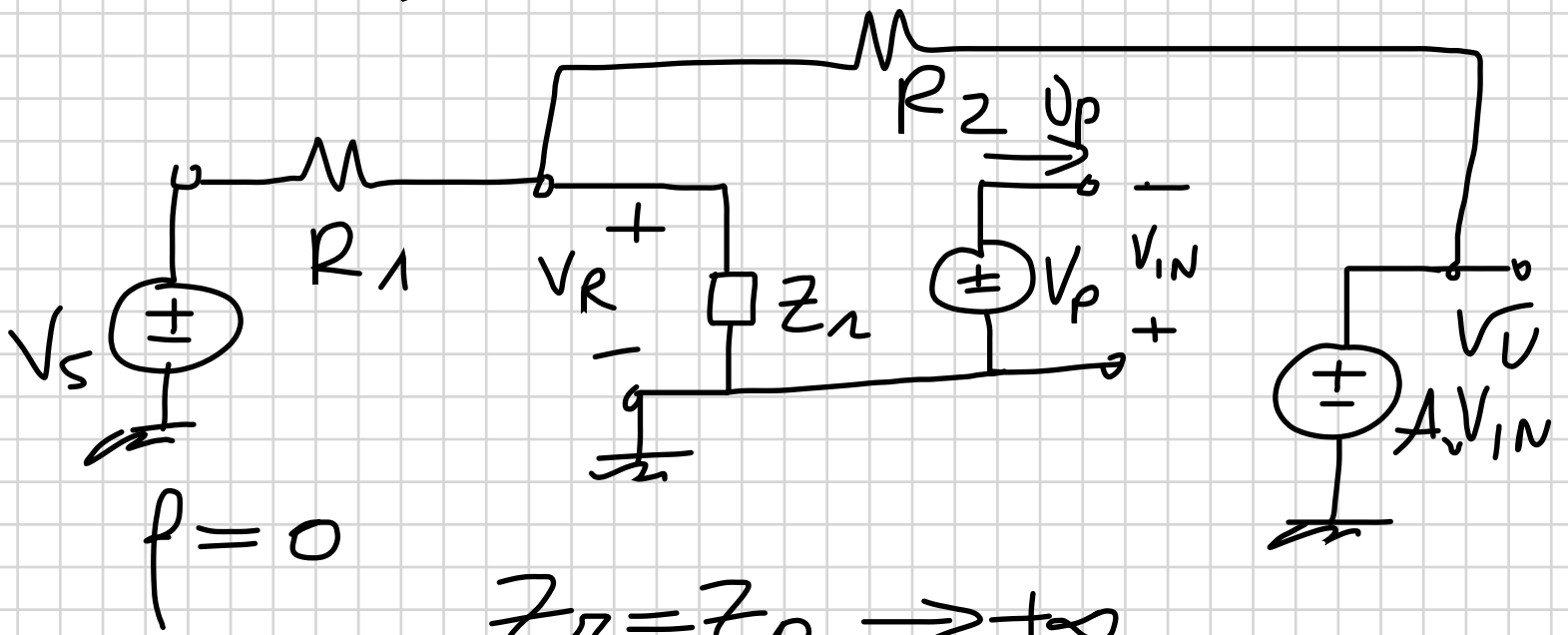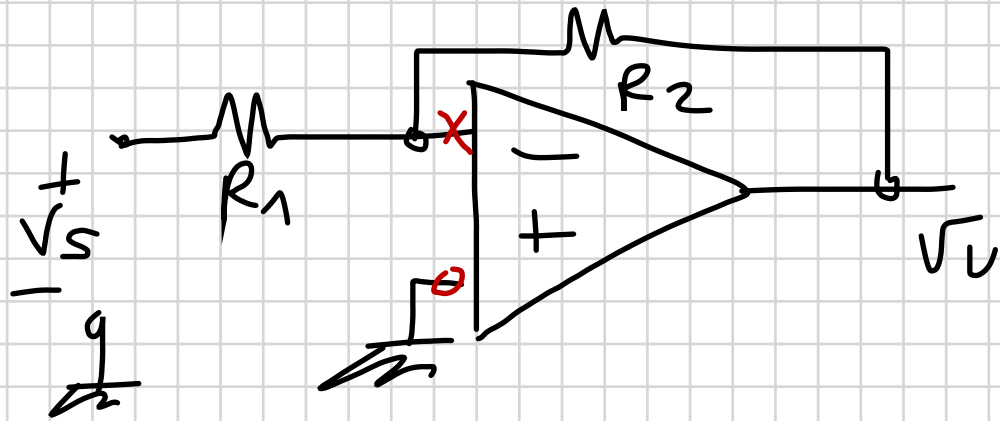


$$\alpha = \frac{V_R}{V_S} \Big|_{V_p=0}$$

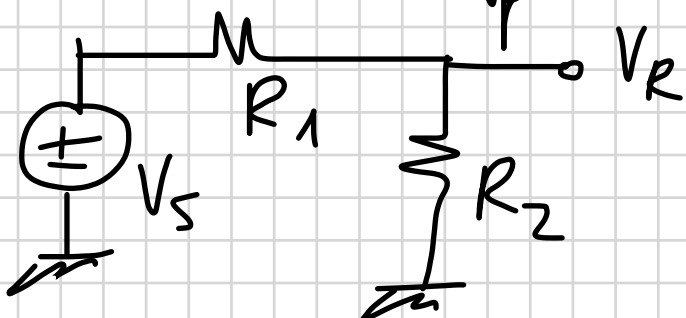

$$\alpha = \frac{R_2}{R_1 + R_2} = \alpha_0$$

$$\beta = \frac{V_R}{V_U} \Big|_{V_S=0}$$

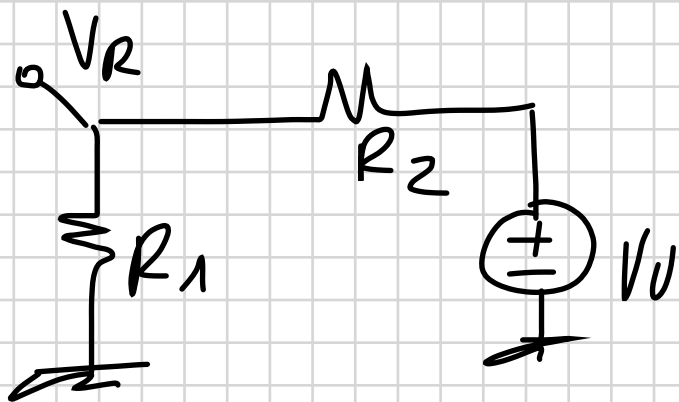

$$\beta = \frac{R_1}{R_1 + R_2} = \beta_0$$

$$A = \frac{V_U}{V_P} \Big|_{V_S=0} = -A_V$$


$$\gamma = \frac{V_U}{V_S} \Big|_{V_P=0} = 0$$

$$A_f = \frac{\alpha A}{1 - \beta A} = \frac{\frac{R_2}{R_1 + R_2} \cdot (-A_V)}{1 + A_V \frac{R_1}{R_2 + R_1}} =$$

$$= \frac{R_2 (-A_V)}{(R_2 + R_1) + A_V R_1}$$


$$\text{Se } A_V \rightarrow +\infty$$

$$A_f = -\frac{R_2}{R_1}$$

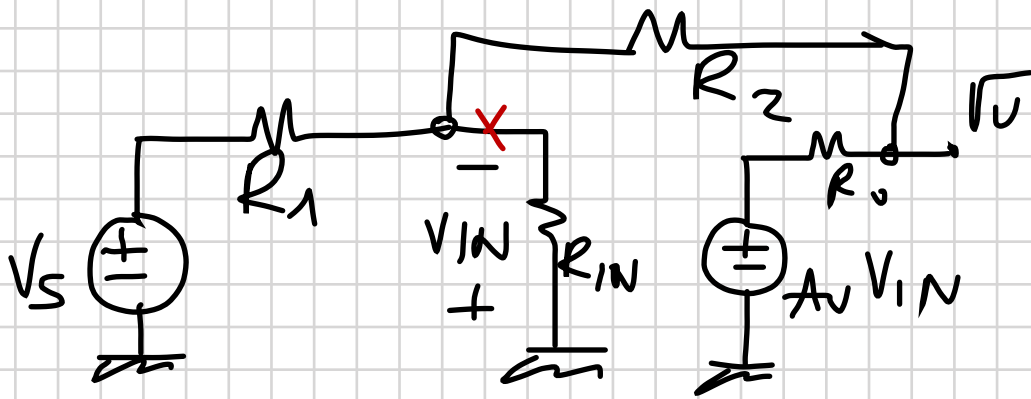


$$A_v = \frac{A_{v,old}}{1 + \frac{s}{\omega_p}}$$

$f=0 \quad Z_L = R_{IN} = Z_P$

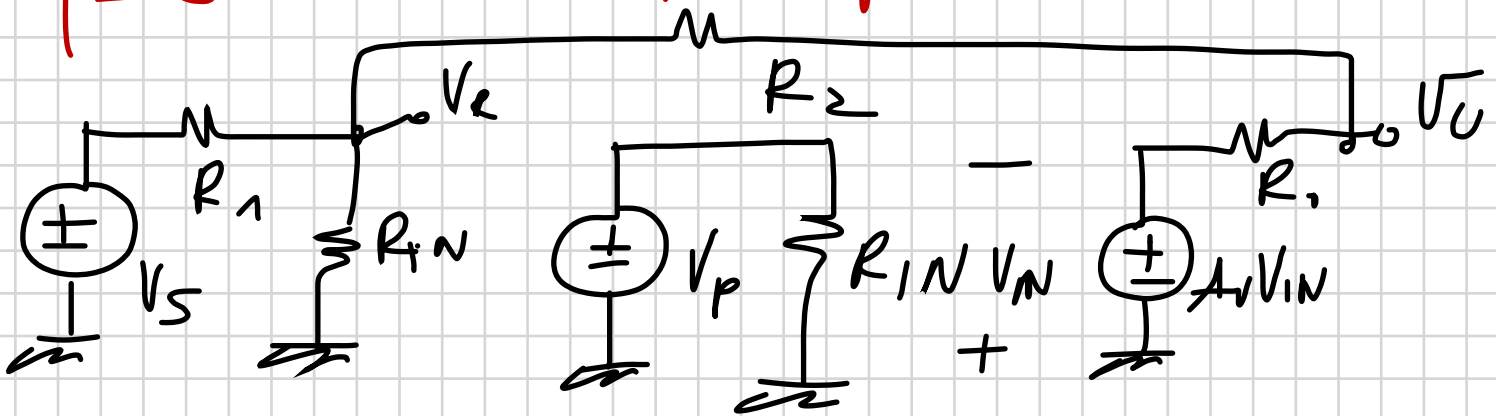


$$\alpha = \frac{V_R}{V_S} \quad | \quad V_P = 0$$

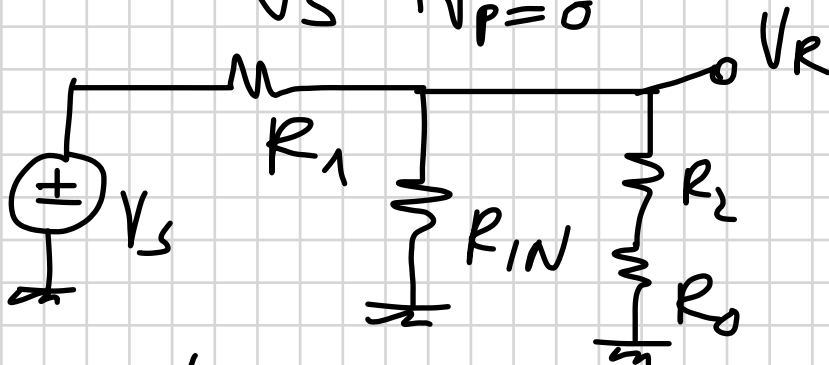


$$\alpha = \frac{R_{IN} \parallel (R_2 + R_o)}{R_1 + R_{IN} \parallel (R_2 + R_o)}$$

$$\beta = \frac{V_R}{V_U} \quad | \quad V_S = 0 \Rightarrow$$

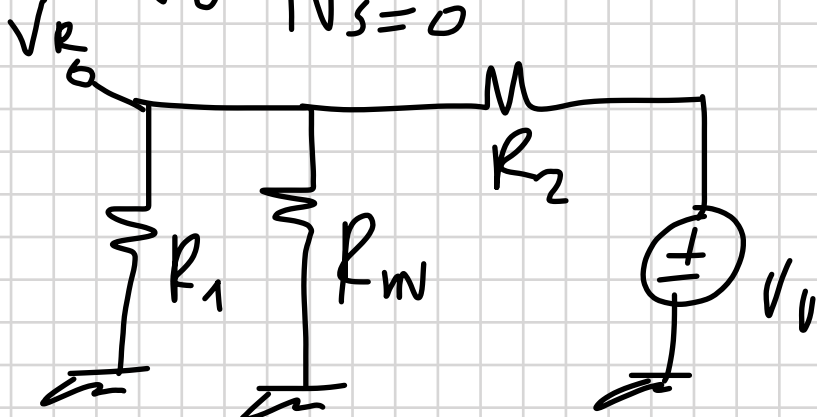



$$\beta = \frac{R_1 \parallel R_{IN}}{R_1 \parallel R_{IN} + R_2}$$

$$A = \frac{V_U}{V_P} \Big|_{V_S=0}$$

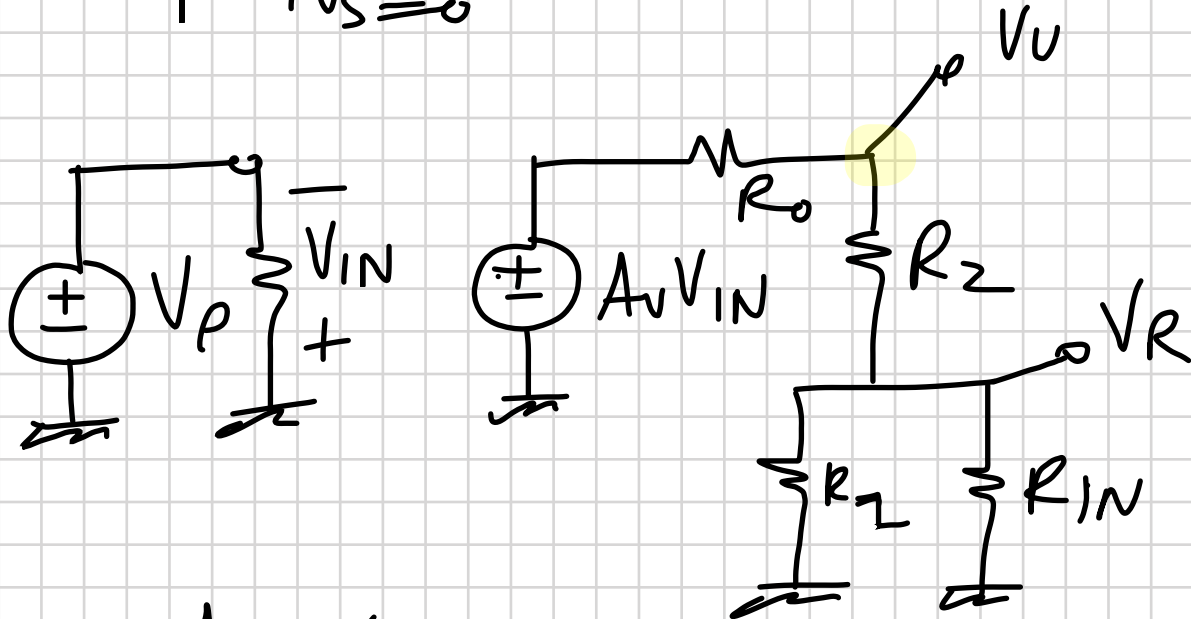

$$A = \frac{-A_{vol} \frac{1 + \frac{s}{\omega_p}}{\omega_p}}{(R_1 \parallel R_{IN} + R_2)} \cdot \frac{R_2}{R_1 \parallel R_{IN} + R_2 + R_0}$$

$$\gamma = \frac{V_U}{V_S} \Big|_{V_P=0}$$

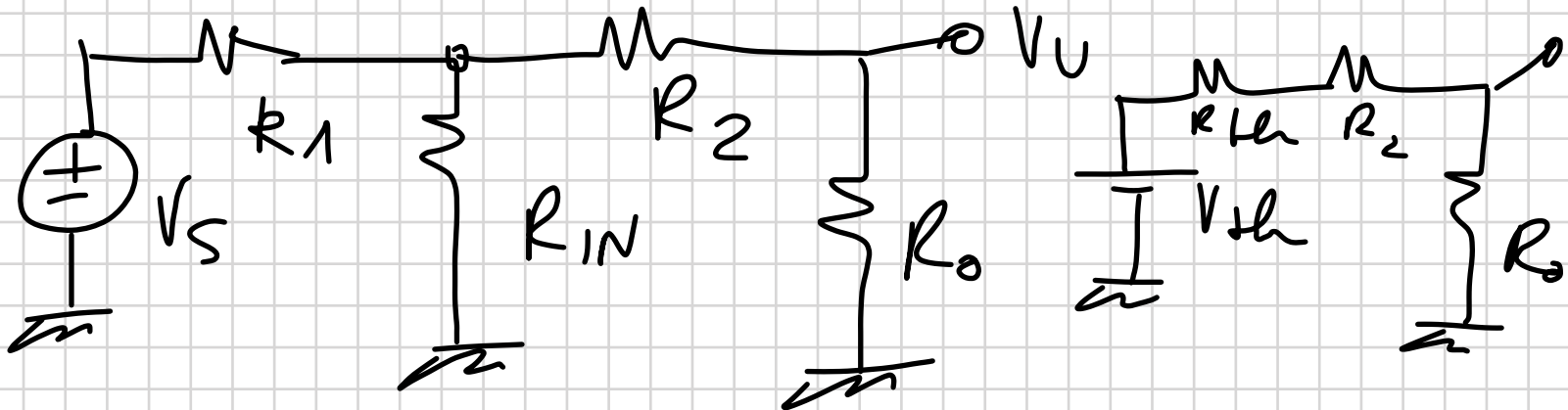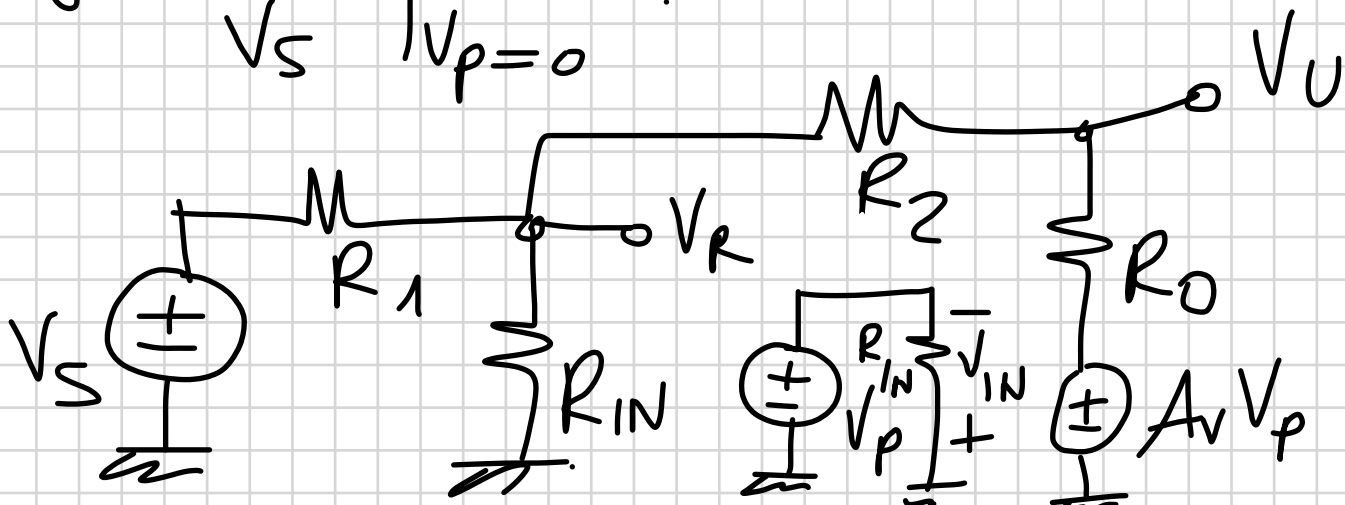

$$\gamma = \gamma_0 = \frac{R_0}{R_2 + R_0 + R_1 \parallel R_{IN}} \cdot \frac{R_{IN}}{R_{IN} + R_1}$$

