

$$\alpha = \alpha_0 \quad ; \quad \beta = \beta_0$$

$$A = - \frac{A_{v0} L \phi}{1 + \frac{s}{\omega_p}} \quad ; \quad \gamma = 0$$

$$A_f = \frac{\alpha A}{1 - \beta A}$$

$$A_f = - \frac{\alpha_0 \frac{A_{v0} L \phi}{1 + \frac{s}{\omega_p}}}{1 + \frac{\beta_0 A_{v0} L \phi}{1 + \frac{s}{\omega_p}}}$$

$$A_f = \frac{- \alpha_0 A_{v0} L \phi}{\left(1 + \frac{s}{\omega_p}\right) + \beta_0 A_{v0} L \phi} =$$

$$- \frac{\alpha_0 A_{v0} L \phi}{1 + \beta_0 A_{v0} L \phi} \cdot \frac{1}{1 + \frac{s}{\omega_p (1 + \beta_0 A_{v0} L \phi)}}$$


$$A_{f0} = \frac{- \alpha_0 A_{v0} L \phi}{1 + \beta_0 A_{v0} L \phi}$$

$$\omega_p' = \omega_p (1 + \beta_0 A_{v0} L \phi)$$

$$(PFB) A_f = \omega_p (1 + \beta_0 A_{v0} L \phi) \frac{- \alpha_0 A_{v0} L \phi}{1 + \beta_0 A_{v0} L \phi} =$$

$$(PGB)_{Af} = \alpha \underbrace{\omega_p A_{v0} \phi}_{(PGB)_A}$$

$$(PGB)_{Af} = \alpha (PGB)_A$$

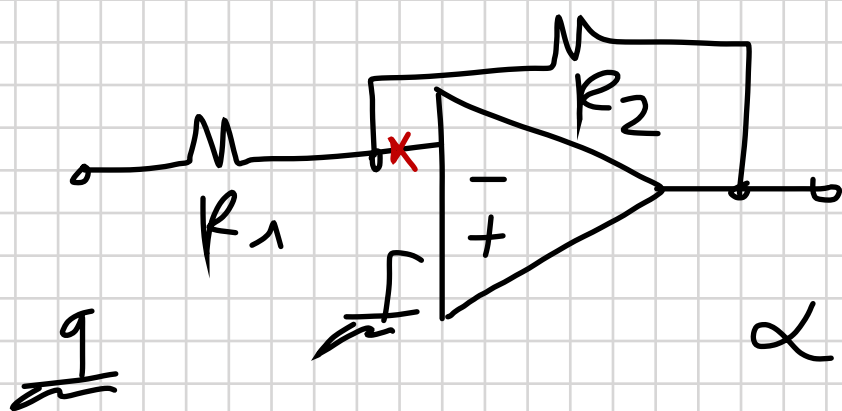

$$A_v = \frac{A_{v0} \phi}{1 + \frac{s}{\omega_p}}$$

$$\alpha = \frac{R_2}{R_1 + R_2}$$

$$\gamma = 0$$

$$\beta = \frac{R_1}{R_1 + R_2}$$



$$A = -\frac{A_{v0} \phi}{1 + \frac{s}{\omega_p}}$$

$$(PGB)_{Af} = \alpha (PGB)_A \quad (PGB)_A = \omega_p A_{v0} \phi$$


$$(PGB)_{Af} = \omega_p' = -\frac{R_2}{R_1}$$

$$\omega_p' \left(1 + \frac{R_2}{R_1}\right) = \frac{R_2}{R_1 + R_2} (\omega_p + A_{v0} \phi)$$
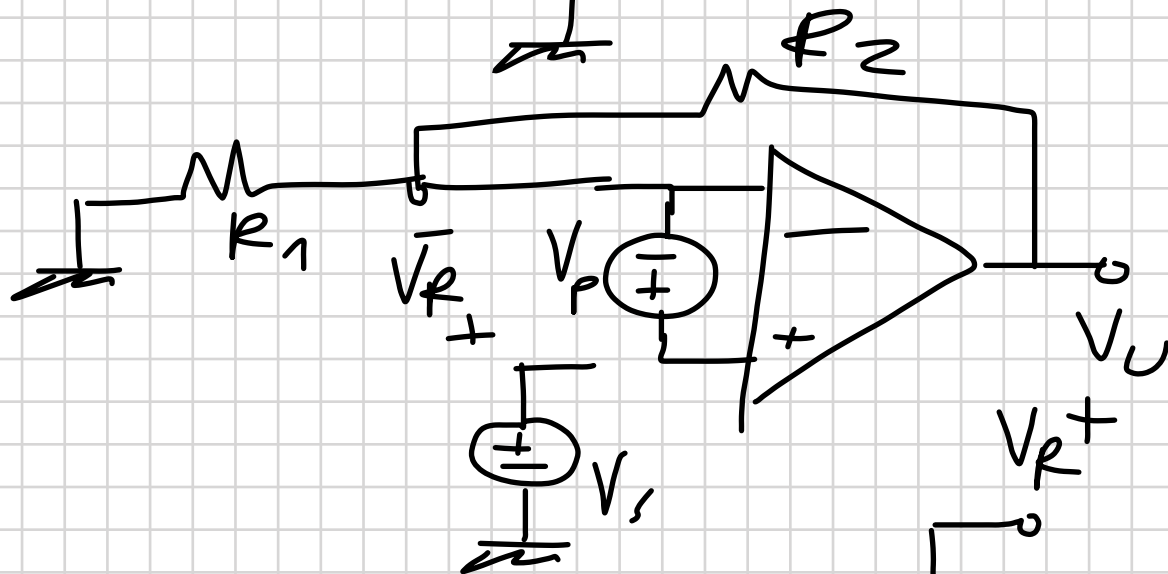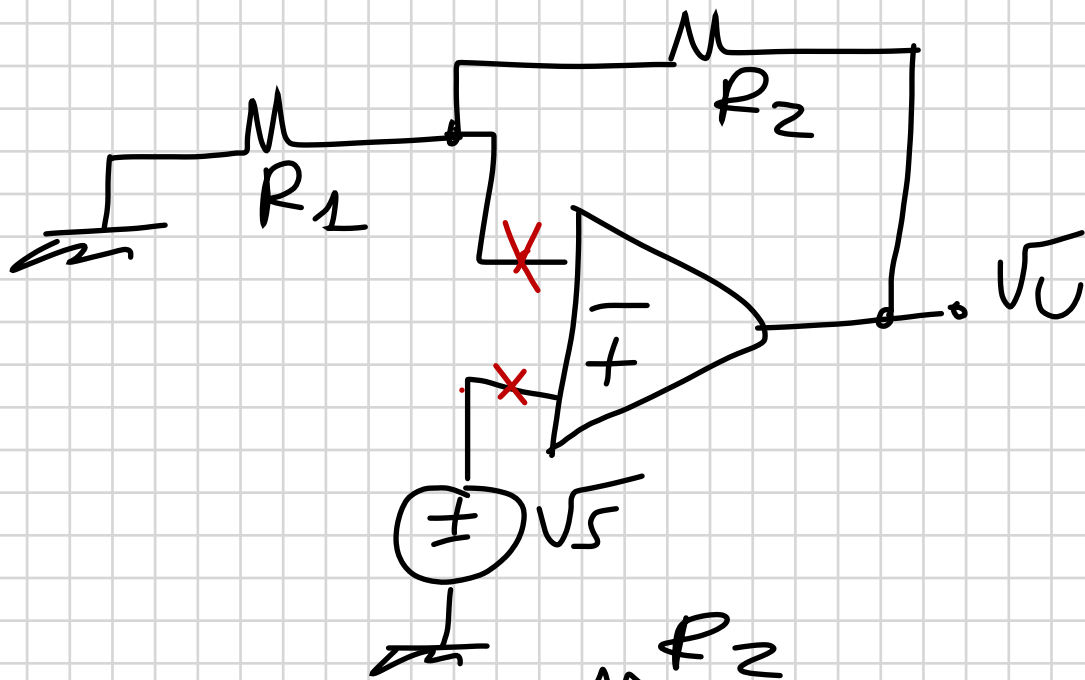
$$\omega_p' = \frac{R_2}{R_1 + R_2} \omega_p (A_{v0} \phi) \frac{R_1}{R_2}$$



$$\alpha = \frac{V_R}{V_S} \Big|_{V_P=0} = 1$$


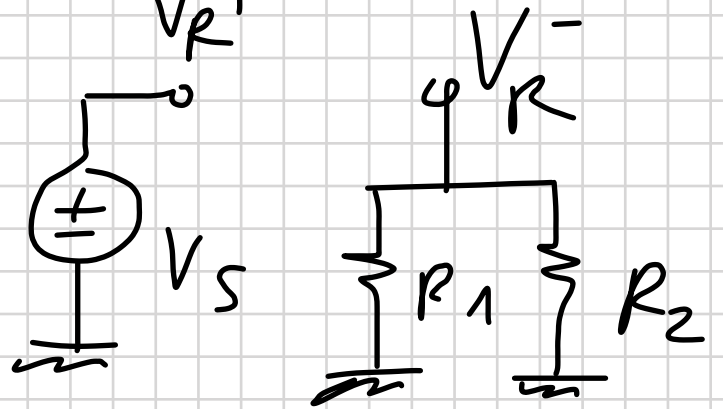


$$A_{f0} = \left(1 + \frac{R_2}{R_1}\right)$$

$$(PGB)_{\#} = A_{f0} \omega_p' = \alpha (PGB)_A =$$

$$A_{f0} \omega_p' = \underbrace{\omega_p}_{\omega_G} A_{vol} \phi \Rightarrow \omega_p' = \frac{\omega_G}{\left(1 + \frac{R_2}{R_1}\right)}$$

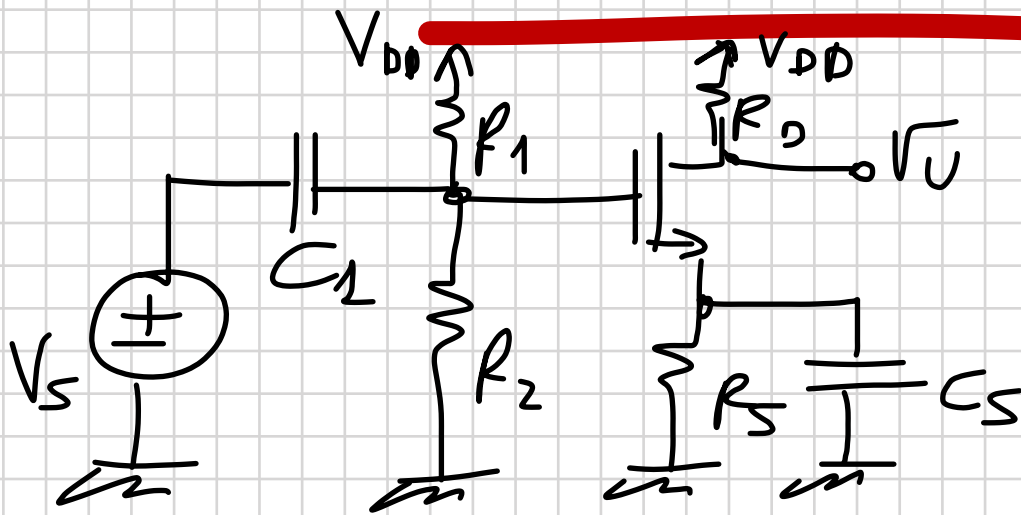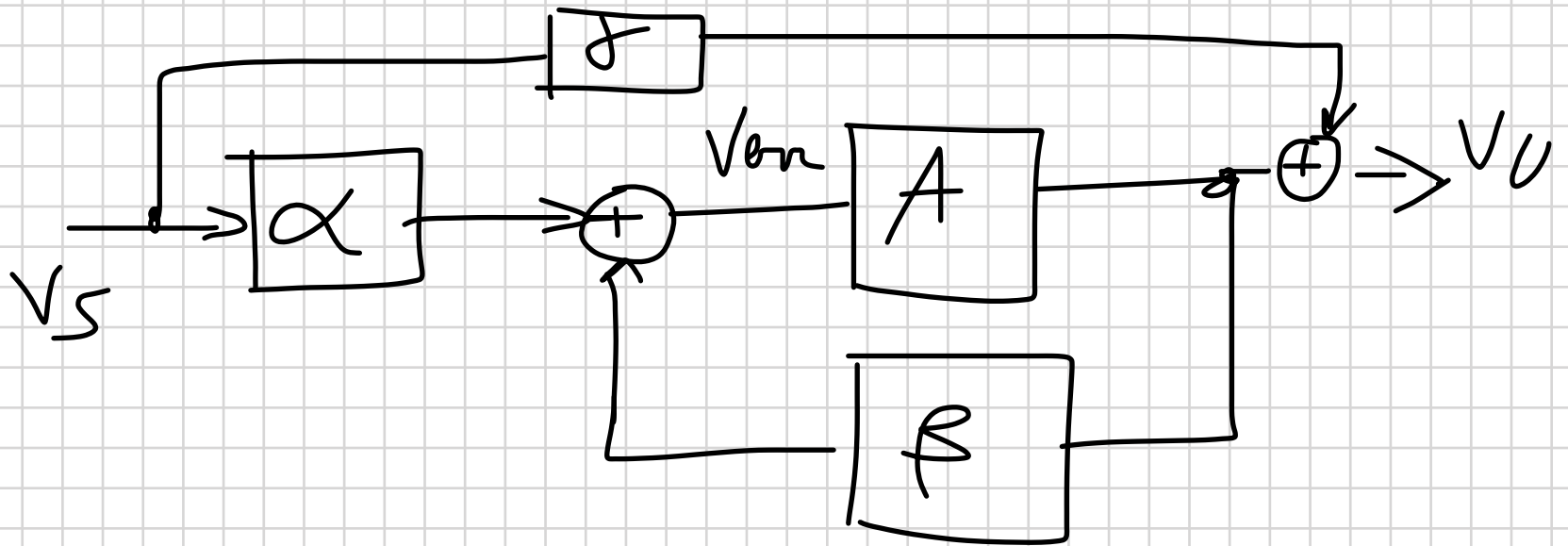
$$A_f = \frac{A_{f0}}{\left(1 + \frac{s}{\omega_p'}\right)}$$





$V_{DD} = 12V$
 $R_D = 1,8 k\Omega$
 $R_S = 0,2 k\Omega$
 $C_1 = 2 \mu F$
 $C_2 = 100 \mu F$

$g_m = 5 mS$

$R_1 || R_2 = 10 k\Omega$

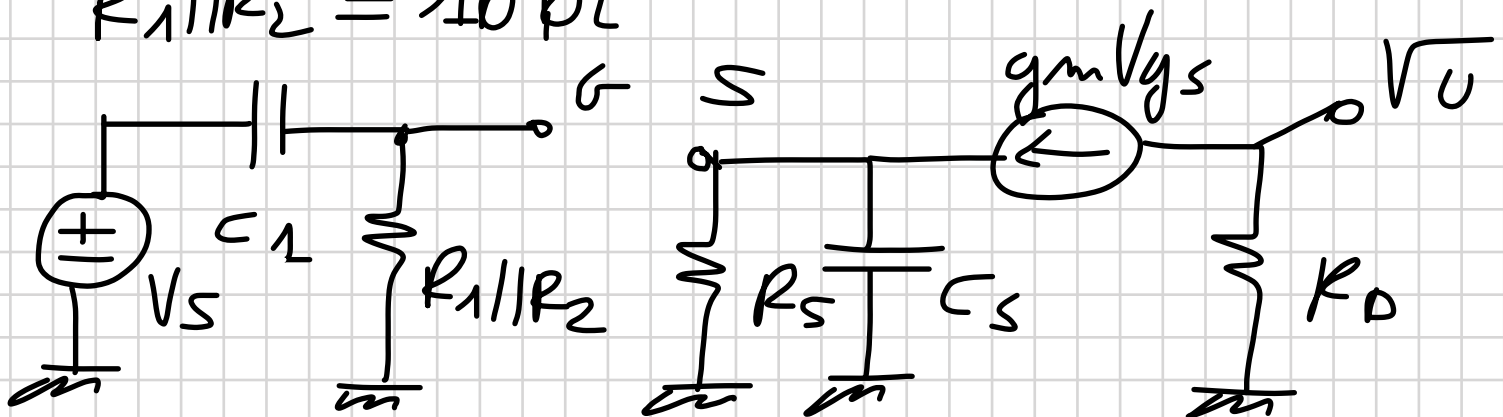

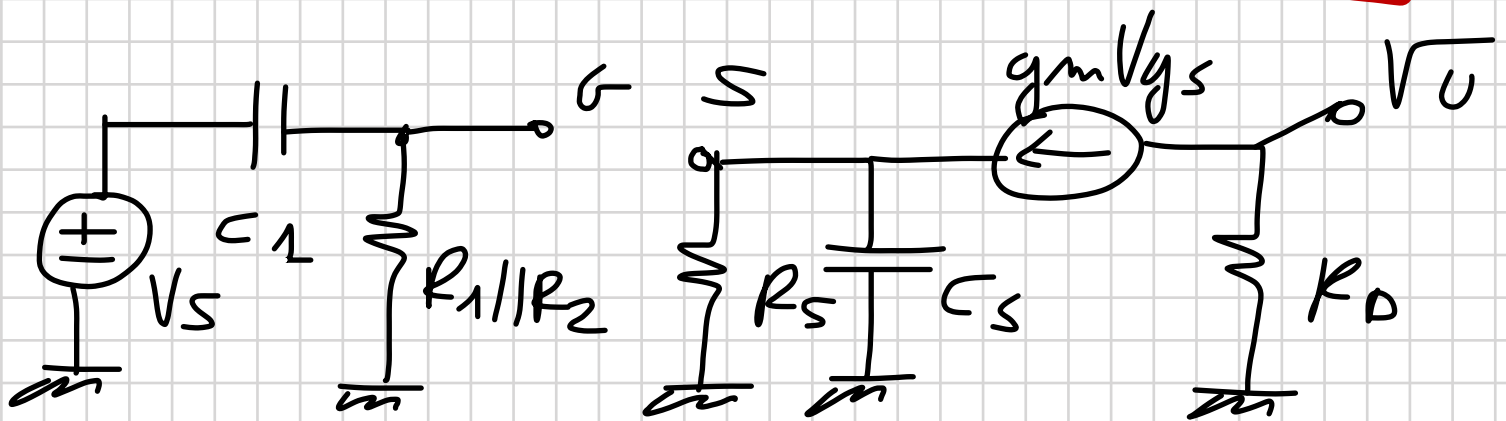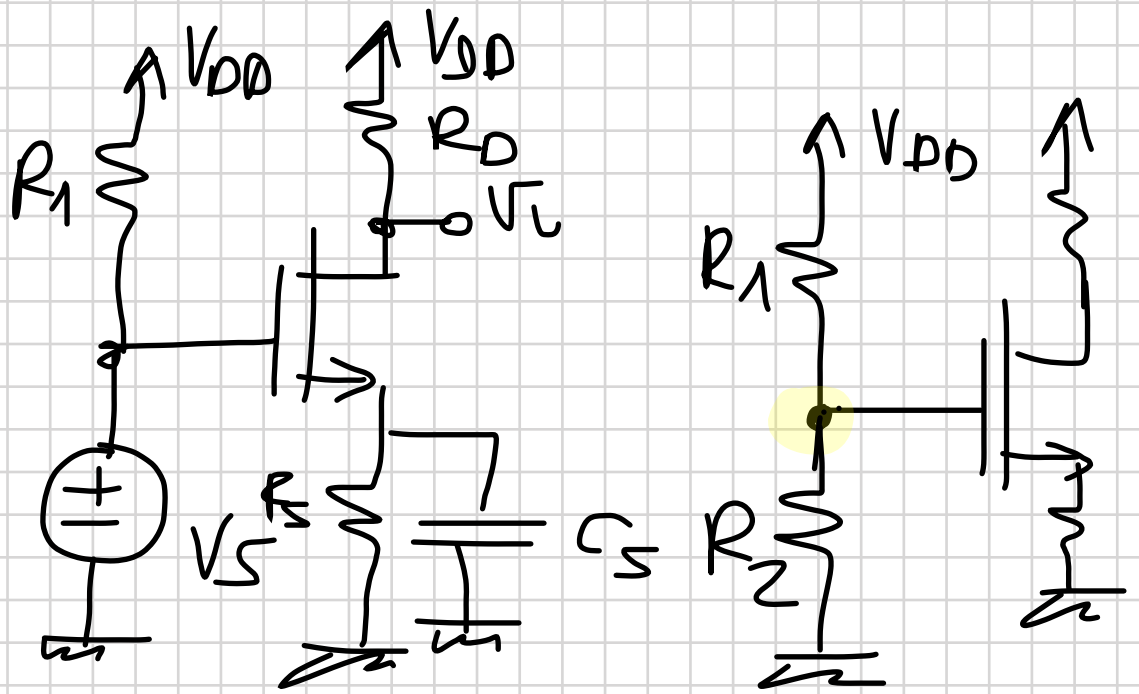

$$A_f = \frac{V_u}{V_s} = \frac{K s \left(1 + \frac{s}{\omega_0}\right)}{\left(\frac{s}{\omega_{p1}} + 1\right) \left(\frac{s}{\omega_{p2}} + 1\right)}$$


$$A_{f\infty} = -g_m R_D \quad \omega_0 = \frac{1}{R_S C_S}$$

$$A_{f\infty} = \frac{K \omega_{p1} \omega_{p2}}{\omega_0} \Rightarrow K = \frac{A_{f\infty} \omega_0}{\omega_{p1} \omega_{p2}}$$

$$\omega_0 = 50 \text{ rad/sec}$$



$$\omega_{p2} = 100 \text{ rad/sec}$$

$$\omega_{p2} = 100 \text{ rad/sec}$$


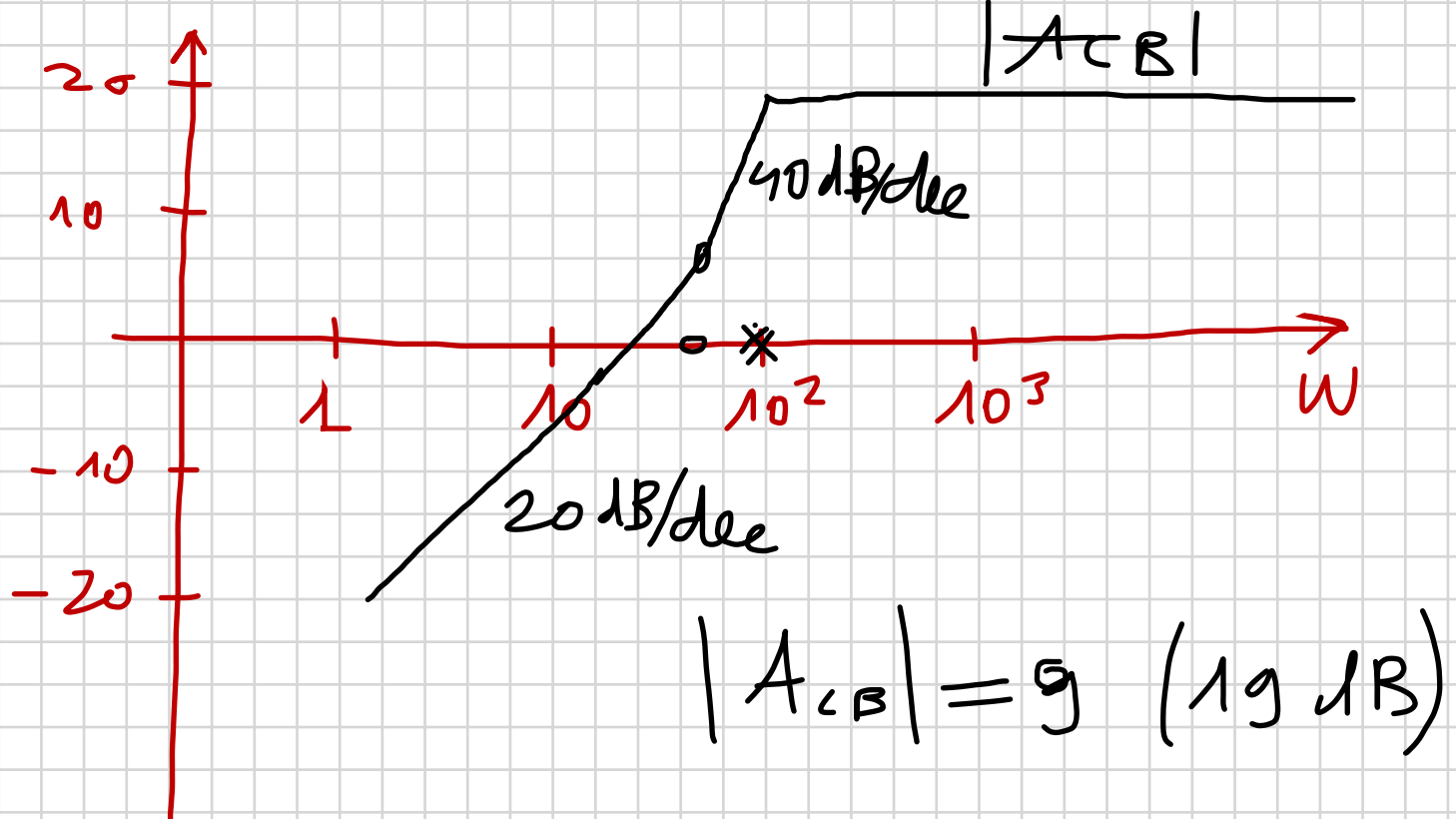


$$r_i = 1 \text{ m}\Omega \quad r_o = 1 \Omega$$

$$r_f = 100 \text{ k}\Omega$$

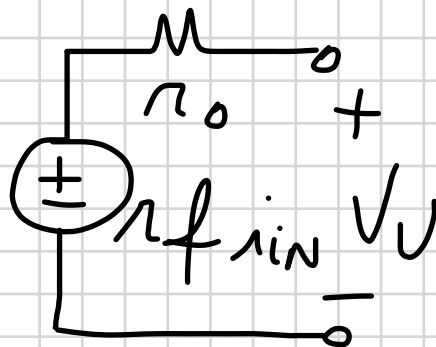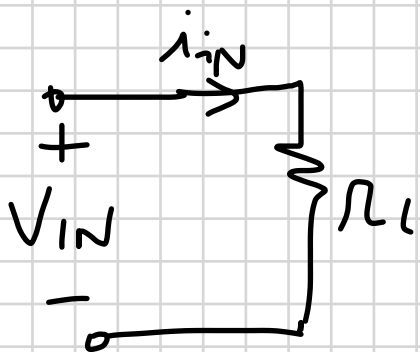

$$f_f = 10$$

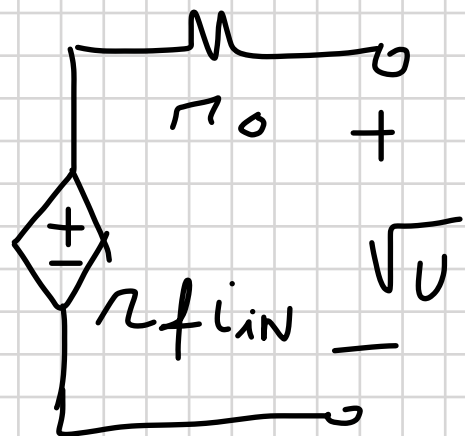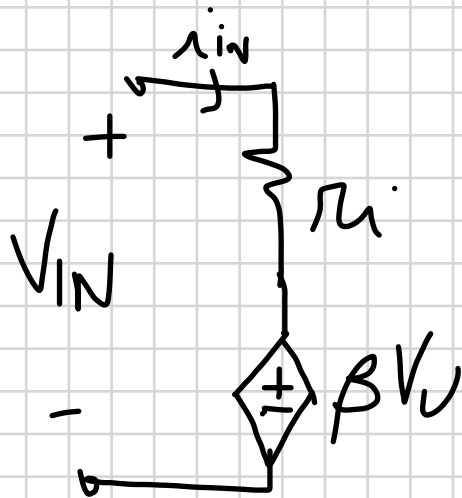

$$V_U = r_f \frac{V_{IN} - \beta V_U}{r_i} \Rightarrow V_U \left(1 + \beta \frac{r_f}{r_i} \right) = \frac{r_f}{r_i} V_{IN}$$

$$f_f = 1 / \left(\frac{r_i}{r_f} + \beta \right) = 10 \Rightarrow \beta < 0,1$$


$$V_{in} = \frac{1}{f_i} i_{in}$$

$$i_{in} = \frac{V_{in} - \beta V_u}{r_i} = \frac{V_{in} (1 - \beta f_f)}{r_i}$$

$$\frac{V_{in}}{i_{in}} = \frac{r_i}{1 - \beta f_f} \approx 10 \text{ k}\Omega$$

$$\omega_{p1} = \frac{1}{C_1 R_{V_{C1}}} \quad R_{V_{C1}} = R_1 // R_2$$
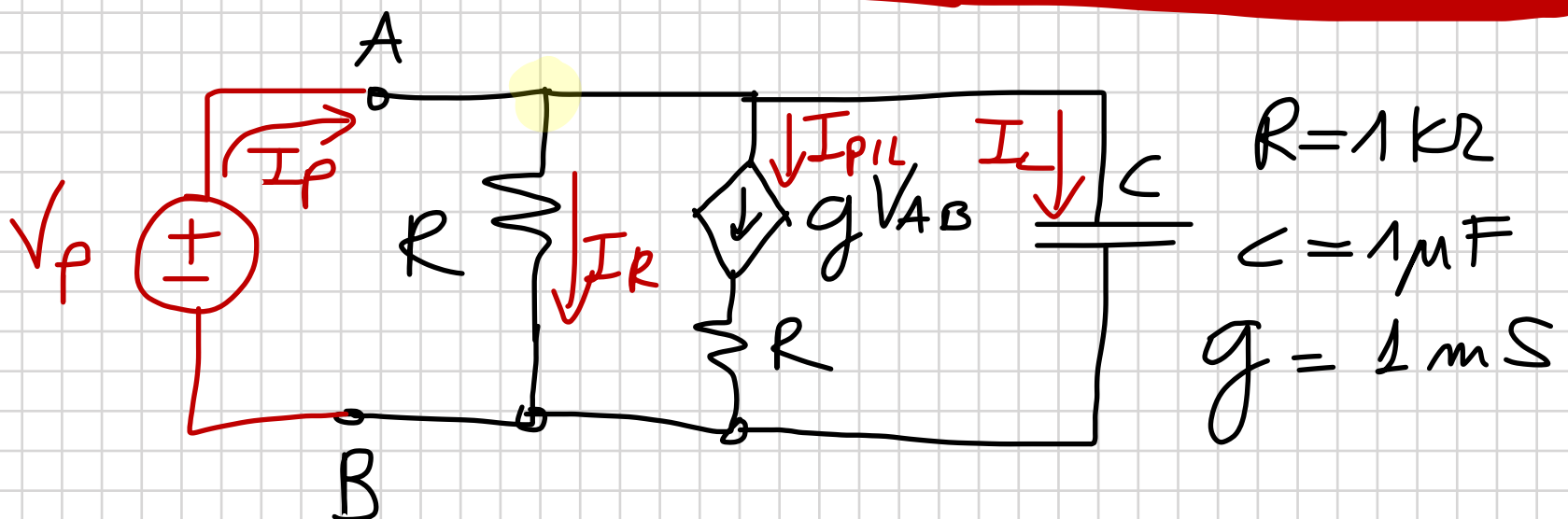
$$\omega_{p2} = \frac{1}{C_2 R_{V_{C2}}} \Rightarrow R_{V_{C2}} = R_s // \frac{1}{g_m}$$




$$Z_{AB} = \frac{V_p}{I_p} \quad I_p = I_R + I_{PIL} + I_C$$

$$I_R = \frac{V_p}{R}; \quad I_{PIL} = g V_p; \quad I_C = C_s V_p$$

$$\frac{V_p}{I_p} = \frac{1}{\frac{1}{R} + g + sC} = \frac{R_0}{\frac{s}{\omega_p} + 1}$$
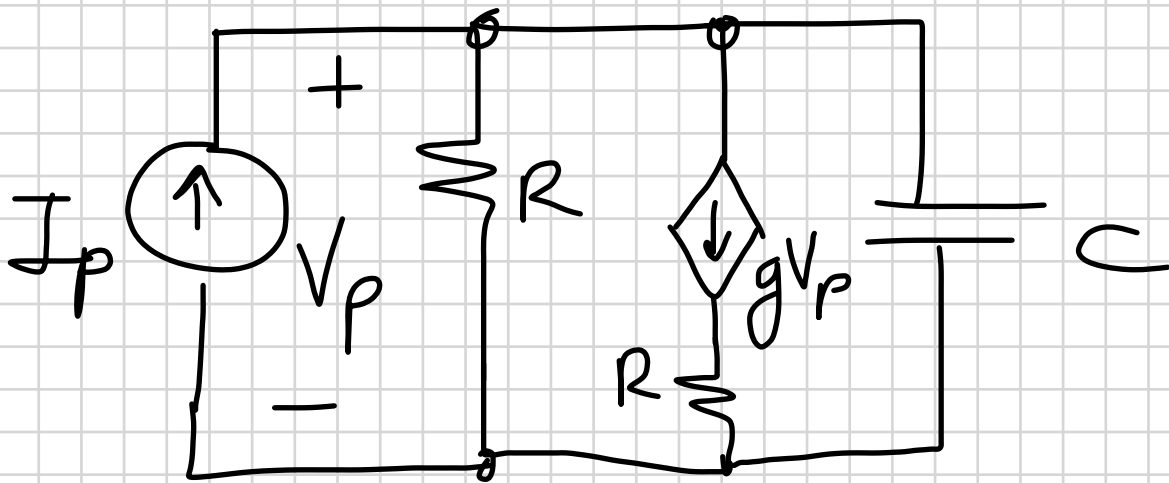
$$R_0 = \frac{R}{1 + Rg} \quad \omega_p = \frac{1}{R_0 C}$$





$$Z = \frac{R_0}{1 + \frac{s}{\omega_p}} \quad R_0 = R \parallel \frac{1}{g}$$

$$\omega_p = \frac{1}{R_0 C} \quad R_{v_c} = R_0$$

$$V_Z = 12V \quad ; \quad r_Z = 0,2 \Omega @ I_Z = 2A$$

$$r_{ZK} = 100 \Omega @ I_{ZK} = 0,1A$$

$$V_{IN} = 16 \div 20V$$

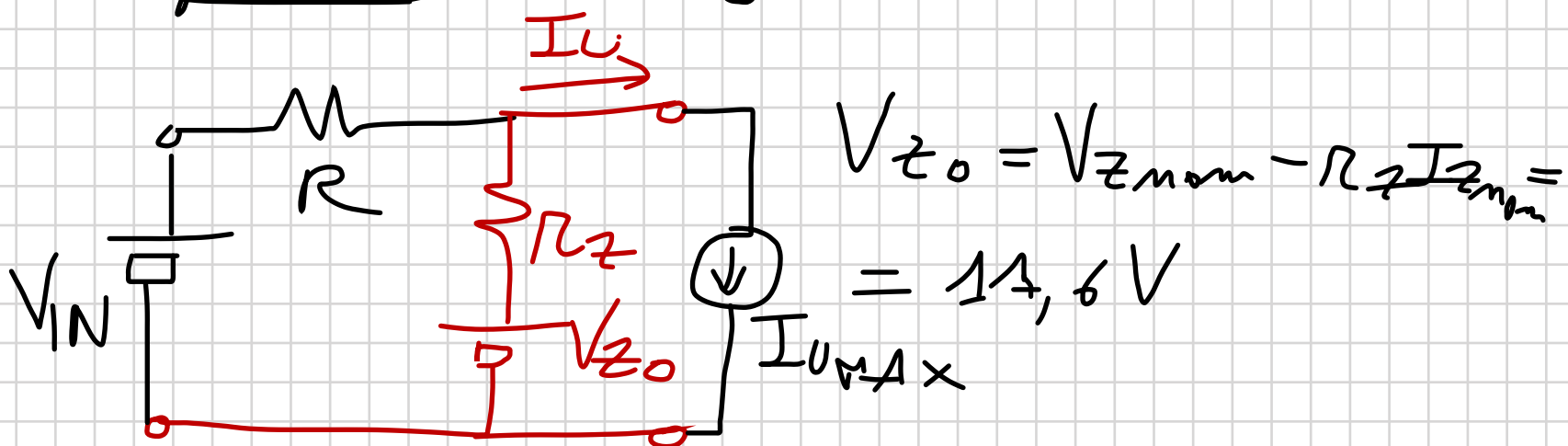
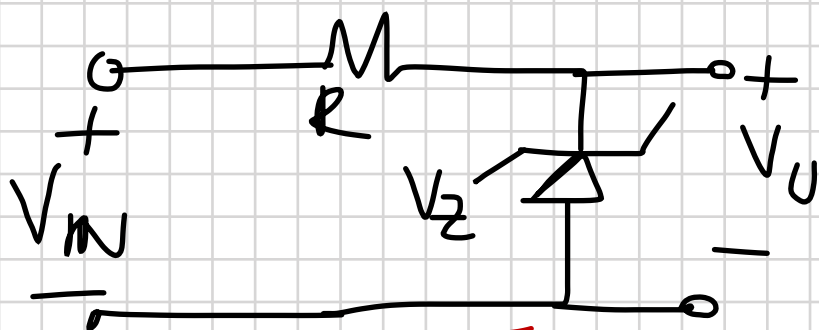


$$P_{Z \text{ MAX}} = V_{Z0} I_{Z \text{ MAX}} + r_Z I_{Z \text{ MAX}}^2$$



$$I_{Z \text{ MAX}} = \frac{(V_{IN})_{\text{MAX}} - V_{Z0}}{R + r_Z}$$

$$I_{ZK} = \frac{(V_{IN})_{\text{MIN}} - V_{Z0}}{R + r_Z} - I_{U \text{ MAX}} \frac{R}{R + r_Z}$$
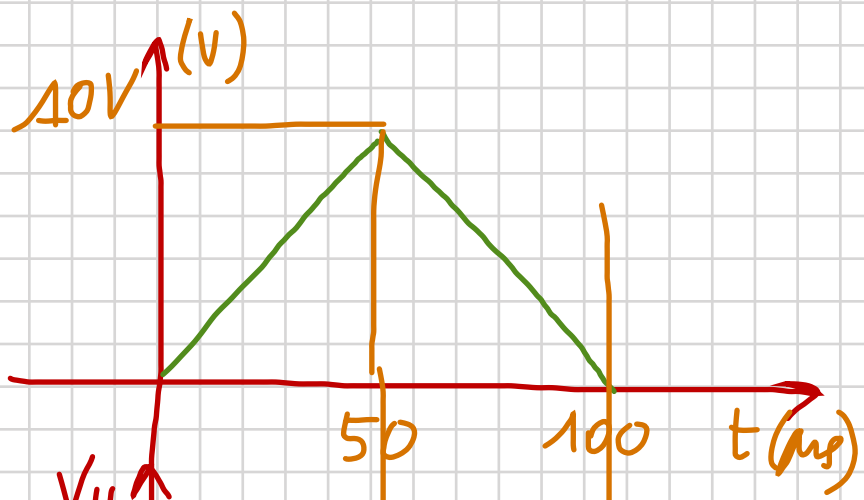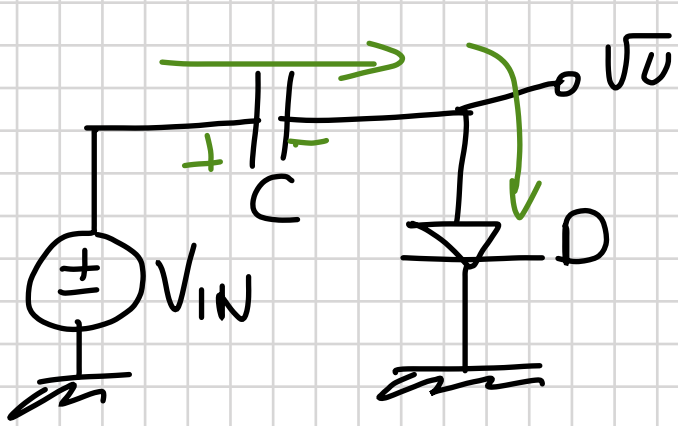
$$R = \frac{(V_{IN})_{\text{MIN}} - V_{Z0} - r_Z I_{ZK}}{I_{ZK} + I_{U \text{ MAX}}} = 3,09 \Omega$$



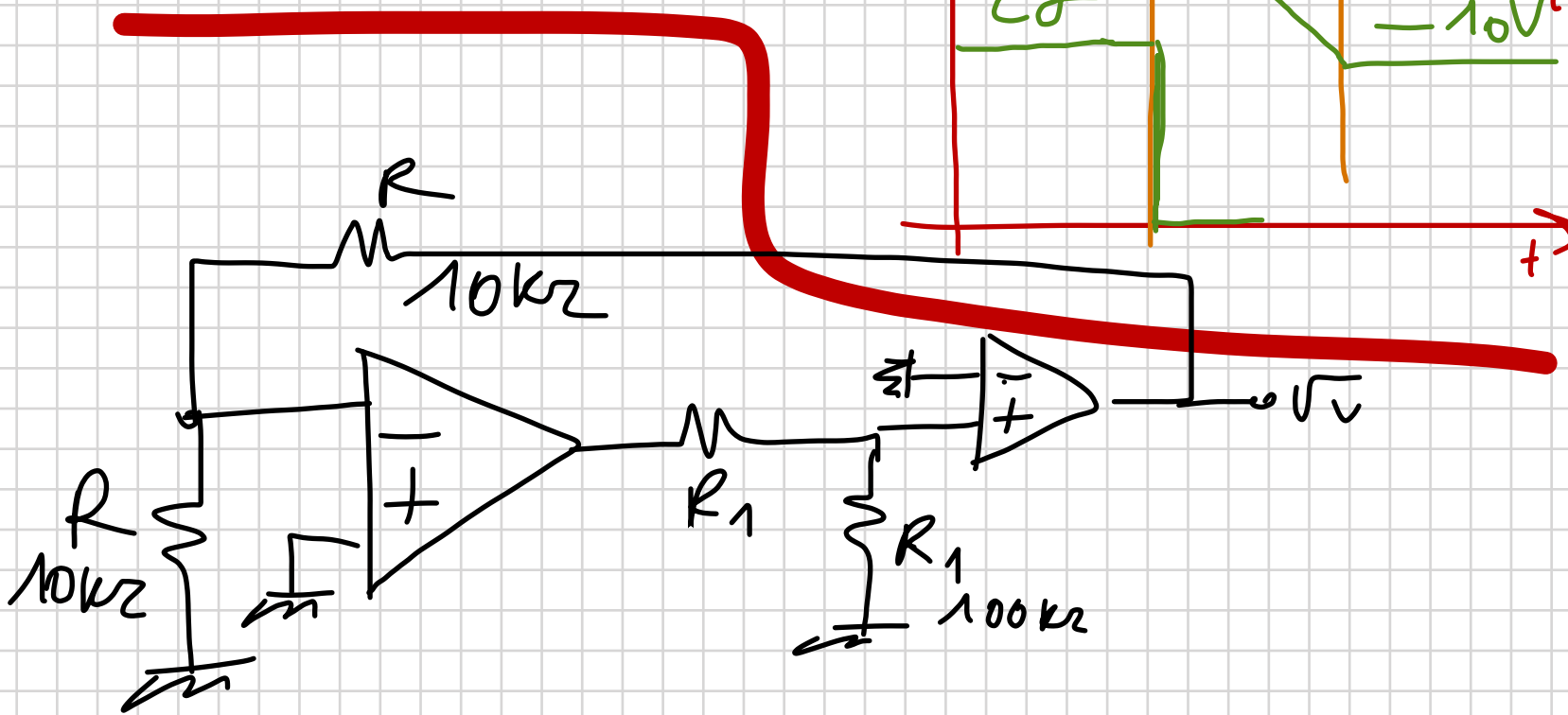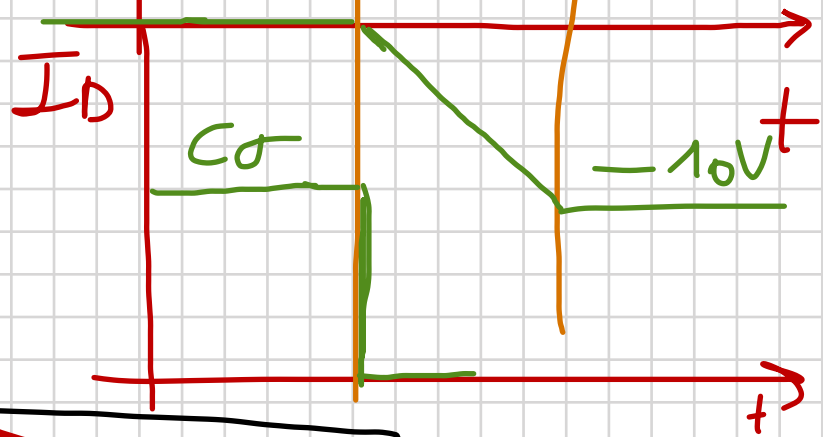
$$i_D = C \frac{dV_{IN}}{dt} = C \sigma$$



$$|V_{io}| < 1 \text{ mV} \quad I_B = 10 \mu A = \frac{I_1 + I_2}{2}$$

$$|I_o| = |I_1 - I_2| < 2 \text{ nA}$$

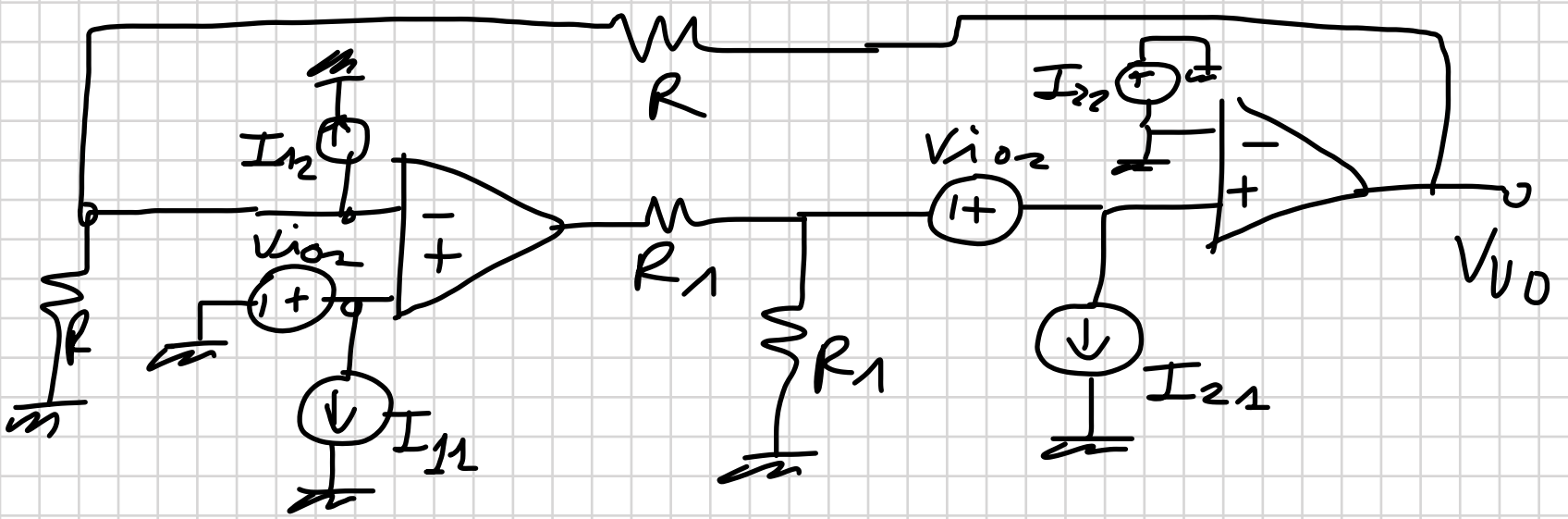


$$V_{U_{I_{11}}} = 0$$

$$V_{U_{V_{io}}} = \left(1 + \frac{R}{R}\right) V_{io}$$

$$V_{U_{I_{12}}} = R I_{12}$$
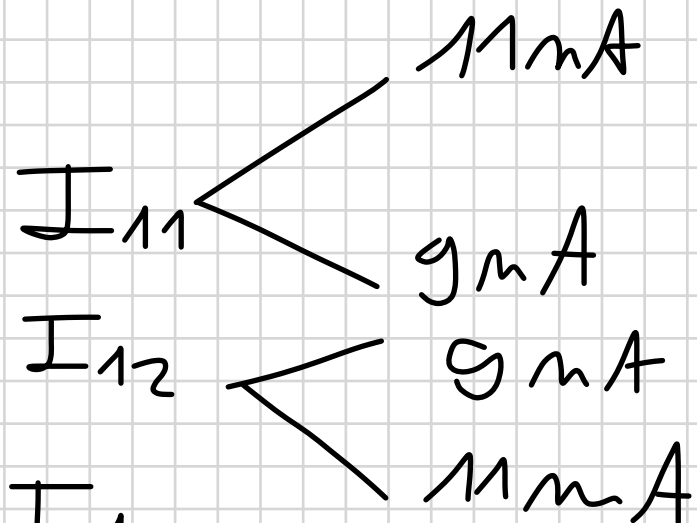
$$V_U = \left(1 + \frac{R}{R}\right) V_{io} + R I_{12}$$



$$I_{12} = 11 \text{mA} \quad V_{io} = 1 \text{mV}$$

$$V_{U_{\text{MAX}}} = 2, 11 \text{mV}$$