
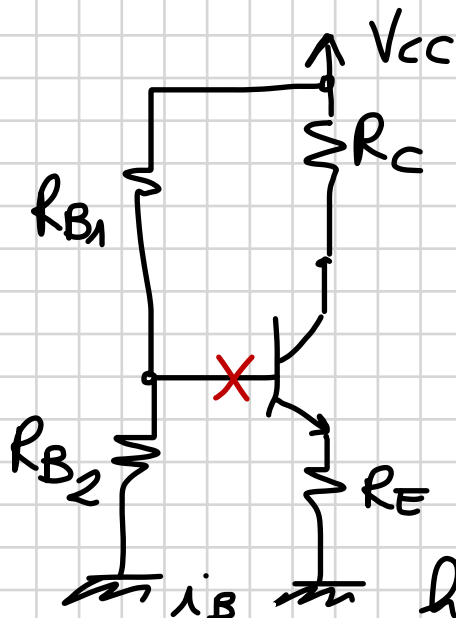


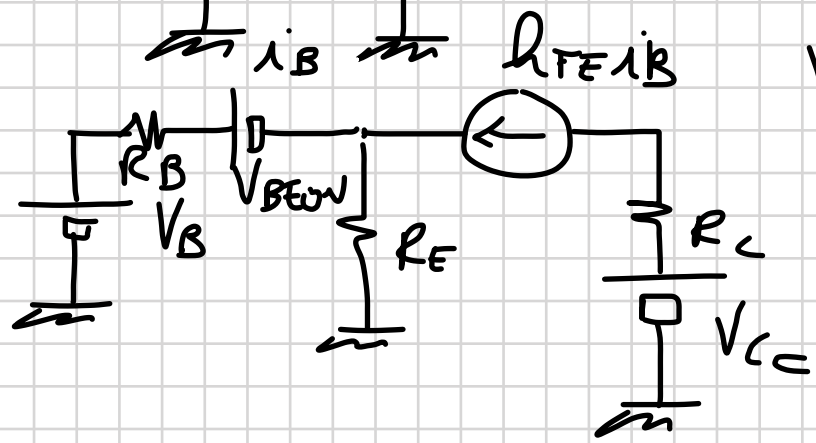- $h_{FE} = 100$
- $\beta_{bb'} = 100\Omega$
- $R_C = 2\text{ k}\Omega$
- $R_E = 0,5\text{ k}\Omega$
- $C_E R_{B1} = 10\text{ k}\Omega$
- $R_{B2} = 2\text{ k}\Omega$
- $C_E = 10\text{ }\mu\text{F}$
- $C_1 \rightarrow +\infty$



$$V_B = \frac{R_{B2} V_{CC}}{R_{B1} + R_{B2}}$$

$$R_B = R_{B1} \parallel R_{B2}$$



$$I_B = \frac{V_B - V_{BE(on)}}{R_B + (h_{FE} + 1) R_E} = 24,92\text{ }\mu\text{A}$$


$$I_C = h_{FE} I_B = 2,492\text{ mA}$$

$$I_E = I_C + I_B = (h_{FE} + 1) I_B = 2,517\text{ mA}$$


$$V_{CE} = V_C - V_E = \underbrace{V_{CC} - R_C I_C}_{V_C} - \underbrace{R_E I_E}_{V_E} = 5,758\text{ V}$$

$$h_{fe} = h_{FE}$$
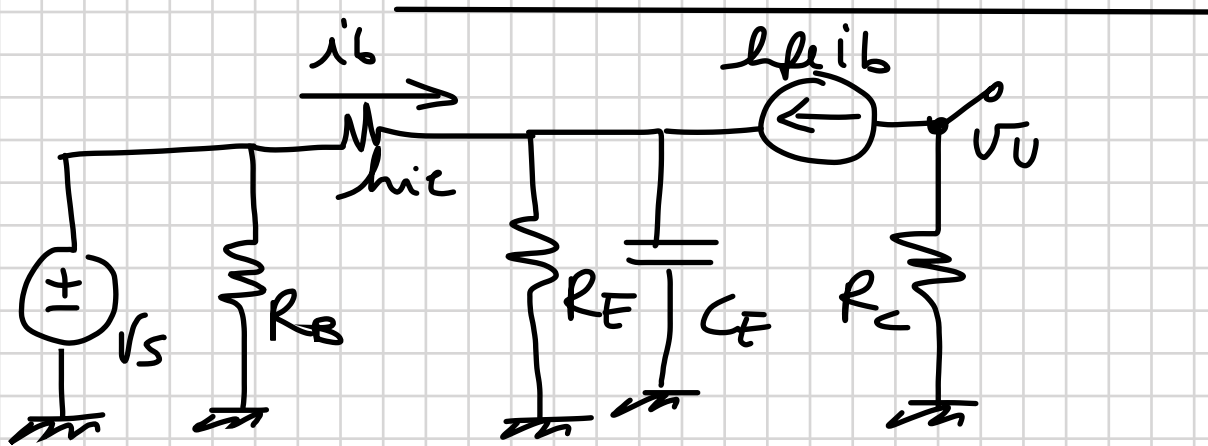
$$h_{ie} = r_{bb'} + \frac{V_T}{I_C} h_{fe} = 1143 \Omega$$


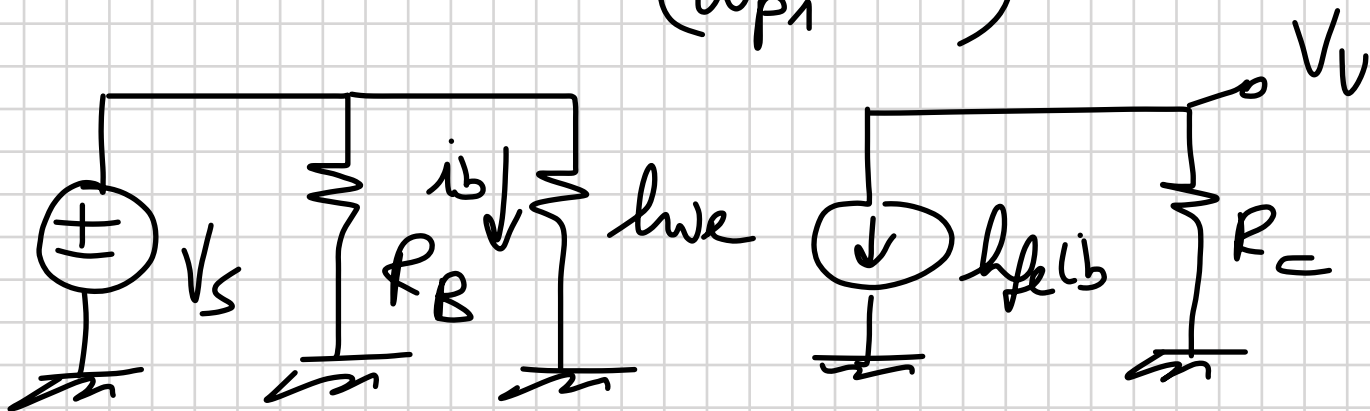
$$A_f(s) = \frac{\sqrt{U}}{\sqrt{s}} = \frac{1}{\left(\frac{s}{\omega_{p1}} + 1\right)}$$




$$V_u = -h_{fe} R_C i_b \quad i_b = \frac{V_s}{h_{ie}}$$

$$\frac{V_u}{V_s} = A_{f0} = - \frac{h_{fe} R_C}{h_{ie}} = -g_m R_C$$

$$A_f = \frac{A_{f0} \left(\frac{s}{\omega_0} + 1\right)}{\left(\frac{s}{\omega_{p1}} + 1\right)}$$


$$A_f = \frac{A_{f0} \left(\frac{s}{\omega_0} + 1 \right)}{\left(\frac{s}{\omega_{p1}} + 1 \right)}$$

$$A_f(s \rightarrow 0) = A_{f0}$$

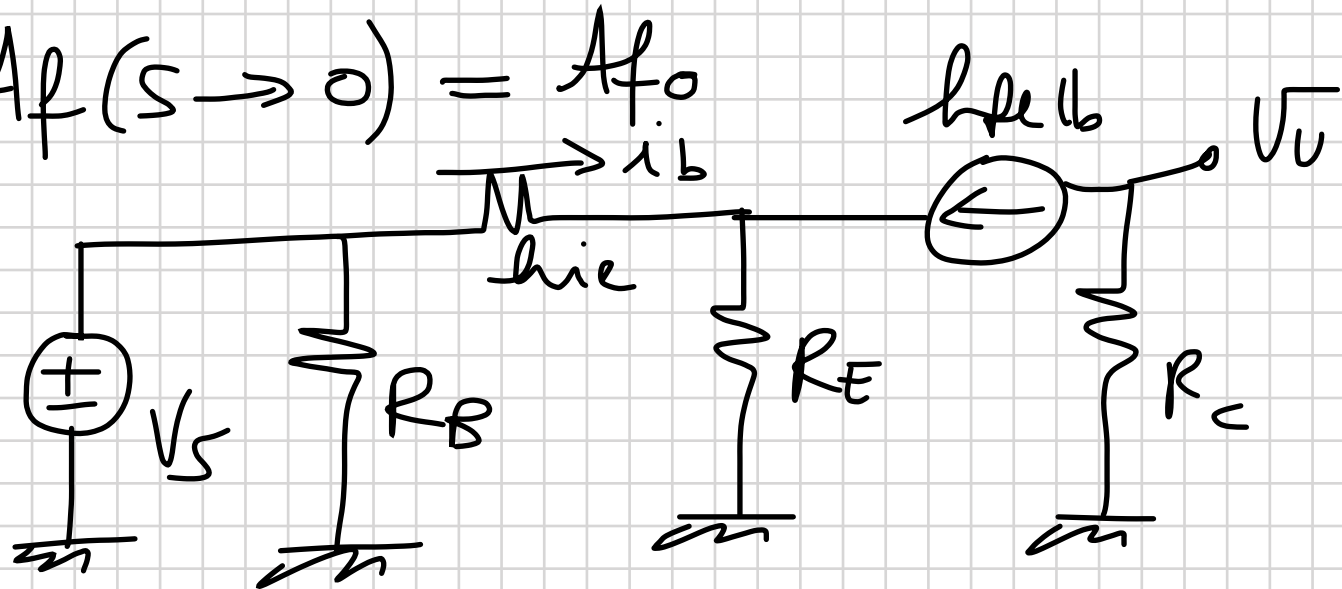

$$A_{f0} = \frac{V_U}{V_S} = \frac{-R_C h_{fe}}{R_E (h_{fe} + 1) + h_{ie}} = -3884$$
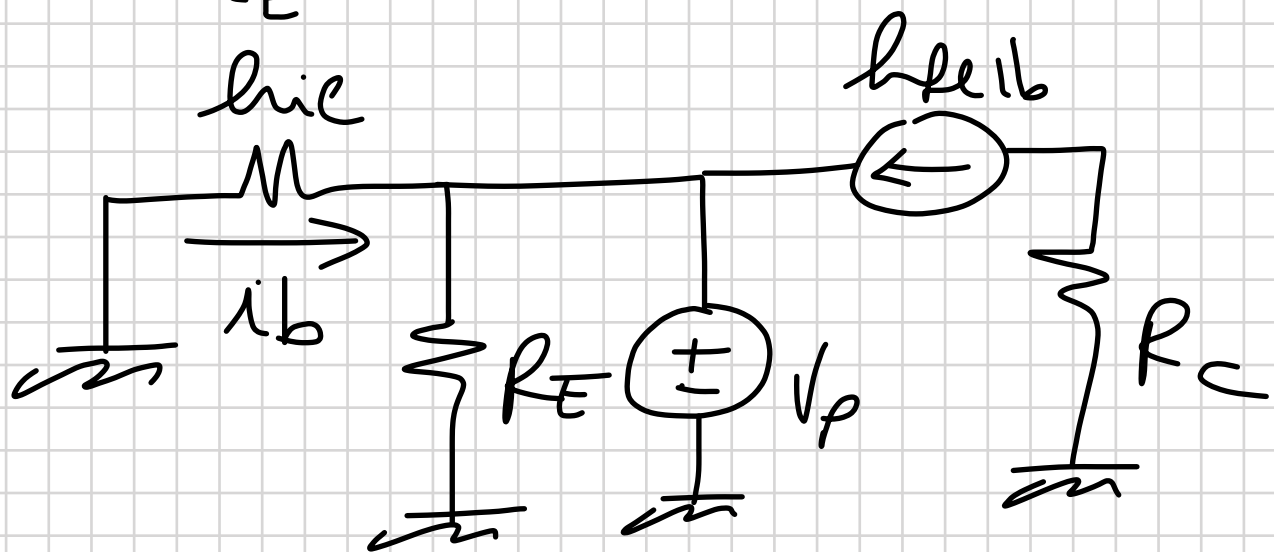
$$\omega_{p1} = \frac{1}{R_{VCE} C_E} \quad ; \quad R_{VCE} =$$



$$R_{VCE} = R_E // \frac{h_{ie}}{h_{fe} + 1}$$

$$A_{f\infty} = \frac{A_{f0} \omega_{p1}}{\omega_0}$$

$$A_{f\infty} = -\frac{h_{fe} R_c}{h_{ie}} = -200$$


$$A_{f0} = -3,884$$

$$\omega_0 = \frac{A_{f0} \omega_{p1}}{A_{f\infty}} \Rightarrow f_0 = \frac{\omega_0}{2\pi} = 159 \text{ kHz}$$

$$f_{p1} = \frac{\omega_{p1}}{2\pi} = 8,19 \text{ kHz}$$

$$R_E \parallel \frac{1}{C_E S} \rightarrow +\infty$$

$$\omega_0 = \frac{1}{R_E C_E}$$

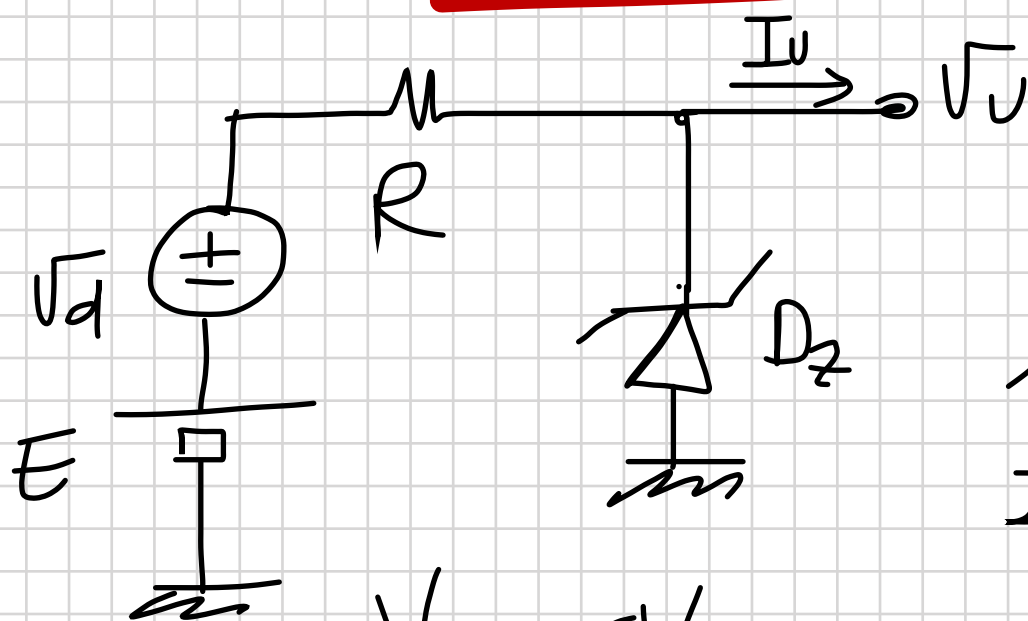


$$10 \text{ V} < E < 12 \text{ V}$$

$$I_u < 100 \text{ mA}$$

$$V_z = 6 \text{ V}, r_z = 4 \Omega @ I_z = 50 \text{ mA}$$
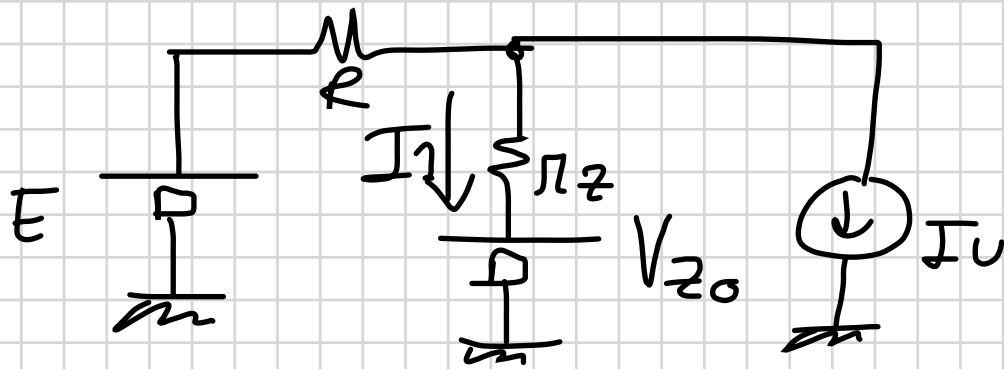
$$r_{zk} = 100 \Omega @ I_{zk} = 1 \text{ mA}$$



$$r_z = 4\Omega \quad V_{z0} = V_z - r_z I_z = 5,8V$$

$$I_1 > 4 I_{zK} = 4mA$$

$$E = E_{MAX} = 12V \quad \wedge \quad I_U = I_{UMAX} = 100mA$$

$$P_E = E_{MAX} I_{EMAX}$$


$$I_{EMAX} = \frac{E - V_{z0}}{R + r_z} + \frac{r_z}{r_z + R} I_U$$

$$P_E = E_{MAX} \left(\frac{E - V_{z0}}{R + r_z} + \frac{r_z}{r_z + R} I_U \right)$$

$$E = E_{min} ; \quad I_U = I_{UMAX}$$

$$I_1 = \frac{E_{min} - V_{z0}}{R + r_z} - \frac{R}{R + r_z} I_U > 4 I_{zK}$$

$$R = 40,23\Omega$$

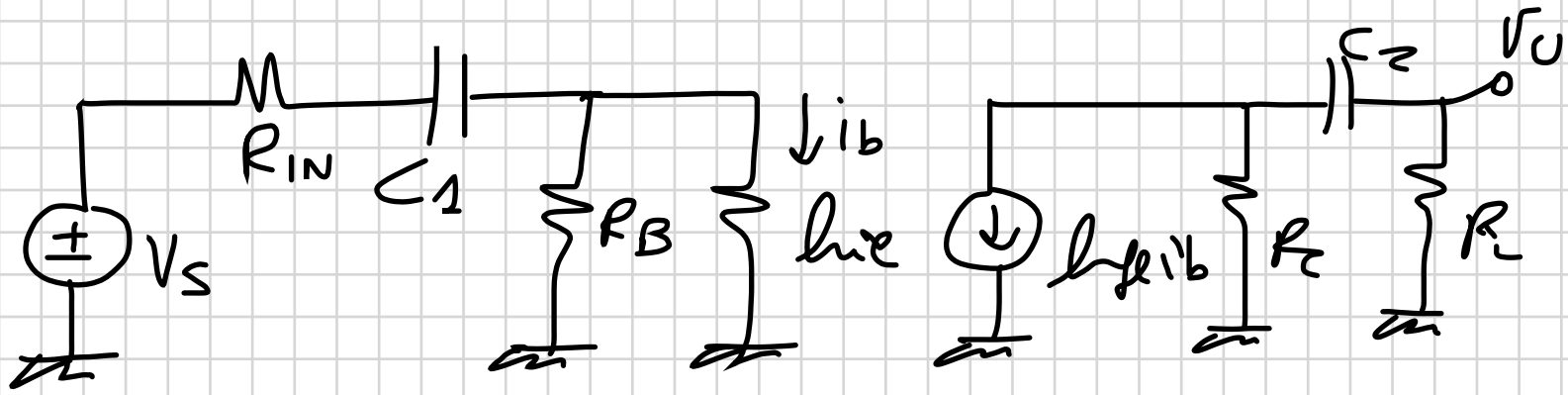


$$A_f(s) = \frac{V_U}{V_S} = \frac{K s^2}{\left(\frac{s}{\omega_{p1}} + 1\right) \left(\frac{s}{\omega_{p2}} + 1\right)}$$


$$\omega_{p1} = \frac{1}{C_1 R_{Vc1}} \quad R_{Vc1} = R_{IN} + R_B // h_{ie}$$


$$\omega_{p2} = \frac{1}{C_2 R_{Vc2}} \quad R_{Vc2} = R_C + R_L$$
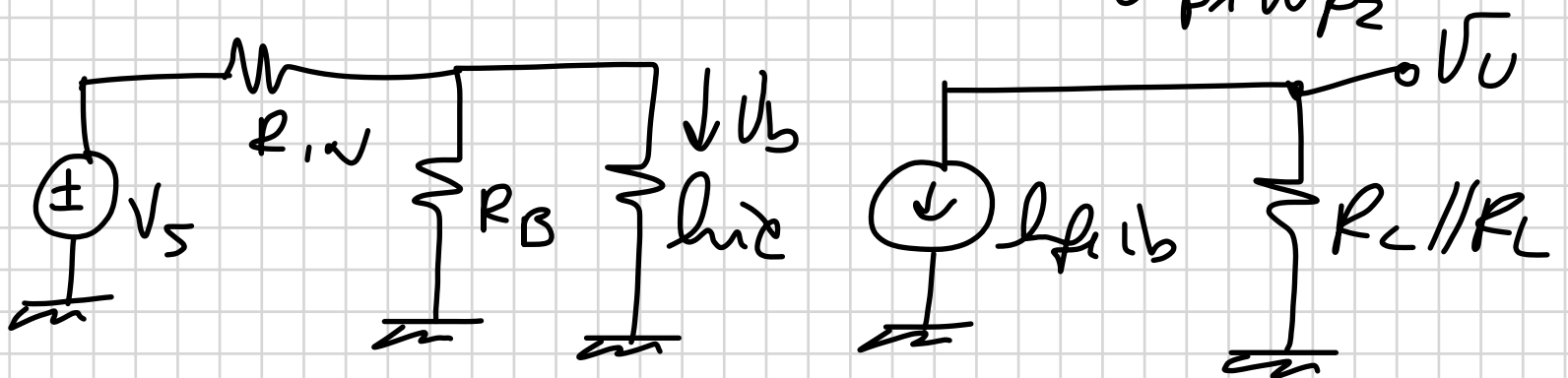
$$A_{f\infty} = K \omega_{p1} \omega_{p2} \Rightarrow K = \frac{A_{f\infty}}{\omega_{p1} \omega_{p2}}$$


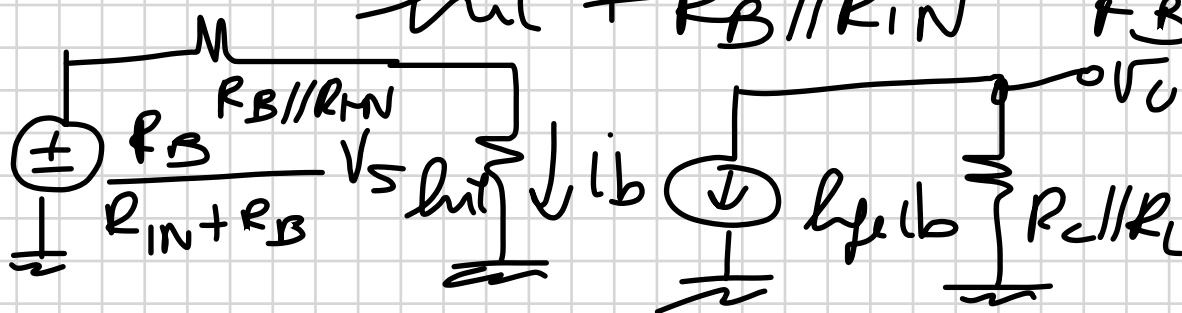
$$A_{f\infty} = - \frac{R_C // R_L h_{fe}}{h_{ie} + R_B // R_{IN}} \cdot \frac{R_B}{R_B + R_{IN}}$$



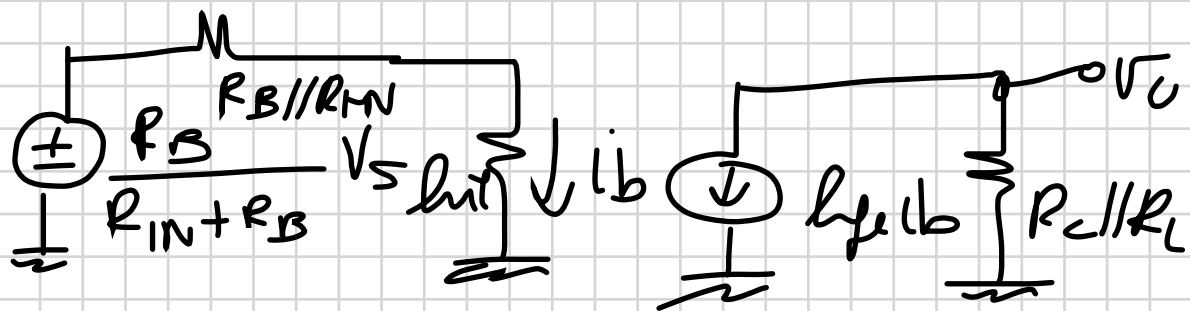

$$V_U = -R_C // R_L h_{fe} i_b$$

$$i_b = \frac{V_s R_B}{R_B + R_{IN}} \cdot \frac{1}{R_B // R_{IN} + h_{ie}}$$