


$$H(s) = \frac{1}{\frac{s^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1}$$

$$H(j\omega) = \frac{1}{1 - \frac{\omega^2}{\omega_0^2} + \frac{j\omega}{Q\omega_0}}$$


$$|H(j\omega)|^2 = \frac{1}{\frac{\omega^2}{Q^2\omega_0^2} + \left(1 - \frac{\omega^2}{\omega_0^2}\right)^2}$$

$$|H(j\omega_0)|^2 = \frac{1}{\frac{1}{Q^2}} = Q^2$$

$$|H(j\omega_0)| = Q$$


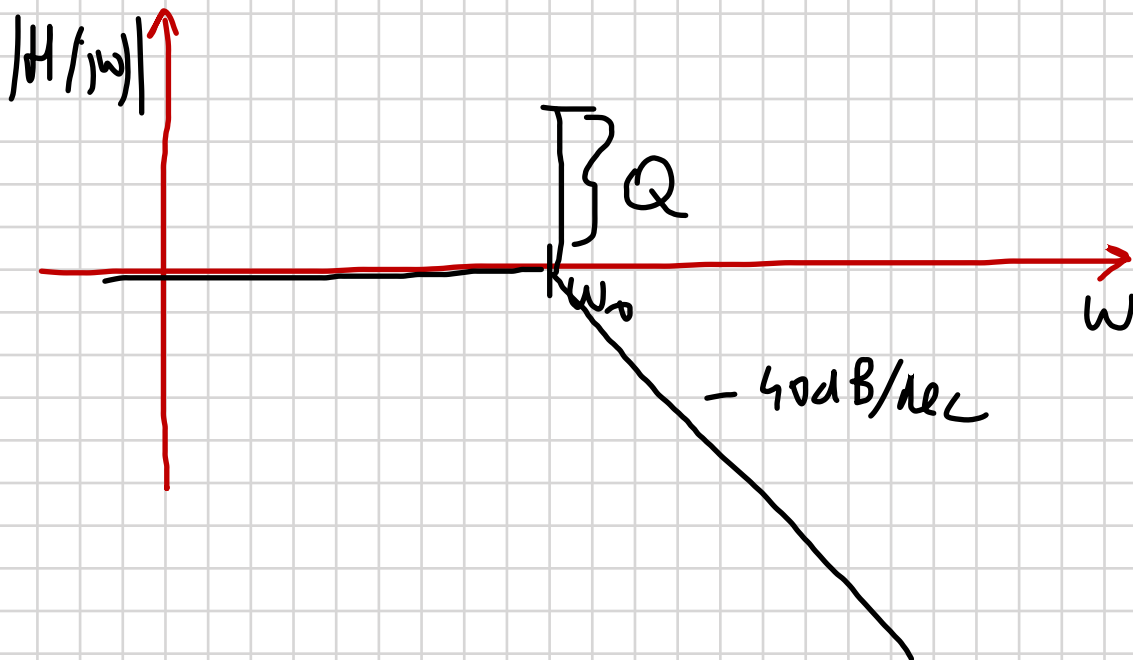

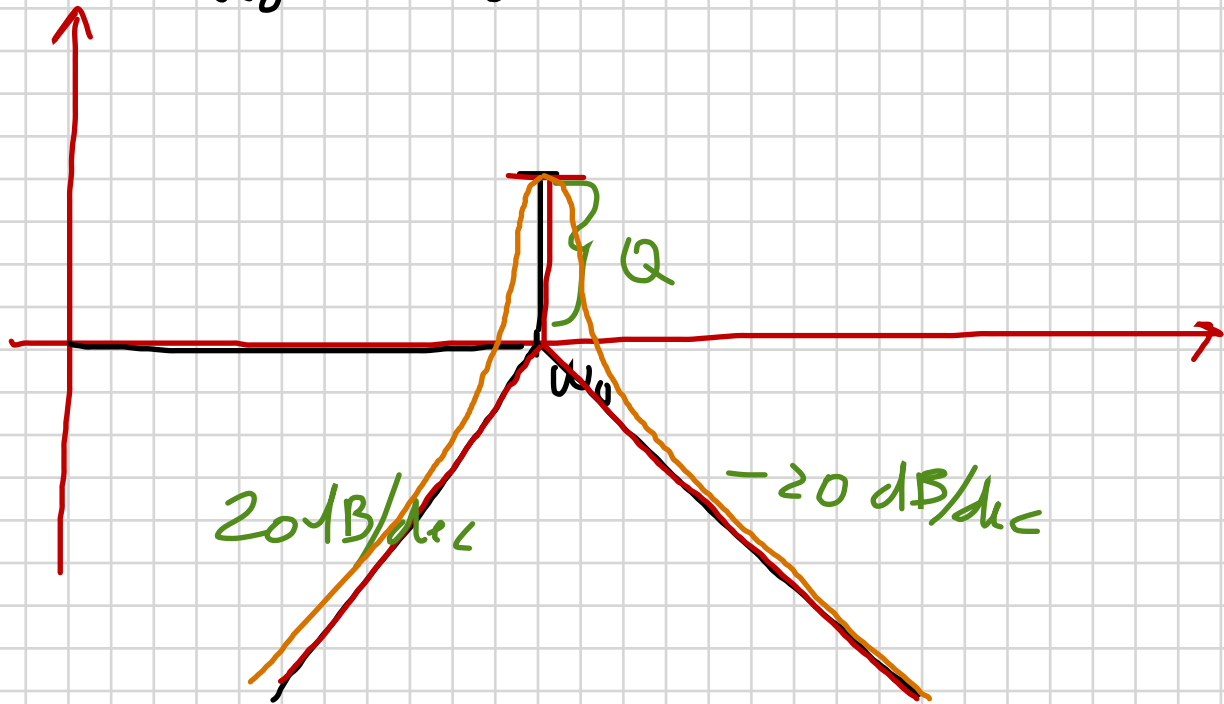
$$H(s) = \frac{kS}{\frac{s^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1}$$




$$H(s) = \frac{s^2}{\omega_0^2} + 1$$

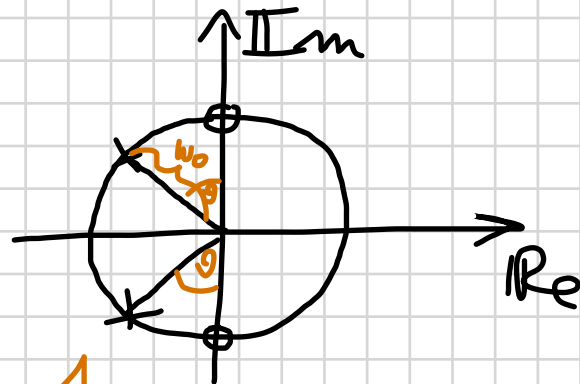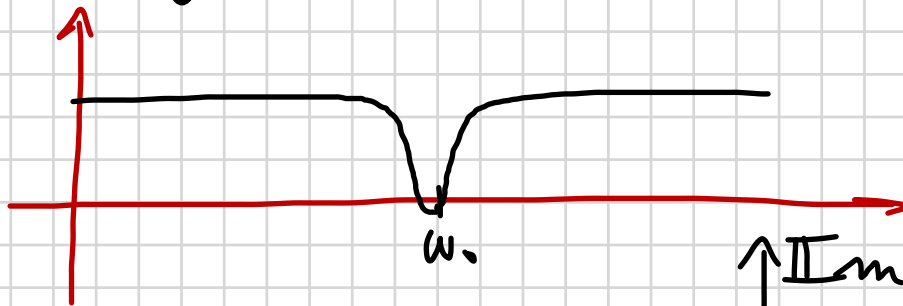
$$\frac{s^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1$$



$$Q = \frac{1}{\sin \theta}$$
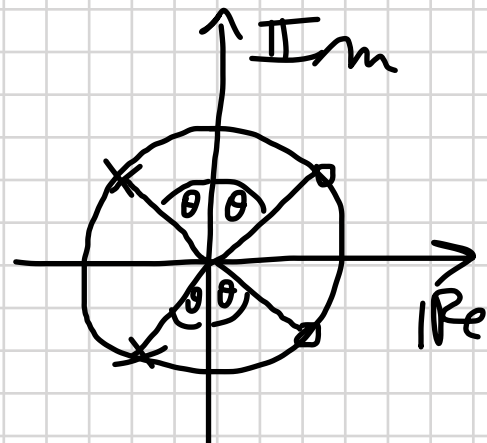
$$H(s) = \frac{\frac{s^2}{\omega_0^2} - \frac{s}{Q\omega_0} + 1}{\frac{s^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1}$$



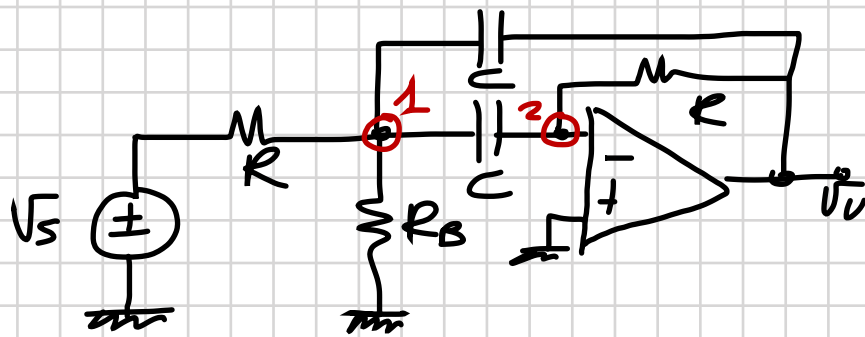

$$\begin{cases} \frac{V_1 - V_s}{R} + \frac{V_1}{R_B} + V_1 C s + (V_1 - V_U) C s = 0 \\ V_U = -R C s V_1 \Rightarrow V_2 = -\frac{V_U}{R C s} \end{cases}$$


$$V_1 \left[\frac{1}{R} + \frac{1}{R_B} + C s + C s + R C^2 s^2 \right] = \frac{V_s}{R}$$

$$V_1 \left[1 + \frac{R}{R_B} + 2 R C s + R^2 C^2 s^2 \right] = V_s$$

$$V_1 = \frac{V_s}{R^2 C^2 s^2 + 2 R C s + \frac{R_B + R}{R_B}}$$

$$V_U = -\frac{R C s V_s}{R^2 C^2 s^2 + 2 R C s + \frac{R_B + R}{R_B}}$$

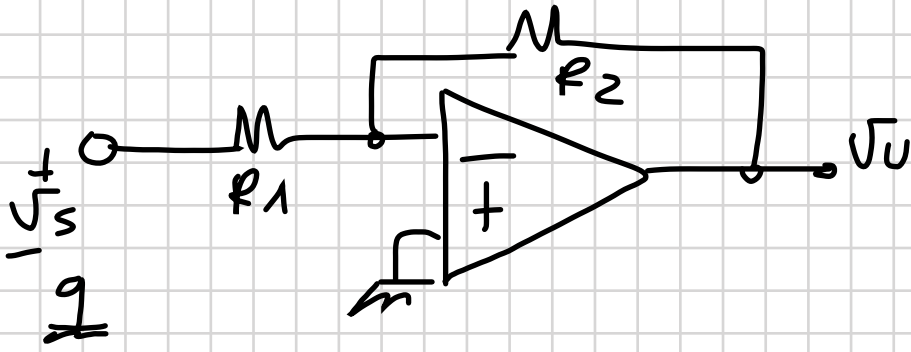
$$H(s) = \frac{V_U}{V_s} = \frac{-R C s}{R^2 C^2 s^2 + 2 R C s + \frac{R_B + R}{R_B}}$$



$$\frac{v_u}{v_s} = -\frac{R_2}{R_1}$$

$$A = A_{VOL} \beta$$

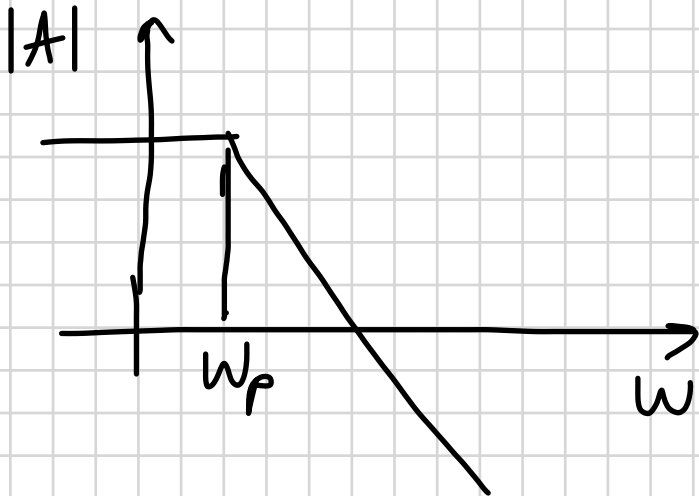
$$A = \frac{A_{VOL} \beta}{1 + \frac{s}{\omega_p}}$$



$$v^- \approx v^+$$

$$v_{INOP} \ll v_s$$

$$v_u = A v_{INOP}$$

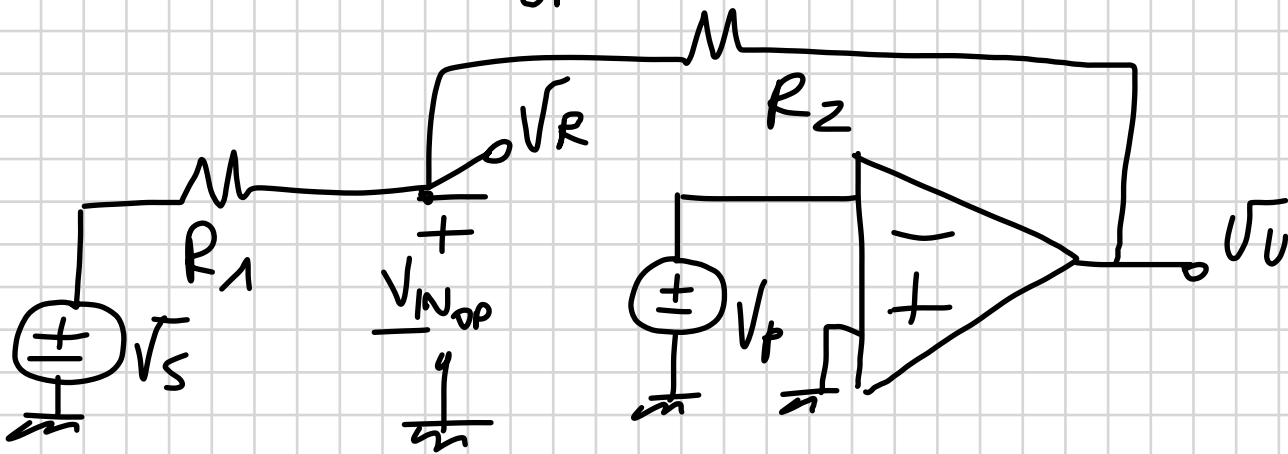

$$v_{INOP} \ll v_s$$

$$v_{INOP} = v_R$$

$$v_R = \frac{\alpha v_s}{1 - \beta A} \ll v_s$$



$$\alpha \ll 1 - \beta A$$

$$|\beta A| \gg 1$$


$$\alpha \ll |\beta A|$$

$$\alpha \approx \alpha_0 < 1$$



$$|\beta A| \gg 1$$

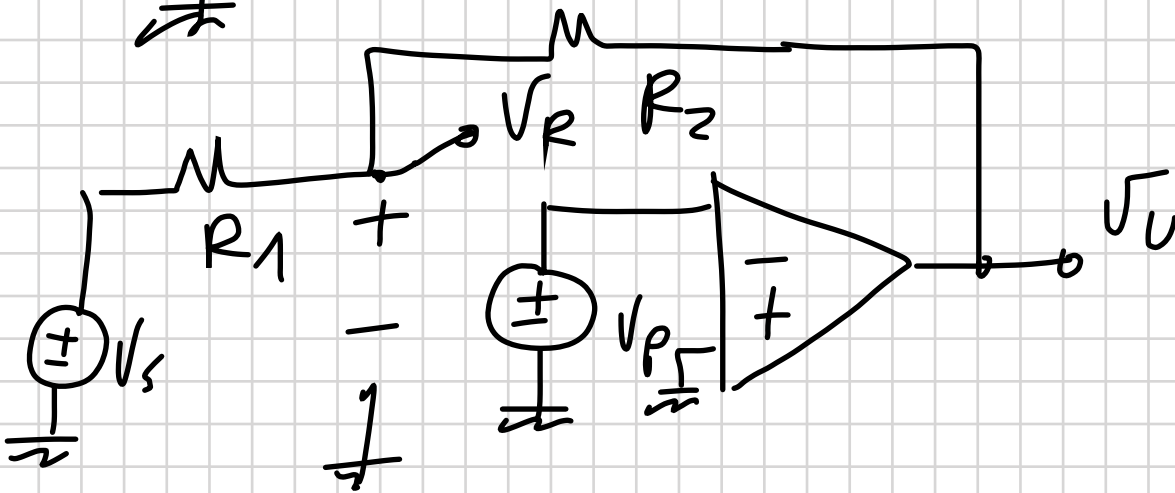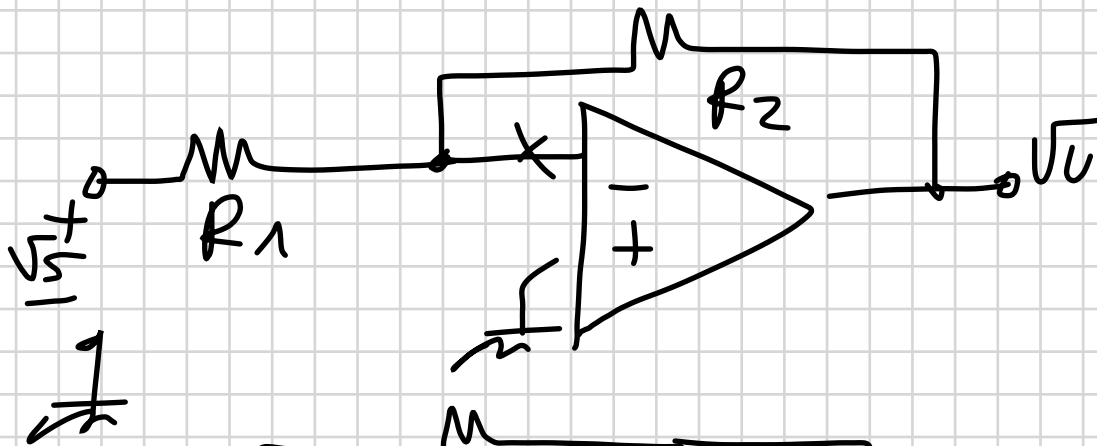

$$\beta A = \frac{v_r}{v_p} \Big|_{v_s=0}$$

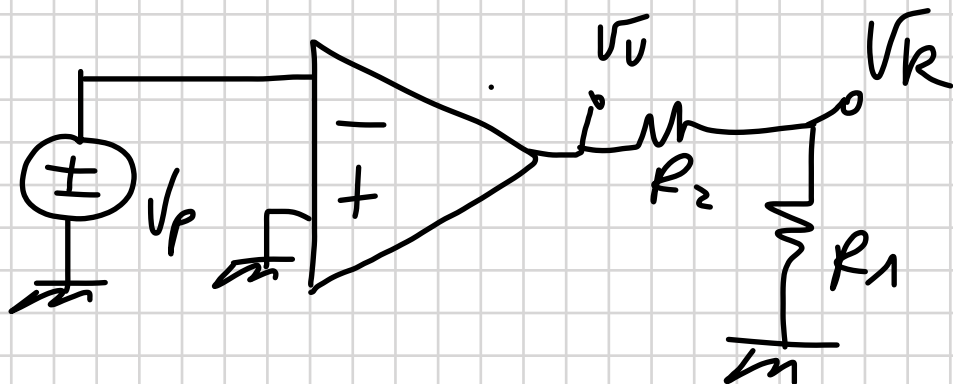

$$\beta A =$$

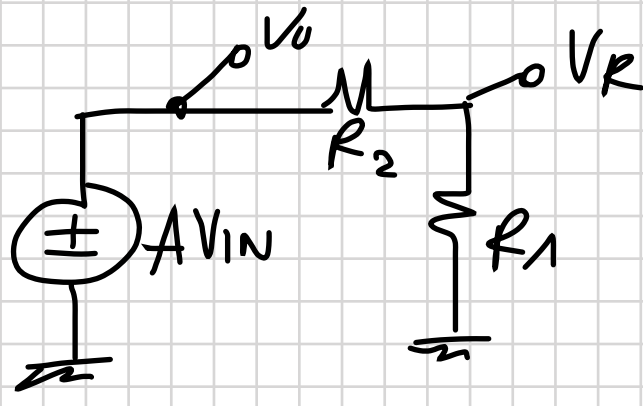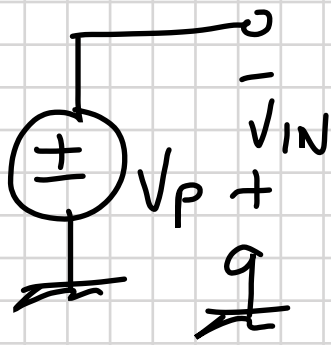

$$A = \frac{A_{VOL} \beta}{1 + \frac{s}{\omega_p}}$$

$$\beta A = \frac{V_R}{V_P} \Big|_{V_S=0} \Rightarrow$$

$$V_U = A V_{IN} \quad V_{IN} = -V_P$$

$$V_U = -A V_P = \frac{-A_{VOL} \beta V_P}{1 + \frac{s}{\omega_p}}$$

$$V_R = \frac{R_1}{R_1 + R_2} V_U$$

$$V_R = \frac{R_1}{R_1 + R_2} \left(-\frac{A_{VOL} \beta}{1 + \frac{s}{\omega_p}} \right) V_P$$

$$\beta A = \frac{V_R}{V_P} = -\frac{A_{VOL} \beta \frac{R_1}{R_1 + R_2}}{1 + \frac{s}{\omega_p}}$$

$$|\beta A| \gg 1$$

$$|\beta A| > 10$$


$$|\beta A| = \frac{A_{VOL} \beta \frac{R_1}{R_1 + R_2}}{\sqrt{1 + \frac{\omega^2}{\omega_p^2}}} = 10 = A_L$$

$$\frac{A_{\text{vol}} \frac{R_1}{R_1 + R_2}}{\sqrt{1 + \frac{\omega^2}{\omega_p^2}}} = A_L = 10$$

$$\frac{A_{\text{vol}}^2 \left(\frac{R_1}{R_1 + R_2} \right)^2}{A_L^2} = 1 + \frac{\omega^2}{\omega_p^2}$$

$$\omega = \omega_p \sqrt{\frac{A_{\text{vol}}^2 \left(\frac{R_1}{R_1 + R_2} \right)^2}{A_L^2} - 1} \quad \underline{\quad}$$

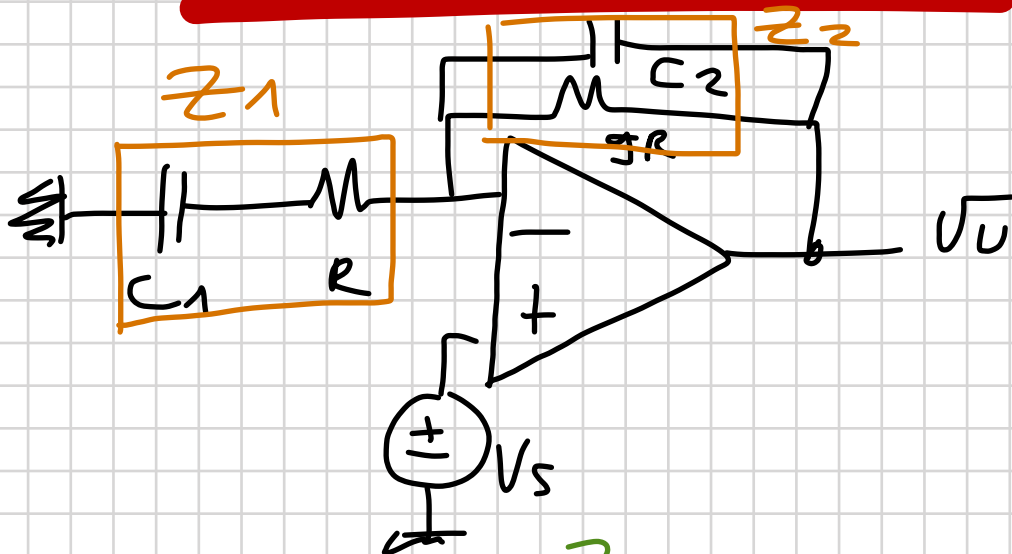
$$\approx \omega_p \frac{A_{\text{vol}}}{A_L} \frac{R_1}{R_1 + R_2}$$



$$R = 1 \text{ k}\Omega$$

$$C_1 = 10 \mu\text{F}$$

$$C_2 = 10 \text{ nF}$$

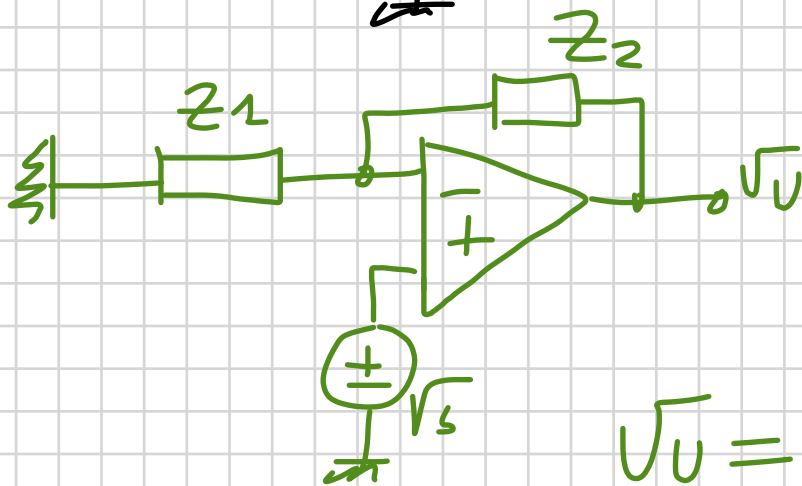

$$V_U = \left(1 + \frac{Z_2}{Z_1} \right) V_S$$

$$z_1 = \frac{RC_1s+1}{C_1s} \quad ; \quad z_2 = \frac{f_2}{R_2C_2s+1}$$

$$V_0 = V_S \left[1 + \frac{R_2 C_1 s}{(R_2 C_2 s + 1)(RC_1 s + 1)} \right] =$$

$$= \frac{(s+z_1)(s+z_2)}{(s+p_1)(s+p_2)} V_S$$

$$p_1 = \frac{1}{RC_1} \quad (f_2 = 15,9 \text{ MHz})$$

$$p_2 = \frac{1}{R_2 C_2} = 111 p_1$$

$$z_1 = 1112 p_1 \quad ; \quad z_2 = 0,09992 p_1$$

$$H(s \rightarrow 0) = \frac{z_1 z_2}{p_1 p_2} = 1$$