

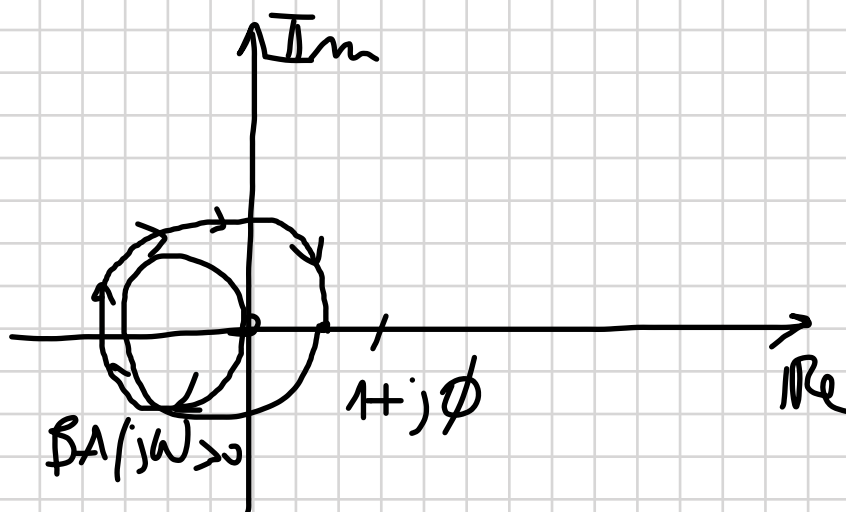
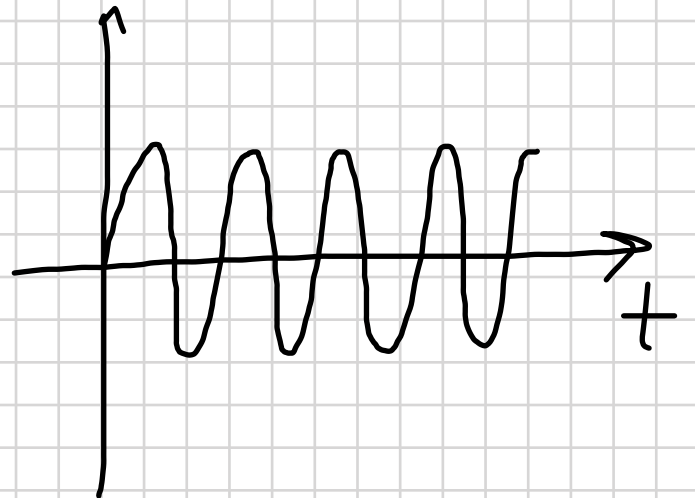
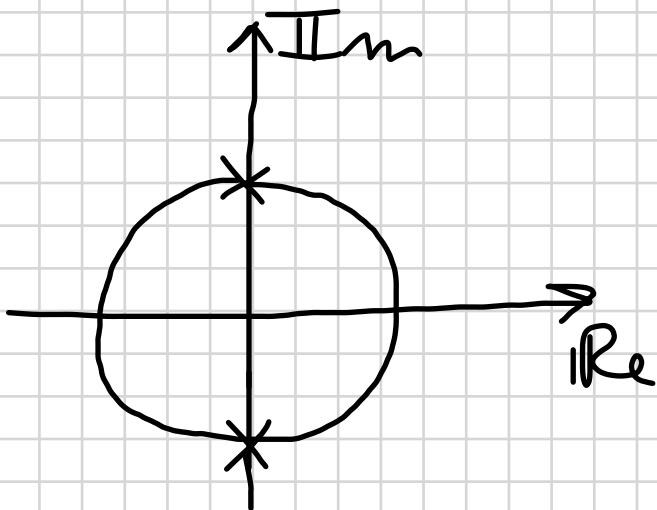
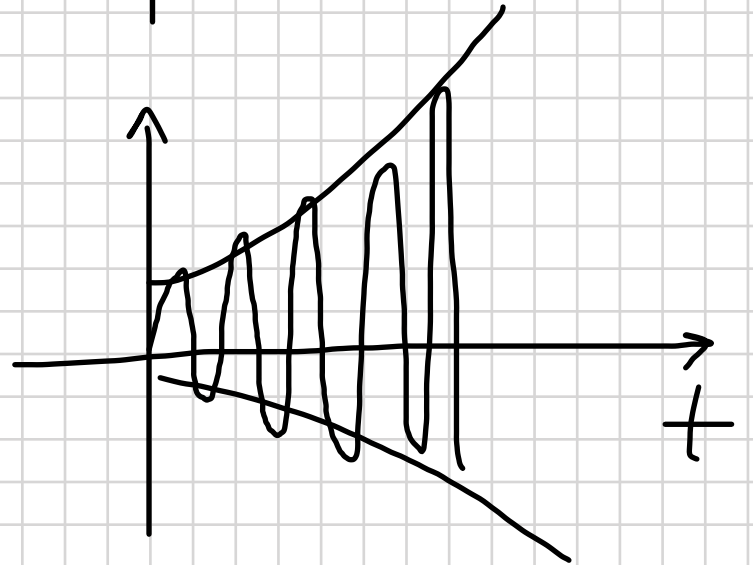
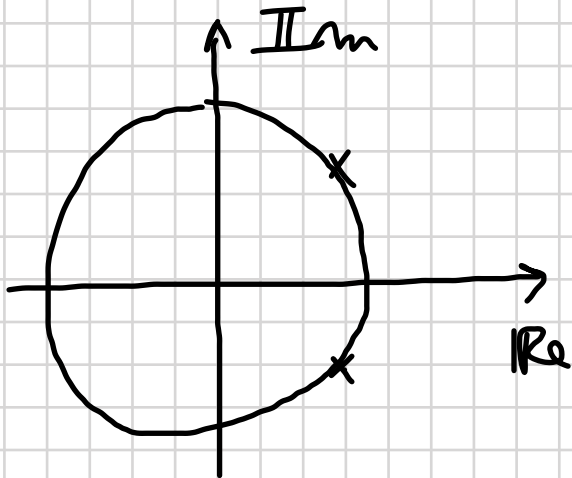
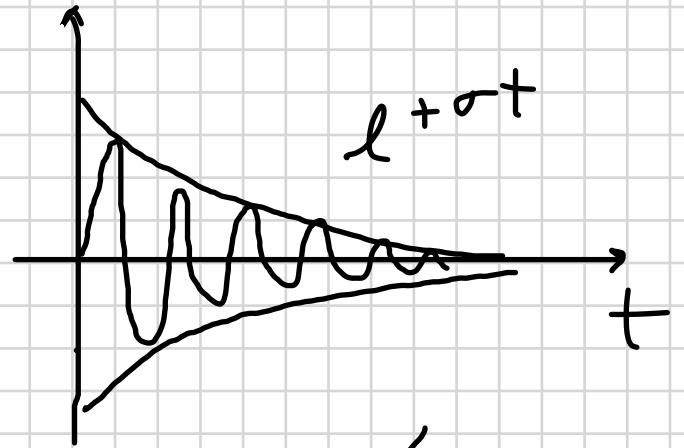
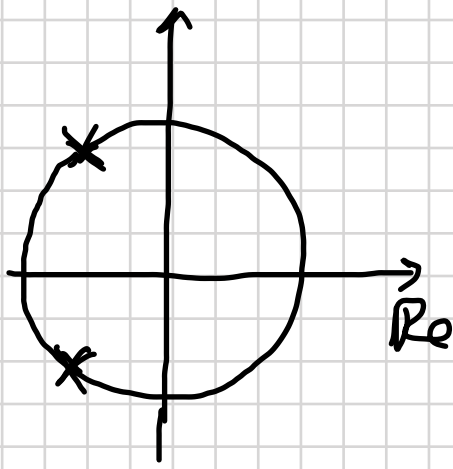
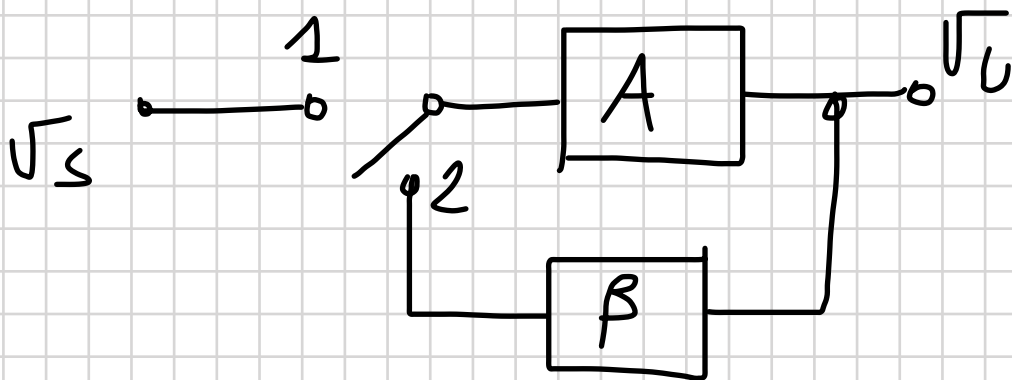


$$S = \sigma + j\omega_0$$

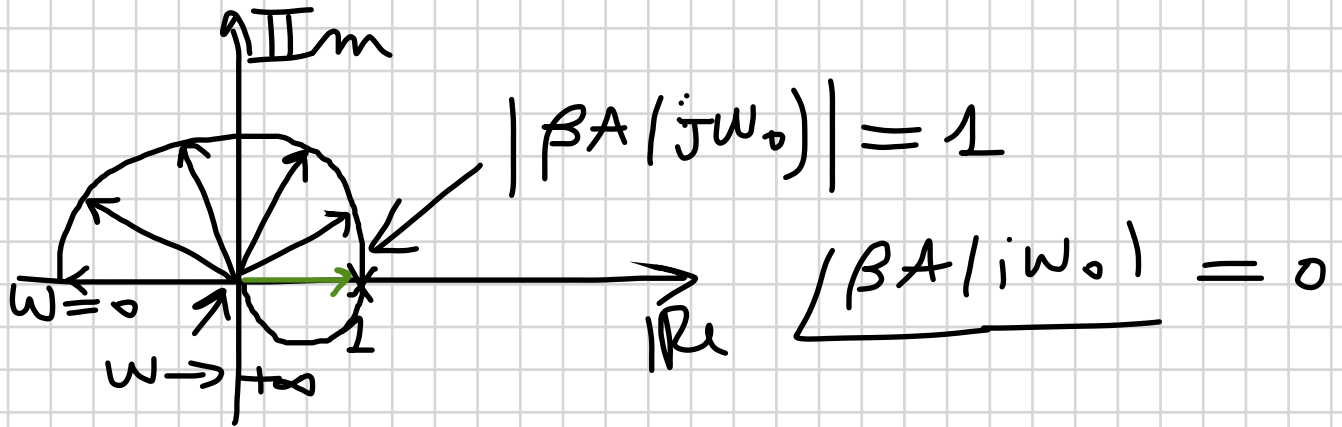

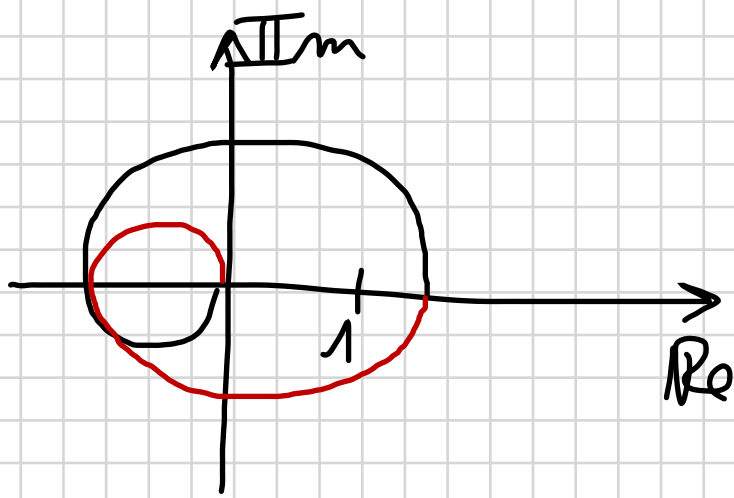

$$V_s = V_m \sin(\omega_0 t) \Rightarrow$$

$$V_u = |A(j\omega_0)| V_m \sin(\omega_0 t + \angle A(j\omega_0))$$

$$V_u = \beta A V_u \quad \boxed{\beta A = 1}$$

A regime


$$\beta A(j\omega_0) = 1$$

$$|\beta A(j\omega_0)| = 1$$


$$\angle \beta A(j\omega_0) = 0$$

$$\beta A(j\omega_0) > 1$$

PONTE DI WIEN

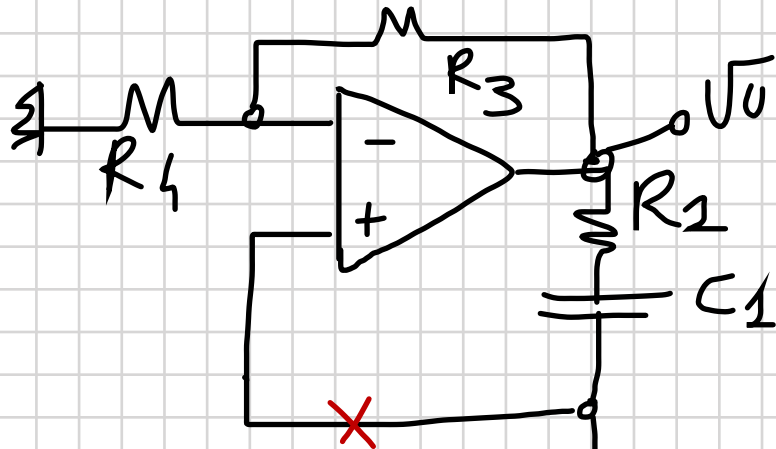

$$\beta A = \frac{V_R}{V_P} \Big|_{V_S=0}$$

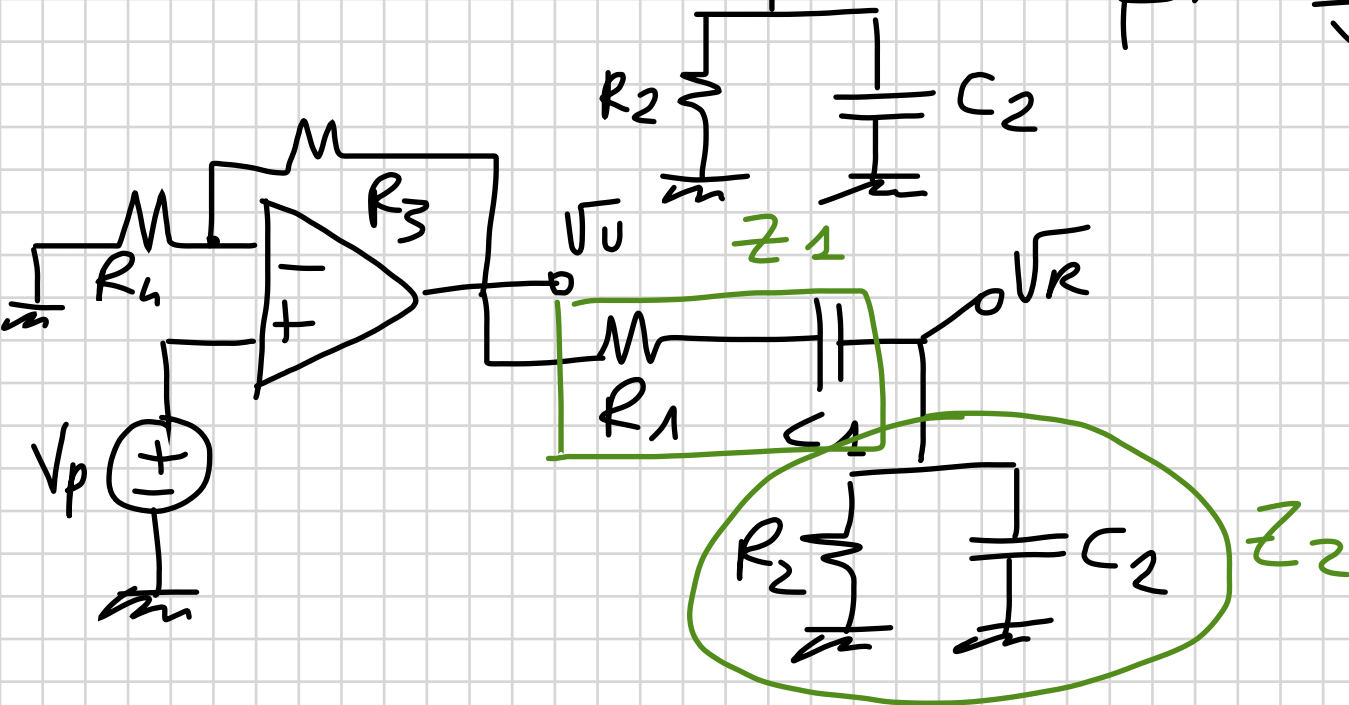

$$\beta A = \frac{Z_2}{Z_1 + Z_2} \left(1 + \frac{R_3}{R_4} \right) \quad Z_2 = R_2 \parallel \frac{1}{C_2 s} = \frac{R_2}{R_2 C_2 s + 1}$$

$$Z_1 = R_1 + \frac{1}{C_1 s} = \frac{R_1 (C_1 s + 1)}{C_1 s}$$

$$\beta A = \left(1 + \frac{R_3}{R_4}\right) \frac{R_2 C_1 S}{R_2 C_1 S + (R_2 C_2 S + 1)(R_1 C_1 S + 1)} =$$

$$= \underbrace{\left(1 + \frac{R_3}{R_4}\right)}_G \frac{R_2 C_1 S}{R_1 C_1 R_2 C_2 S^2 + (R_1 C_1 + R_2 C_2 + R_2 C_1) S + 1}$$

$$R_1 = R_2 = R \quad ; \quad C_1 = C_2 = C$$

$$\beta A(s) = \frac{G R C S}{R^2 C^2 S^2 + 3 R C S + 1}$$

$$\beta A(j\omega) = \frac{G j\omega R C}{\underbrace{1 - R^2 C^2 \omega^2}_{\text{denominator}} + 3 R C j\omega}$$

$$\beta A(j\omega_0) \geq 1$$

$$\angle \beta A(j\omega_0) = 0$$

$$1 - R^2 C^2 \omega_0^2 = 0$$

$$\omega_0 = \frac{1}{RC}$$



$$\beta A(j\omega_0) = \frac{G \cancel{j\omega_0} R C}{3 R C \cancel{j\omega_0}} = \boxed{\frac{G}{3}}$$



$$G > 3 \Rightarrow \left(1 + \frac{R_3}{R_4}\right) > 3$$

$$R_3 > 2R_4 \quad \text{INNESCO}$$

$$R_3 = 2R_4$$

A REGIM

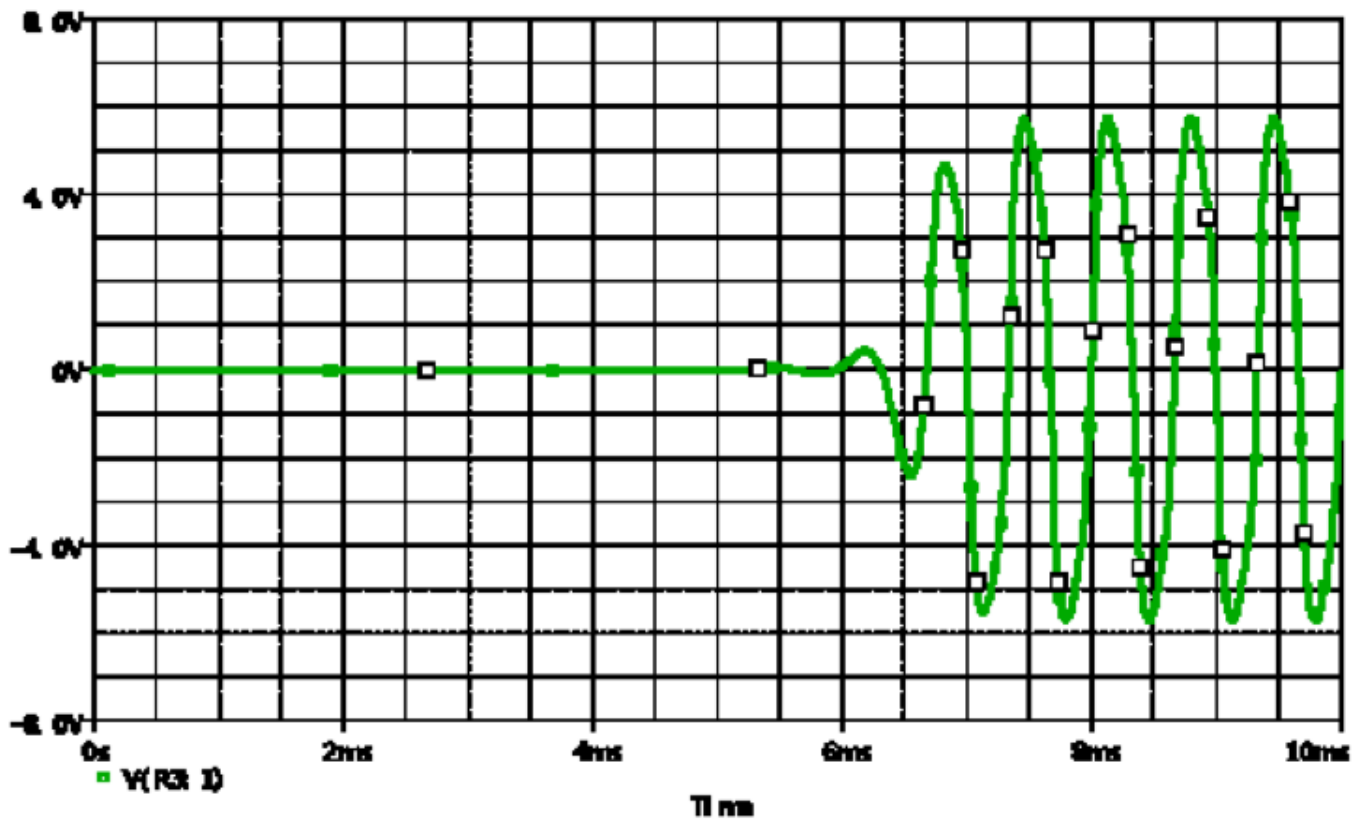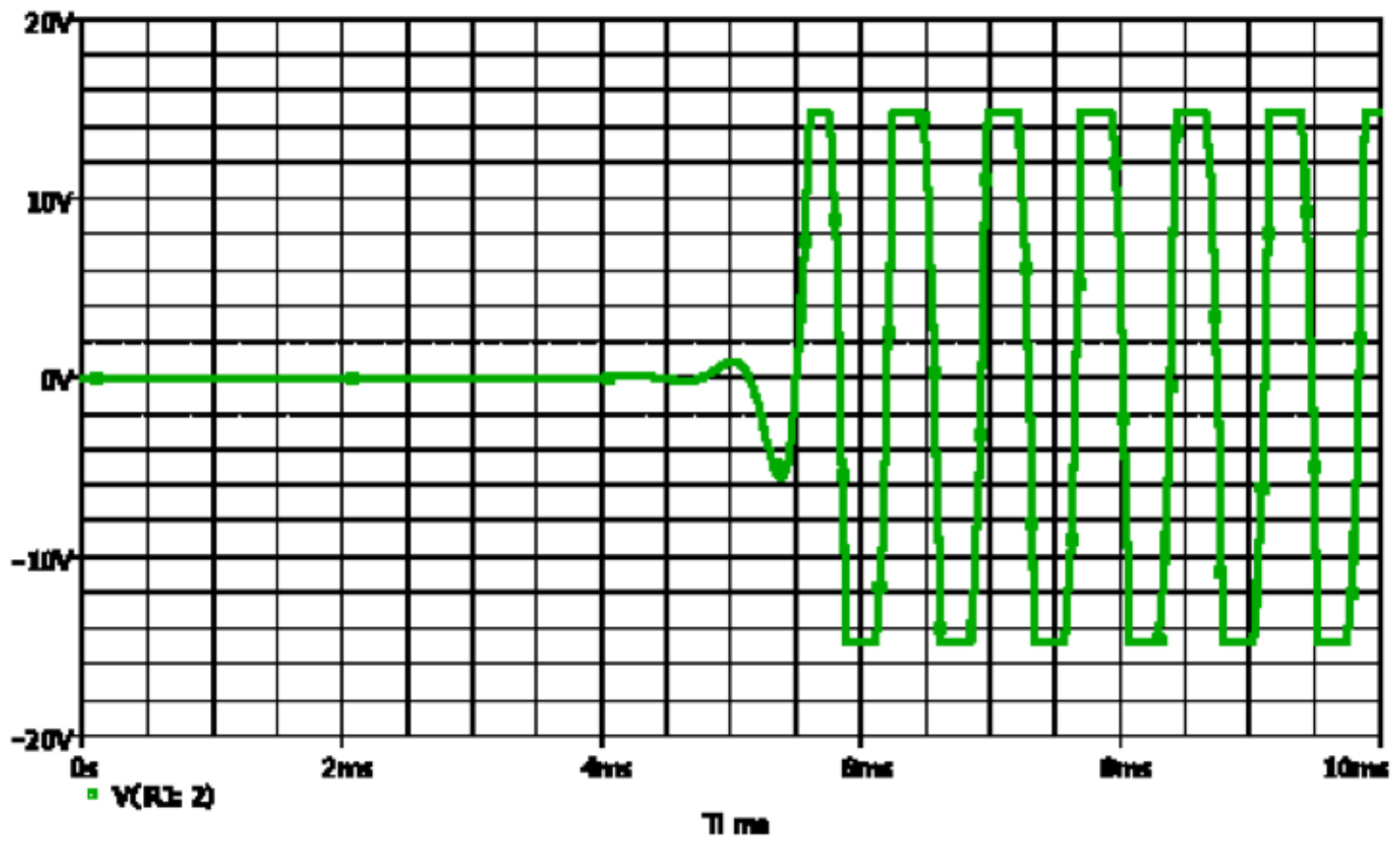

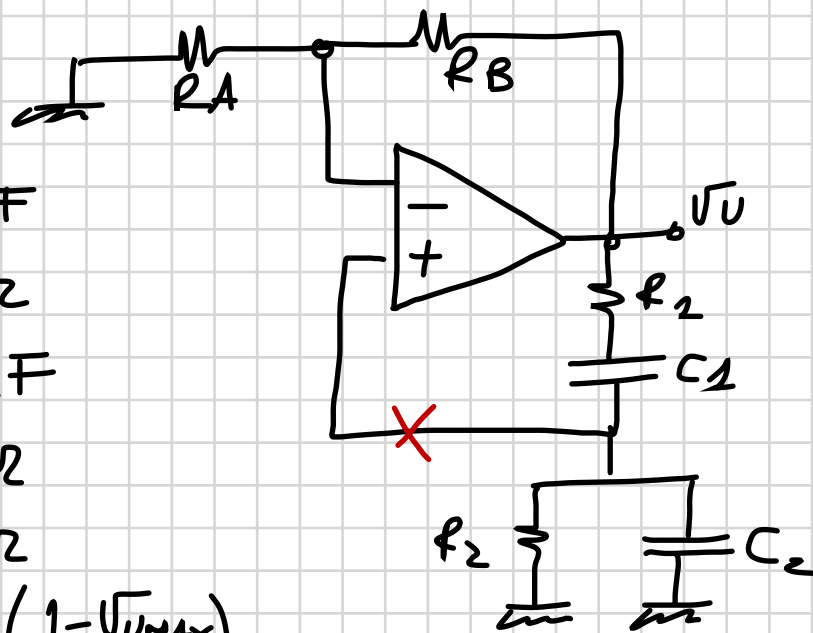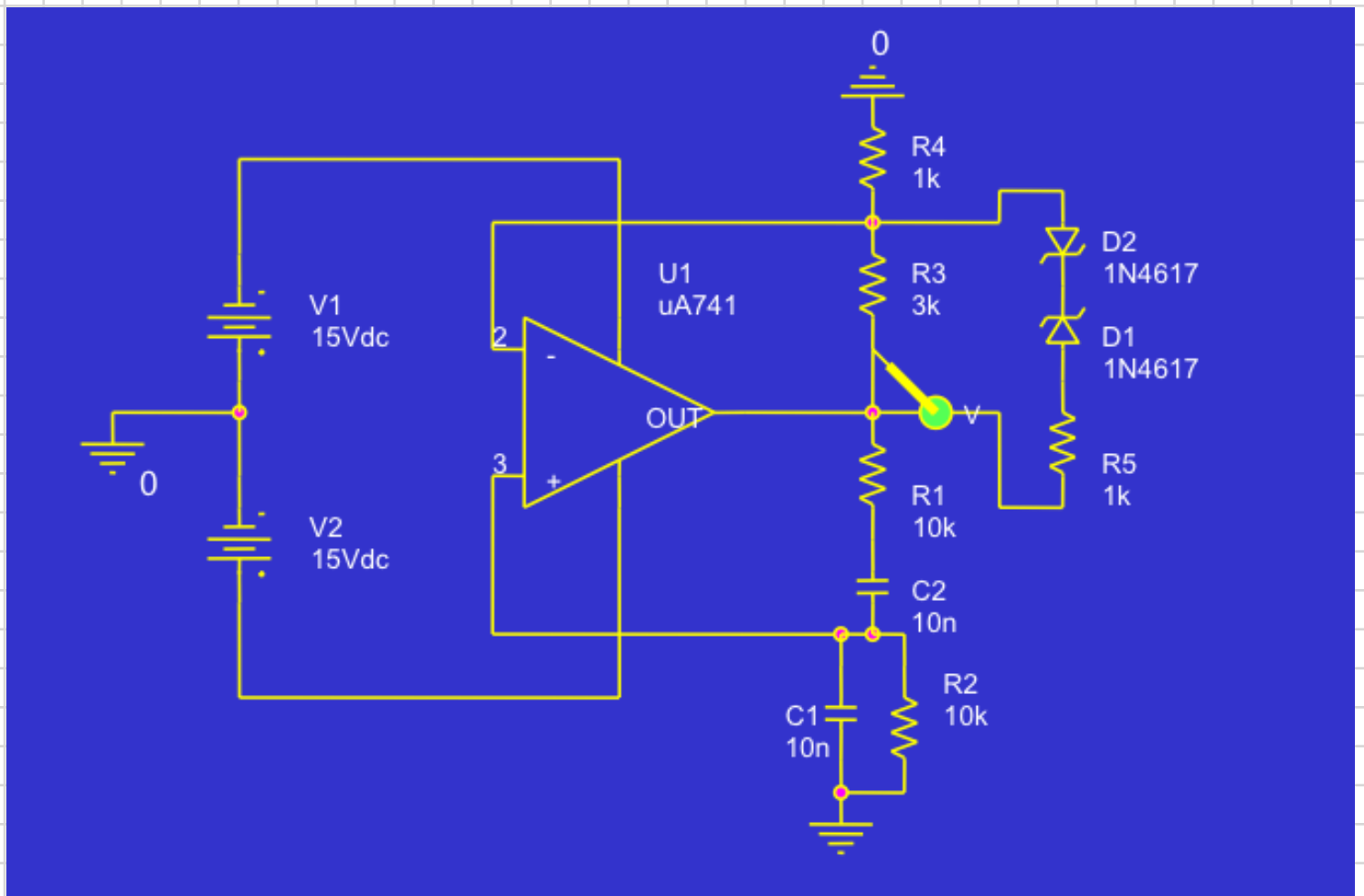

- $C_1 = 1\mu F$
- $R_1 = 1k\Omega$
- $C_2 = 2\mu F$
- $R_2 = 2k\Omega$
- $R_A = 1k\Omega$
- $R_B = R_o \left(1 - \frac{V_{Umax}}{V_o} \right)$
- $R_o = 6k\Omega$
- $V_o = 5V$

$$\beta A(s) = \left(1 + \frac{R_B}{R_A} \right) \frac{R_2 C_1 s}{R_1 R_2 C_1 C_2 s^2 + (R_A C_1 + R_2 C_2 + R_2 C_1) s + 1}$$

$$\beta A(j\omega) = \left(1 + \frac{R_B}{R_A} \right) \frac{j\omega R_2 C_1}{1 - R_1 R_2 C_1 C_2 \omega^2 + j\omega (R_A C_1 + R_2 C_2 + R_2 C_1)}$$

$$\underline{|BA(j\omega_0)| = 0} \Rightarrow 1 - R_1 R_2 C_1 C_2 \omega_0^2 = 0$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = 500 \text{ rad/sec}$$

$$|BA(j\omega_0)| > 1$$


$$|BA(j\omega_0)| = \left(1 + \frac{R_B}{R_A}\right) \frac{R_2 C_1}{R_1 C_1 + R_2 C_2 + R_2 C_1} > 1$$

$$R_B = ? = R_0$$

$$|BA(j\omega_0)| = 2 > 1$$

$$\left[1 + \frac{R_0}{R_A} \left(1 - \frac{V_{U_{MAX}}}{V_0}\right)\right] \cdot \frac{R_2 C_1}{R_1 C_1 + R_2 C_2 + R_2 C_1} = 1$$

$$V_{U_{MAX}} = 2,92 \text{ V}$$

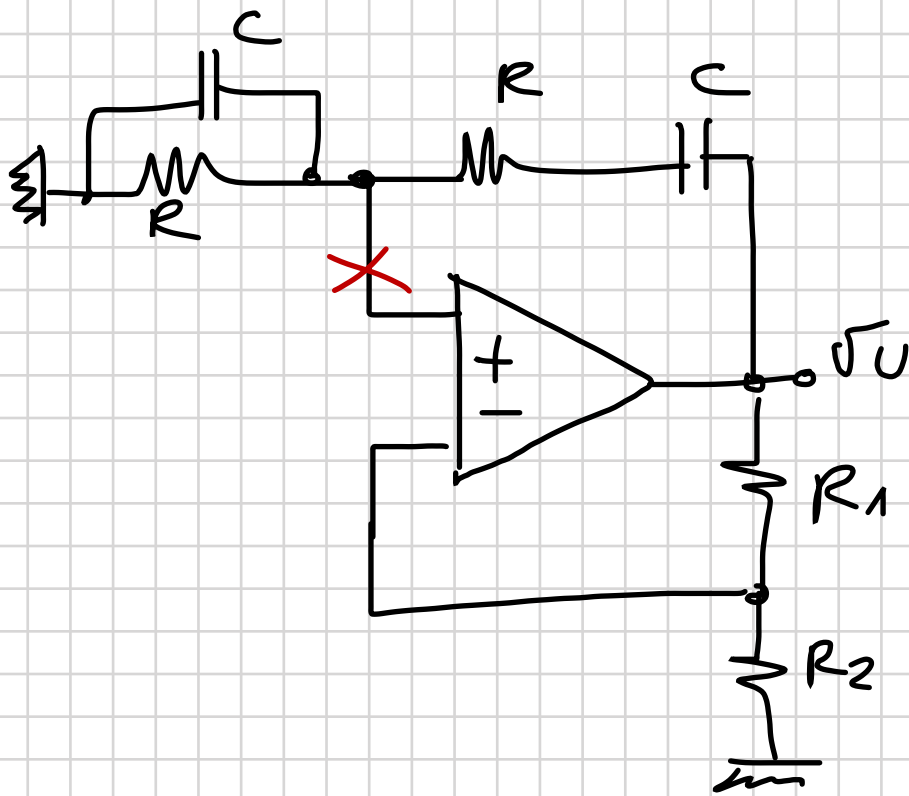

$$R = 10 \text{ k}\Omega$$

$$C = 100 \text{ nF}$$

$$R_1 = 5R_2 e^{-\frac{V_U}{V_M}}$$

$$R_2 = 1 \text{ k}\Omega$$

$$V_M = 5,457 \text{ V}$$

$V_U = \text{AMPIEZZA OSCILLAZIONE}$

$$\beta A(s) = \frac{RCs}{R^2C^2s^2 + 3RCs + 1} \left(1 + \frac{R_1}{R_2}\right)$$

$$\beta A(j\omega) = \frac{RCj\omega}{1 - R^2C^2\omega^2 + 3RCj\omega} \underbrace{\left(1 + \frac{R_1}{R_2}\right)}_G$$

$$\omega_0 = \frac{1}{RC} \Rightarrow f_0 = 159 \text{ MHz}$$

$$|\beta A(j\omega_0)| = \frac{G}{3} = 2 > 1$$

$$|\beta A(j\omega_0)| = 1 \cdot \frac{1 + 5 e^{-\frac{V_U}{V_M}}}{3} = 1$$

$$V_U = V_M \ln(2,5) = 5 \text{ V}$$