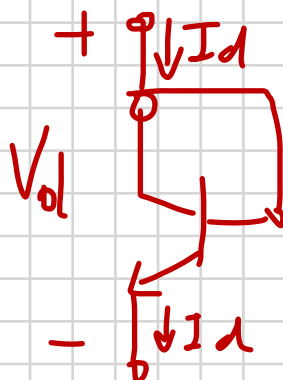




$$I_c = I_s \left(e^{+\frac{V_{BE}}{V_T}} - 1 \right)$$



$$I_d = I_s \left(e^{\frac{V_d}{V_T}} - 1 \right)$$

$$I_{c1} = I_s \left(e^{\frac{V_{BE1}}{V_T}} - 1 \right)$$

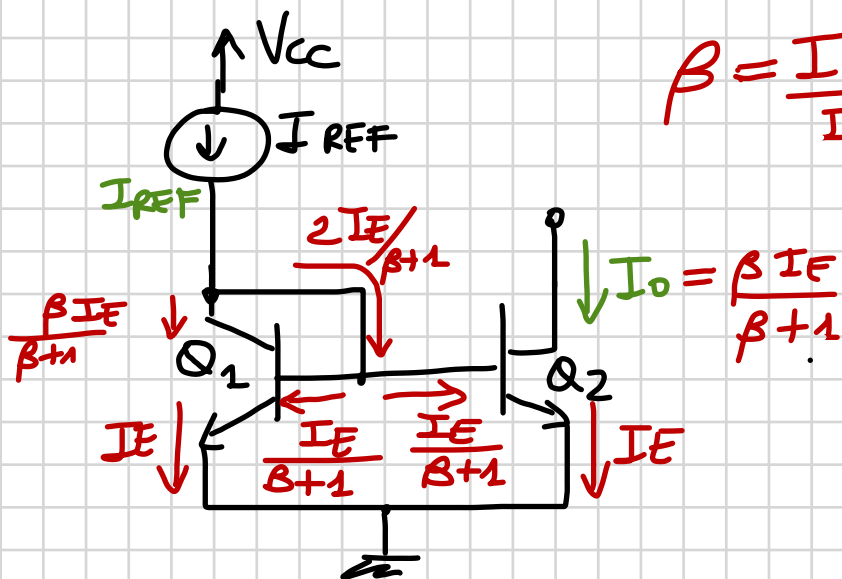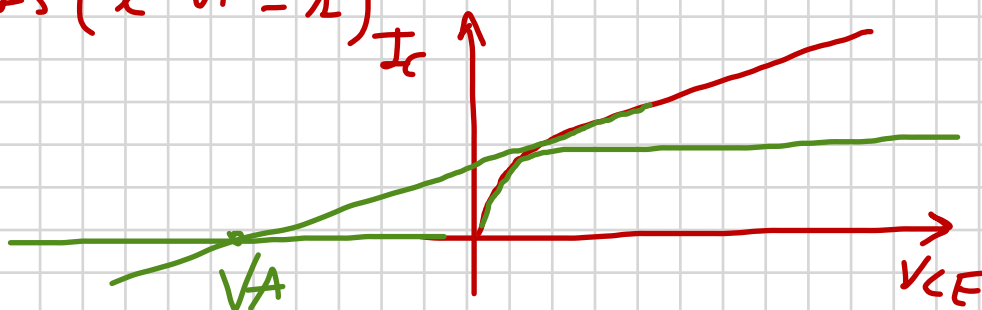
$$I_{c2} = I_s \left(e^{\frac{V_{BE2}}{V_T}} - 1 \right)$$




$$\beta = \frac{I_c}{I_B}$$

$$I_{REF} = \frac{\beta I_E}{\beta+1} + \frac{2 I_E}{\beta+1} = \frac{\beta+2}{\beta+1} I_E = \frac{\beta+2 I_O}{\beta}$$


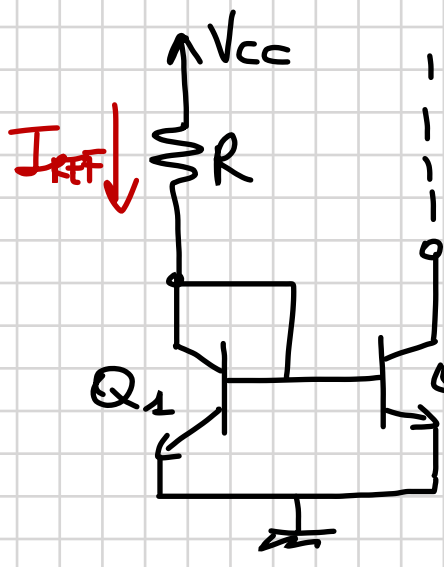
$$\frac{I_O}{I_{REF}} = \frac{\beta}{\beta+2}$$



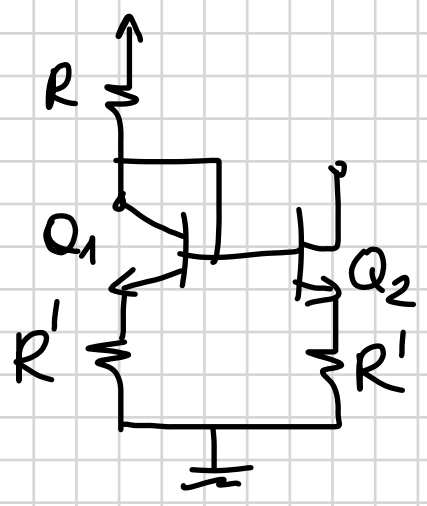$I_0 \approx I_{REF}$
 $I_{REF} = \frac{V_{CC} - V_{BE}}{R}$




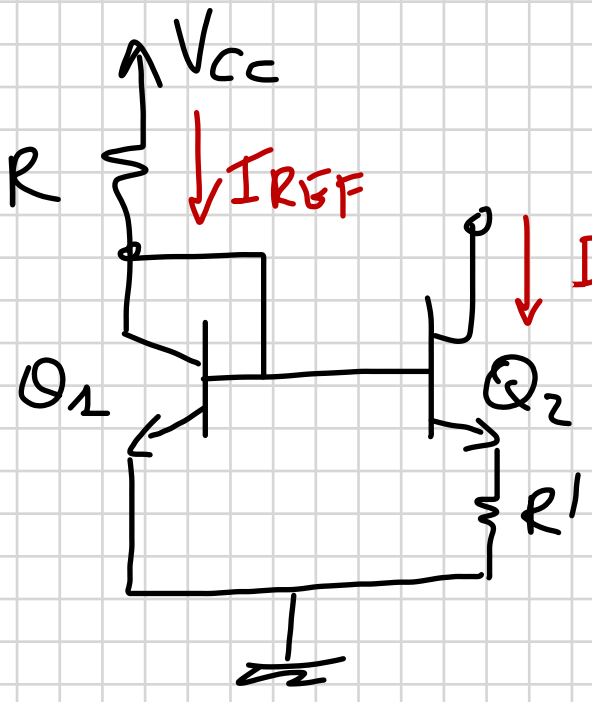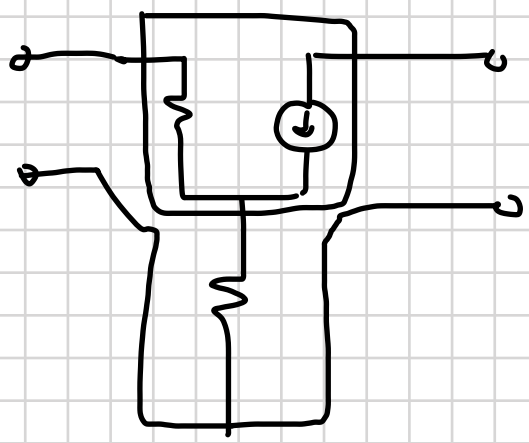$R' I_{C1} + V_{BE1} =$
 $R' I_{C2} + V_{BE2}$



$V_{BE1} = V_{BE2} + R' I_{C2}$
 $V_{BE1} > V_{BE2}$
 $I_{C1} > I_{C2}$
 $I_{REF} > I_0$

WIDLAR

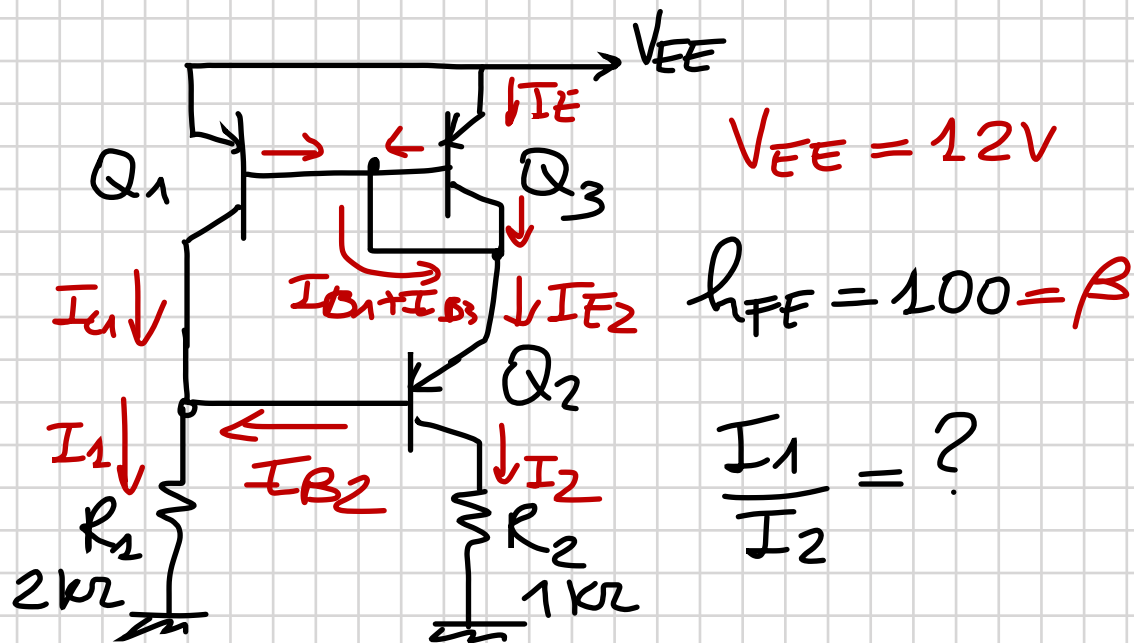

$$I_{B3} = \frac{I_E}{\beta + 1}$$

$$I_{E3} = I_{E2} = I_E$$

$$I_{B1} = \frac{I_E}{\beta + 1}$$

$$I_{C1} = \frac{\beta}{\beta + 1} I_E = I_{C3}$$

$$I_{E2} = I_{C3} + I_{B1} + I_{B3} = \frac{\beta}{\beta + 2} I_E + \frac{2 I_E}{\beta + 2} = \frac{\beta + 2}{\beta + 1} I_E$$


$$I_1 = I_{C1} + I_{B2} = \frac{\beta}{\beta + 1} I_E + \frac{\beta + 2}{(\beta + 1)^2} I_E$$

$$I_1 = \frac{\beta^2 + 2\beta + 2}{(\beta + 1)^2} I_E$$

$$I_2 = \frac{\beta}{\beta + 1} I_{E2} = \frac{\beta(\beta + 2)}{(\beta + 1)^2} I_E$$

$$\frac{I_1}{I_2} = \frac{\beta^2 + 2\beta + 2}{\beta(\beta + 2)} = 1,000196$$
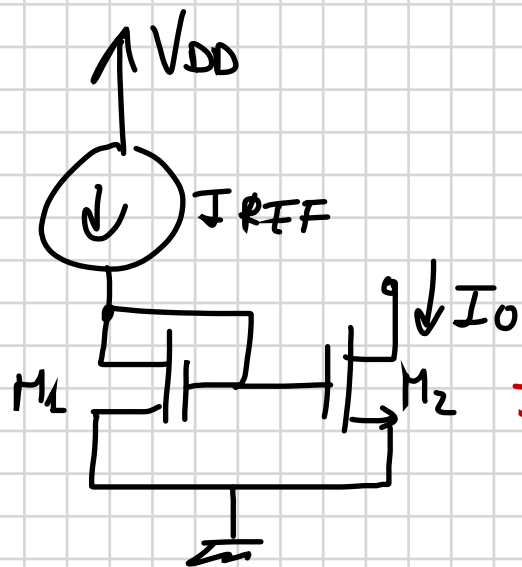
$$I_1 = \frac{V_{EE} - 2V_{EB}}{R_2} = 5,3 \text{ mA}$$



$$I_1 = k_1 (V_{GS1} - V_T)^2$$

$$I_2 = k_2 (V_{GS2} - V_T)^2$$



$$V_{T1} = V_{T2} = V_T$$

$$I_1 = I_{REF}$$

$$\frac{I_1}{I_2} = \frac{k_1 \cancel{(V_{GS1} - V_T)^2}}{k_2 \cancel{(V_{GS2} - V_T)^2}} =$$

$$= \frac{k_1}{k_2} = \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2} = \frac{I_{REF}}{I_O}$$

$$I = k (V_{GS} - V_T)^2$$

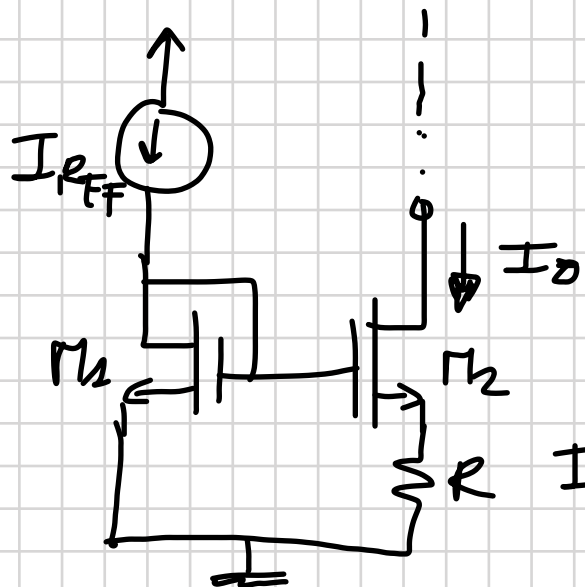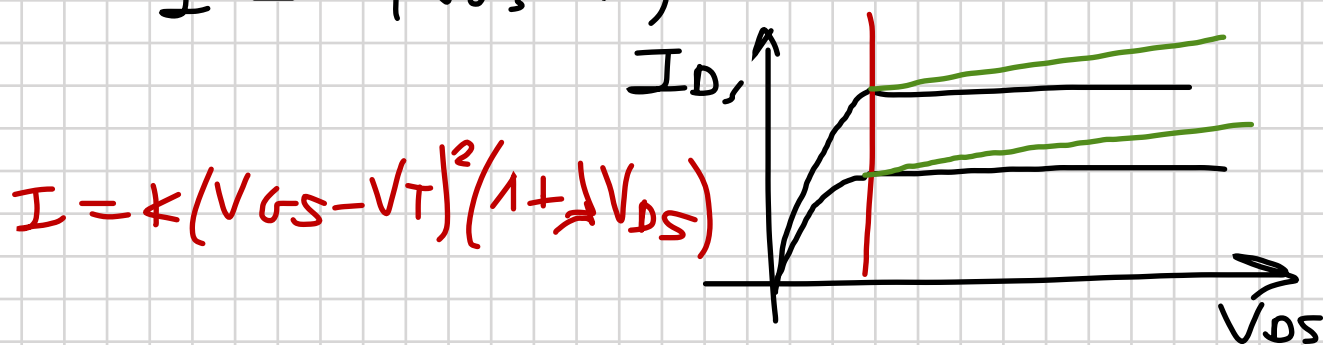

$$I_1 = k_1 (V_{GS1} - V_T)^2 = I_{REF}$$

$$I_2 = k_2 (V_{GS2} - V_T)^2$$

$$V_{GS2} = V_{GS1} - R I_2$$

$$I_2 = k_2 \left[(V_{GS1} - V_T) - R I_2 \right]^2 =$$

$$= k_2 (V_{GS1} - V_T)^2 - 2 k_2 R (V_{GS1} - V_T) I_2 + k_2 R^2 I_2^2$$


$$k_2 (V_{GS1} - V_T)^2 = \frac{k_2}{k_1} I_1$$

$$(V_{GS1} - V_T) = \sqrt{\frac{I_1}{k_1}}$$


$$k_2 R^2 I_2^2 - \left[1 + 2k_2 R \sqrt{\frac{I_1}{k_1}} \right] I_2 + \frac{k_2}{k_1} I_2 = 0$$

$$I_2 = \underbrace{\left[1 + 2k_2 R \sqrt{\frac{I_1}{k_1}} \right]}_A \mp \sqrt{A^2 - 4 \frac{R^2 k_2^2}{k_1} I_1}$$

$$2k_2 R^2$$

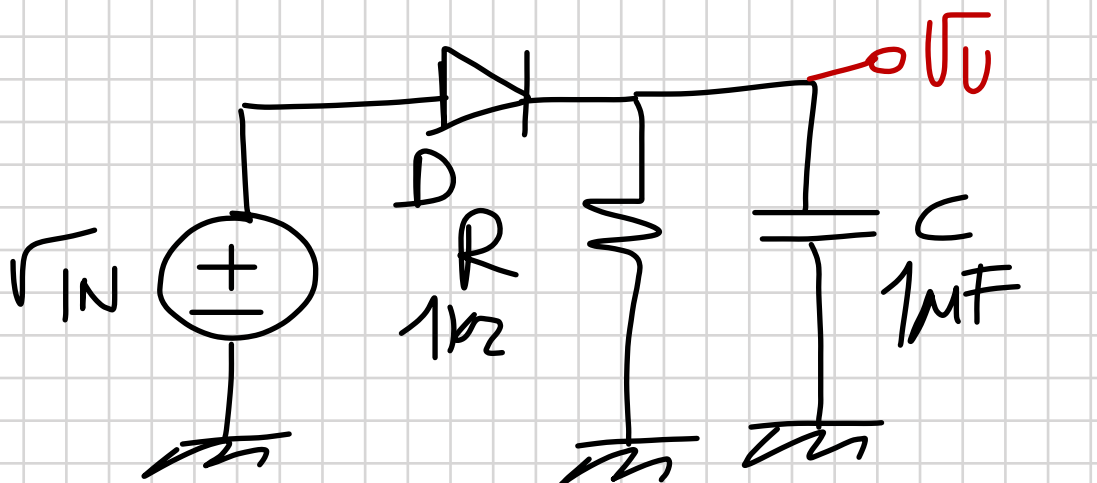

$$T = 8ms$$

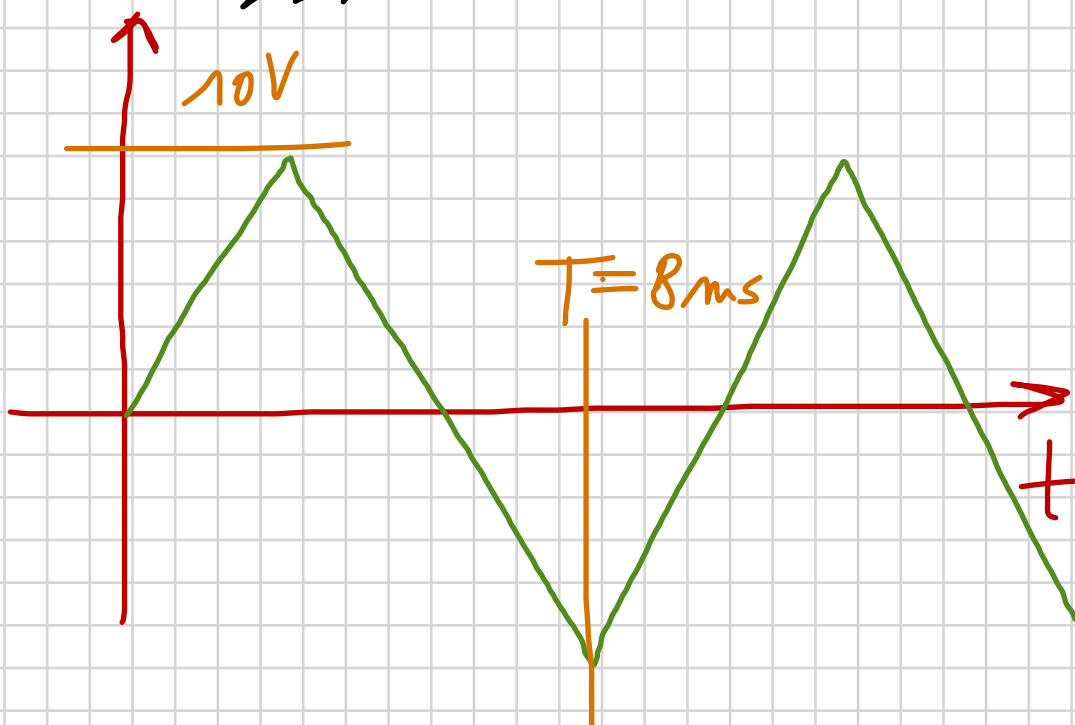


$$r_i = 1 \text{ k}\Omega$$

$$r_f = 100 \Omega$$

$$r_o = 100 \Omega$$

$$r_f' = 1 \Omega$$

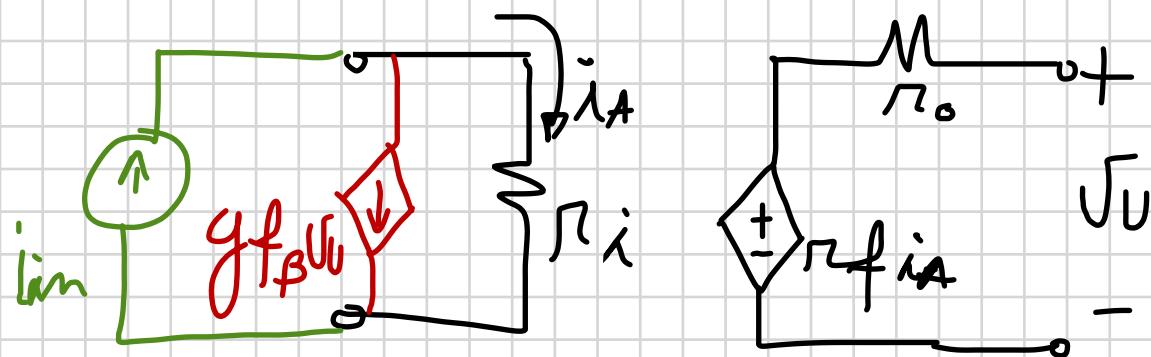

$$r_f' = \frac{V_U}{i_{in}} \Big|_{i_U=0} = \frac{r_f (i_{in} - g_{f\beta} V_U)}{i_{in}} =$$

$$\Rightarrow \frac{r_f}{1 + r_f g_{f\beta}} i_{in} = V_U$$

$$1 + r_f g_{f\beta} = \frac{r_f}{r_f'} = 1000 \Rightarrow \underline{\underline{g_{f\beta} = 0,999}}$$

$$r_i' = \frac{V_{in}}{i_{in}} = \frac{1 \text{ A } r_i}{i_{in}} = \frac{1 \text{ k}\Omega}{1 + r_f g_{f\beta}} = 0,1 \Omega$$

$$r_o' = \frac{V_U}{i_U} \Big|_{i_{in}=0} = \frac{r_o i_U + r_f (-g_{f\beta} V_U)}{i_U} = 0,1 \Omega$$