

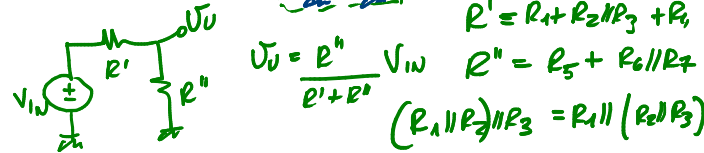
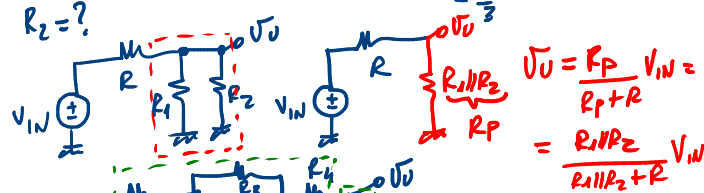
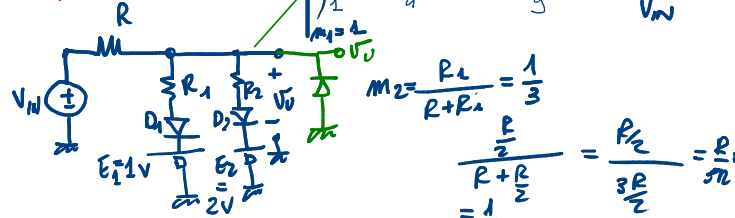



V_{1N}	V_0
1	1
4	2
9	3

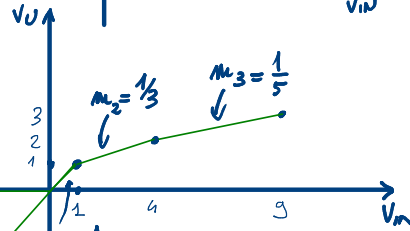
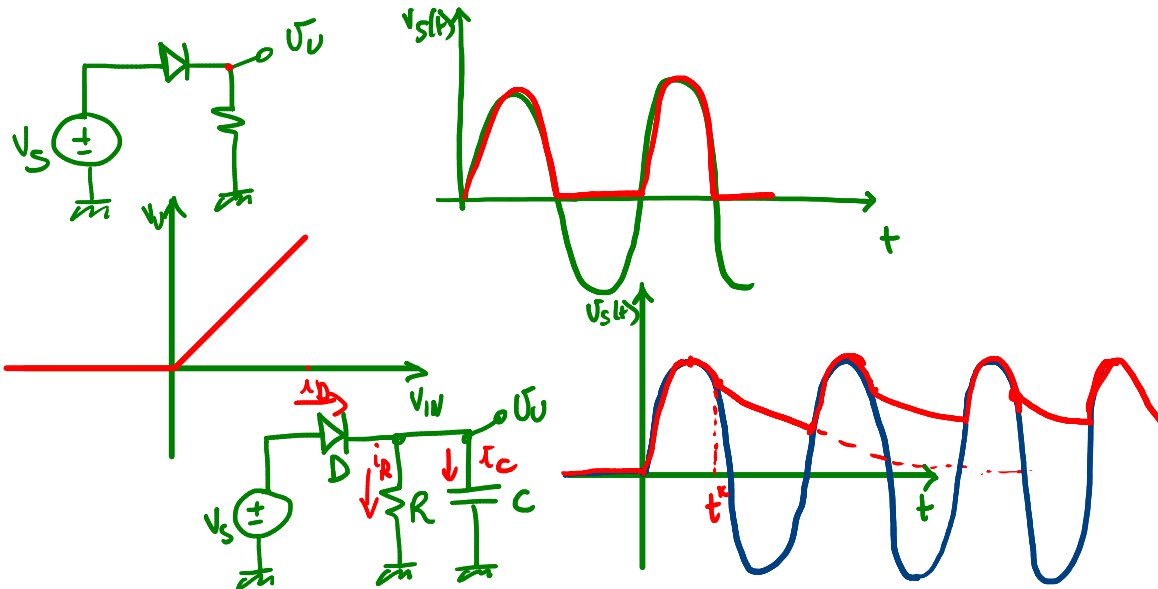
$$\frac{R_1 R_2}{R_1 R_2 + R} = m_3 = \frac{1}{5}$$




Se D é ON $\Rightarrow v_u = v_s$


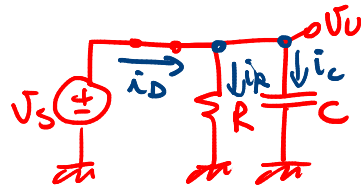


$$\begin{aligned}
 i_D &= i_R + i_C = \\
 &= \frac{v_s}{R} + C \frac{dv_u}{dt} = \\
 &= \frac{v_s}{R} + C \frac{dv_s}{dt} > 0
 \end{aligned}$$
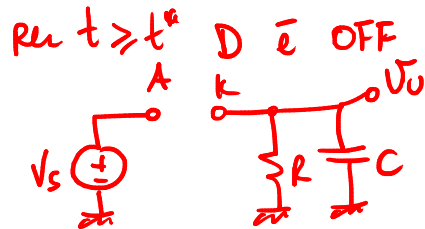
$$t^* : \left(\frac{v_s(t^*)}{R} + C \frac{dv_s(t)}{dt} \right)_{t=t^*} = 0$$



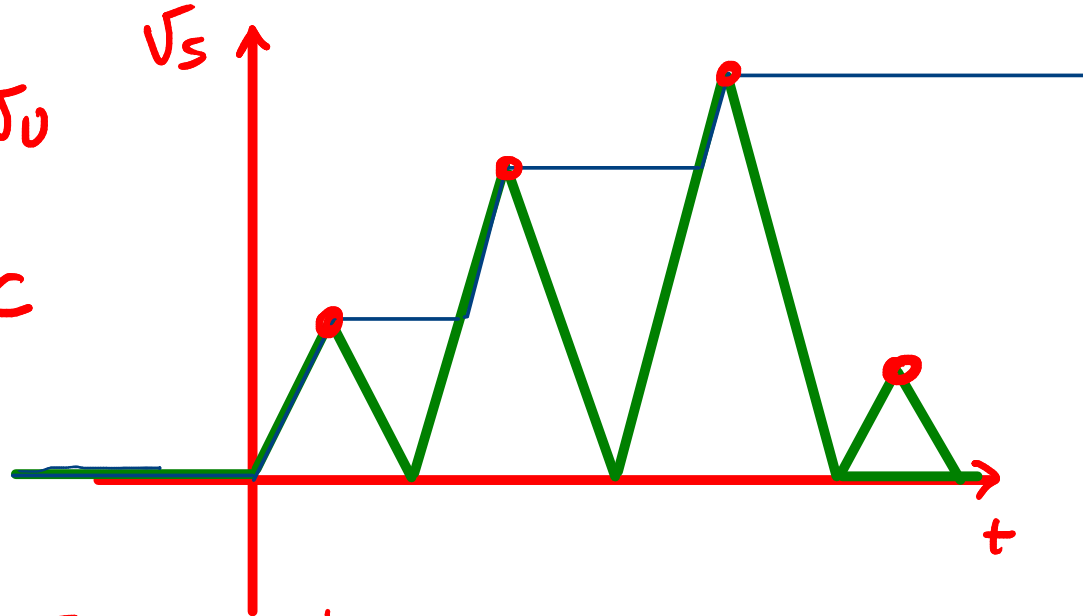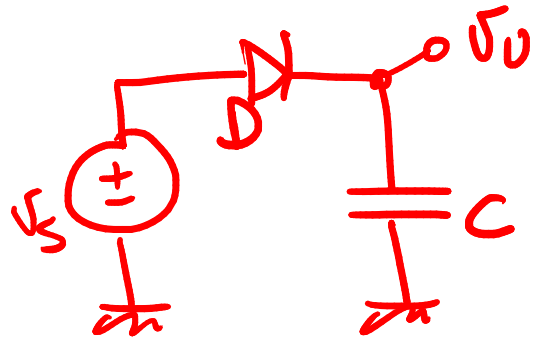per $t = t^*$ $v_u = v_s(t^*) - \frac{(t-t^*)}{\tau}$
 per $t > t^*$ $v_u(t) = v_s(t^*) e^{-\frac{(t-t^*)}{\tau}}$
 $\tau = RC$



$$v_s(t) = [1 + m(t)] \sin(\omega t)$$