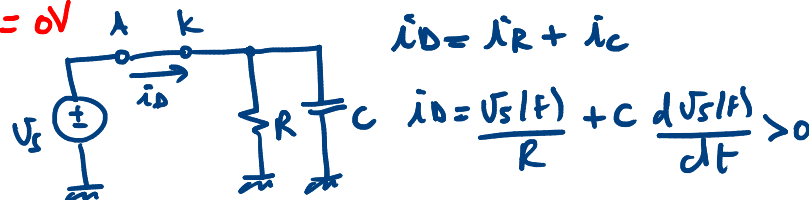


$$V_c(t < 0) = 0V$$

Se D é ON:



$$i_D = i_R + i_C$$

$$i_D = \frac{V_s(t)}{R} + C \frac{dV_s(t)}{dt} > 0$$

$$V_s: \begin{cases} \sigma t & 0 \leq t \leq T \\ -\sigma(t-T) + V_p & T < t \leq 2T \end{cases} \quad \sigma = \frac{V_p}{T} \text{ [V/s]}$$

$$i_D = \frac{-\sigma(t-T) + V_p}{R} - C\sigma \quad i_D(t=t^*) = 0$$

$$-\sigma(t^*-T) + V_p = RC\sigma \quad -\sigma t^* + \sigma T + V_p = RC\sigma$$

$$t^* = \frac{\sigma T + V_p - RC\sigma}{\sigma}$$

$$\text{para } t \geq t^* \quad V_o(t) = V_o(t^*) e^{-\frac{t-t^*}{RC}}$$

$$v_o(t) = V_o + v_n(t) = V_o + r(t)$$


$$RF = \frac{\text{rms}\{v_o(t)\}}{V_o} = \frac{\text{rms}\{r(t)\}}{V_o}$$

$$\eta_R = \frac{\text{Potenza di uscita dovuta alla continua}}{\text{Potenza totale}}$$

$$V_o = \frac{1}{T} \int_0^T v_o(t) dt \quad v_{eff} = \sqrt{\frac{1}{T} \int_0^T v_o^2(t) dt}$$

$$\begin{aligned} v_{eff}^2 &= \frac{1}{T} \int_0^T [V_o + r(t)]^2 dt = \frac{1}{T} \int_0^T [V_o^2 + 2V_or(t) + r^2(t)] dt = \\ &= V_o^2 + \underbrace{\frac{1}{T} \int_0^T r^2(t) dt}_{R_{eff}^2} = V_o^2 + R_{eff}^2 \end{aligned}$$
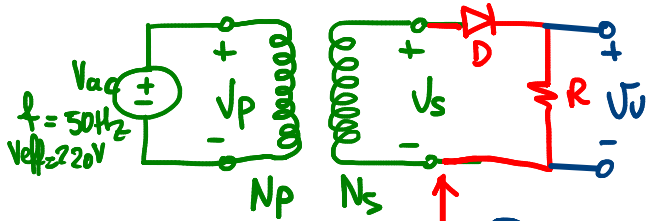
$$RF = \frac{R_{eff}}{V_o} = \frac{\sqrt{v_{eff}^2 - V_o^2}}{V_o} \quad \eta_R = \frac{V_o^2}{v_{eff}^2}$$



$$\frac{V_p}{V_s} = \frac{N_p}{N_s}$$

$$V_s = V_m \sin(\omega t)$$

$$V_v = \frac{V_m}{T} \int_0^{\frac{T}{2}} \sin(\omega t) dt = \frac{V_m}{\pi} \approx 0,318 V_m$$


$$\omega = \frac{2\pi}{T}$$

$$V_{eff} = V_m \sqrt{\frac{1}{T} \int_0^{\frac{T}{2}} \sin^2(\omega t) dt} = V_m \sqrt{\frac{1}{2T} \int_0^{\frac{T}{2}} [1 - \cos(2\omega t)] dt} =$$

$$= \frac{V_m}{2} = 0,5 V_m$$

$$RF = \frac{\sqrt{V_{eff}^2 - V_v^2}}{V_v} = \sqrt{\frac{\pi^2}{4} - 1} \approx 1,211$$
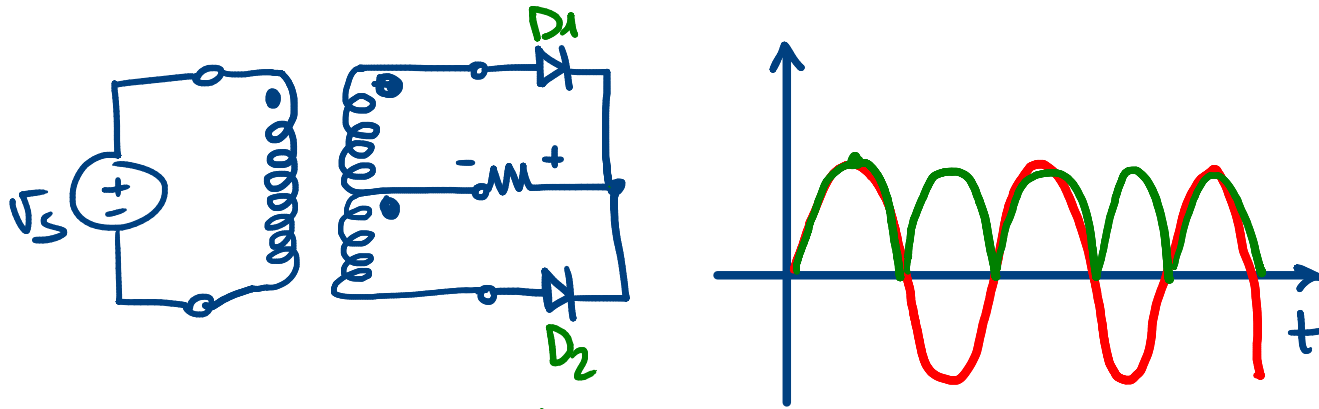
$$\eta_r = \frac{V_v^2}{V_{eff}^2} = \frac{4}{\pi^2} = 0,4053$$



$$v_u = |V_m \sin(\omega t)|$$

$$V_U = \frac{2V_m}{T} \int_0^{\frac{T}{2}} \sin(\omega t) dt = \frac{2V_m}{\pi} = 0,6366 V_m$$



$$V_{\text{eff}} = V_m \sqrt{\frac{2}{T} \int_0^{\frac{T}{2}} \sin^2(\omega t) dt} = V_m \sqrt{\frac{1}{T} \int_0^{\frac{T}{2}} 1 - \cos(2\omega t) dt} =$$

$$= \frac{V_m}{\sqrt{2}} = 0,7101 V_m$$

$$RF = \frac{\sqrt{V_{\text{eff}}^2 - V_U^2}}{V_U} = \sqrt{\frac{\pi^2}{8} - 1} = 0,4834$$

$$M_R = \frac{V_U^2}{V_{\text{eff}}^2} = \frac{8}{\pi^2} = 0,8106$$

PONTE DI GRAETZ

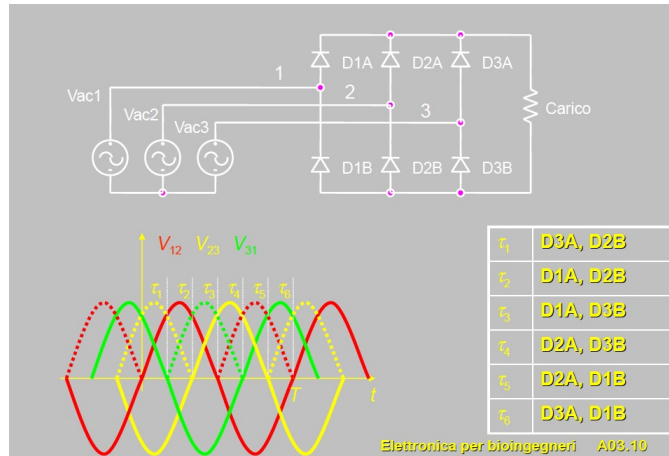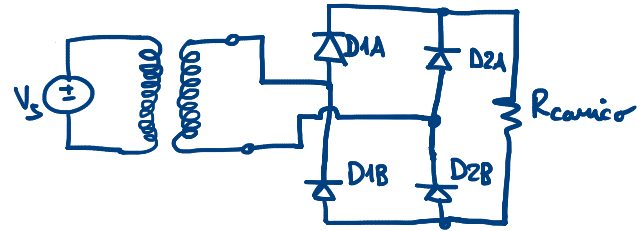


$$V_u = \frac{6V_M}{T} \int_{\frac{2T}{12}}^{\frac{4T}{12}} \sin(\omega t) dt = \frac{3V_M}{\pi} \left(\cos\left(\frac{\pi}{3}\right) - \cos\left(\frac{2\pi}{3}\right) \right) = \frac{3V_M}{\pi} = 0.9549 \cdot V_M$$

$$V_{Ueff} = V_M \sqrt{\frac{6}{T} \int_{\frac{2T}{12}}^{\frac{4T}{12}} \sin^2(\omega t) dt} = V_M \sqrt{\frac{3}{T} \int_{\frac{2T}{12}}^{\frac{4T}{12}} (1 - \cos(2\omega t)) dt} =$$





$$= V_M \sqrt{\frac{3}{T} \left(\frac{T}{6} + \frac{\sqrt{3}}{2\omega} \right)} = V_M \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{4\pi}} = 0.9958 \cdot V_M$$




$$RF = \frac{\sqrt{V_{Ueff}^2 - V_u^2}}{V_u} = 0.04197$$
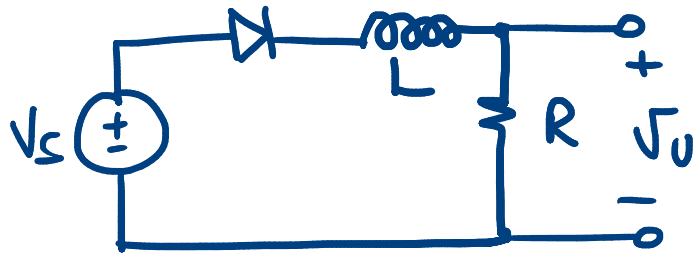
$$\eta_R = \frac{V_u^2}{V_{Ueff}^2} = 0.9982$$


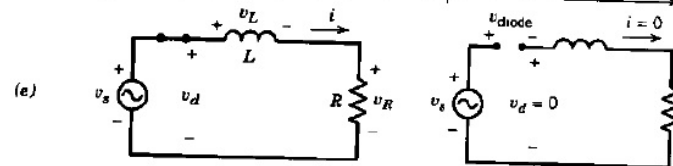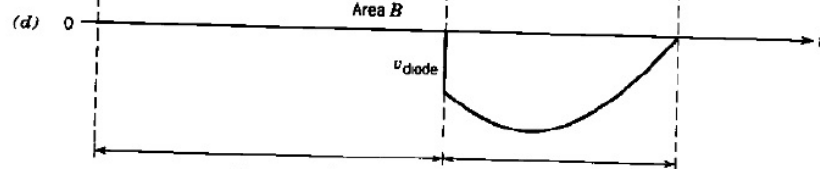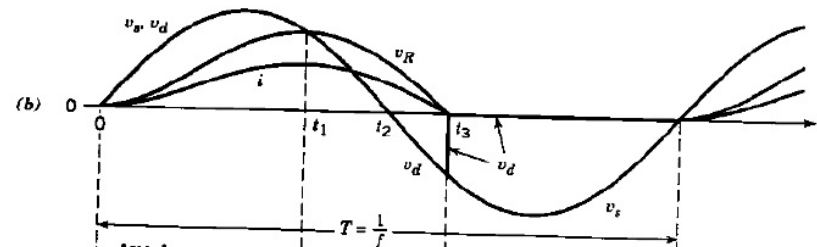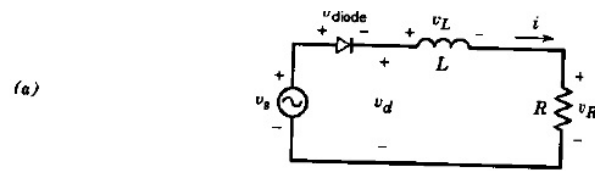
$$v_o(j\omega) = \frac{R}{R + Lj\omega} v_s(j\omega)$$



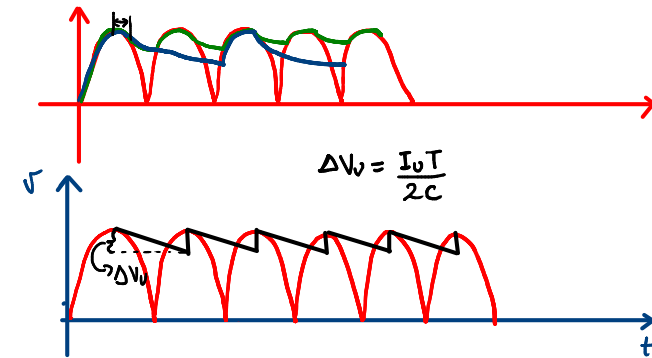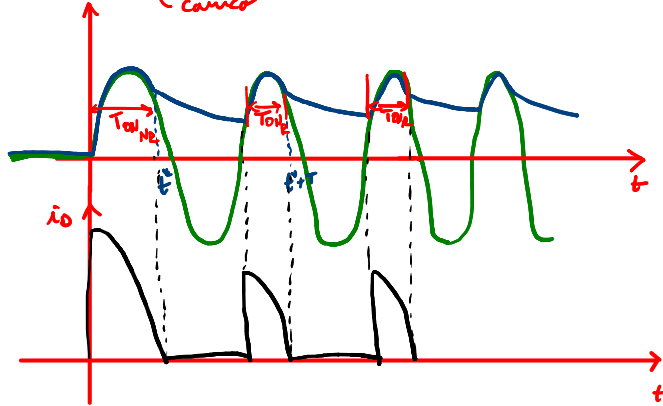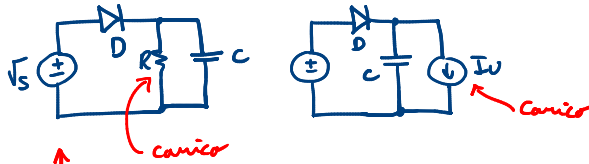

$$V_v = V_m - \frac{\Delta V_v}{2} = V_m - \underbrace{\left(\frac{T}{4C}\right) I_D}_{R_L I_D}$$

$$V_{eff} = \sqrt{\frac{2}{T} \int_0^T (V_m - I_D t)^2 dt} = \sqrt{V_m^2 - 2V_m R_L I_D + \frac{4}{3}(R_L I_D)^2}$$

$$RF = \frac{\sqrt{V_{eff}^2 - V_v^2}}{V_v} = \frac{R_L I_D}{\sqrt{3}(V_m - R_L I_D)}$$

