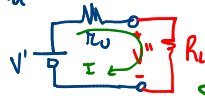


$$V_{nom} > V'$$




$$V_{nom} = V' + 2z \approx V$$

$$S_V = \frac{\delta V'}{\delta V_d} < 0,1 ; S_T = \frac{\delta V'}{\delta T} ; \kappa_U = \frac{\delta V'}{\delta U_0}$$




$$V'' = R_L I = \frac{R_L}{R_u + R_L} V'$$
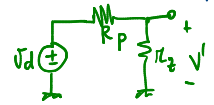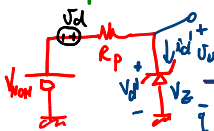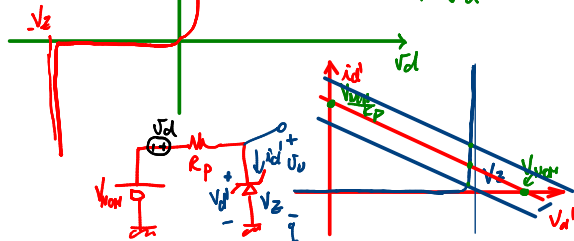
$$\text{Se } \kappa_U \ll R_L \Rightarrow V'' \approx V'$$





$$\frac{\delta V'}{\delta V_d} = \frac{\kappa_z}{R_p + \kappa_z} = S_V$$

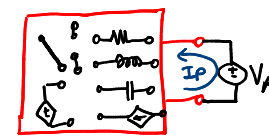
$$V' = \frac{\kappa_z}{R_p + \kappa_z} V_d$$



$$z_p = \frac{V_p}{I_p}$$

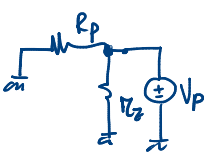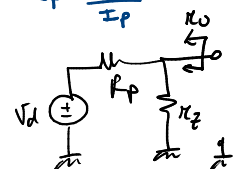


$$\kappa_U = \kappa_z \parallel R_p$$

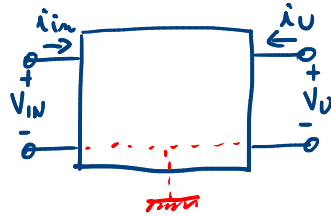



$$V_u = A_v V_{in}$$

$$i_u = A_i i_{in}$$

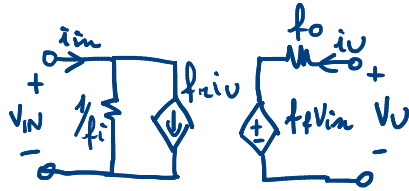

$$\begin{cases} V_u = f_v V_{in} + f_o i_u \\ i_{in} = f_i V_{in} + f_a i_u \end{cases}$$

Se \$f_a = 0\$

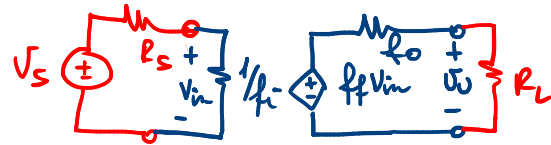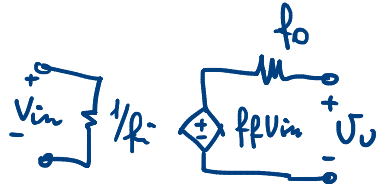

$$V_u = f_v V_{in} \cdot \frac{R_L}{R_L + f_o}$$

$$V_{in} = \frac{1/f_i}{1/f_i + R_s} V_s$$

$$V_u = \underbrace{\frac{R_L}{R_L + f_o} \cdot f_v \cdot \frac{1/f_i}{1/f_i + R_s}}_{A_v} \cdot V_s$$