
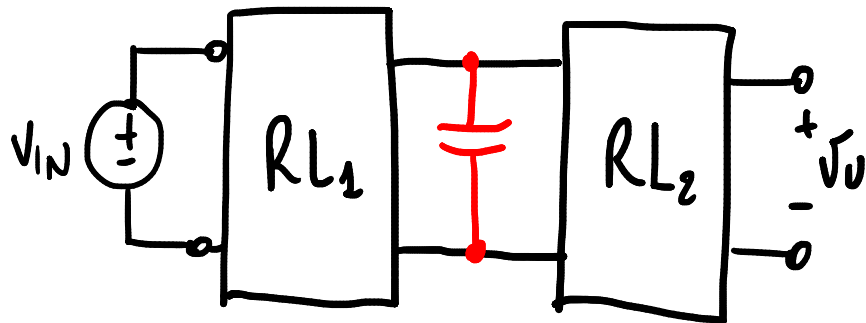

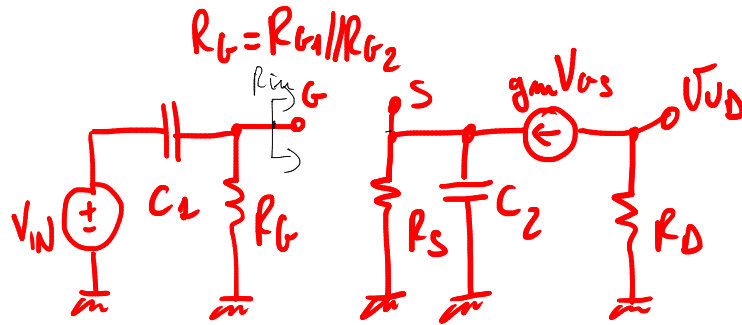
$$A_{v_D} = \frac{-g_m R_D}{1 + \underbrace{g_m R_S}_{=0}} \rightarrow A_{v_D}' \rightarrow -g_m R_D > A_{v_D}$$





$$\omega_{p1} = \frac{1}{R_{G1} C_1}$$

$$R_{G1} = R_G$$

$$\omega_{p2} = \frac{1}{R_{G2} C_2}$$

$$R_{G2} = R_S // \frac{1}{g_m}$$

$R_{in} \rightarrow \infty$

$$A_{vD}(s) = \frac{V_{OD}}{V_{IN}} = \frac{A_{vD0} s (s + \omega_0)}{(s + \omega_{p1})(s + \omega_{p2})}$$

$$A_{vD0} = -g_m R_D \neq 0 \Rightarrow \text{grades num} = \text{grades den.} = 2$$


$$V_{GS} = V_G - V_S \quad V_S = g_m \cdot \left( R_S // \frac{1}{C_2 s} \right) V_{GS} = g_m Z_S V_{GS}$$

$$V_{GS} = V_G - g_m Z_S V_{GS}$$

$$V_{GS} = \frac{V_G}{1 + g_m Z_S}$$

$$V_{OD} = -g_m R_D V_{GS}$$

$$\omega_0 = \frac{1}{R_S C_2}$$

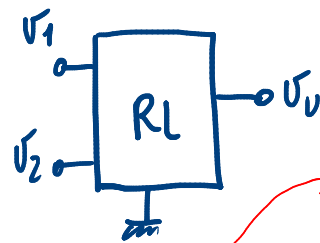

$$v_0 = A_d(v_1 - v_2)$$

$$v_0 = A_1 v_1 + A_2 v_2$$

$$v_d = v_1 - v_2$$

$$v_c = \frac{v_1 + v_2}{2}$$

$$\begin{cases} v_d + v_2 = v_1 \\ v_c = \frac{v_1 + v_2}{2} \end{cases} \Rightarrow v_c = \frac{v_d + v_2 + v_2}{2} = \frac{v_d}{2} + v_2$$

$$\begin{cases} v_2 = v_c - \frac{v_d}{2} \\ v_1 = v_c + \frac{v_d}{2} \end{cases}$$



$$v_0 = A_1 \left( v_c + \frac{v_d}{2} \right) + A_2 \left( v_c - \frac{v_d}{2} \right) =$$

$$= \frac{A_1 - A_2}{2} v_d + (A_1 + A_2) v_c =$$





$$\underbrace{\frac{A_1 - A_2}{2}}_{A_d} \quad \underbrace{(A_1 + A_2)}_{A_c} =$$

$$v_0 = A_d v_d + A_c v_c$$

$$\text{CHRR} = \frac{A_d}{A_c}$$

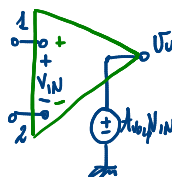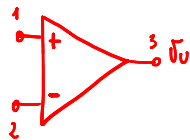

$A_{VOL} \phi$

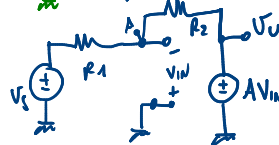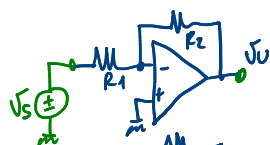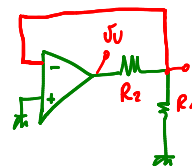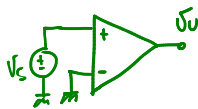

$$U_U = A V_{IN}$$

$$V_{IN} = -V_A$$


$$V_A = \frac{R_2}{R_1 + R_2} V_S + \frac{R_1}{R_1 + R_2} U_U$$

$$U_U = -\frac{A R_2}{R_1 + R_2} V_S - \frac{A R_1}{R_1 + R_2} U_U$$



$$U_U \left[ 1 + \frac{A R_1}{R_1 + R_2} \right] = -\frac{A R_2}{R_1 + R_2} V_S$$

$$A_U = \frac{U_U}{V_S} = \frac{-\frac{A R_2}{R_1 + R_2}}{1 + \frac{A R_1}{R_1 + R_2}} \quad \begin{matrix} A \gg 1 \\ A \rightarrow \infty \end{matrix}$$
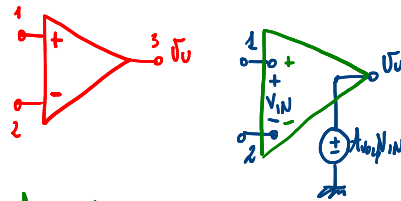
$$A_U = \frac{-\frac{A R_2}{R_1 + R_2}}{\frac{A R_1}{R_1 + R_2}} = -\frac{R_2}{R_1}$$



$A_{VOL} \phi$

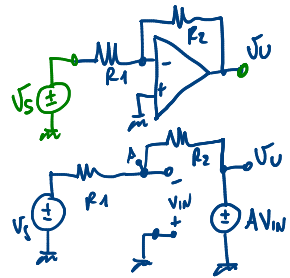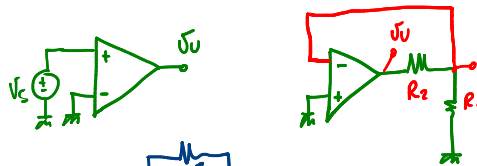

$$V_U = A V_{IN}$$

$$V_{IN} = -V_A$$

$$V_A = \frac{R_2}{R_1 + R_2} V_S + \frac{R_1}{R_1 + R_2} V_U$$

$$V_U = -\frac{A R_2}{R_1 + R_2} V_S - \frac{A R_1}{R_1 + R_2} V_U$$

$$V_U \left[ 1 + \frac{A R_1}{R_1 + R_2} \right] = -\frac{A R_2}{R_1 + R_2} V_S$$

$$A_V = \frac{V_U}{V_S} = \frac{-\frac{A R_2}{R_1 + R_2}}{1 + \frac{A R_1}{R_1 + R_2}} \quad \begin{matrix} A \gg 1 \\ A \rightarrow \infty \end{matrix}$$

$$A_V = \frac{-\frac{A R_2}{R_1 + R_2}}{\frac{A R_1}{R_1 + R_2}} = -\frac{R_2}{R_1}$$