
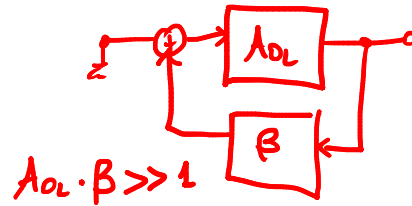



$$U_U = - \frac{A R_2}{1 + A \frac{R_1}{R_1 + R_2}} \cdot U_S$$

A_f

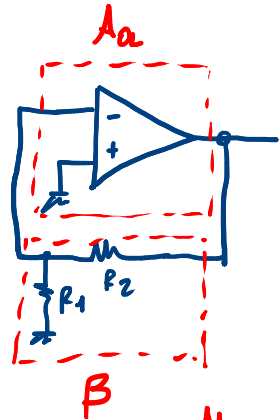pu $A \rightarrow +\infty \Rightarrow A_f \rightarrow - \frac{R_2}{R_1}$



$$A = A_{OL} \phi$$

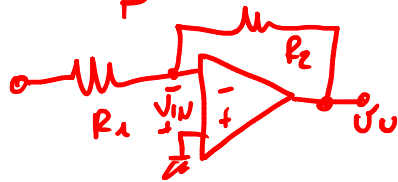


$$U_U = A_{OL} \phi \cdot U_{IN}$$

$$U_{IN} = \frac{U_U}{A_{OL} \phi}$$

$$U_U = - \frac{A R_2}{1 + A \frac{R_1}{R_1 + R_2}} U_S$$

$$U_{IN} = - \frac{\cancel{A} R_2}{1 + A \frac{R_1}{R_1 + R_2}} \cdot \frac{1}{\cancel{A}} U_S$$
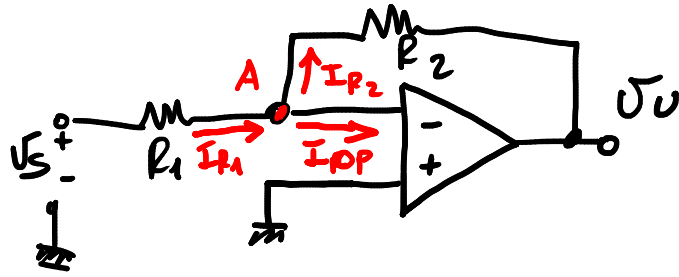
$$\lim_{A \rightarrow +\infty} U_{IN} = \phi$$





$$V^+ = 0 \quad V^+ \approx V^- \approx 0V \Rightarrow V_A \approx 0V$$

$$I_{R_1} = I_{OP} + I_{R_2} \quad I_{OP} = 0 \Rightarrow I_{R_1} \approx I_{R_2}$$

$$I_{R_1} = \frac{V_S - V_A}{R_1} = \frac{V_S}{R_1} = I_{R_2}$$
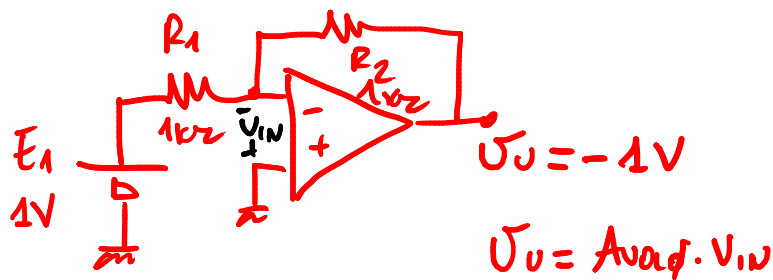
$$V_U = V_A - R_2 I_{R_2} = -R_2 \cdot \frac{V_S}{R_1} = - \underbrace{\frac{R_2}{R_1}}_{A_f} V_S$$



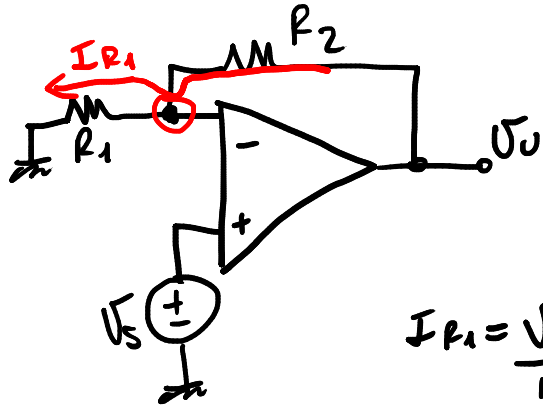

$$V^+ \approx V^-$$


$$V^+ = V_s \Rightarrow V^- \approx V_s$$

$$I_{R_1} = \frac{V_s}{R_1}$$

$$V_o = V^- + R_2 I_{R_2} = V_s + R_2 \frac{V_s}{R_1} =$$

$$= \left(1 + \frac{R_2}{R_1}\right) V_s$$






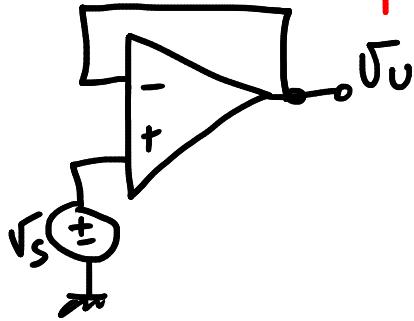
$$\underbrace{\left(1 + \frac{R_2}{R_1}\right)}_{A_f}$$



$$V_o = V^-$$


$$V^+ \approx V^-$$
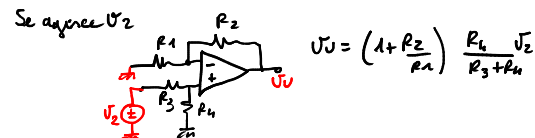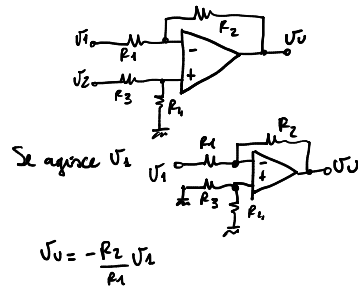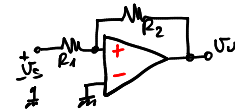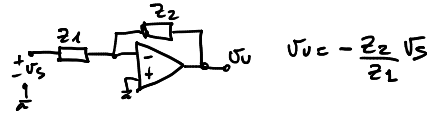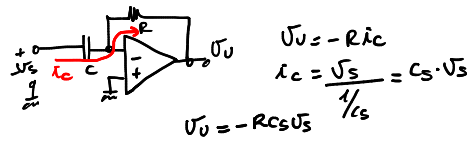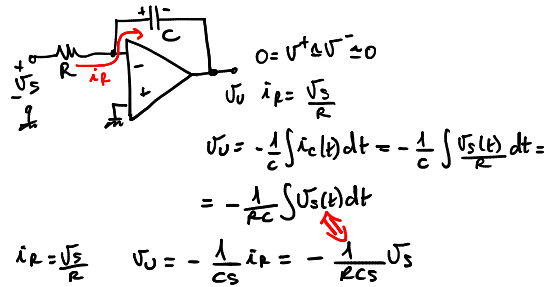
$$V_s = V^+ \Rightarrow V_o \approx V_s$$




$$U_U = -\frac{R_2}{R_1} U_1 + \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3 + R_4} U_2 = -\frac{R_2}{R_1} U_1 + \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3} \frac{U_2}{1 + \frac{R_4}{R_3}}$$

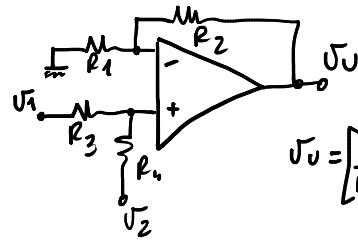
Se $\frac{R_2}{R_1} = \frac{R_4}{R_3} \Rightarrow U_U = -\frac{R_2}{R_1} (U_1 - U_2)$


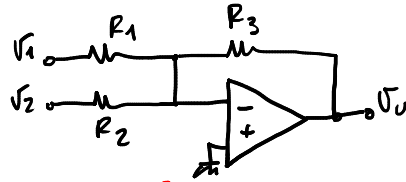
$$V_U = \left[\frac{R_4}{R_3 + R_4} V_1 + \frac{R_3}{R_3 + R_4} V_2 \right] \left(1 + \frac{R_2}{R_1} \right)$$


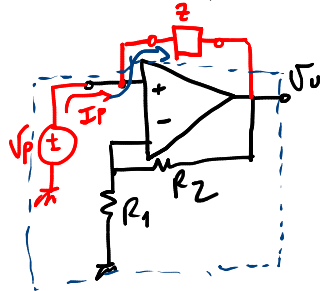
$$V_U = - \left(\frac{R_3}{R_1} V_1 + \frac{R_3}{R_2} V_2 \right)$$




$$V^+ = V_p$$

$$V^+ \approx V^- \approx V_U$$

$$V_U = \left(1 + \frac{R_2}{R_1} \right) V_p$$

$$I_p = \frac{V_p - V_U}{R_1} = \frac{V_p - \left(1 + \frac{R_2}{R_1} \right) V_p}{R_1}$$

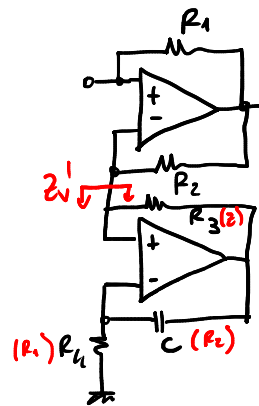
$$\frac{V_p}{I_p} = Z_{in} = - \frac{R_1 R_2}{R_1}$$







$$Z_U' = - R_3 R_4 C s$$

$$Z_U = - \frac{R_1 Z_U'}{R_2} \quad (R_1) Z_U'$$

$$Z_U = \frac{R_1 R_3 R_4 C s}{R_2}$$

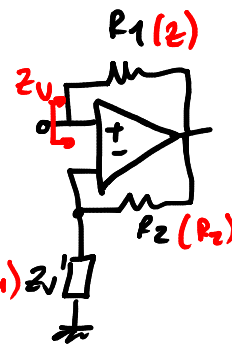

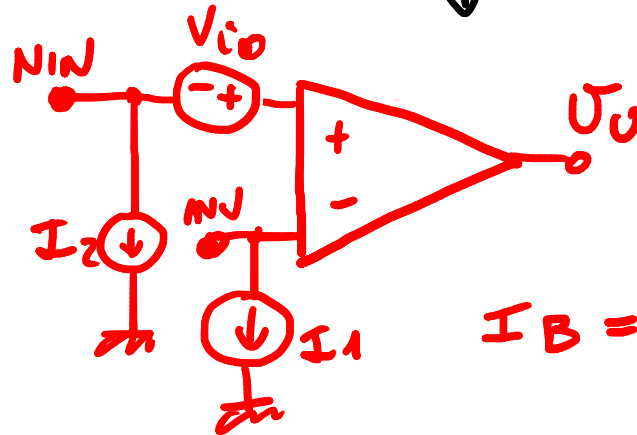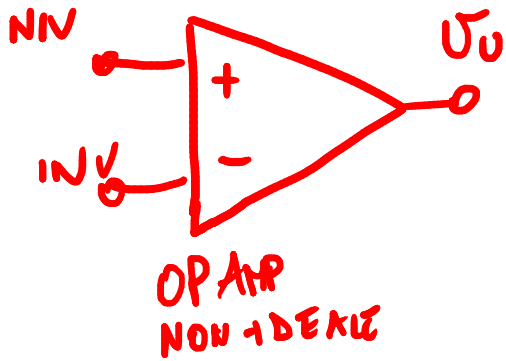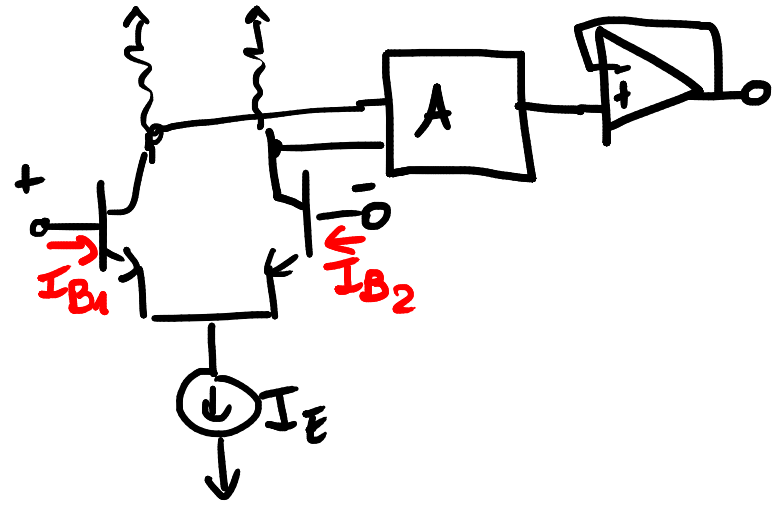
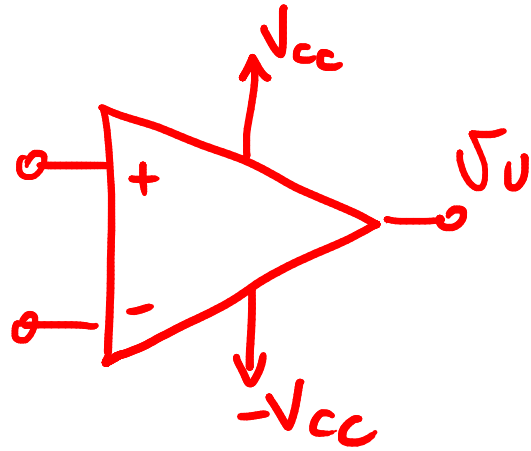


$$I_B = \frac{I_1 + I_2}{2}$$


$$I_{off} = |I_1 - I_2|$$

$$I_1 = \begin{cases} I_B + \frac{I_{off}}{2} \\ I_B - \frac{I_{off}}{2} \end{cases}$$
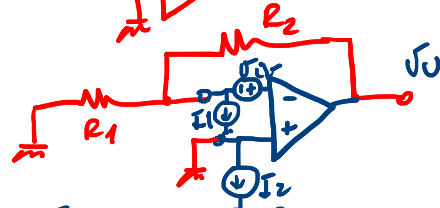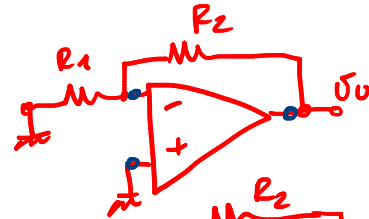
$$I_2 = \begin{cases} I_B - \frac{I_{off}}{2} \\ I_B + \frac{I_{off}}{2} \end{cases}$$




Se agisce I_2

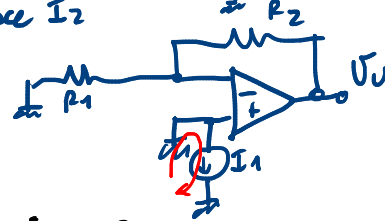



Se agisce I_1

$$U_{oI_2} = 0V$$

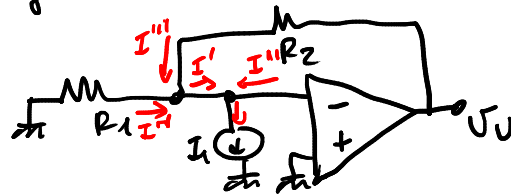

$$U_{oI_1} = R_2 I_1$$


Se agisce V_{io}

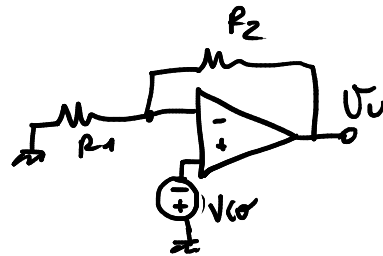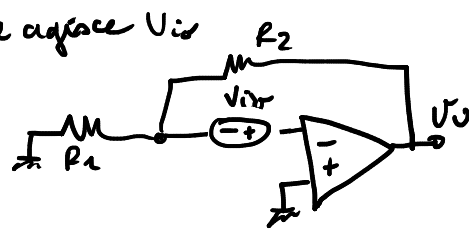

$$U_{oio} = -U_{io} \left(1 + \frac{R_2}{R_1} \right)$$

$$U_{Tot} = R_2 I_1 - U_{io} \left(1 + \frac{R_2}{R_1} \right)$$
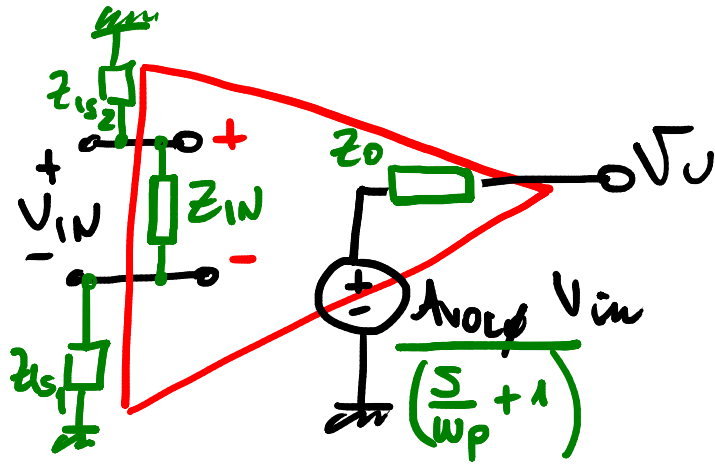
$$\begin{cases} V_{io} < 0 \\ I_1 = I_B + \frac{I_{off}}{2} \end{cases}$$



$$A_d = \frac{A_{VOL} \delta}{1 + \frac{s}{\omega_p}}$$

$$V_O = A_d V_d + A_c V_c = A_d \left(V_d + \frac{V_c}{CMRR} \right) \quad CMRR = \frac{A_d}{A_c}$$