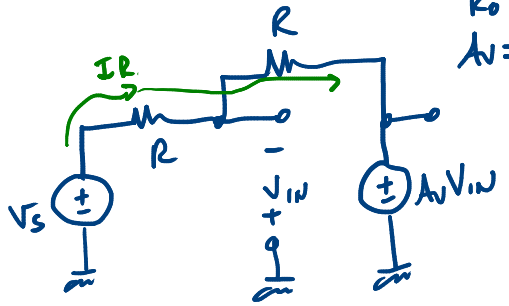


$$I_{P_s} = \frac{V_s}{R}$$

$$\frac{V_s}{I_{P_s}} = R$$

$R_{in} \rightarrow \infty$
 $R_o \rightarrow 0$
 $A_v = 10$





$$I_R = \frac{-V_{in} - A_v V_{in}}{R} = \frac{-V_{in}(1 + A_v)}{R}$$

$$-V_{in} = V_s - R I_R \Rightarrow I_R = \frac{V_s - R I_R (1 + A_v)}{R}$$


$$R[1 + (1 + A_v)] I_R = V_s(1 + A_v)$$

$$\frac{V_s}{I_R} = R + \frac{R}{1 + A_v}$$

$$Z_{in} = \frac{R}{1 - A_v}$$

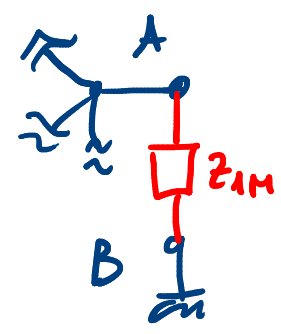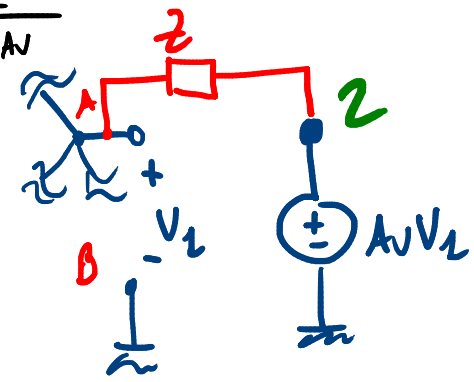

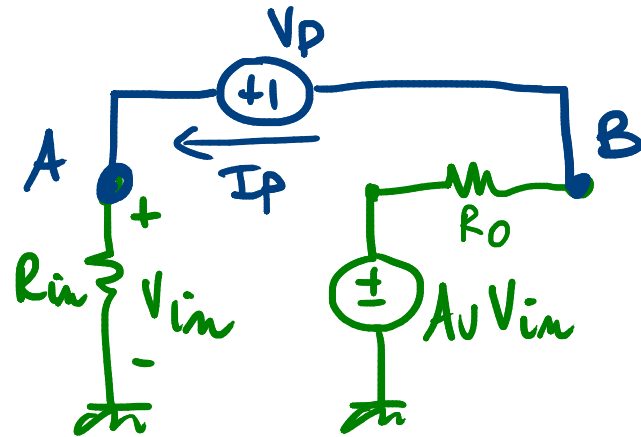
$$Z_{out} = \frac{Z}{1 - \frac{1}{A_v}}$$






$$\begin{aligned}
 V_{IN} &= V_p + A_v V_{IN} - R_o I_p \\
 V_{IN} &= R_{in} I_p
 \end{aligned}
 \left. \begin{array}{l} \\ \end{array} \right\} R_{in} I_p = V_p + A_v R_{in} I_p - R_o I_p$$


$$V_p = [R_{in}(1 - A_v) + R_o] I_p$$
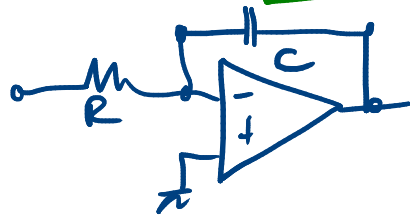
$$R_{VAB} = \frac{V_p}{I_p} = R_{in}(1 - A_v) + R_o$$



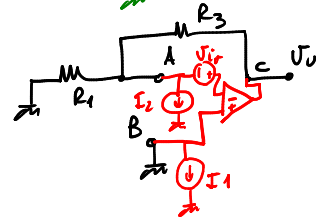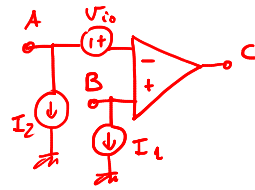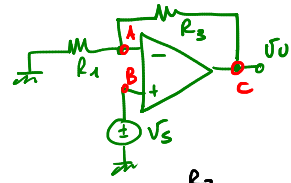


Agisce I1

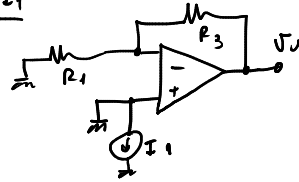


$$V_U = 0$$

Agisce Vio

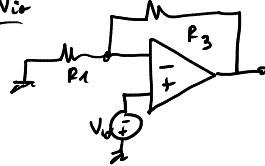

$$V_{U_{Vio}} = -V_{io} \left(1 + \frac{R_3}{R_1}\right)$$

Agisce I2

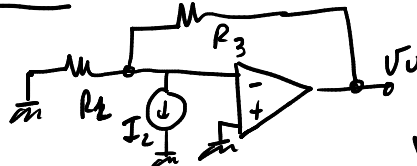

$$V_{U_{I2}} = R_3 I_2$$


$$V_U = R_3 I_2 - V_{io} \left(1 + \frac{R_3}{R_1}\right)$$

$$I_B = \frac{I_1 + I_2}{2} \quad I_{io} = |I_1 - I_2|$$

$$V_{io} \begin{cases} < 5 \text{ mV} \\ > -5 \text{ mV} \end{cases}$$

$$I_1 = \begin{cases} \frac{I_B + I_{io}}{2} \\ \frac{I_B - I_{io}}{2} \end{cases} \quad I_2 = \begin{cases} \frac{I_B - I_{io}}{2} \\ \frac{I_B + I_{io}}{2} \end{cases}$$
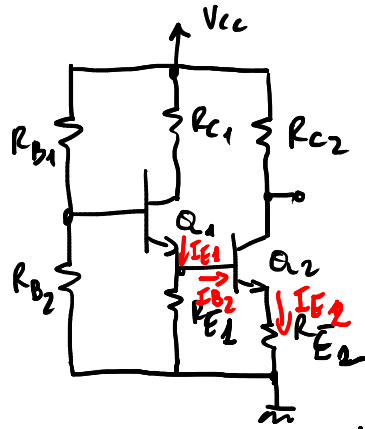
$$V_{U_{max}} = 10,09 \text{ mV} \quad \begin{cases} V_{io} = -5 \text{ mV} \\ I_2 = I_B + \frac{I_{io}}{2} = 90 \text{ nA} \end{cases}$$



$$I_{E2} = (\beta_{FE} + 1) I_{B2}$$

$$I_{B2} = \frac{I_{E2}}{\beta_{FE} + 1} = I_{B1}$$

$$V_{B2} = V_{BEON} + R_{E2} I_{E2}$$

$$V_{B2} = ? = R_{C1} (I_{E1} - I_{B2})$$

$$R_{E2} = \frac{R_{C1} (I_{E1} - I_{B2}) - V_{BEON}}{I_{E2}} = 640 \Omega$$

$$V_{B2} = V_{E1} = 1,98V$$

$$V_{CE2} = V_{C2} - V_{E2}$$

$$V_{C2} = V_{CC} - R_{C2} I_{C2} = V_{CC} - R_{C2} \frac{\beta_{FE} I_{E2}}{\beta_{FE} + 1} = 3,09V$$

$$V_{E2} = R_{E2} I_{E2} = 1,28V$$

$$V_{CE2} = 1,81V$$

Q2 in ZAD OK

$$V_{CE1} = V_{C1} - V_{E1}$$

$$V_{C1} = V_{CC} - R_{C1} I_{C1} =$$


$$= V_{CC} - R_{C1} \frac{\beta_{FE} I_{E1}}{\beta_{FE} + 1} =$$

$$= 6,059V$$

$$V_{CE1} = 4,079V$$

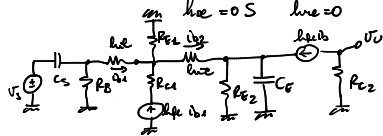
Q1 in ZAD OK

$R_{E2} = 600\Omega$ $h_{fe1} = h_{fe2} = h_{fe} = 300$
 $h_{re1} = h_{re2} = h_{re} = 4.8\mu\Omega$
 $h_{oe} = 0.5$ $h_{ue} = 0$



$$A_U(s) = A_{U0} \frac{s}{(s + \omega_{p1})(s + \omega_{p2})}$$

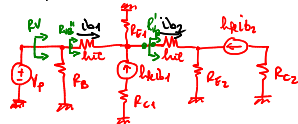$\omega_{p1} \ll \omega_{p2}$ $\omega_{p1} = \frac{1}{C_E1 R_{E1}}$



$$R_{ia} = R_B \parallel \left[h_{ie} + (R_{C1} + R_{E2}(h_{fe} + 1)) \right] = 17.866k\Omega$$


$$R_{iB1} = h_{ie} + R_{E2}(h_{fe} + 1)$$

$$R_{iB2} = h_{ie} + R_{E1}(h_{fe} + 1) \quad R_{UE} = R_{iB2} \parallel R_{E2}$$

$$R_{iE} = R_B \parallel R_{iB1}$$

$$\omega_{p1} = \frac{1}{C_E1 R_{iE}} = 55.97 \text{ rad/sec}$$

Calculate ω_{p2}

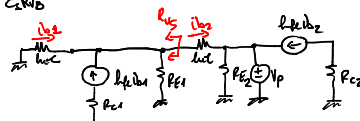


$$R_{iCE} = R_{C1} \parallel R_{iCE1}$$

$$R_{iCE1} = \frac{h_{ie} + R_{E2}}{h_{fe} + 1} \quad R_{iE2} = R_{C1} \parallel \left[\frac{h_{ie}}{h_{fe} + 1} \right]$$

$$R_{iCE} = 15.58\Omega \quad \omega_{p2} = 64.17 \text{ Mrad/sec}$$
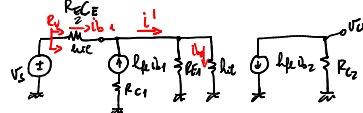
$$\omega_0 = \frac{1}{R_{iCE}} = 1667 \text{ Mrad/sec}$$



$$V_U = -h_{fe} i_{B2} R_{C2} \quad i_{B2} = \frac{R_{C1}}{R_{C1} + h_{ie}} \cdot i'$$

$$i' = (h_{fe} + 1) i_{B1}$$

$$i_{B1} = \frac{V_S}{R_{iE}} \quad R_{iE} = h_{ie} + (R_{C1} + R_{E2})(h_{fe} + 1)$$

$$A_{U0} = -h_{fe} R_{C2} \cdot \frac{R_{C1}}{R_{C1} + h_{ie}} \cdot \frac{(h_{fe} + 1)}{h_{ie} + (R_{C1} + R_{E2})(h_{fe} + 1)} = -275.9 (48.82dB)$$