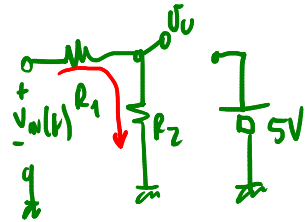


$0 \leq t \leq 1 \text{ ms} : D_1 \text{ ON} \wedge D_2 \text{ OFF}$




$$V_o(t) = \frac{R_2}{R_1 + R_2} V_{in}(t)$$

$1 \text{ ms} < t \leq 2 \text{ ms} : D_1 \text{ ON} \wedge D_2 \text{ OFF}$

$$V_o(t) = \frac{R_2}{R_1 + R_2} V_{in}(t)$$

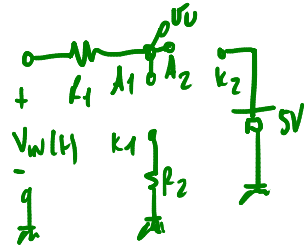$2 \text{ ms} < t \leq 4 \text{ ms} : D_1 \text{ OFF} \wedge D_2 \text{ OFF}$




$$V_o(t) = V_{in}(t)$$

$$\overline{V_o(t)} = \frac{1}{T} \int_0^T V_o(t) dt = \frac{2.5 - 2.25}{4 \cdot 2} = \frac{2.5}{4} = \frac{1.25}{2} = 0.625 \text{ V}$$

$$V_{GS1} = V_{G1} - V_{S1}$$
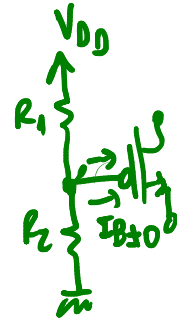
$$V_{G1} = \frac{R_2}{R_1 + R_2} V_{DD}$$



$$I_B \ll \frac{V_{DD}}{R_1 + R_2}$$

$$V_{S1} = ? = R_S I_{DS1}$$

$$\begin{cases} V_{GS1} = \frac{R_2}{R_1 + R_2} V_{DD} - R_S I_{DS1} \\ I_{DS1} = \frac{k}{2} (V_{GS1} - V_T)^2 \end{cases}$$

$$R_S^2 I_{DS1}^2 - \left[2R_S (V_{G1} - V_T) + \frac{2}{k} \right] I_{DS1} + (V_{G1} - V_T)^2 = 0$$

$$I_{DS1} = \begin{cases} 1 \text{ mA} & \text{OK} & V_{GS1} \geq V_T \\ 1.5675 \text{ mA} & \end{cases}$$

$$V_{GS1} = 2 \text{ V} \geq V_T = 1 \text{ V} \quad \underline{\text{OK inversion}}$$

$$I_{DS1} = I_{DS2} = 1 \text{ mA} \quad V_{GS1} = 2 \text{ V} \Rightarrow V_{GS2} = 2 \text{ V}$$

$$V_{DS1}, V_{DS2}$$

$$V_{G2} = \frac{R_{G4}}{R_{G4} + R_{G3}} V_{DD} = 8 \text{ V}$$

$$V_{S2} = V_{G2} - V_{S2} = 6 \text{ V} = V_{D2}$$

$$V_{DS1} = V_{D1} - V_{S1} = 2 \text{ V} \Rightarrow V_{GS1} - V_T = 1 \text{ V}$$


Sat. M_1 verificata

$$V_{S1} = R_S I_{DS1} = 4 \text{ V}$$

$$V_{DS2} = V_{D2} - V_{S2} \quad V_{D2} = V_{DD} - R_{D2} \cdot I_{DS1} = 8 \text{ V}$$

$$V_{DS2} = V_{D2} - V_{S2} = 2 \text{ V} \Rightarrow V_{GS2} - V_T = 1 \text{ V}$$

Sat M_2 verificata

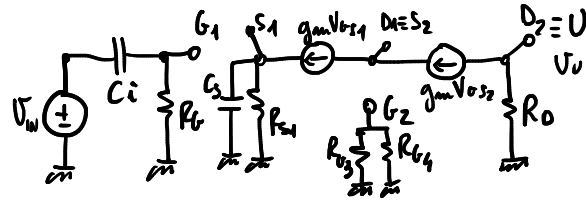



$$A_V(s) = \frac{V_U(s)}{V_W(s)} = \frac{A_{V0} S (S + \omega_0)}{(S + \omega_{p1})(S + \omega_{p2})}$$


$$\omega_{p1} = \frac{1}{C_i R_b} = 40 \text{ rad/sec}$$

$$\omega_{p2} = \frac{1}{C_s R_{s1} \parallel \frac{1}{g_m}} = 2,25 \text{ Mrad/sec}$$

$$\omega_0 = \frac{1}{C_s R_{c1}} = 250 \text{ Krad/sec}$$


calculator A_{V0}

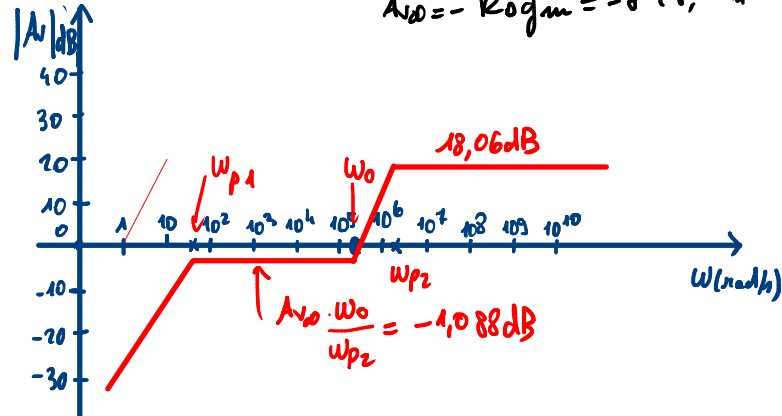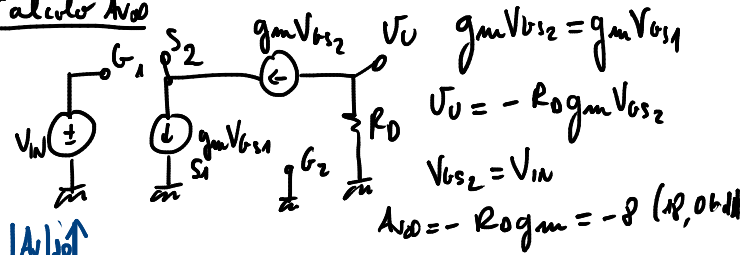

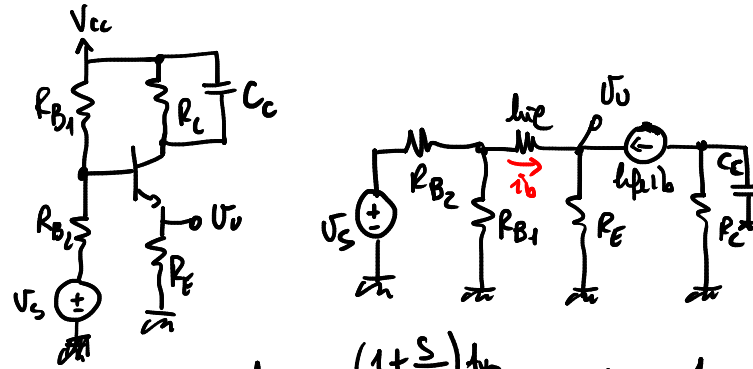

$$A_v(s) = \frac{(1 + \frac{s}{\omega_0}) A_{v0}}{(1 + \frac{s}{\omega_{p1}})}$$

$$\omega_{p1} = \frac{1}{C_c R_c}$$

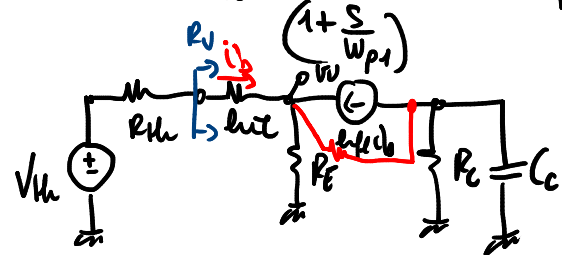

$$V_{th} = \frac{R_{B1}}{R_{B1} + R_{B2}} V_s \quad R_{th} = R_{B1} \parallel R_{B2} \quad V_o = + R_c (\beta + 1) i_b$$

$$R_v = R_{th} + R_E (\beta + 1) \quad i_b = \frac{V_{th}}{R_{th} + R_v} \quad V_o = + R_c (\beta + 1) \frac{V_{th}}{R_{th} + R_v}$$

$$\frac{V_o}{V_s} = + \frac{R_c (\beta + 1)}{R_{th} + R_v} \cdot \frac{R_{B1}}{R_{B1} + R_{B2}} = A_v(s)$$

$$A_v(s) = \frac{A_{v0} \left(1 + \frac{s}{\omega_0}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right)} \quad \omega_{p1} = \frac{1}{R_c C_c}$$