
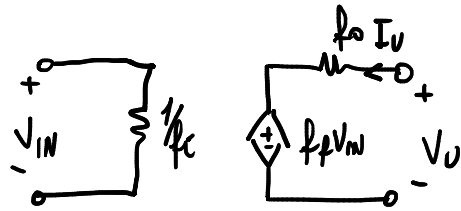


$$V_U = f_o I_U + f_f V_{IN}$$

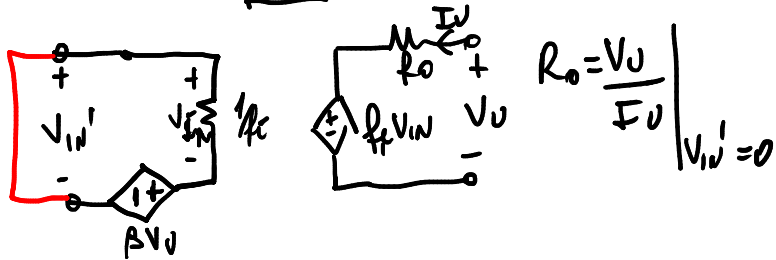

$$R_o = \frac{V_U}{I_U} \Big|_{V_{IN}=0}$$



$$R_o = \frac{V_U}{I_U} \Big|_{V_{IN}'=0}$$

$$V_{IN} = -\beta V_U$$


$$V_U = f_o I_U + f_f V_{IN}$$

$$V_U = f_o I_U - \beta f_f V_U$$

$$V_U [1 + \beta f_f] = f_o I_U$$

$$\frac{V_U}{I_U} = R_o = \frac{f_o}{1 + \beta f_f}$$

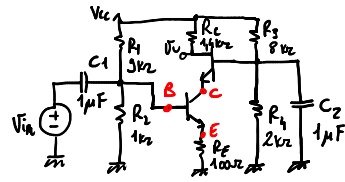
$$\beta = \frac{f_o - R_o}{R_o f_f} = 9,99$$



$V_{CC} = 10V$
 $\beta_{FE} = 100$
 $R_1 \text{ e } R_2 \text{ uguali}$
 $r_{bb'} = 100 \Omega$
 $I_{C1} = 3 \text{ mA}$
 $I_{C2} = 3 \text{ mA}$


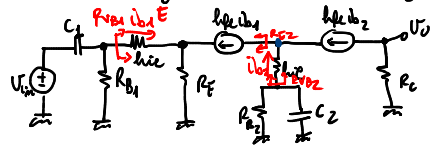
$$r_{in} = r_{bb'} + \frac{V_T}{I_C} \beta_{FE} = 367 \Omega$$



$$R_{B1} = R_1 \parallel R_2$$

$$R_{B2} = R_3 \parallel R_4$$

$$h_{FE} i_{b1} = (h_{FE} + 1) i_{b2}$$


$$i_{b2} = \frac{h_{FE} i_{b1}}{(h_{FE} + 1)}$$

$$A_v(s) = \frac{V_{out}}{V_{in}} = \frac{h_{FE} \omega (S + \omega_0)}{(S + \omega_{p1})(S + \omega_{p2})}$$

$$\omega_0 = \frac{1}{R_{B2} C_2} \quad \omega_{p2} = \frac{1}{C_2 R_{Vc2}}$$


$$R_{Vc2} = ? = R_{B1} \parallel R_{Vb1} \quad R_{Vb1} = r_{in} + R_E (h_{FE} + 1)$$
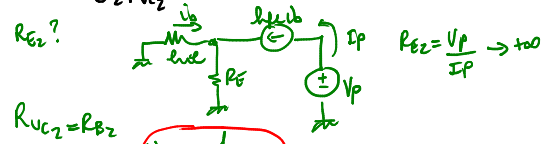
$$\omega_{p1} = \frac{1}{C_2 R_{Vc2}} \Rightarrow R_{Vc2} = R_{B2} \parallel R_{Vb2} \quad R_{Vb2} = r_{in} + R_{E2} (h_{FE} + 1)$$



$$R_{Vc2} = R_{B2}$$

$$\omega_{p1} = \frac{1}{C_2 R_{B2}}$$

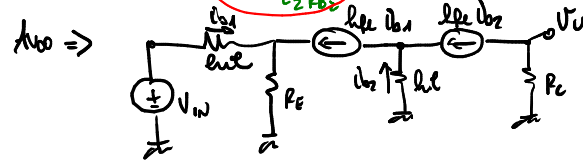


$$V_{out} = -R_C h_{FE} i_{b2} \quad h_{FE} i_{b1} = (h_{FE} + 1) i_{b2} \quad i_{b2} = \frac{h_{FE} i_{b1}}{h_{FE} + 1}$$

$$i_{b1} = \frac{V_{in}}{R_{in}} = \frac{V_{in}}{r_{in} + R_E (h_{FE} + 1)}$$

$$A_{v0} = -R_C h_{FE} \frac{h_{FE}}{(h_{FE} + 1)} \cdot \frac{1}{r_{in} + R_E (h_{FE} + 1)} = -12,53 \text{ (22 dB)}$$

$\beta_{FE} = 300$
 $r_{be} = 900\Omega$

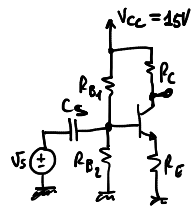$\beta_{FE} = 100$
 $I_C = 2\text{mA}$
 $A_{CB} \geq 10 \quad f \in [100\text{Hz}, 20\text{kHz}]$



$$A_{V_{CB}} = \left| - \frac{R_C \beta_{FE}}{r_{be} + R_E (\beta_{FE} + 1)} \right| \approx \left| - \frac{R_C}{R_E} \right| \geq 10$$


$R_C = 4\text{k}\Omega \quad R_E = 200\Omega$

$V_C = V_{CC} - R_C I_C = 7\text{V}$

$V_E = R_E \frac{(\beta_{FE} + 1) I_C}{\beta_{FE}} = 0,404\text{V}$

$V_{CE} = 6,596\text{V}$
 $I_C = 2\text{mA}$
 $I_B = 20\mu\text{A}$

$V_B = V_E + V_{BE(on)} = 1,104\text{V}$

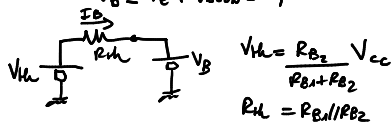


$V_{th} = \frac{R_{B2}}{R_{B1} + R_{B2}} V_{CC}$
 $R_{th} = R_{B1} // R_{B2}$

$V_{th} = R_{th} I_B + V_E$

$\frac{R_{B2}}{R_{B1} + R_{B2}} V_{CC} = R_{th} I_B + V_E$

$\begin{cases} R_{B2} V_{CC} = R_{B1} R_{B2} I_B + (R_{B1} + R_{B2}) V_E \\ R_{B1} + R_{B2} = 100\text{k}\Omega \end{cases}$

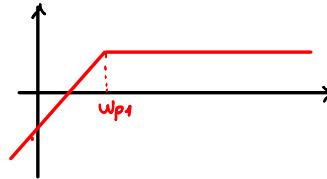$A_V(s) = \frac{A_{V_{CB}} S}{(S + \omega_{p1})}$



$\omega_{p1} \ll 628 \text{ rad/sec}$

$r_{be} = r_{be}' + \frac{V_T}{I_C} \beta_{FE} = 4,8\text{k}\Omega$


$\omega_{p1} = \frac{1}{C_S R_{V_{CS}}}$

$R_{V_{CS}} = R_{B1} // R_{B2} // [r_{be} + R_E (\beta_{FE} + 1)]$

$\omega_{p1} \ll 628 \text{ rad/sec} = \bar{\omega}$

$\frac{1}{C_S R_{V_{CS}}} \ll \bar{\omega}$

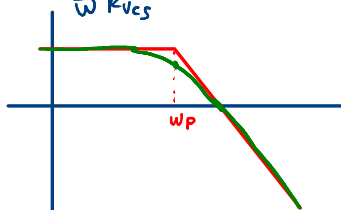$C_S \gg \frac{1}{\bar{\omega} R_{V_{CS}}}$



$A(s) = \frac{A_{CB} \omega_p}{s + \omega_p}$

$|A(j\omega_p)| = \frac{A_{CB} \omega_p}{\sqrt{\omega_p^2 + \omega_p^2}} =$

$\frac{A_{CB} \omega_p}{\sqrt{2} \omega_p}$