

$$A = \left( \frac{R_B}{R_A} + 1 \right) \quad \beta = \frac{z_2}{z_2 + z_1} \quad z_1 = R_1 + \frac{1}{C_1 s} = \frac{R_1 C_1 s + 1}{C_1 s}$$

$$z_2 = R_2 \parallel \frac{1}{C_2 s} = \frac{R_2}{R_2 C_2 s + 1}$$

$$\beta A = \frac{\frac{R_2}{R_2 C_2 s + 1}}{\frac{R_2}{R_2 C_2 s + 1} + \frac{R_1 C_1 s + 1}{C_1 s}} \cdot \left( 1 + \frac{R_B}{R_A} \right) = \left( 1 + \frac{R_B}{R_A} \right) \frac{R_2 C_1 s}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 s + R_2 C_2 s + R_2 C_1) + 1}$$

$$\begin{aligned} \beta A(j\omega_I) > 1 &\Rightarrow |\beta A(j\omega_I)| > 1 \wedge \angle \beta A(j\omega_I) = 0 \\ \beta A(j\omega_0) = 1 &\Rightarrow |\beta A(j\omega_0)| = 1 \wedge \angle \beta A(j\omega_0) = 0 \end{aligned}$$

$$\beta A(j\omega) = \left( 1 + \frac{R_B}{R_A} \right) \frac{j\omega R_2 C_1}{1 - R_1 R_2 C_1 C_2 \omega^2 + j\omega (R_1 C_1 + R_2 C_2 + R_2 C_1)}$$



$$\omega_0 = \omega_I = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = 500 \text{ rad/sec}$$

$$\beta A(j\omega_0) = \left( 1 + \frac{R_B}{R_A} \right) \frac{R_2 C_1}{R_1 C_1 + R_2 C_2 + R_2 C_1}$$

$$\text{Se } R_B = R_0 \Rightarrow |\beta A(j\omega_I)| = 2 > 1$$

$$\left[ 1 + \frac{1}{R_A} R_0 \left( 1 - \frac{V_{\text{max}}}{V_0} \right) \right] \frac{R_2 C_1}{R_1 C_1 + R_2 C_2 + R_2 C_1} = 1$$

$$V_{\text{max}} = 2,92 \text{ V}$$

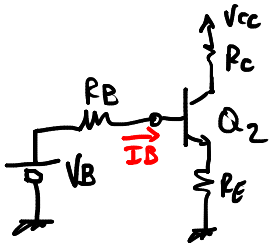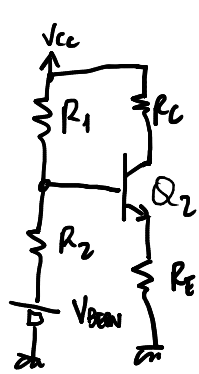

$$R_B = ? = R_1 \parallel R_2 = 4,5 k\Omega$$

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} + V_{BEON} \frac{R_1}{R_1 + R_2} = 2,63V$$

$$V_B = R_B I_B + V_{BEON} + R_E (h_{FE} + 1) I_B$$


$$I_B = \frac{V_B - V_{BEON}}{R_B + R_E (h_{FE} + 1)} = 18,43 \mu A$$

$$I_B = I_{B2}$$

$$I_{C2} = h_{FE} I_{B2} = 9,217 mA$$

$$V_{CE2} = V_{C2} - V_{E2} \quad V_{C2} = V_{CC} - R_C I_{C2} =$$
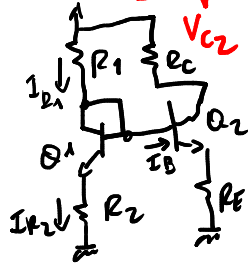
$$V_{CE2} = \underbrace{V_{CC} - R_C I_{C2}}_{V_{C2}} - \underbrace{R_E \left( \frac{h_{FE} + 1}{h_{FE}} \right) I_{C2}}_{V_{E2}} = 8,936V$$





$$I_{R2} = \frac{V_{BEON} + R_E I_{C2} - V_{BEON}}{R_2} = I_{E1} = \frac{R_E I_{C2}}{R_2}$$

$$I_{B1} = \frac{I_{E1}}{h_{FE} + 1} = 737,3 \mu A$$



$$I_{C1} = 0,3687 mA$$

$$V_{CE1} = V_{BEON} = 0,7V$$

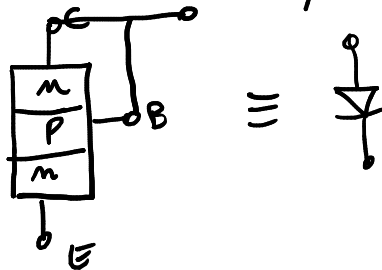

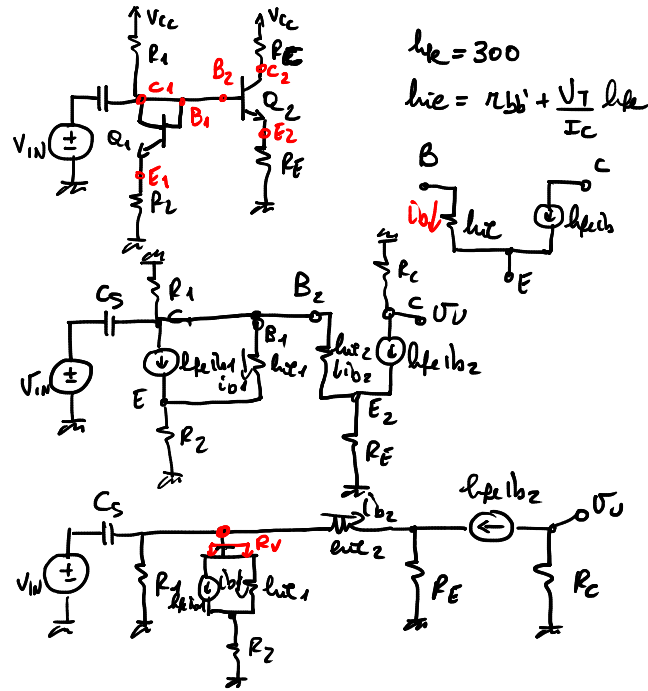


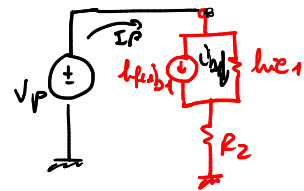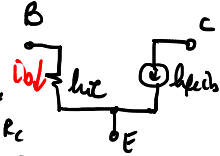$h_{fe} = 300$   
 $h_{ie} = r_{bb'} + \frac{V_T}{I_C} h_{fe}$




$R_V = \frac{V_p}{I_p}$   
 $I_p = (h_{fe} + 1) i_{b1}$   
 $V_p = h_{ie} i_{b1} + R_2 (h_{fe} + 1) i_{b1}$

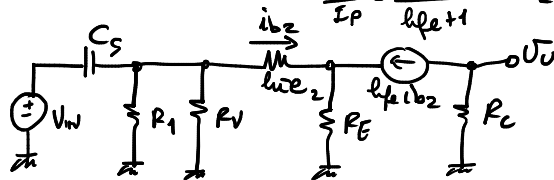$\frac{V_p}{I_p} = \frac{h_{ie}}{h_{fe} + 1} + R_2$



$A_v(s) = \frac{V_o}{V_i} = \frac{A_{v0} S}{(S + \omega_p)}$   
 $A_{v0} = \frac{-R_C h_{fe}}{h_{ie} + R_E (h_{fe} + 1)}$

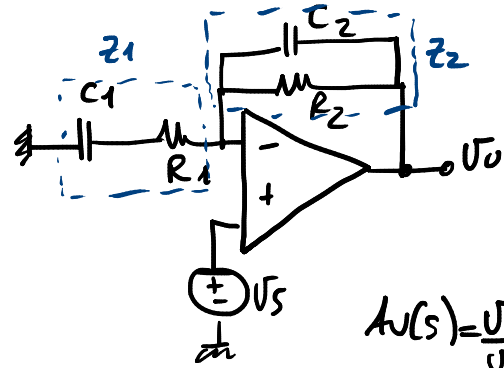$\omega_p = \frac{1}{C_S \cdot R_{in} R_{out} [h_{ie2} + R_E (h_{fe} + 1)]}$




$$z_1 = R_1 + \frac{1}{C_1 s} = \frac{R_1 C_1 s + 1}{C_1 s}$$

$$z_2 = R_2 \parallel \frac{1}{C_2 s} = \frac{R_2}{1 + R_2 C_2 s}$$

$$A(s) = \frac{V_U}{V_S} = \left( 1 + \frac{z_2}{z_1} \right) =$$

$$= \left[ 1 + \frac{R_2}{(1 + R_2 C_2 s)} \cdot \frac{C_1 s}{(R_1 C_1 s + 1)} \right] =$$
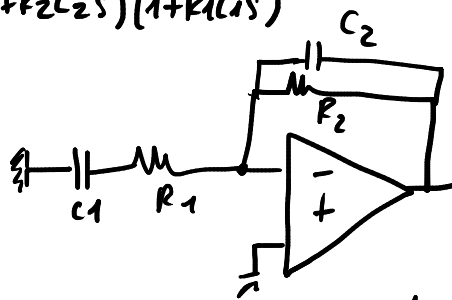
$$= \frac{(R_1 C_1 s + 1)(R_2 C_2 s + 1) + R_2 C_1 s}{(1 + R_2 C_2 s)(1 + R_1 C_1 s)} = \frac{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_2 C_2 + R_2 C_1) s + 1}{(1 + R_2 C_2 s)(1 + R_1 C_1 s)}$$



$$R_{vc1} = ? = R_1$$

$$\omega_{p1} = \frac{1}{R_1 C_1}$$

$$R_{vc2} = R_2 \parallel R_V'$$



$$R_{AB} = R_{in} (1 + A_v) + R_o$$

$$R_{in} = R_{inop} \parallel z_1$$

$$R_V' = (R_{inop} \parallel z_1) (1 + A_v) \rightarrow +\infty$$

$$R_{vc2} = R_2$$