

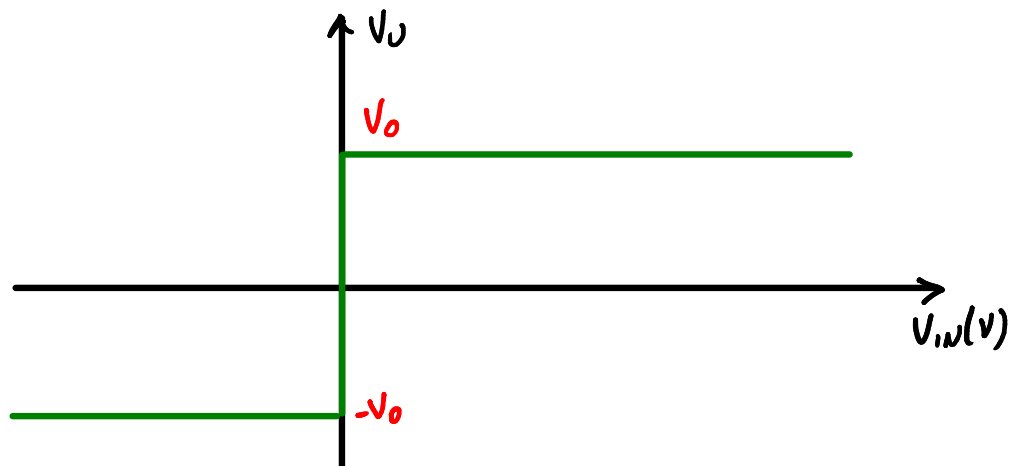
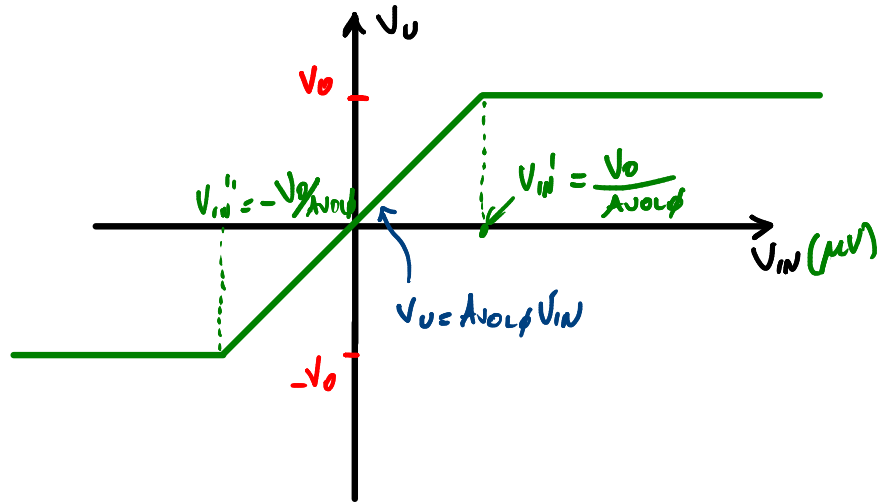
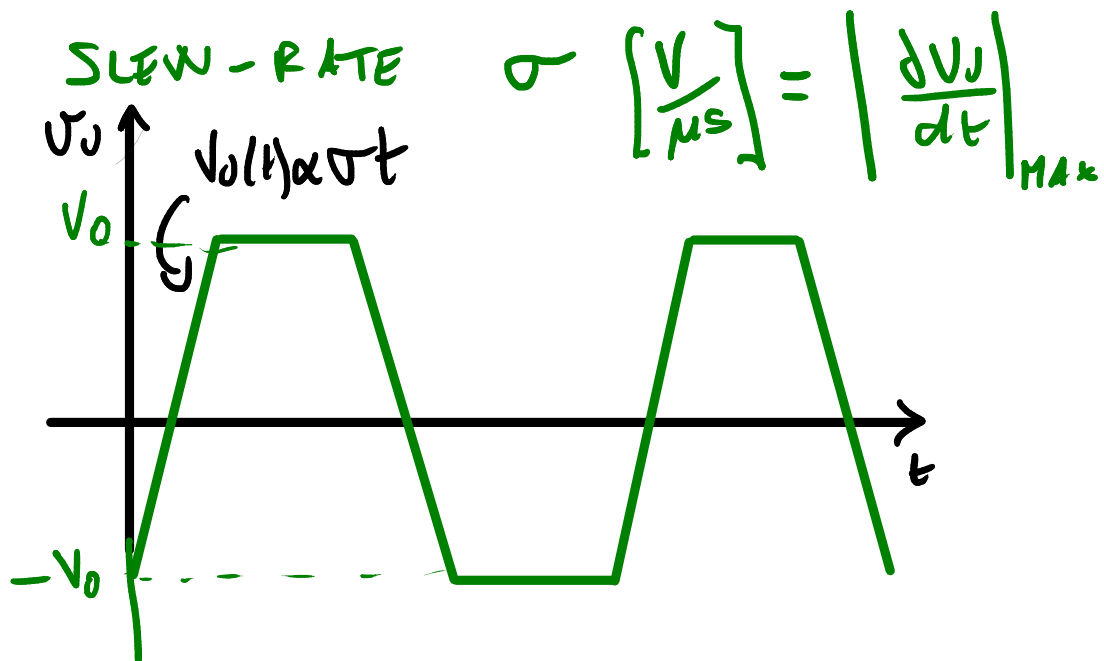



-> A_d dipendente da ω $A_d = \frac{A_{vol}}{1 + \frac{s}{\omega_p}}$


-> A_v nell'AMP INV:
 -> ricavati V_o'
 -> ricavati ω_p'
 -> PGB \approx constant

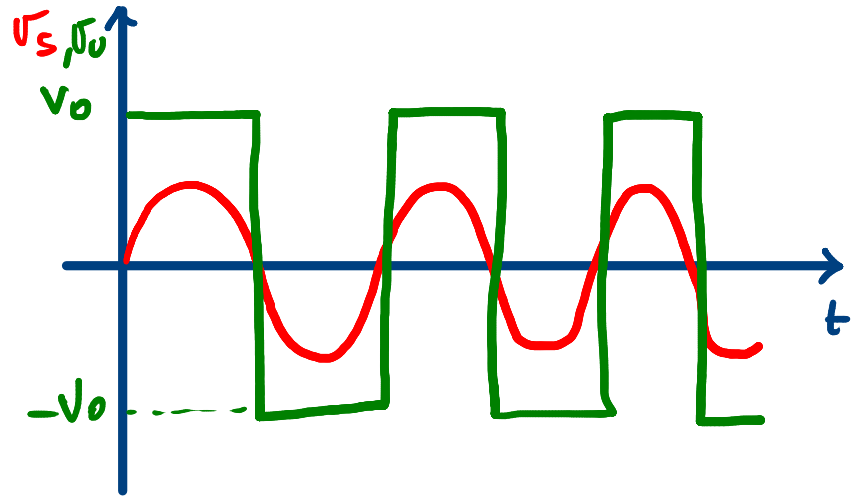-> A_v nell'AMP INV con $R_{in} \neq \infty$




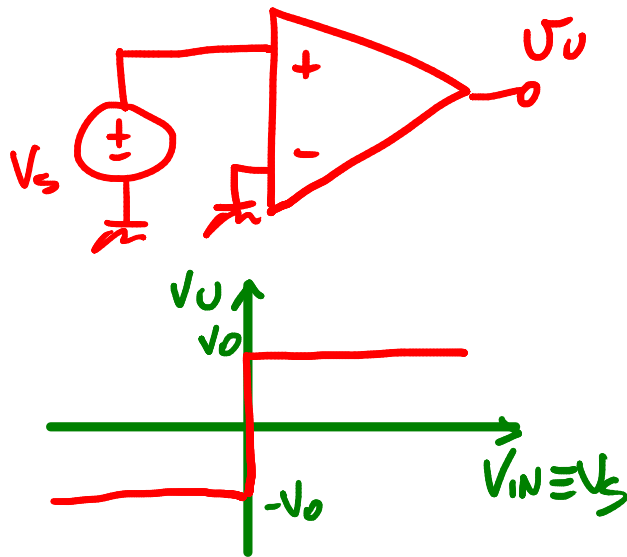

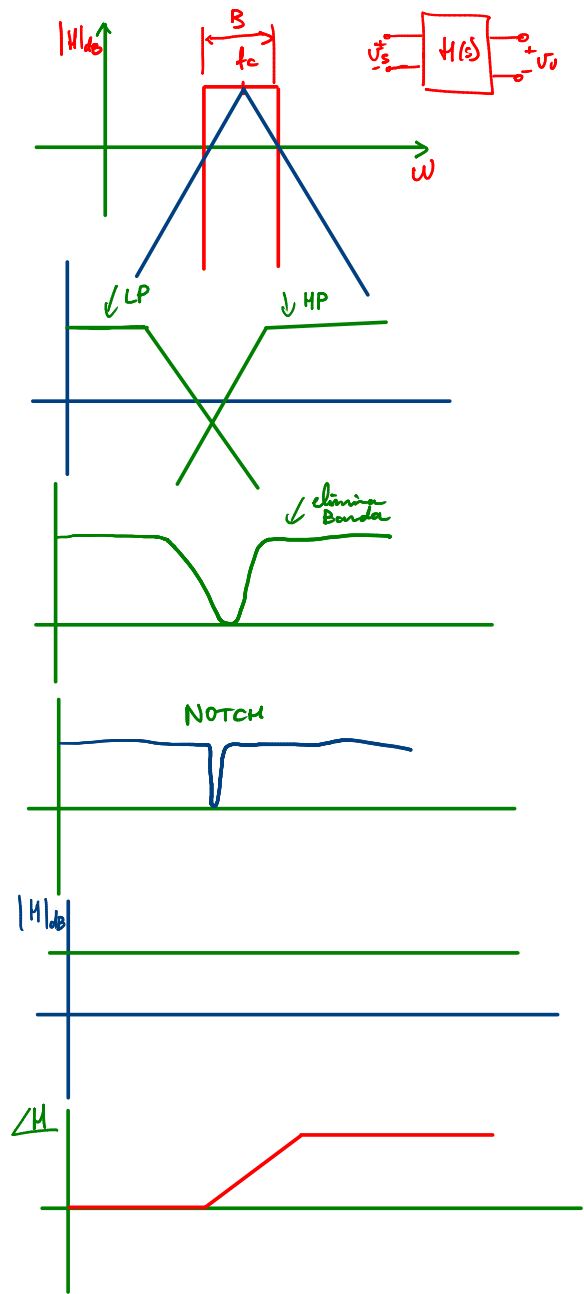

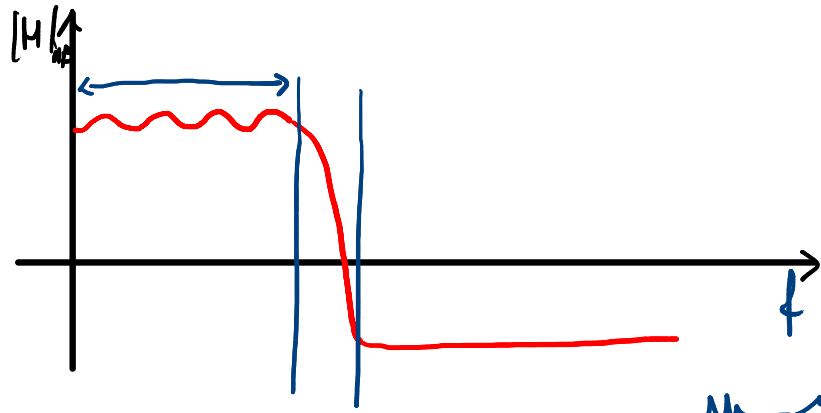


$H(s) = \underline{\hspace{10em}}$

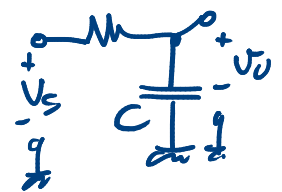

$$H(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$$



$$A_0 = 1$$

$$\omega_p = \frac{1}{CR}$$

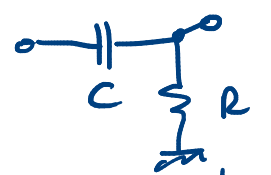

$$H(s) = \frac{sRC}{1 + \frac{s}{\omega_p}}$$

$$\omega_p = \frac{1}{CR}$$

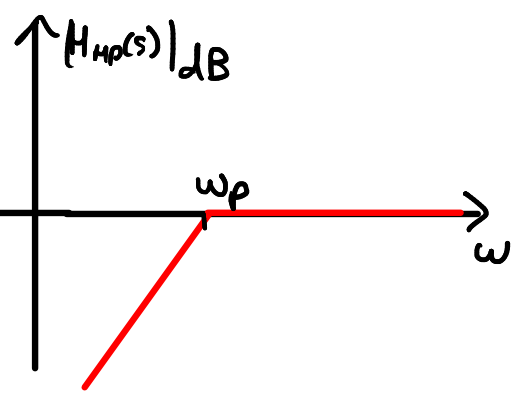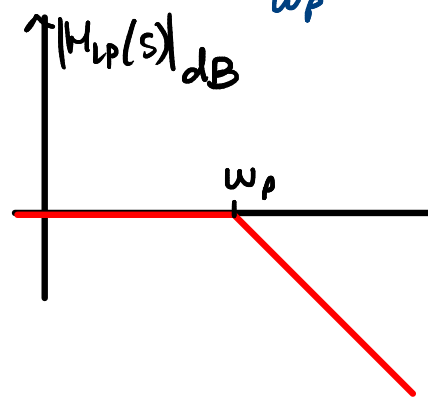

$$H(s) = \frac{k_2 s^2 + k_1 \frac{\omega_0}{Q} s + k_0 \omega_0^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

$$k_2 = 0 \wedge k_1 = 0 \wedge k_0 = 1 : \text{LP}$$

$$k_2 = 1 \wedge k_1 = 0 \wedge k_0 = 0 : \text{HP}$$

$$k_2 = 0 \wedge k_1 = 1 \wedge k_0 = 0 : \text{BP}$$

Reiezione di Banda: $k_2 = 1 \wedge k_1 = 0 \wedge k_0 = 1$

Passa tutto: $k_2 = 1 \wedge k_1 = -1 \wedge k_0 = 1$

$$D[H(s)] = \frac{s^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1$$

$$H(j\omega) = -\frac{\omega^2}{\omega_0^2} + 1 + \frac{j\omega}{Q\omega_0}$$

$$|H(j\omega_0)| = \frac{1}{Q}$$

$$|H(j\omega)|^2 = \left(1 - \frac{\omega^2}{\omega_0^2}\right)^2 + \left(\frac{\omega}{\omega_0 Q}\right)^2 = \left(\frac{\omega}{\omega_0}\right)^4 - \left(\frac{\omega}{\omega_0}\right)^2 \left(2 - \frac{1}{Q^2}\right) + 1$$

$$Q^2 > 2$$

$$\min |H(\omega)| = \frac{1}{Q} \sqrt{1 - \frac{1}{4Q^2}} \quad \text{when } \frac{\omega}{\omega_0} = 1 - \frac{1}{2Q^2}$$