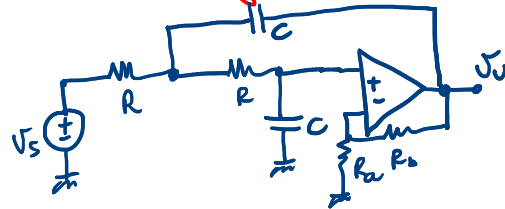



Sallen & Key




$\beta A \gg 1$





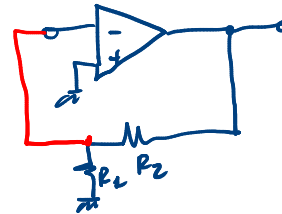$A = \frac{A_{volp}}{1 + \frac{s}{\omega_p}}$




$\beta A \gg 1$

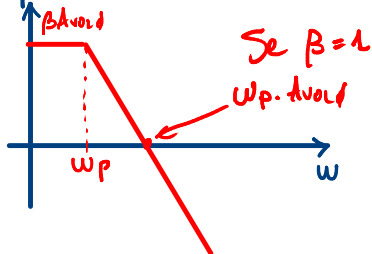

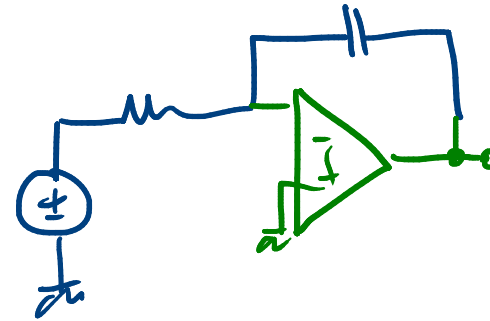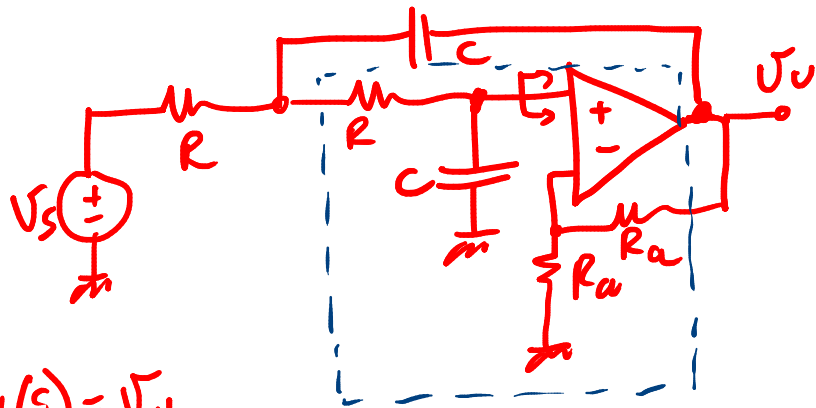


$$A_v(s) = \frac{V_o}{V_s} =$$

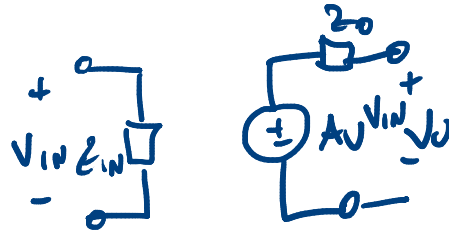

$$Z_{IN} = R + \frac{1}{Cs} \parallel R_{iop} = R + \frac{1}{Cs}$$

$$Z_O = \phi$$

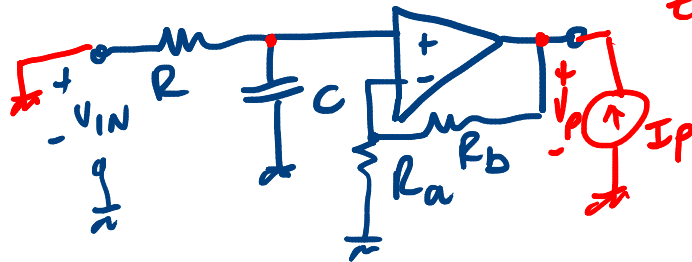
$$Z_O = \frac{V_p}{I_p} = \frac{0}{I_p} = 0$$



$$A_v = \frac{A_{vo}}{\left(1 + \frac{s}{\omega_p}\right)}$$

$$A_{vo} = \left(1 + \frac{R_b}{R_a}\right)$$

$$\omega_p = \frac{1}{RC}$$

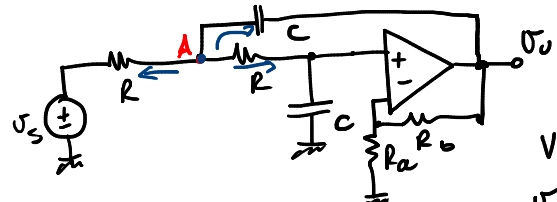

$$A_U = 1 + \frac{R_b}{R_a}$$

$$V^+ \approx V^-$$

$$V_U = \left(1 + \frac{R_b}{R_a}\right) V^+$$

$$\frac{V_A - V_S}{R} + \frac{V_A - V^+}{R} + (V_A - V_U)C_s = 0$$

$$V^+ = \frac{1}{C_s} \quad V_A = \frac{V_A}{1 + RC_s}$$

$$V_A = (1 + RC_s) V^+$$

$$V^+ = \frac{V_U}{A_U}$$

$$V_A = (1 + RC_s) \frac{V_U}{A_U}$$

$$(V_A - V_S) + V_A - V^+ + RC_s(V_A - V_U) = 0$$

$$2V_A - V_S - V^+ + RC_s(V_A - V_U)$$


$$2(1 + RC_s) \frac{V_U}{A_U} - V_S - \frac{V_U}{A_U} + RC_s \left[(1 + RC_s) \frac{V_U}{A_U} - V_U \right] = 0$$



$$A(s) = \frac{V_U(s)}{V_S(s)} = \frac{A_U}{RC^2s^2 + (3 - A_U)RCs + 1}$$

$$\frac{s^2}{\omega_0^2} + \frac{s}{\omega_0 Q} + 1$$

$$\omega_0 = \frac{1}{RC}$$

$$Q = \frac{1}{3 - A_U}$$

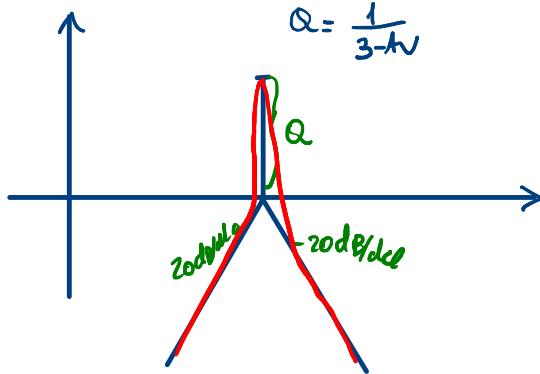

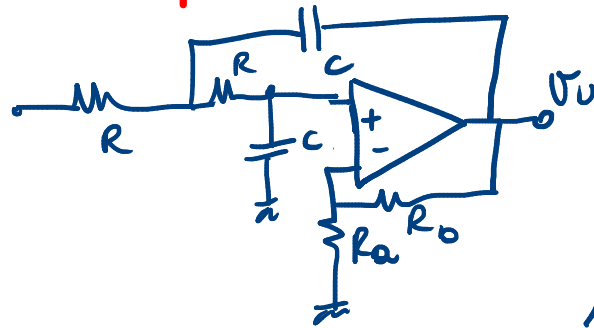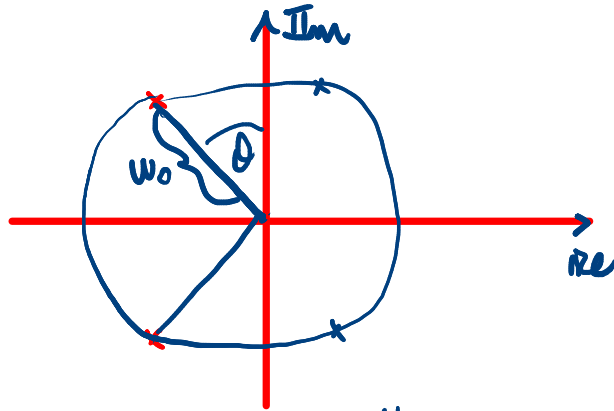


$$A(s) = \frac{A_V}{R^2 C^2 s^2 + (3 - A_V) R C s + 1}$$


$$R \rightarrow \frac{1}{C s} \quad C s \rightarrow \frac{1}{R}$$

$$A(s) = \frac{A_V}{\frac{s^2 + (3 - A_V) + 1}{\frac{C^2 R^2 s^2}{R C s}}} =$$
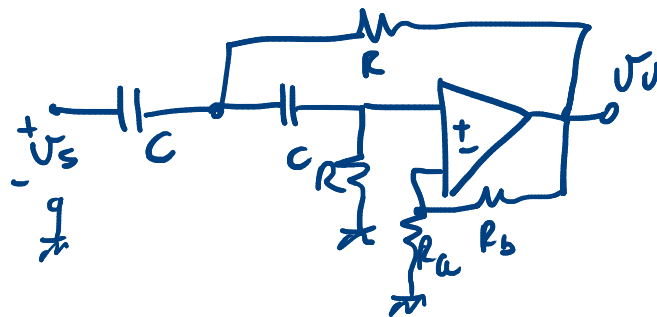
$$A(s) = \frac{A_V R^2 C^2 s^2}{R^2 C^2 s^2 + (3 - A_V) R C s + 1}$$



Filtro passa banda

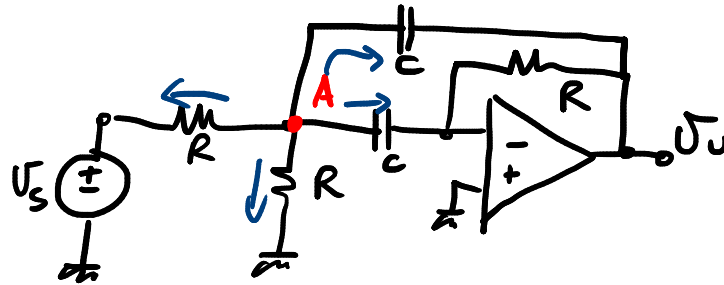

$$V_U = -RCsV_A$$

$$V_A = -\frac{1}{RCs}V_U$$

$$\frac{V_A - V_S}{R} + \frac{V_A}{R} + V_A c s + (V_A - V_U) C s = 0$$

$$V_A - V_S + V_A + RCsV_A + RCs(V_A - V_U) = 0$$


$$V_A(2 + RCs) - RCsV_U = V_S$$

$$-\frac{2}{RCs}(1 + RCs)V_U - (RCs)V_U = V_S$$


$$+2(1 + RCs)V_U + (RCs)^2V_U = -RCsV_S$$

$$V_U [R^2c^2s^2 + 2RCs + 2] = -RCsV_S$$
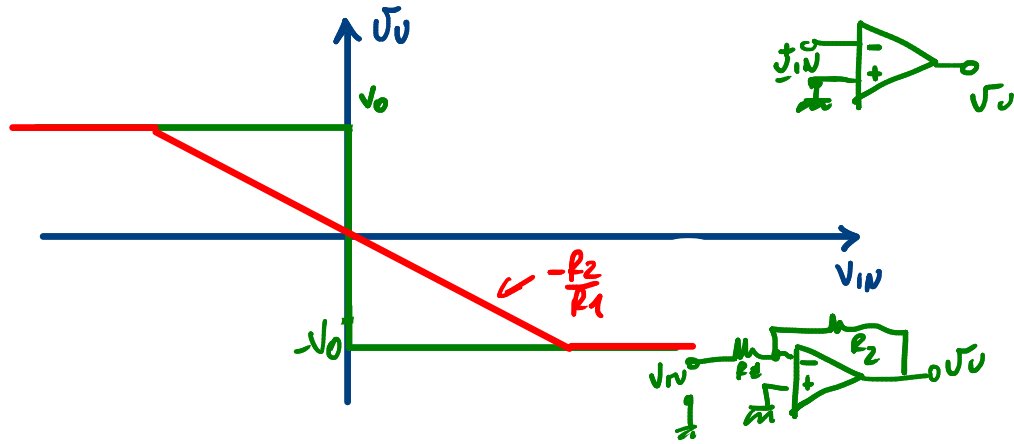
$$\frac{V_U}{V_S} = -\frac{RCs}{R^2c^2s^2 + 2RCs + 2}$$



$$V_O = -\frac{R_2}{R_1} V_{IN}$$

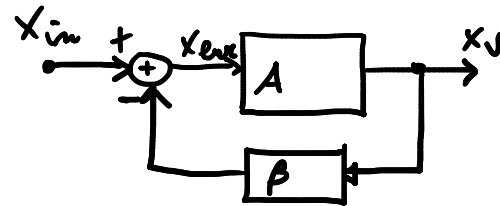

$$x_{err} = x_{in} - \beta x_O$$

$$x_O = A x_{err}$$

$$x_O = A(x_{in} - \beta x_O)$$



$$x_O = \frac{A x_{in}}{1 + \beta A}$$

$$x_{err} = \frac{x_O}{A} = \frac{x_{in}}{1 + \beta A}$$

$$x_O = \frac{1}{\beta} \frac{\beta A}{1 + \beta A} x_{in}$$


$$A_f = \frac{x_O}{x_{in}}$$
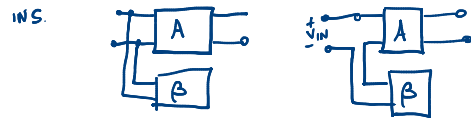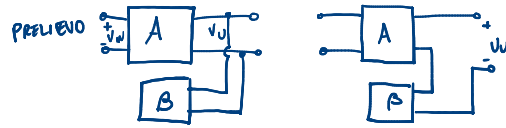
$$\text{Se } \beta A \gg 1 \quad A_f \rightarrow \frac{1}{\beta}$$




$$V_N = Z_V I_N$$

$$Z_V = \frac{V_N}{I_N}$$

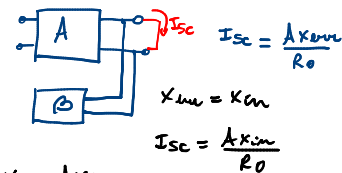

$$V_o = x_u = \frac{A x_{in}}{1 + \beta A}$$
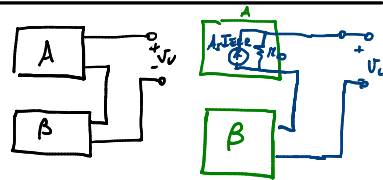
$$R_o' = \frac{V_o}{I_{sc}} = \frac{A x_{in}}{(1 + \beta A) A x_{in}} \frac{R_o}{A x_{in}} = \frac{R_o}{1 + \beta A}$$



$$V_o = R_o \cdot A_s I_{ERR} = R_o A_s I_s$$

$$I_{sc} = \frac{A_s}{1 + \beta A_s} I_s$$

$$R_o' = \frac{V_o}{I_{sc}} = \frac{R_o A_s I_s}{\frac{A_s}{1 + \beta A_s} I_s} = R_o (1 + \beta A_s)$$

$$\omega_p' = \omega_p (1 + \beta A_{vo(d)})$$

$$A_f = \frac{A}{1 + \beta A} \quad A = \frac{A_{vo(d)}}{1 + \frac{s}{\omega_p}}$$

$$A_f = \frac{A_{vo(d)}}{1 + \beta A_{vo(d)}} \frac{1}{\left(\frac{s}{\omega_p} + 1\right)}$$