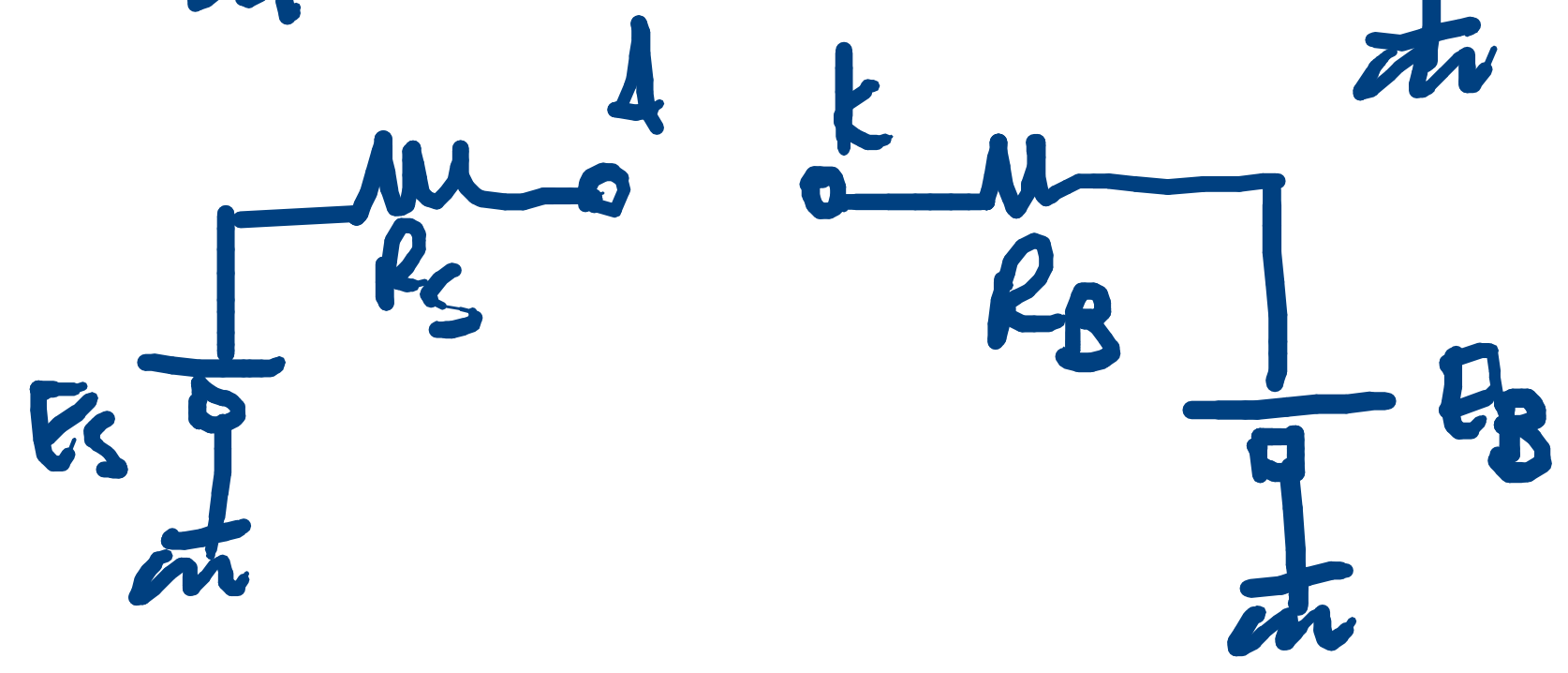



$$I_D = \frac{E_S - E_B}{R_S + R_B} = 1mA$$

$I_D > 0$




OFF:  $V_A < 0$
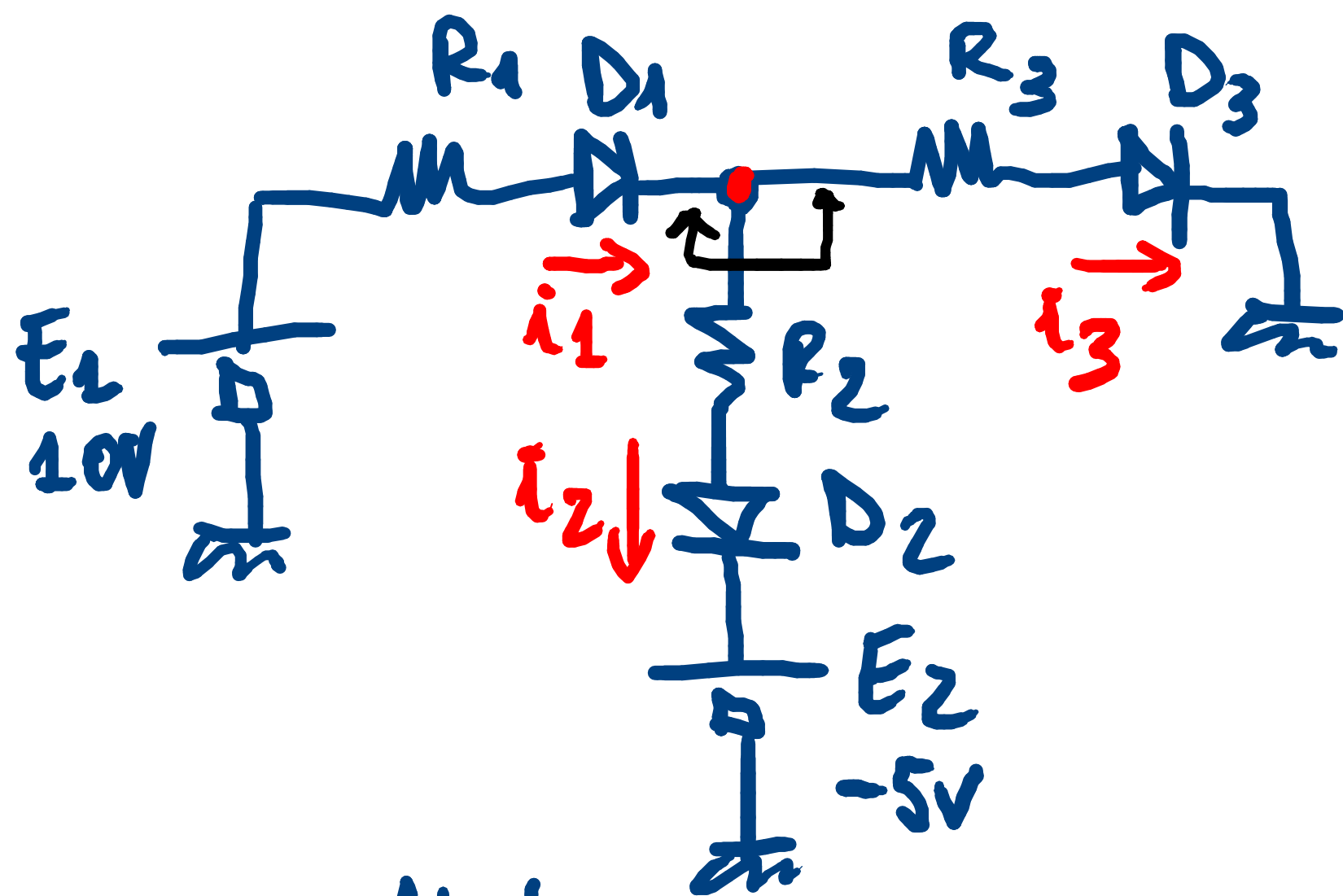
$$V_A = V_A - V_K = E_S - E_B = 2V \geq 0$$



$$R_1 = R_2 = R_3 = 1k\Omega$$


$$V_{Di} \quad V_i = 1.3 = 0V$$

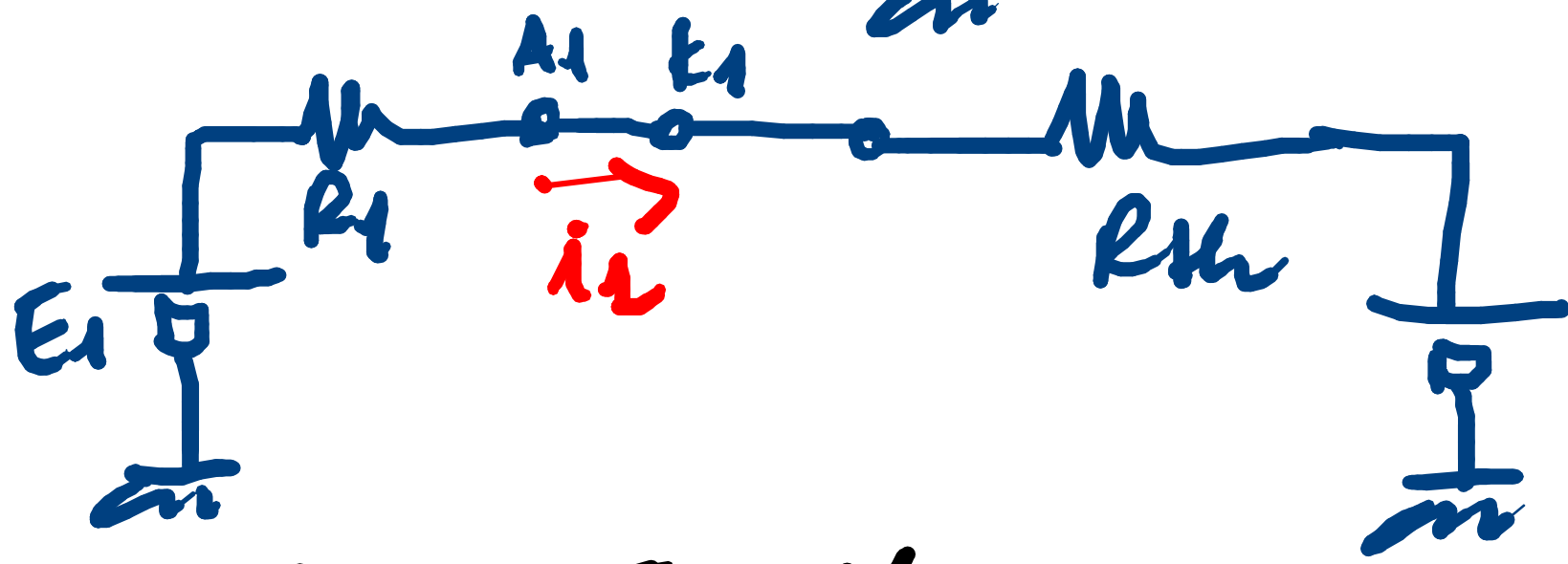

$$R_{th} = R_2 \parallel R_3$$

$$V_{th} = \frac{E_2 R_3}{R_2 + R_3}$$

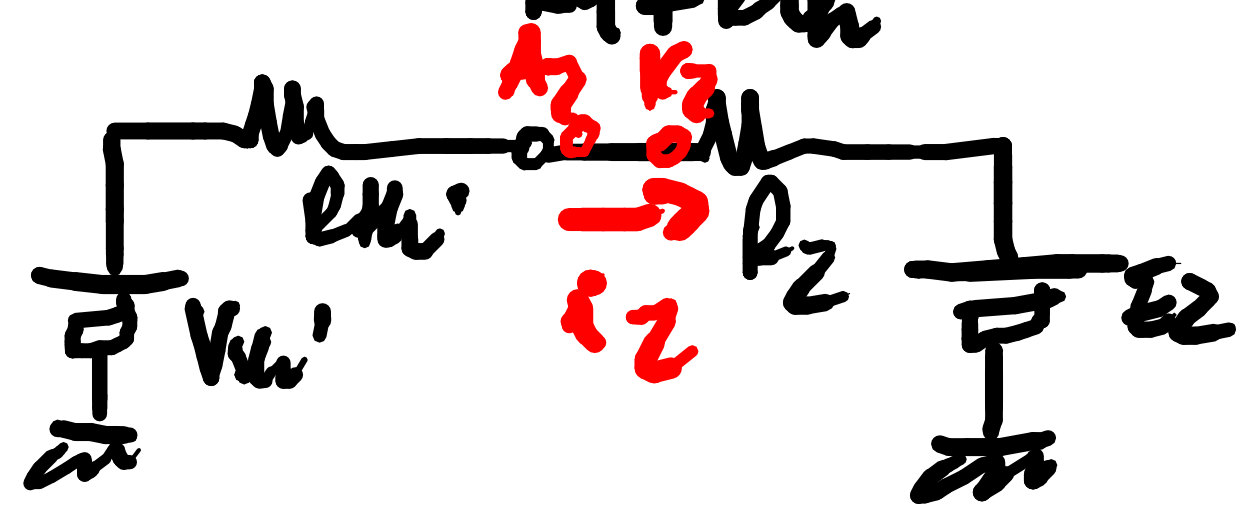
$$i_1 = \frac{E_1 - V_{th}}{R_1 + R_{th}}$$



$$i_2 = \frac{V_{th}' - E_2}{R_{th}' + R_2}$$

$$i_3 = i_1 - i_2$$
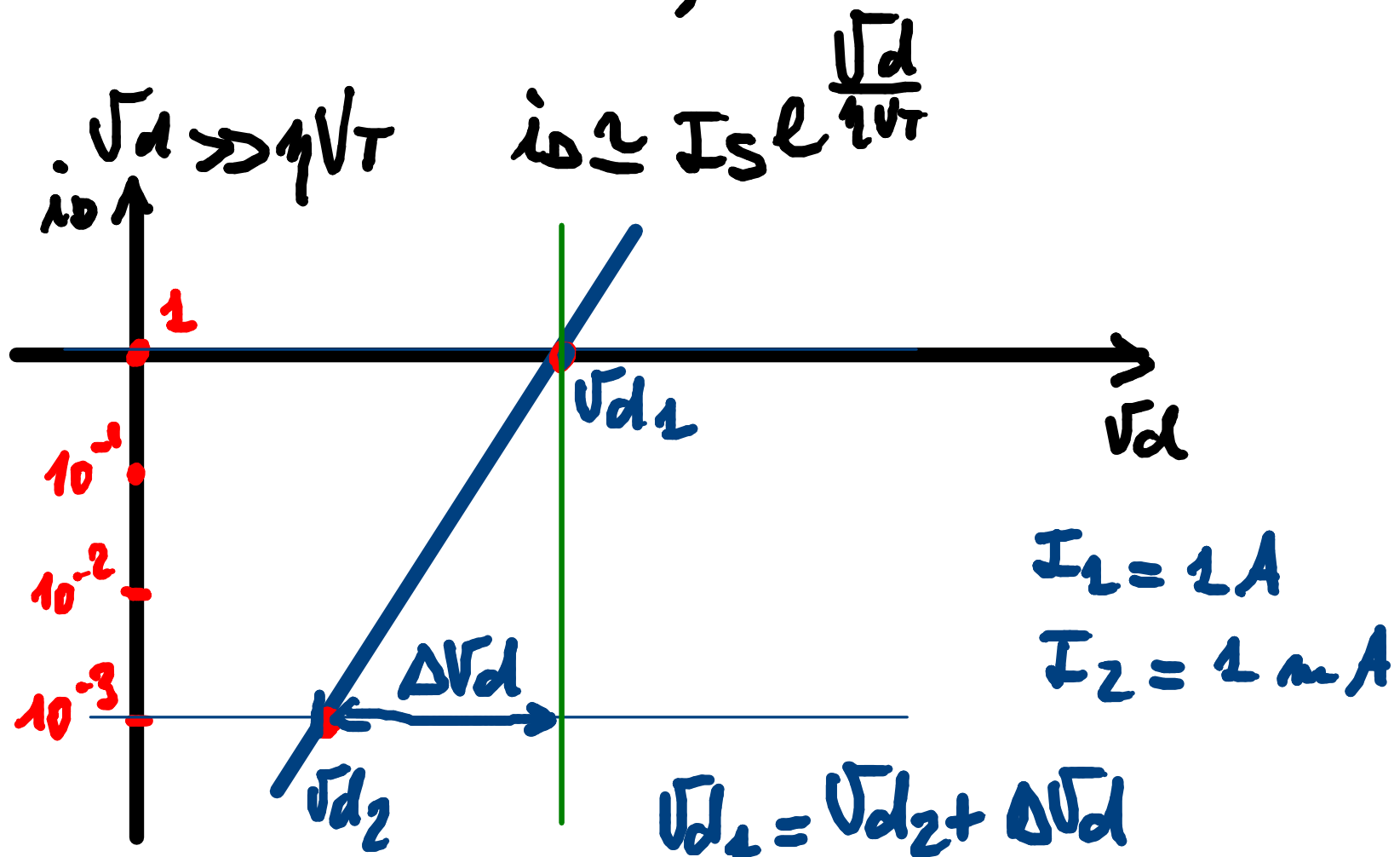
$$i_D = I_S \left( e^{\frac{V_d}{nV_T}} - 1 \right)$$



$$I_1 = I_S e^{\frac{V_{d1}}{nV_T}} = I_S e^{\frac{V_{d2} + \Delta V_d}{nV_T}}$$

$$I_2 = I_S e^{\frac{V_{d2}}{nV_T}}$$

$$\frac{I_1}{I_2} = \frac{10^3 \cancel{I_2}}{\cancel{I_2}} = \frac{\cancel{I_S}}{\cancel{I_S}} \frac{e^{\frac{V_{d2}}{nV_T}} \cdot e^{\frac{\Delta V_d}{nV_T}}}{e^{\frac{V_{d2}}{nV_T}}}$$

$$10^3 = e^{\frac{\Delta V_d}{nV_T}} \quad \frac{\Delta V_d}{nV_T} = \ln 10^3 = 3 \ln 10$$

$$\eta = \frac{\Delta V_d}{V_T \cdot 3 \cdot \ln 10}$$

$$i_d = I_S \left( e^{\frac{V_d}{V_T}} - 1 \right) \quad V_T = \frac{k_B T}{q}$$

$$I_S(T)$$

$$\frac{dI_S(T)}{dT} = I_S(T) \cdot \frac{0,072}{K}$$

$$I_S(T) = I_S(T_0) e^{0,072(T-T_0)}$$

$$I_S(T_1) = 2 I_S(T_0) = I_S(T_0) e^{0,072(T_1-T_0)}$$

$$T_1 = T_0 + \frac{\ln(2)}{0,072} = T_0 + 9,627 \text{ K}$$

$V_d$ 

$$I_0 = I_S \left( e^{\frac{V_d}{V_T}} - 1 \right)$$

$$V_d = \eta V_T \ln \left( \frac{I_0 + I_S}{I_S} \right)$$

$$V_T = \frac{k_B T}{q}$$

$$\frac{\delta V_d}{\delta T} = \frac{V_d}{T} + \eta V_T \frac{I_S}{I_0 + I_S} \left( -\frac{I_0}{I_S^2} \right) I_S \cdot 0,072$$

$$I_S \ll I_0$$

$$\frac{\delta V_d}{\delta T} = \frac{V_d}{T} - 0,072 \cdot \eta V_T$$

2mV	1°C
-----	-----

