


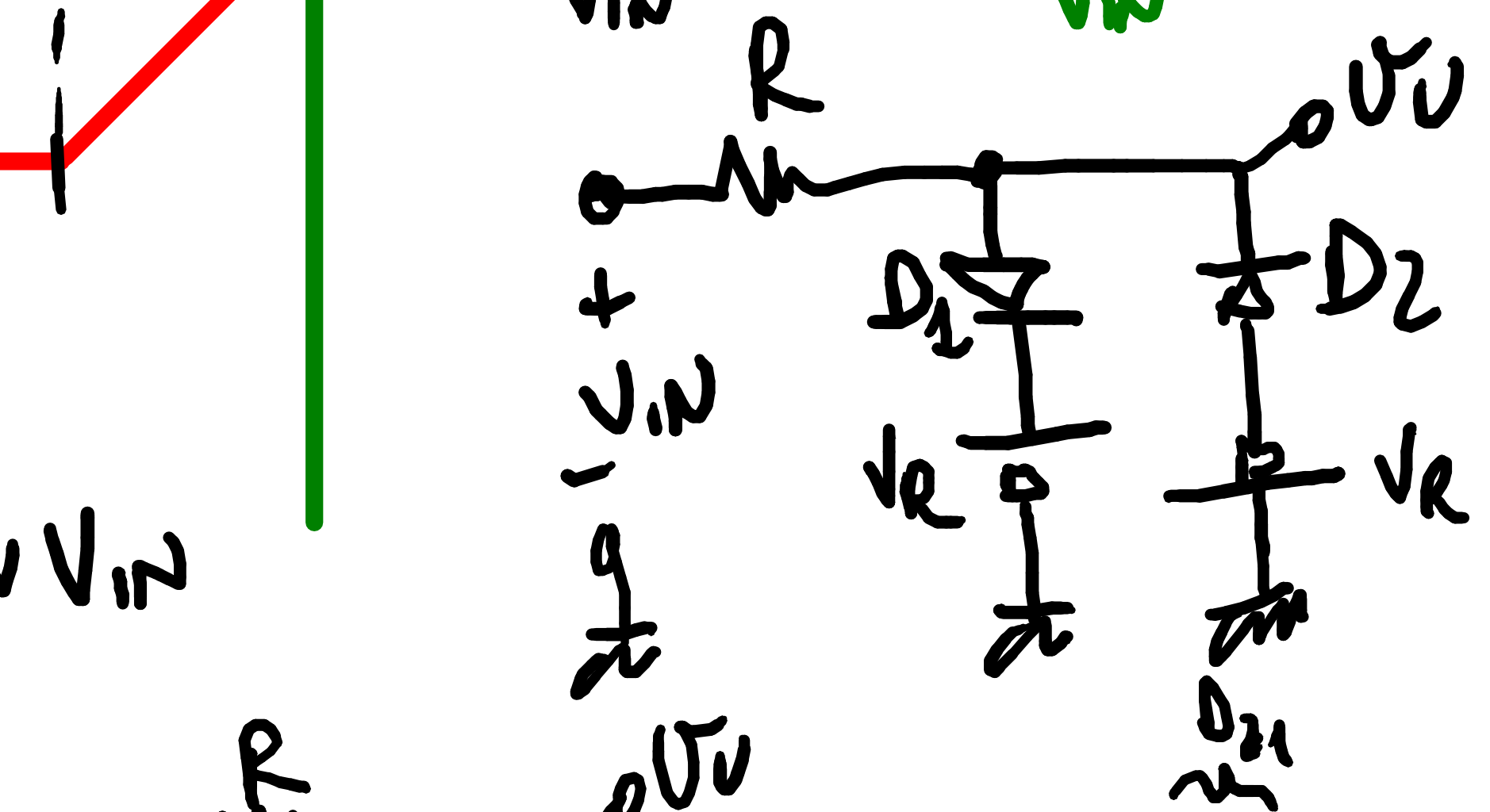


D_1 OFF
 D_2 ON
 $V_O = A_v V_{IN}$

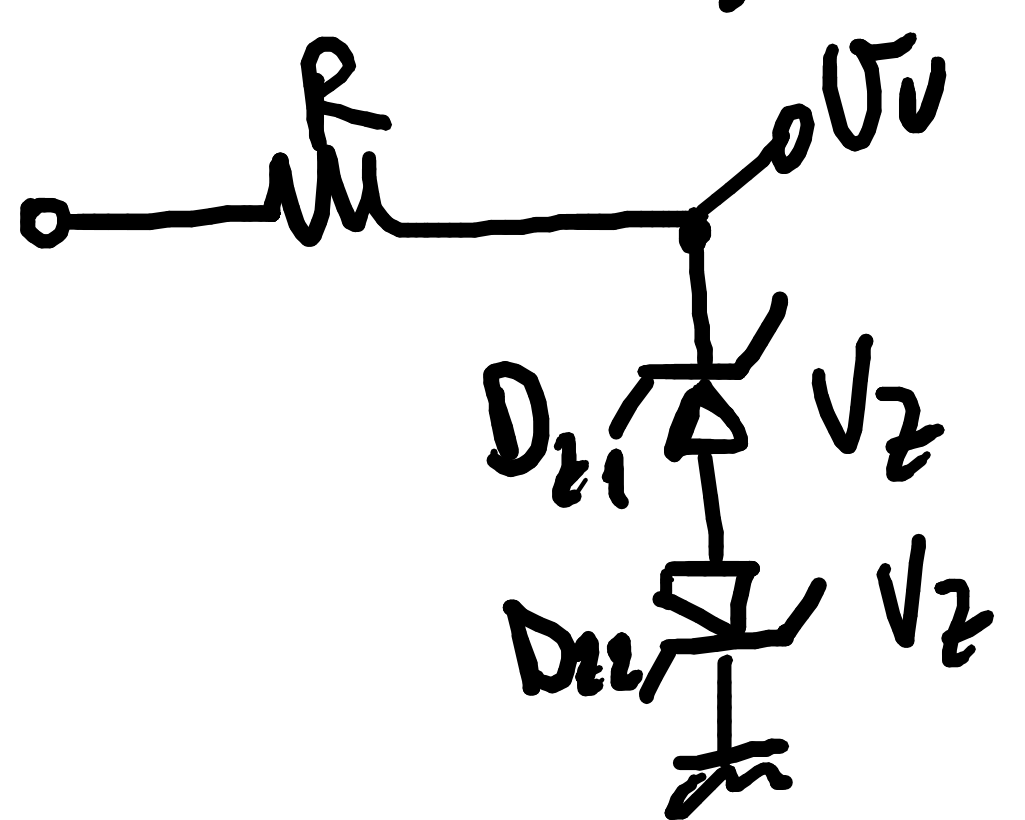


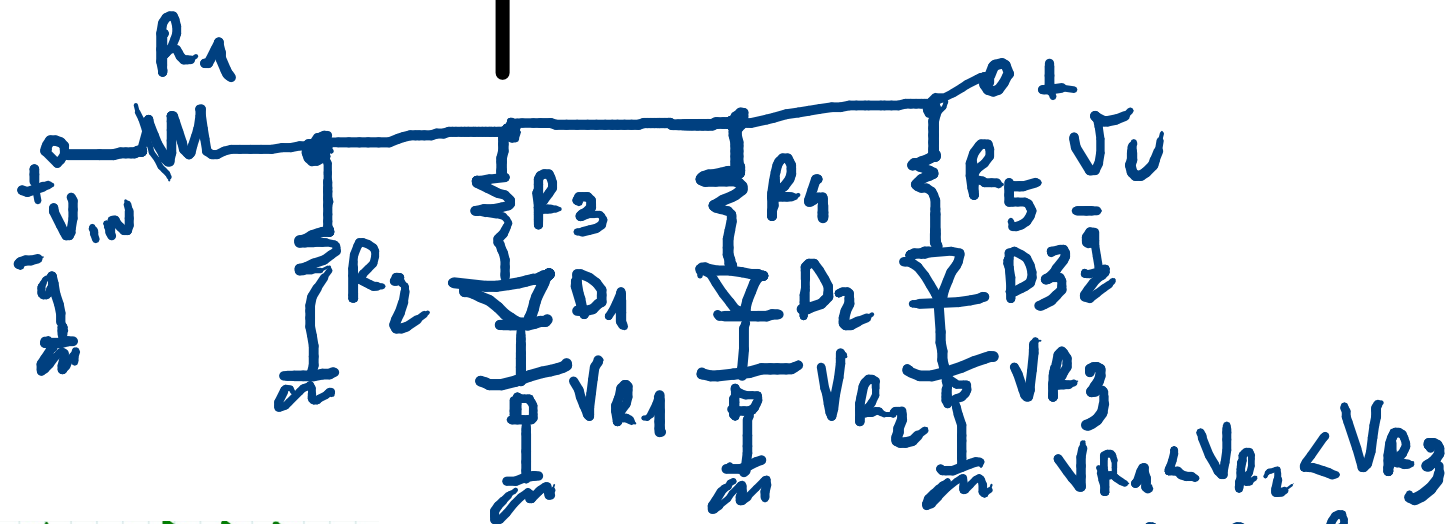$V_{UP} = V_Z + V_R$
 $V_{LOW} = -(V_Z + V_R)$



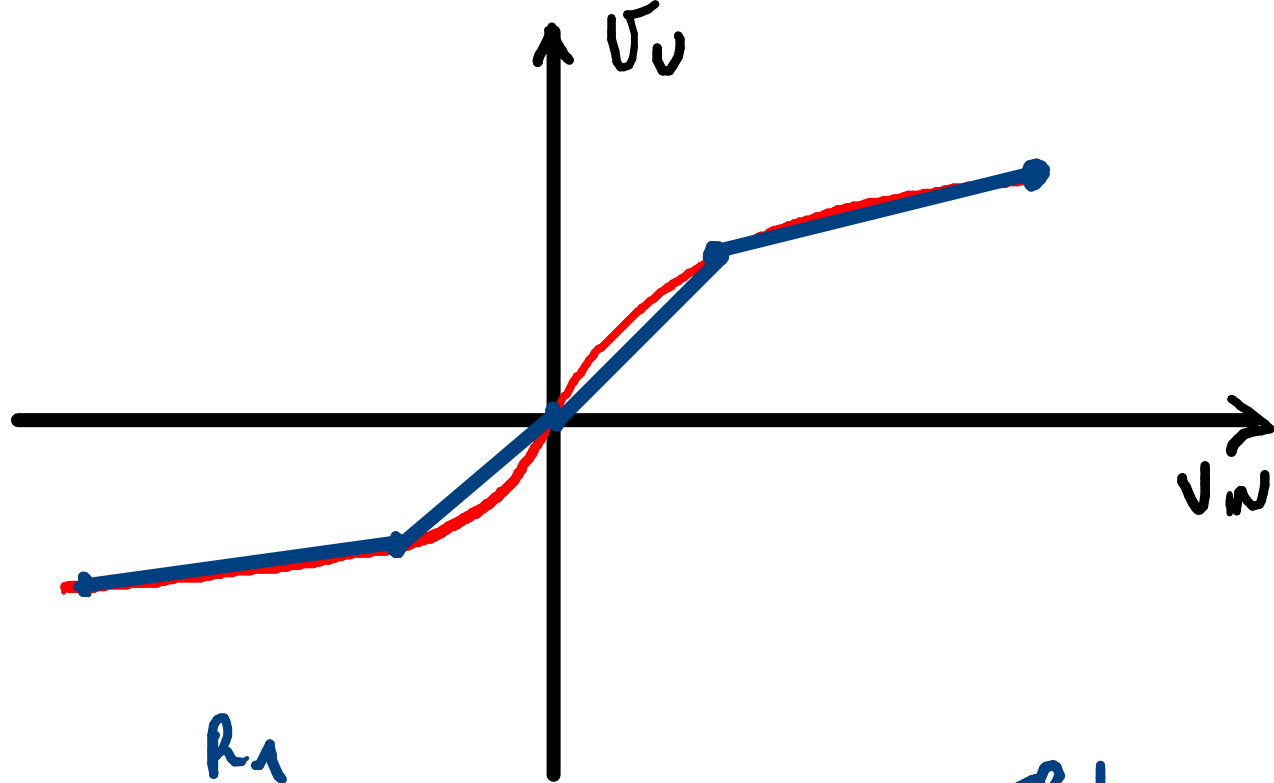


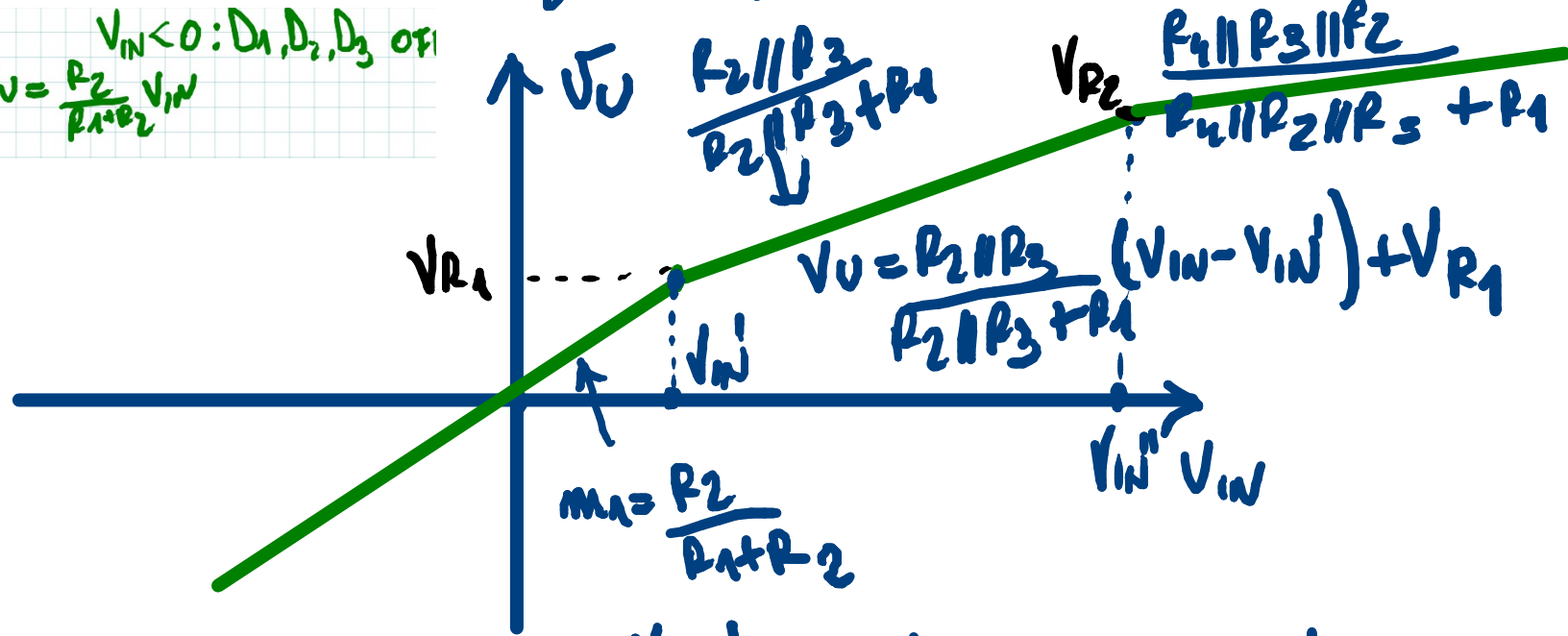$V_{IN} < 0: D_1, D_2, D_3 \text{ off}$
 $V_U = \frac{R_2}{R_1 + R_2} V_{IN}$



$$V_{IN}' \Rightarrow V_{R1} = \frac{R_2}{R_2 + R_1} V_{IN}'$$


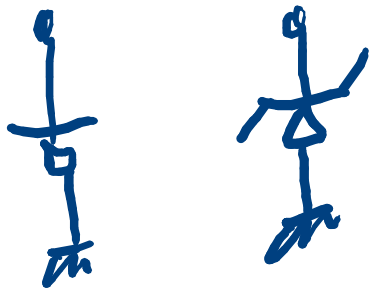
$$V_{IN}' = \frac{R_2 + R_1}{R_2} V_{R1}$$



$$f(x) = \sqrt{x}$$

$$-10V \leq V_{IN} \leq 10V$$


V_{IN}	V_U
1	1
4	2
9	3
16	4
25	5
36	6
49	7
64	8
81	9
100	10

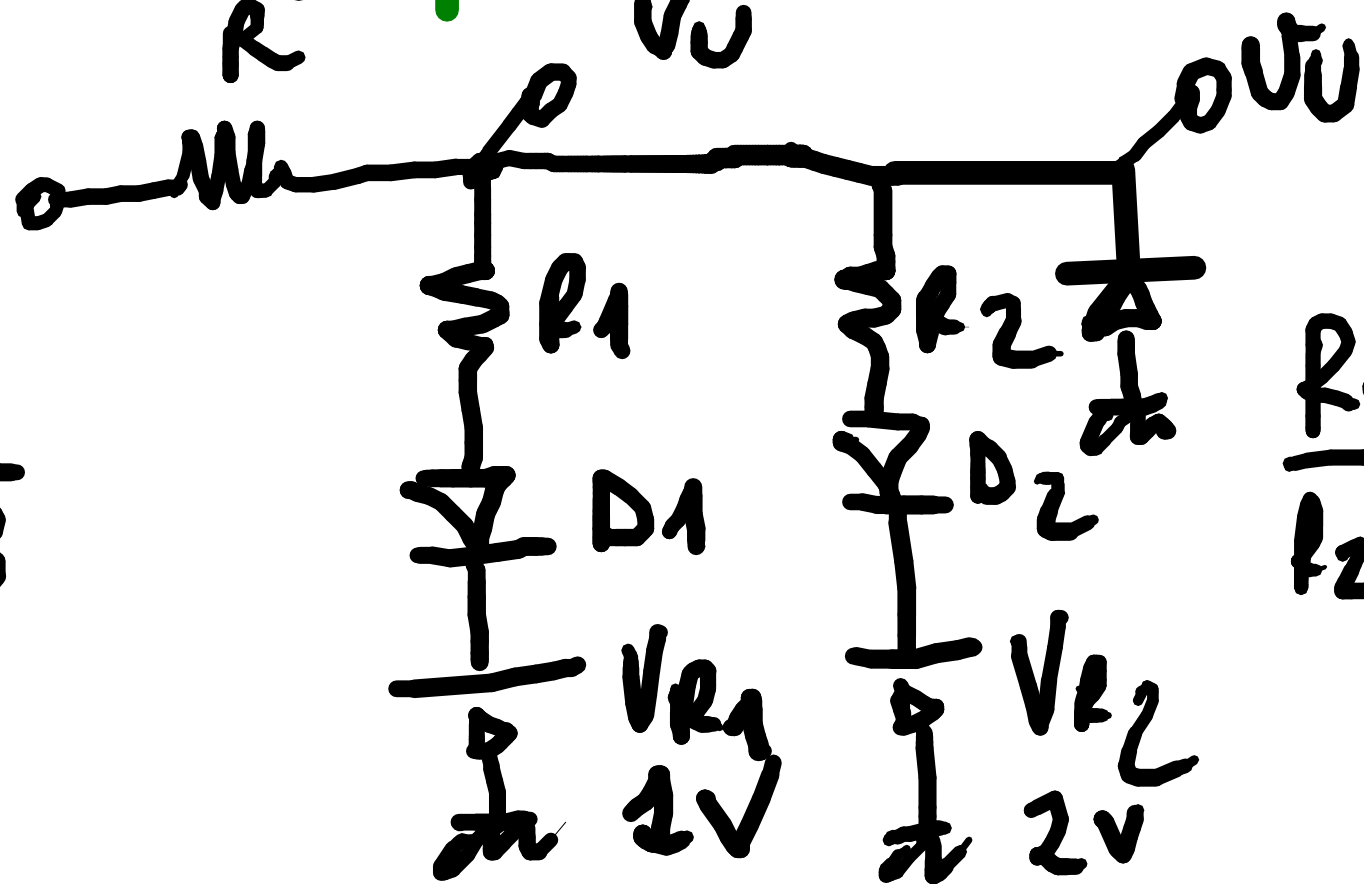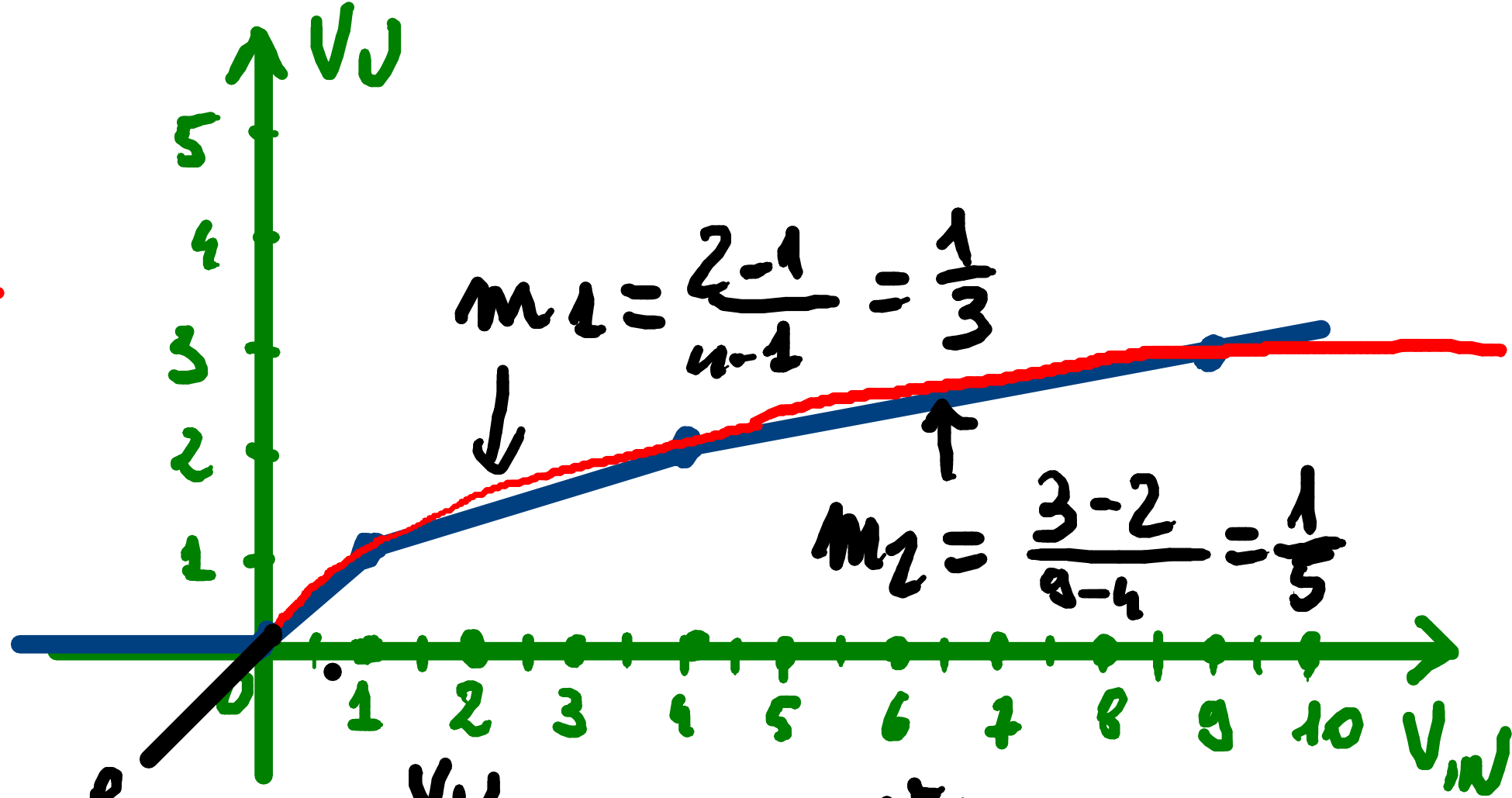

$$\frac{R_1}{R+R_1} = \frac{1}{3}$$

$$R_1 = \frac{R}{2}$$

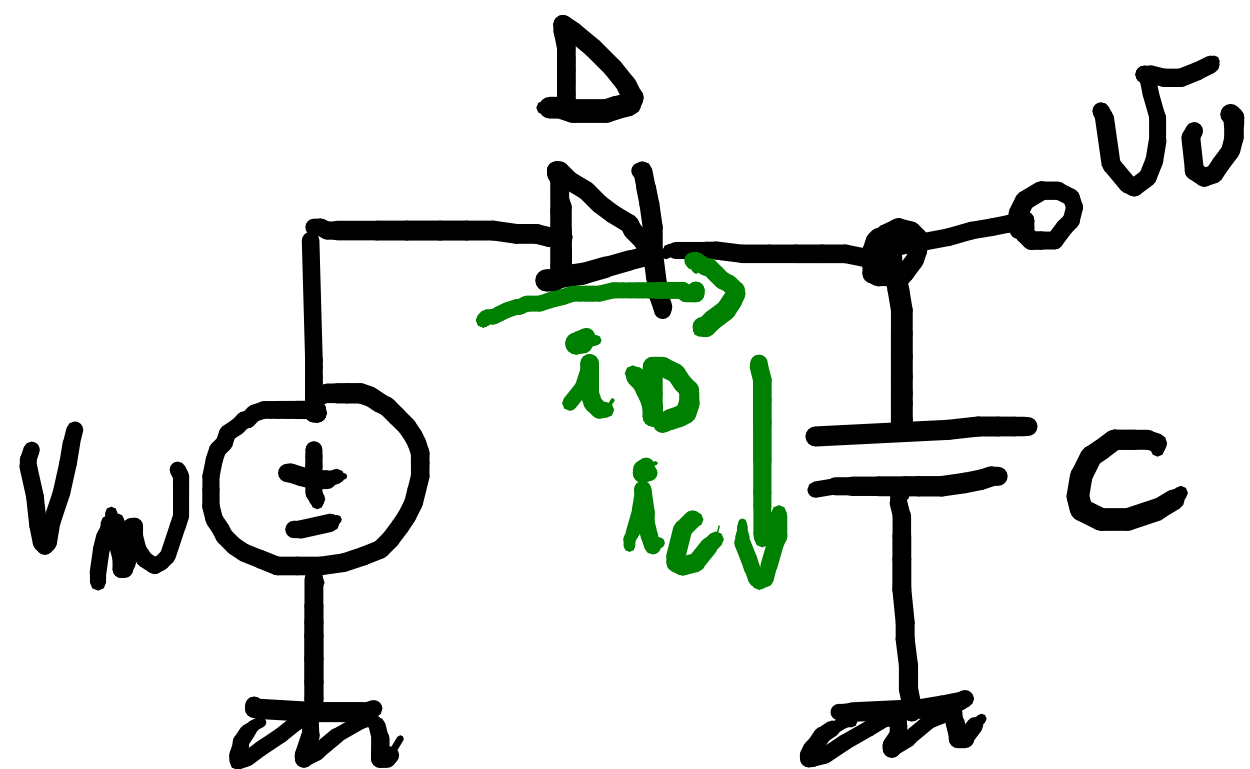
$$\frac{R_2 \parallel R_1}{R_2 \parallel R_1 + R} = \frac{1}{5}$$




$$V_C = V_{IN}$$

$$i_C = C \frac{dV_C}{dt} = C \frac{dV_{IN}}{dt} = i_D$$

$V_{IN}(t)$

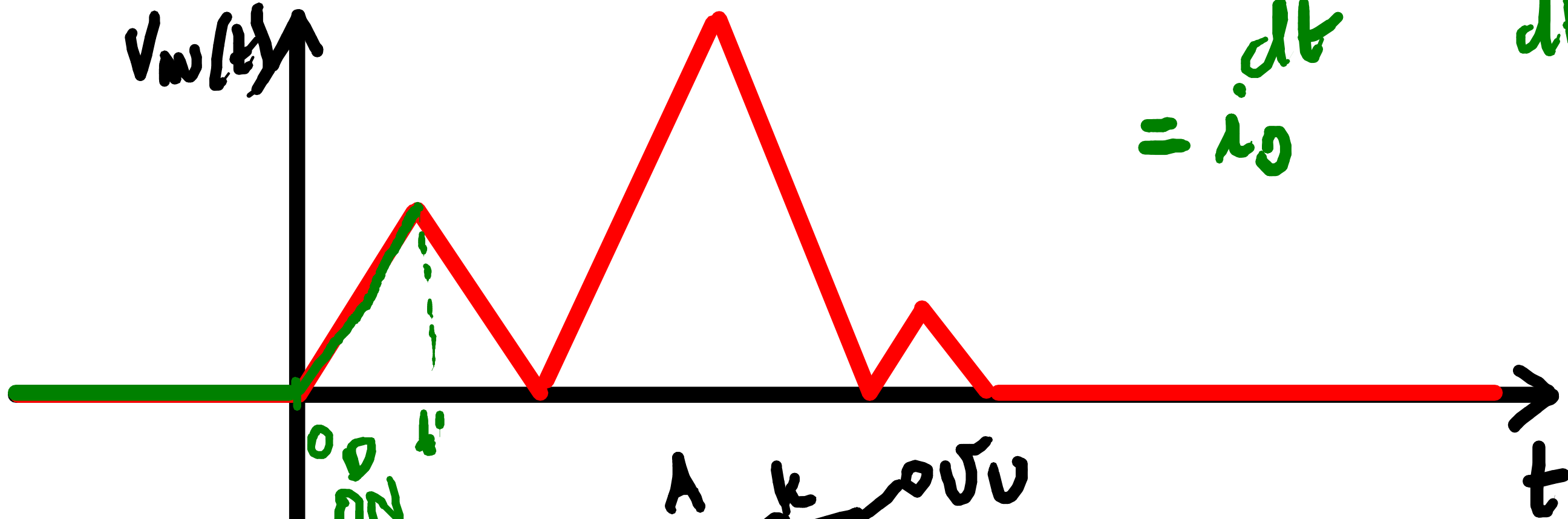



$t' < 0$
ON

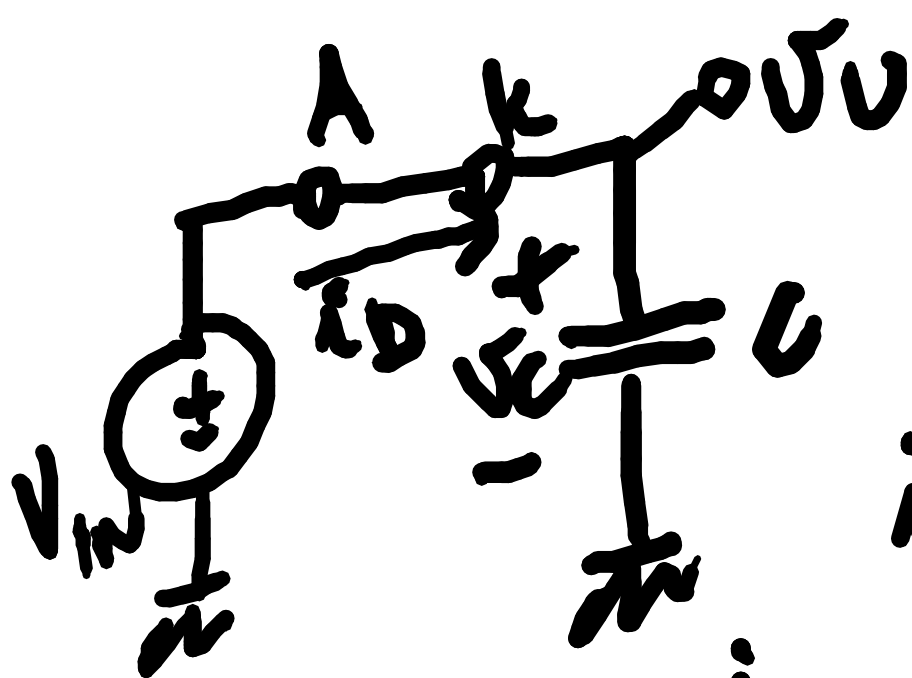

$$V_C = V_U = V_{IN}$$

$$i_D > 0$$
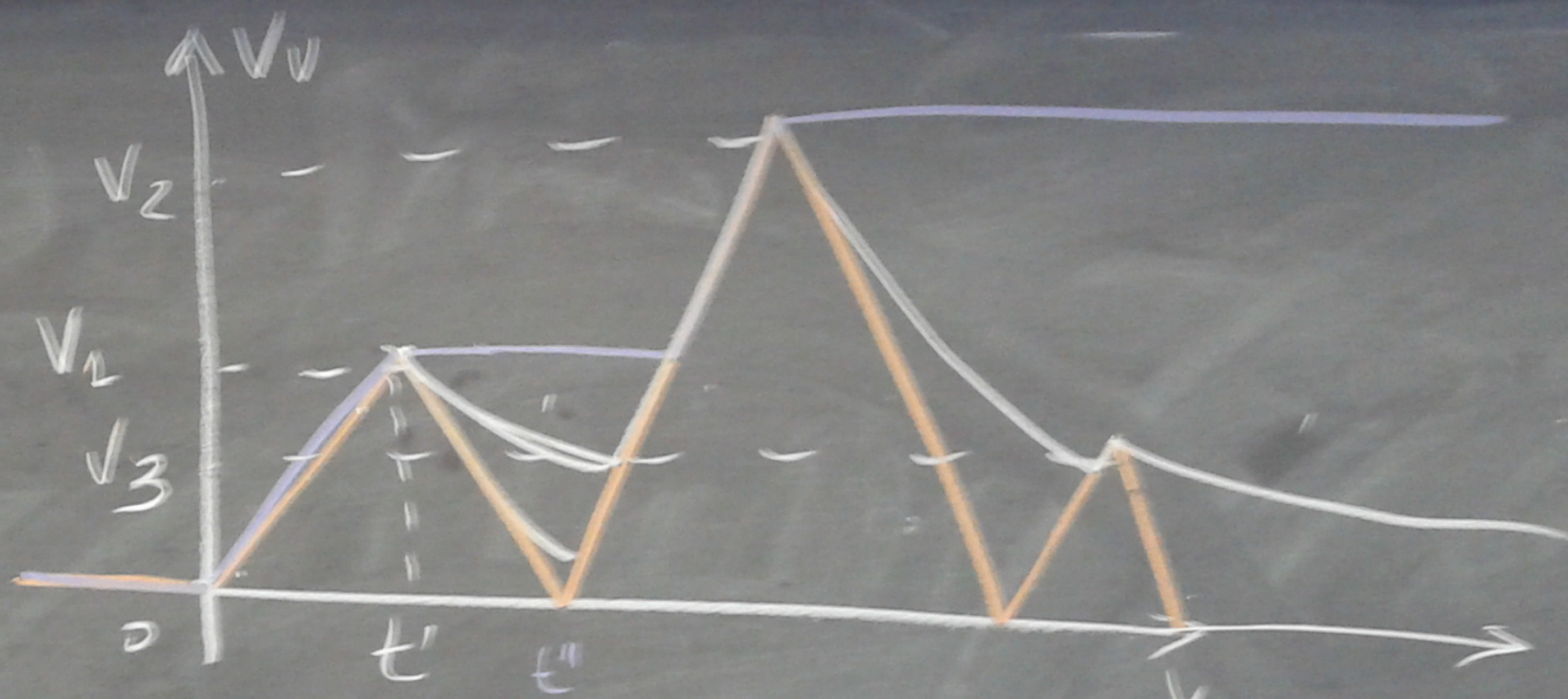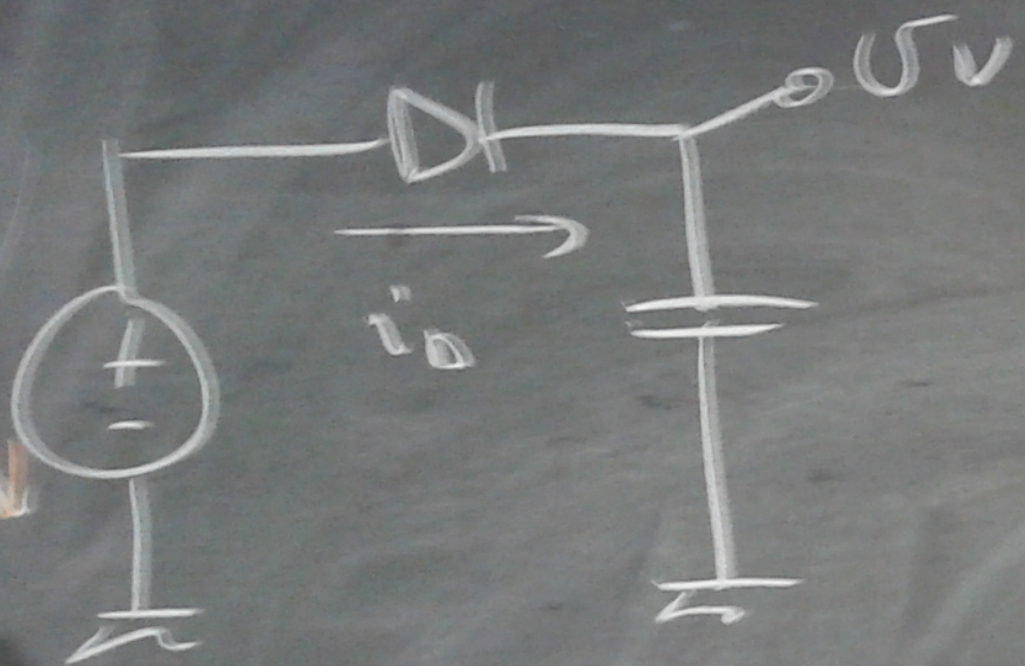
$$i_C = i_D = C \frac{dV_C}{dt} = C \frac{dV_{IN}}{dt} > 0$$



$$i_c = C \frac{dV_{vw}}{dt} = i_D$$

