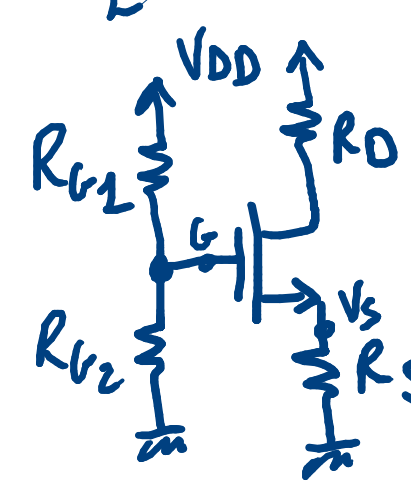


$R_{G1} = 150\text{ k}\Omega$
 $R_{G2} = 50\text{ k}\Omega$
 $R_D = 4\text{ k}\Omega$
 $R_S = 1\text{ k}\Omega$

$$k = \mu_n C_{ox} \frac{W}{L} = 2\text{ mA/V}^2$$

$$K = \mu_n C_{ox} \frac{W}{L} = 2\text{ mA/V}^2, V_{DD} = 12\text{ V}$$



$V_T = 1\text{ V}$
 $V_G = \frac{R_{G2}}{R_{G1} + R_{G2}} V_{DD} = 3\text{ V}$
 Mo. sat:
 $I_{DS} = \frac{k}{2} (V_{GS} - V_T)^2$

$$\begin{cases} I_{DS} = \frac{k}{2} (V_{GS} - V_T)^2 \\ V_G = V_{GS} + R_S I_{DS} \end{cases}$$

$$\frac{R_S k}{2} V_{GS}^2 - R_S k V_{GS} V_T + V_{GS} + \frac{R_S k}{2} V_T^2 = 0$$

$$V_{GS}^2 - V_{GS} - 2 = 0 \Rightarrow V_{GS} = \begin{cases} -1\text{ V} & \text{NO} \\ 2\text{ V} & \text{OK} \end{cases}$$


$$\boxed{V_{GS} \geq V_T}$$

$$I_{DS} = 1\text{ mA}$$


$$V_{DS} = V_D - V_S = \underbrace{V_{DD} - R_D I_{DS}}_{V_D} - \underbrace{R_S I_{DS}}_{V_S} = 7\text{ V}$$

$$V_{DS} = 7\text{ V} \geq V_{GS} - V_T = 1\text{ V} \quad \underline{\text{OK Sat}}$$
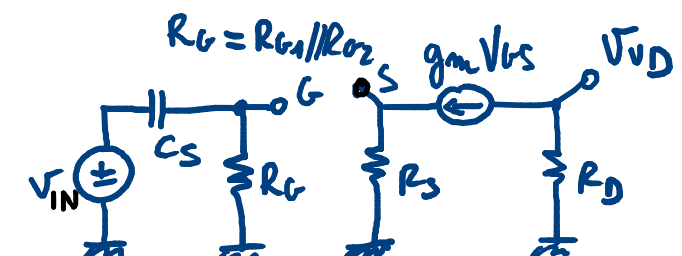
$$g_m = \frac{\delta I_{DS}}{\delta V_{GS}} = k (V_{GS} - V_T) = 2\text{ mA/V}$$


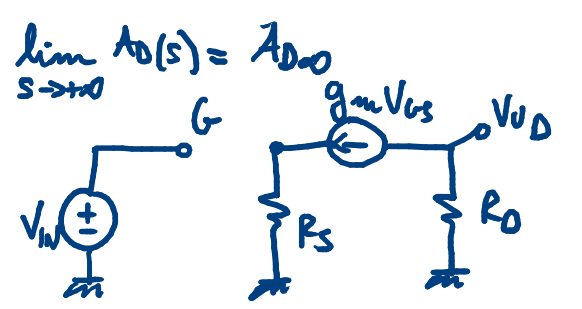
$$A_D = \frac{V_{OD}}{V_{IN}} = \frac{A_{D0} s}{(s + \omega_p)} \quad \omega_p = \frac{1}{C_S R_{VCS}}$$



$$\lim_{s \rightarrow 0} A_D(s) = A_{D0}$$

$$V_G = V_{IN} \quad V_{OD} = -R_D g_m V_{GS}$$

$$V_{GS} = V_G - V_S$$


$$V_S = R_S g_m V_{GS}$$

$$V_{GS} = V_G - R_S g_m V_{GS}$$


$$V_{GS} = \frac{V_G}{1 + R_S g_m} = \frac{V_{IN}}{1 + R_S g_m}$$

$$V_{OD} = \frac{-R_D g_m V_{IN}}{1 + R_S g_m}$$
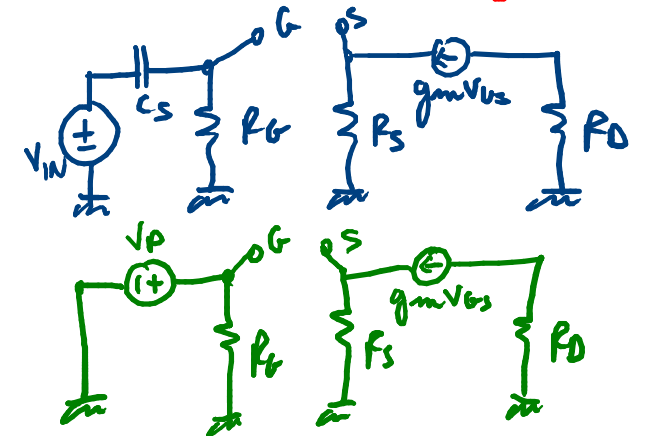
$$A_{D0} = \frac{V_{OD}}{V_{IN}} = \frac{-R_D g_m}{1 + R_S g_m} \approx -\frac{R_D}{R_S} \quad (R_S g_m \gg 1)$$



$$\omega_p = \frac{1}{R_G C_S}$$

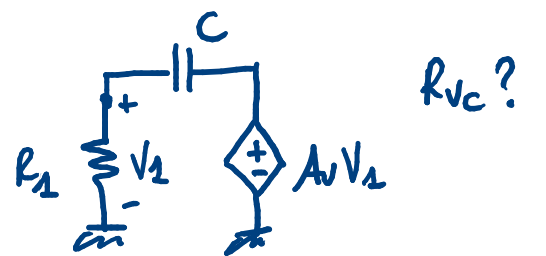


$$V_P = R_1 I_P + A_V V_2$$

$$V_2 = -R_1 I_P$$


$$V_P = R_1 I_P - A_V R_1 I_P$$

$$V_P / I_P = R_1 (1 - A_V)$$

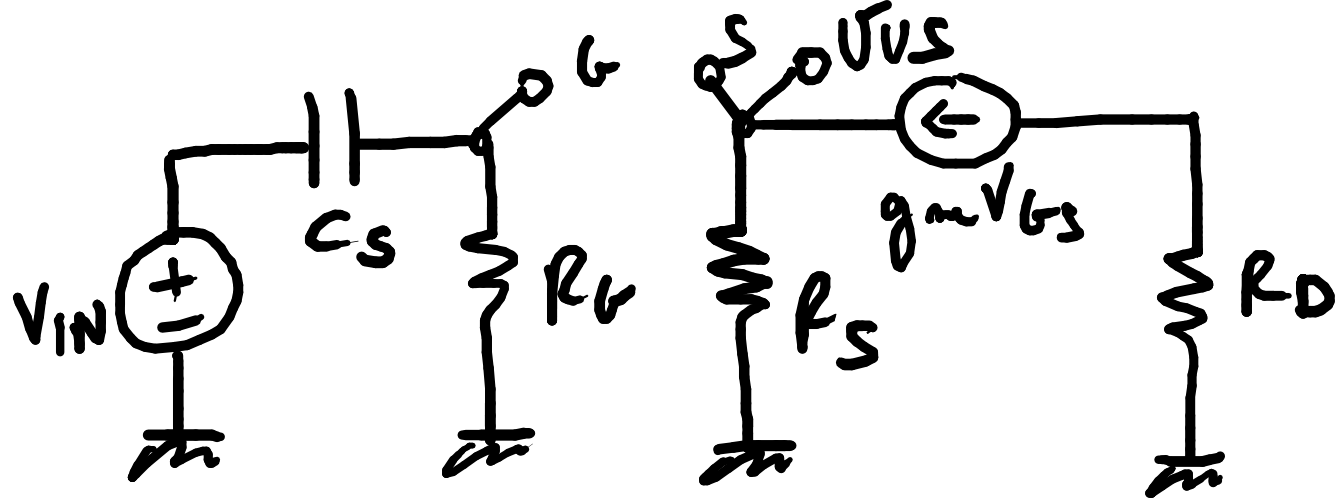

$$A_v(s) = \frac{A_{v\infty} s}{(s + \omega_p)}$$

$$\omega_p = \frac{1}{C_s R_G}$$



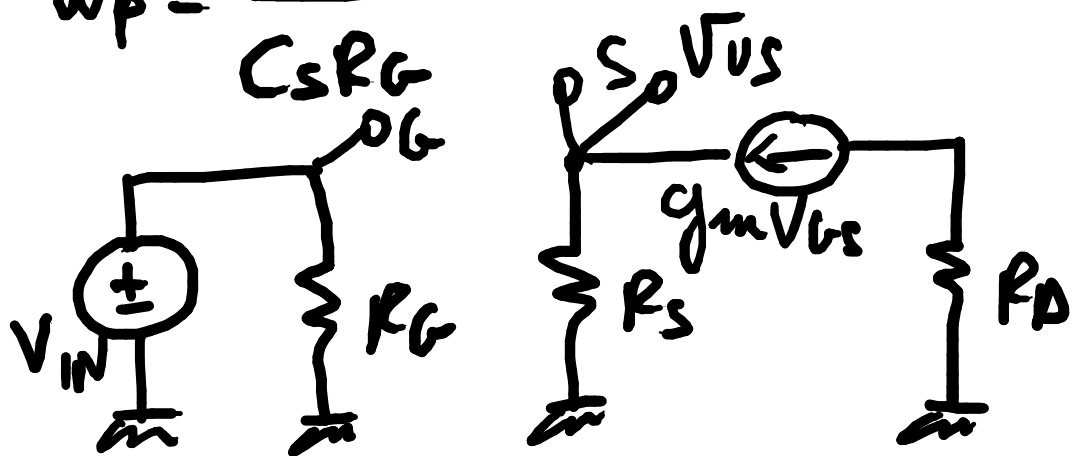


$$A_{v\infty} = \frac{V_{us}}{V_{in}}$$

$$V_{us} = R_s g_m V_{gs}$$


$$V_{gs} = \frac{V_G}{1 + R_s g_m} \Rightarrow V_{us} = \frac{R_s g_m V_{in}}{1 + g_m R_s}$$
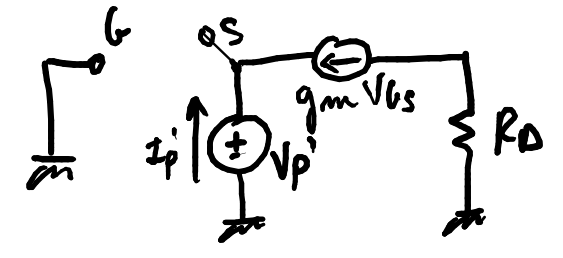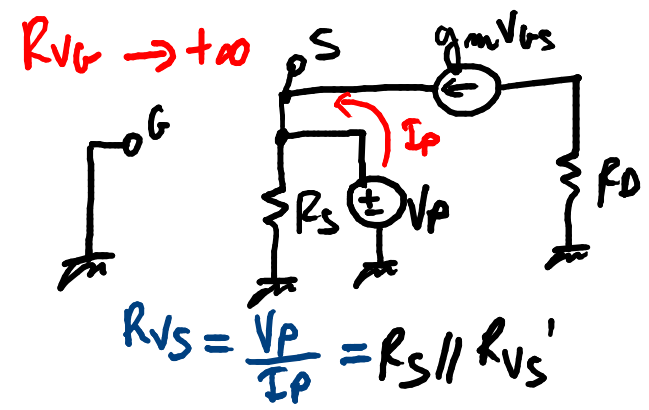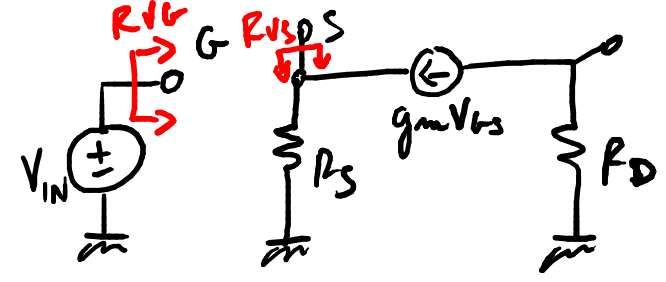
$$A_{v\infty} = \frac{R_s g_m}{1 + R_s g_m} \underset{R_s g_m \gg 1}{\approx} 1$$




$R_{V_S'} = \frac{V_{P'}}{I_{P'}} \Rightarrow I_{P'} = -g_m V_{G_S}$
 $V_{G_S} = -V_{P'} \Rightarrow I_{P'} = g_m V_{P'}$

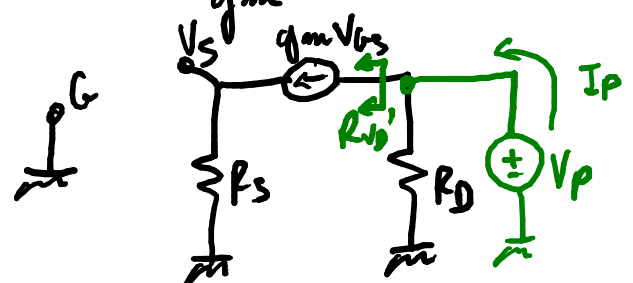$R_{V_S'} = \frac{1}{g_m} \Rightarrow R_{V_S} = R_S \parallel \frac{1}{g_m}$



$R_{V_D} = \frac{V_P}{I_P} = R_D \parallel R_{V_D'}$

Calculer $R_{V_D'}$

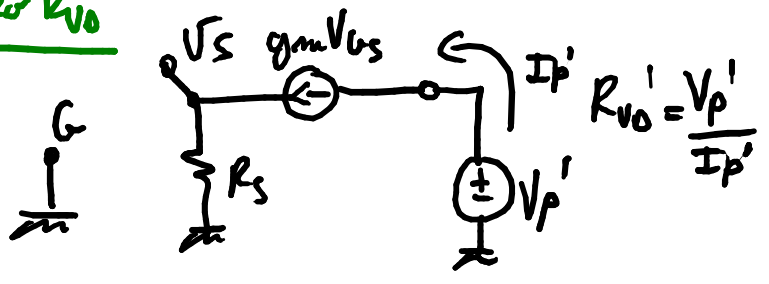


$I_{P'} = g_m V_{G_S}$

$V_{G_S} = V_G - V_S \quad V_S = R_S g_m V_{G_S}$
 $V_G = 0V$


$V_{G_S} = -R_S g_m V_{G_S} \Rightarrow V_{G_S} = 0V$

$I_{P'} = 0A \Rightarrow R_{V_D'} \rightarrow +\infty$


$R_{V_D} = R_D$

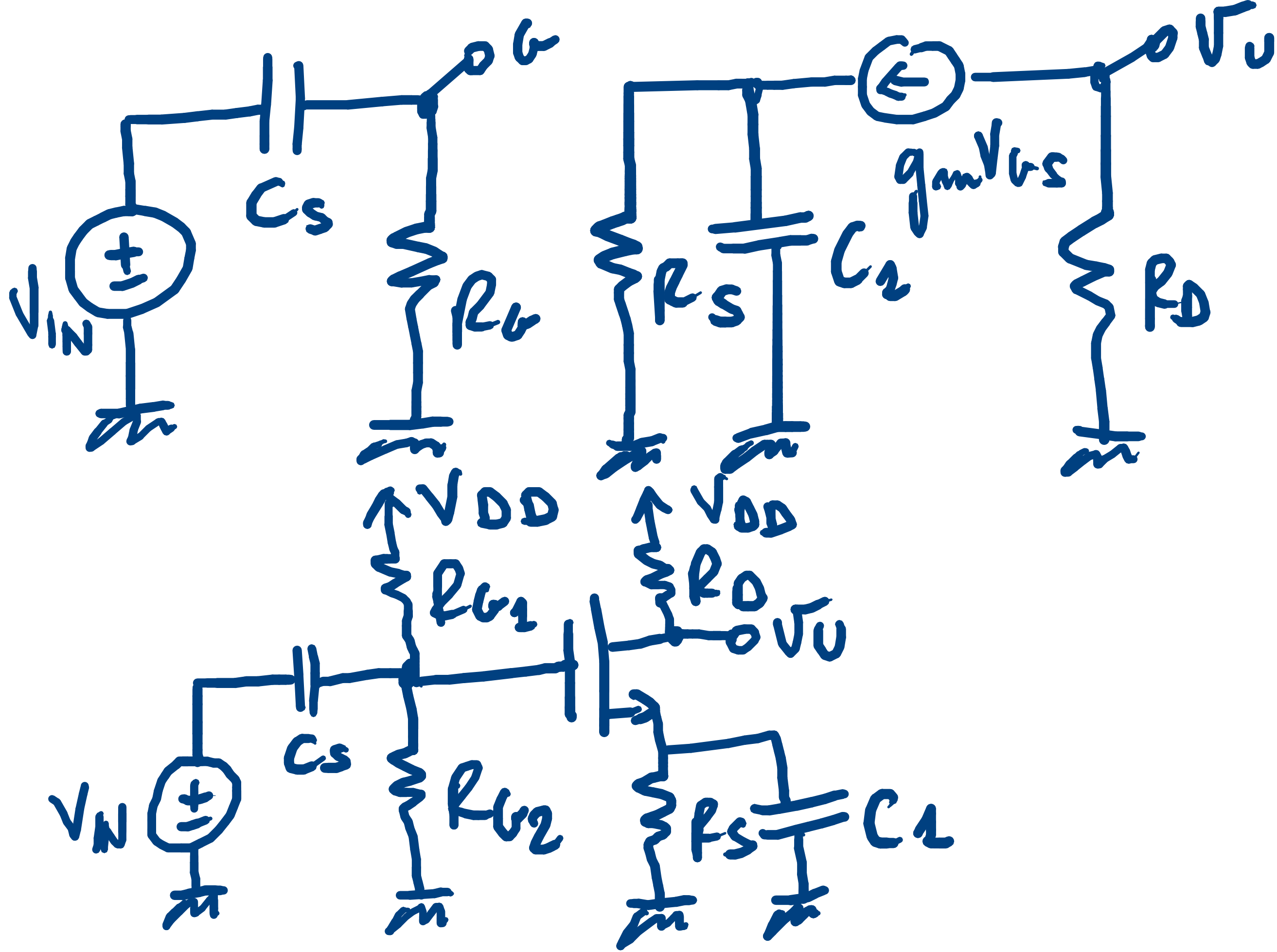
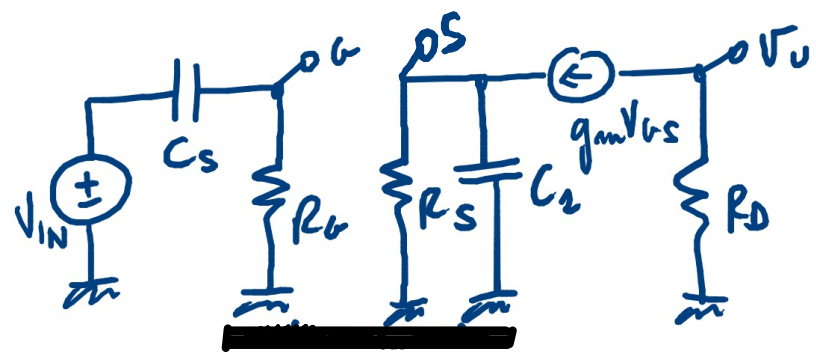
$$A_{V_{DD}} = \frac{-g_m R_D}{1 + g_m R_S}$$



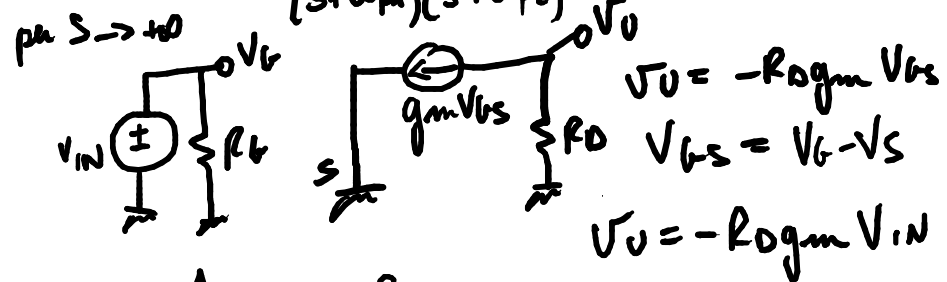
$$A_V(s) = \frac{A_{V0} s (s + \omega_0)}{(s + \omega_{p1})(s + \omega_{p2})}$$



$$A_{V0} = -R_D g_m$$

$$\omega_{p1} = \frac{1}{C_S R_{VCS}} = \frac{1}{C_S R_G}$$
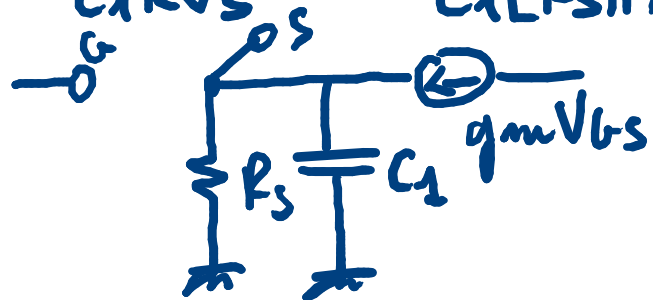
$$\omega_{p2} = \frac{1}{C_1 R_{VS}} = \frac{1}{C_1 [R_S \parallel 1/g_m]}$$



$$V_{GS} = V_G - V_S = V_G - Z_S g_m V_{GS}$$

$$Z_S = R_S \parallel \frac{1}{C_1 s}$$

$$V_{GS} = V_G - Z_S(s) g_m V_{GS}$$


Se $Z_S(s_0) \rightarrow +\infty$

$$V_{GS} \approx -Z_S(s_0) g_m V_{GS}$$


$$V_{GS} = 0V \Rightarrow V_O = ? = -R_D g_m V_{GS}$$

$$V_O = 0V$$
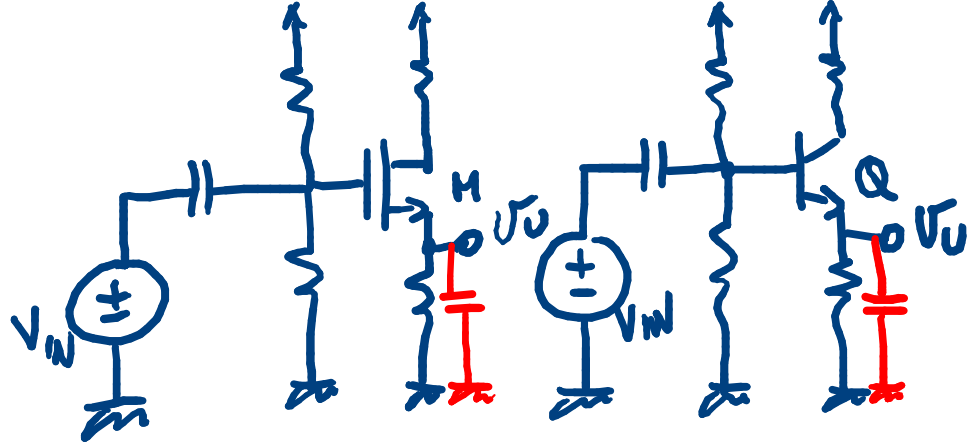
$$s_0 = -\frac{1}{R_S C_1} \Rightarrow \omega_0 = \frac{1}{R_S C_1}$$



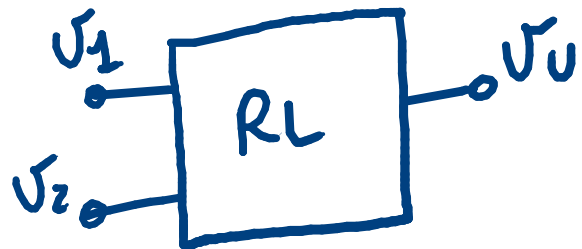
$$h_{fe} = \frac{\Delta I_c}{\Delta I_b}$$



$$V_u = A_1 V_1 + A_2 V_2$$

$$\begin{cases} V_d = V_1 - V_2 & \Rightarrow V_1 = V_d + V_2 \\ V_c = \frac{V_1 + V_2}{2} & V_c = \frac{V_d + V_2 + V_2}{2} \end{cases}$$
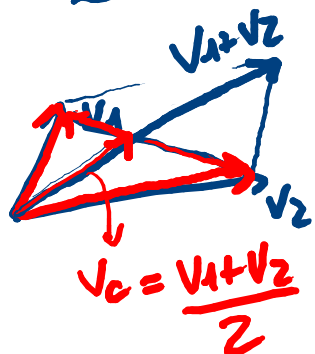
$$V_c = \frac{V_d}{2} + V_2 \Rightarrow \begin{cases} V_2 = V_c - \frac{V_d}{2} \\ V_1 = V_c + \frac{V_d}{2} \end{cases}$$




$$\begin{aligned} V_u &= A_1 \left(V_c + \frac{V_d}{2} \right) + A_2 \left(V_c - \frac{V_d}{2} \right) = \\ &= \underbrace{\left[\frac{A_1 - A_2}{2} \right]}_{A_d} V_d + \underbrace{(A_1 + A_2)}_{A_c} V_c \end{aligned}$$

$$V_u = A_d V_d + A_c V_c$$

$$CHRR = \frac{A_d}{A_c} \gg 1$$

COMMON
MODE
REJECTION
RATIO

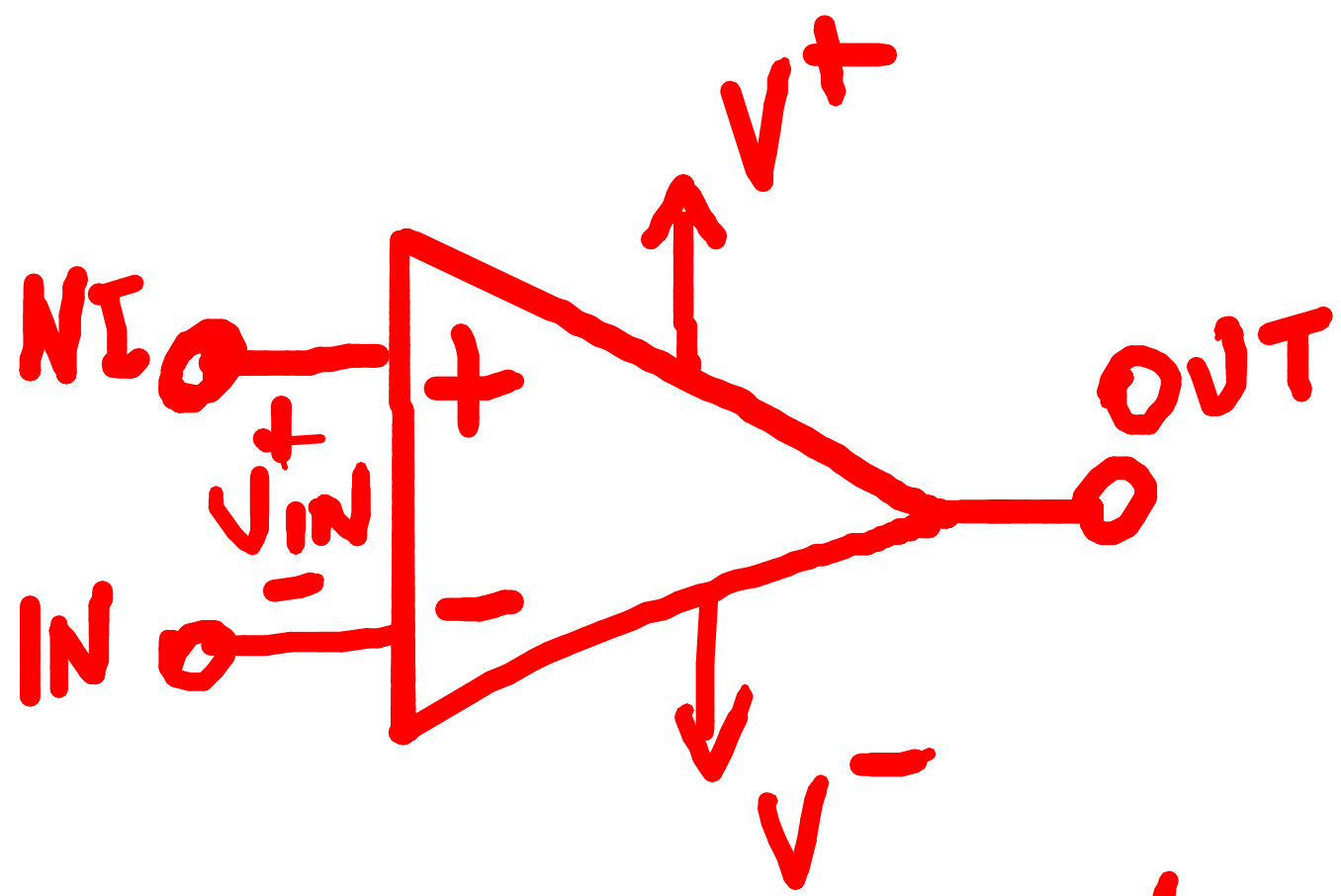

$$V_O = A_{VOL} \phi V_{IN}$$

