
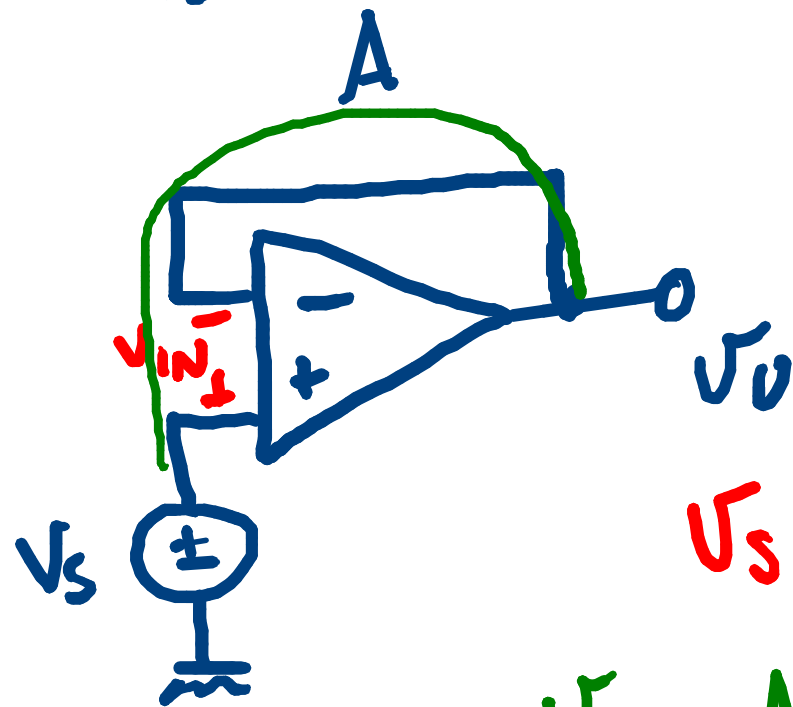
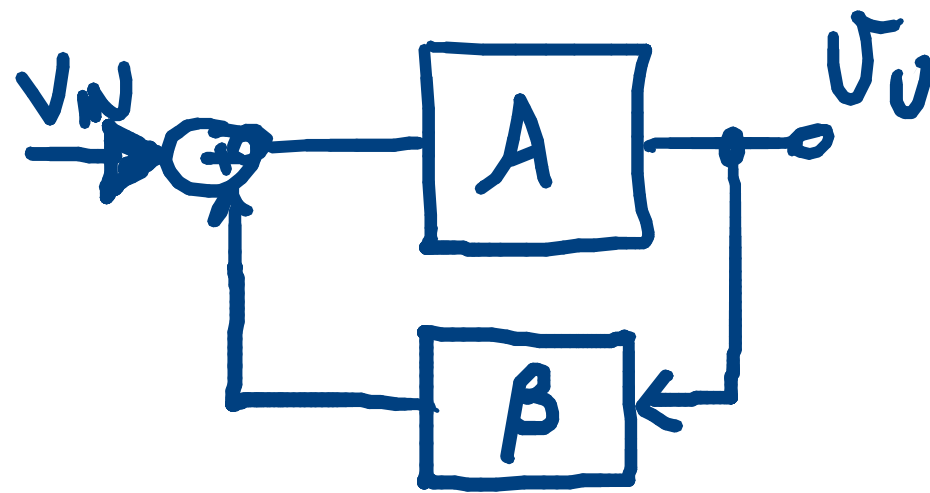


$$V_U = A V_{IN}$$

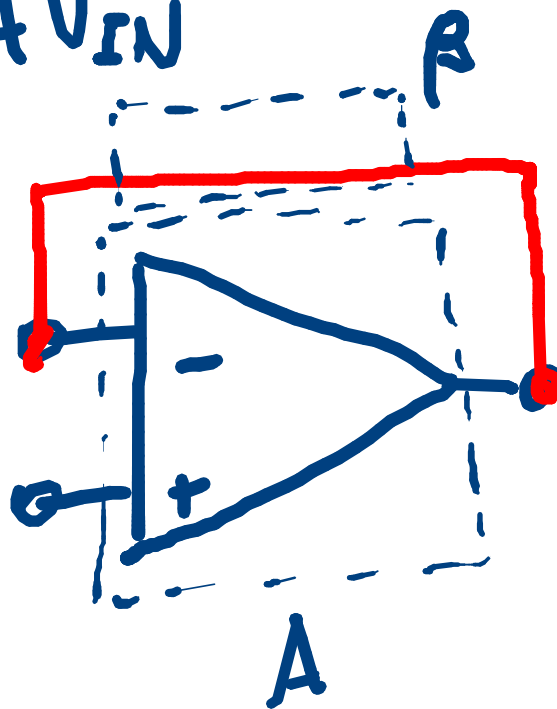


$$V_U = A V_{IN}$$

$$V_S = V_{IN} + V_U \Rightarrow V_{IN} = V_S - V_U$$



$$V_U = A (V_S - V_U) \Rightarrow$$

$$V_U (1 + A) = A V_S$$
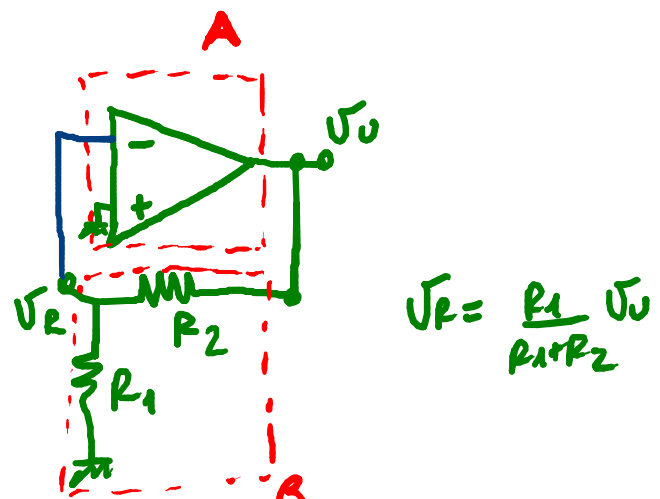
$$V_U = \frac{A V_S}{1 + A} \approx V_S$$




$$V_R = \frac{R_1}{R_1 + R_2} V_0$$

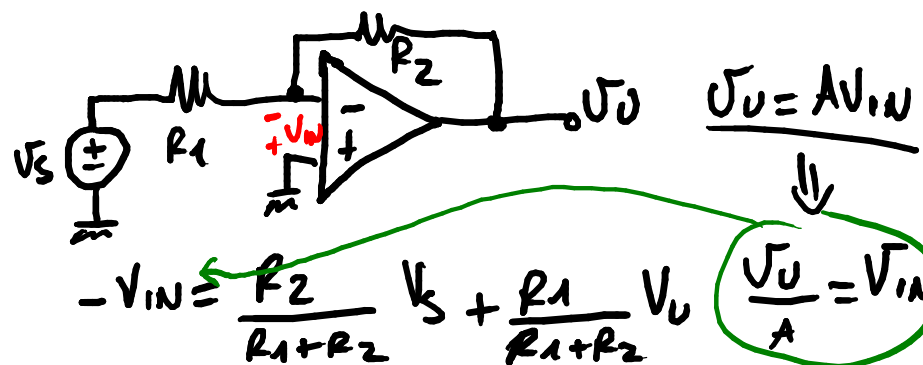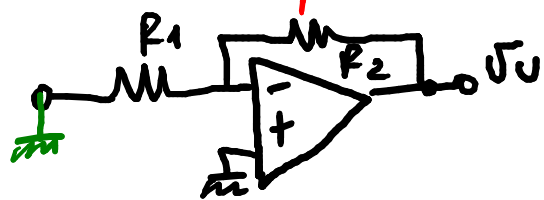

$$V_0 = A V_{in}$$
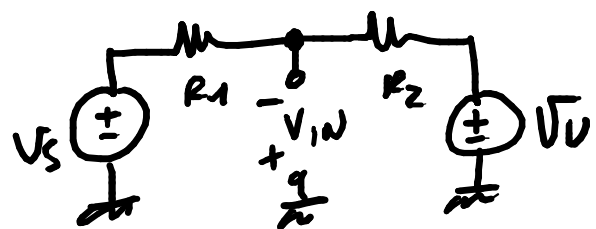
$$-V_{in} = \frac{R_2}{R_1 + R_2} V_s + \frac{R_1}{R_1 + R_2} V_0 \quad \left(\frac{V_0}{A} = V_{in} \right)$$



$$\frac{-V_0}{A} = \frac{R_2}{R_1 + R_2} V_s + \frac{R_1}{R_1 + R_2} V_0$$

$$-V_0 = \frac{A R_2}{R_1 + R_2} V_s + A \frac{R_1}{R_1 + R_2} V_0$$

$$-\left(1 + A \frac{R_1}{R_1 + R_2}\right) V_0 = \frac{A R_2}{R_1 + R_2} V_s$$


$$V_0 = \frac{-\frac{A R_2}{R_1 + R_2} V_s}{\left(1 + A \frac{R_1}{R_1 + R_2}\right)}$$

$$\approx -\frac{A R_2}{R_1 + R_2} V_s = -\frac{R_2}{R_1} V_s$$

$$V_0 = A V_{in} \quad V_{in} = \frac{V_0}{A}$$

$$V_{in} = -\left[\frac{R_2}{R_1 + R_2} \frac{A}{\left(1 + A \frac{R_1}{R_1 + R_2}\right)} \right] V_s$$
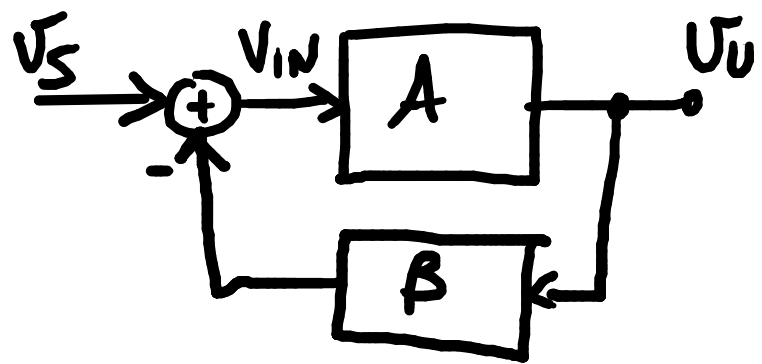
$$V_{in} \rightarrow 0 \quad \text{as } A \rightarrow \infty$$



$$V_{IN} = V_S - \beta V_U$$


$$V_U = A V_{IN}$$

$$V_U = A (V_S - \beta V_U) \Rightarrow$$

$$V_U (1 + \beta A) = A V_S \Rightarrow V_U = \frac{A}{1 + \beta A} V_S$$

$$V_{IN} = \frac{V_U}{A} = \frac{1}{1 + \beta A} V_S$$
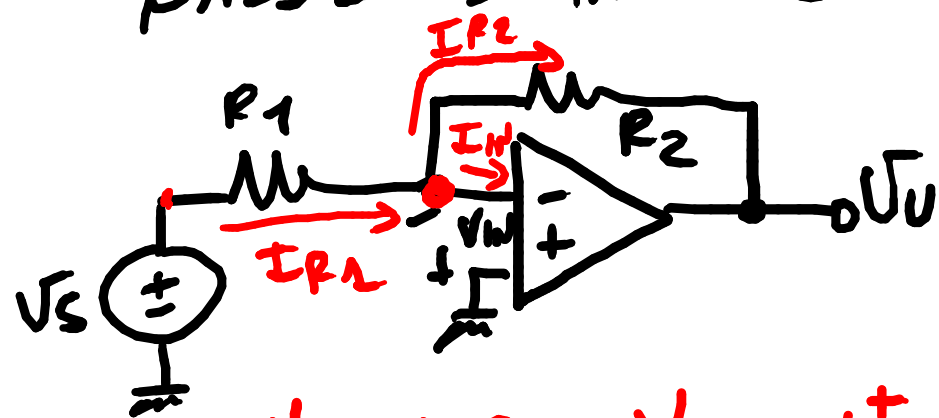
$$\beta A \gg 1 \Rightarrow V_{IN} \rightarrow 0$$



$$V_{IN} \rightarrow 0 \quad V_{IN} = V^+ - V^-$$


$$V^+ = 0V \Rightarrow V^- \approx 0V$$

$$I_{R1} = \frac{V_S}{R_1}$$


$$I_{R1} = I_{R2} + I_{IN} = I_{R2}$$

$$V_U = -R_2 I_{R2} = -R_2 I_{R1} = -\frac{R_2}{R_1} V_S$$

$$R_1 = R_2 = R$$

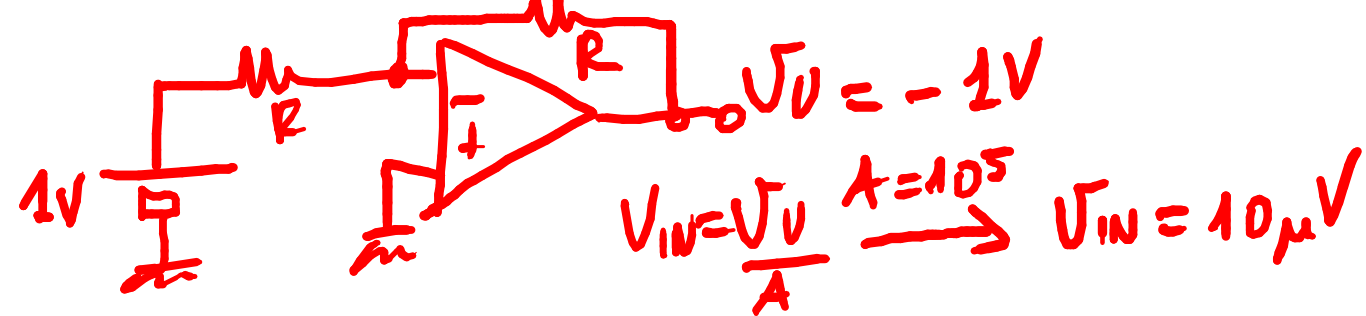


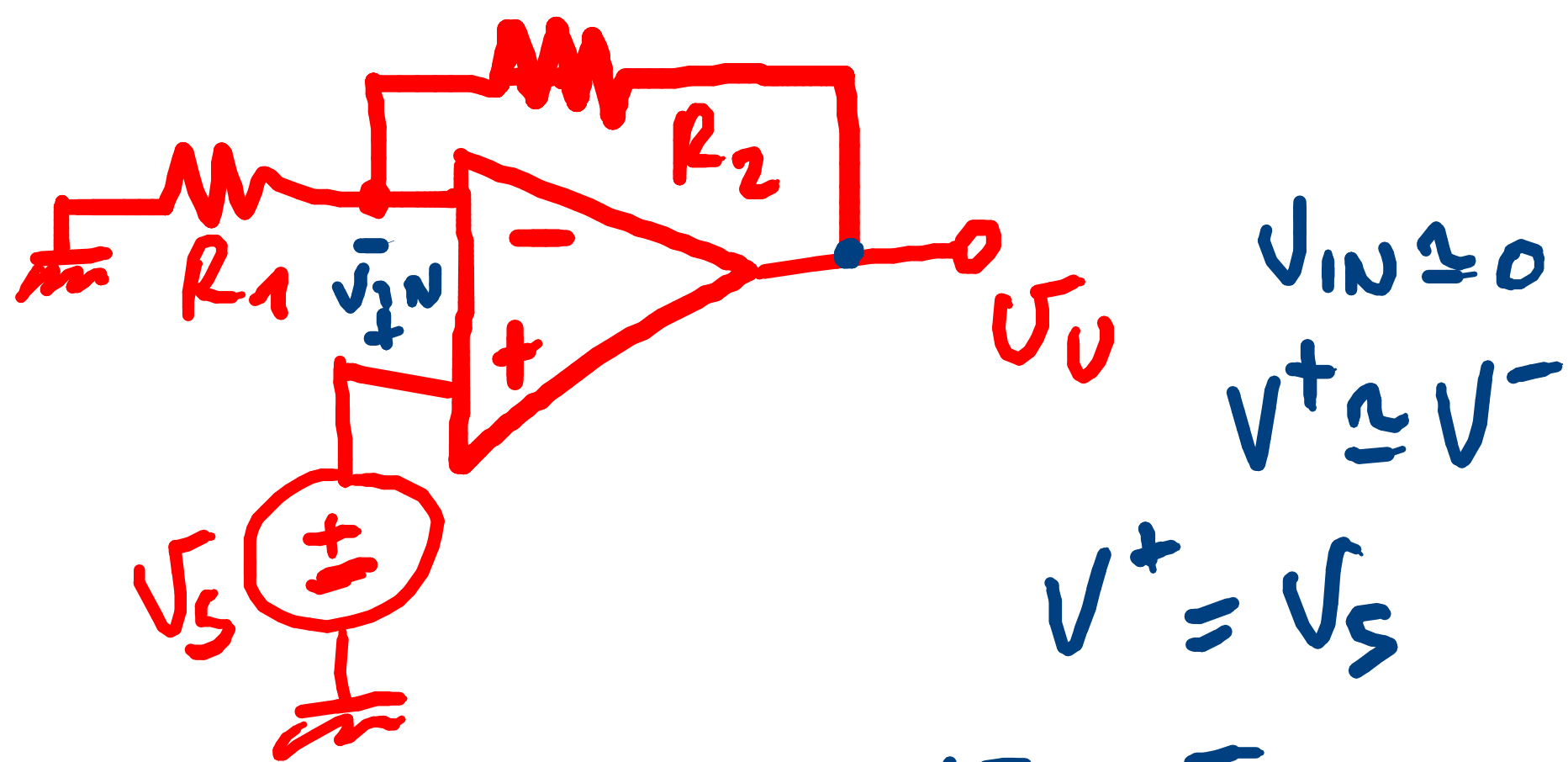
$$V_{IN} = \frac{V_U}{A} \xrightarrow{A=10^5} V_{IN} = 10 \mu V$$



$$V^- = \frac{R_1}{R_1 + R_2} V_U = V_S$$

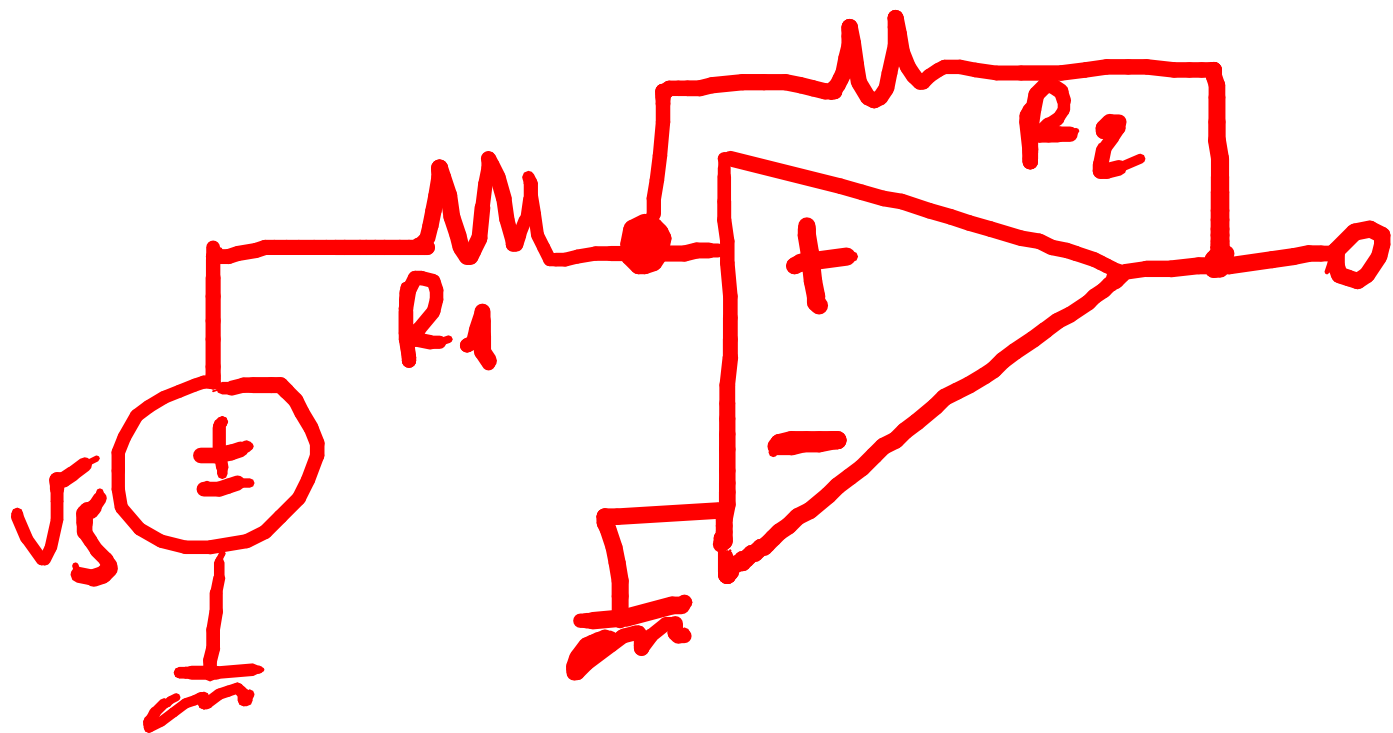
$$V_U = \left(\frac{R_1 + R_2}{R_1} \right) V_S = \left(1 + \frac{R_2}{R_1} \right) V_S$$



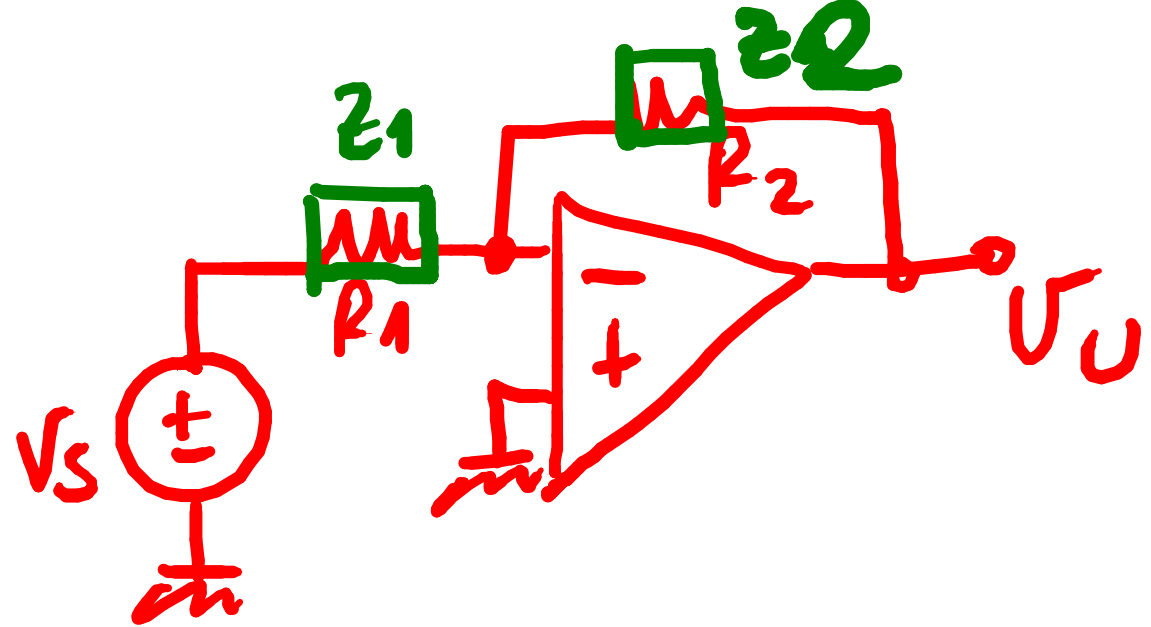




$$V_U = -\frac{Z_2}{Z_1} V_S$$

$$Z_2 = \frac{1}{Cs} \quad Z_1 = R$$

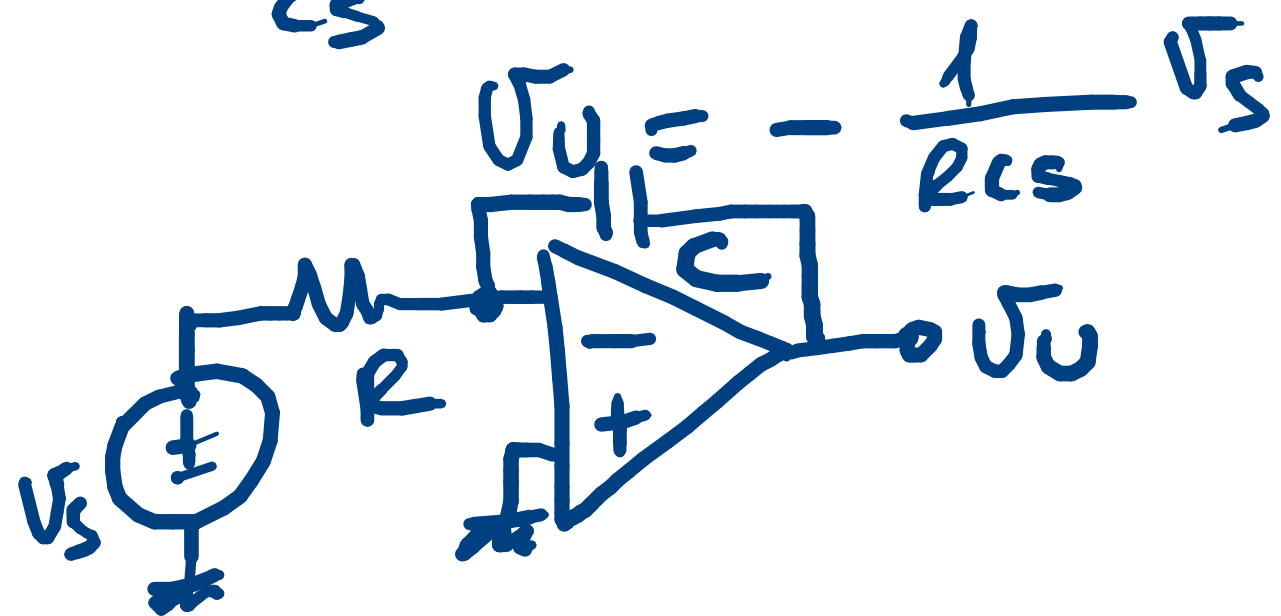

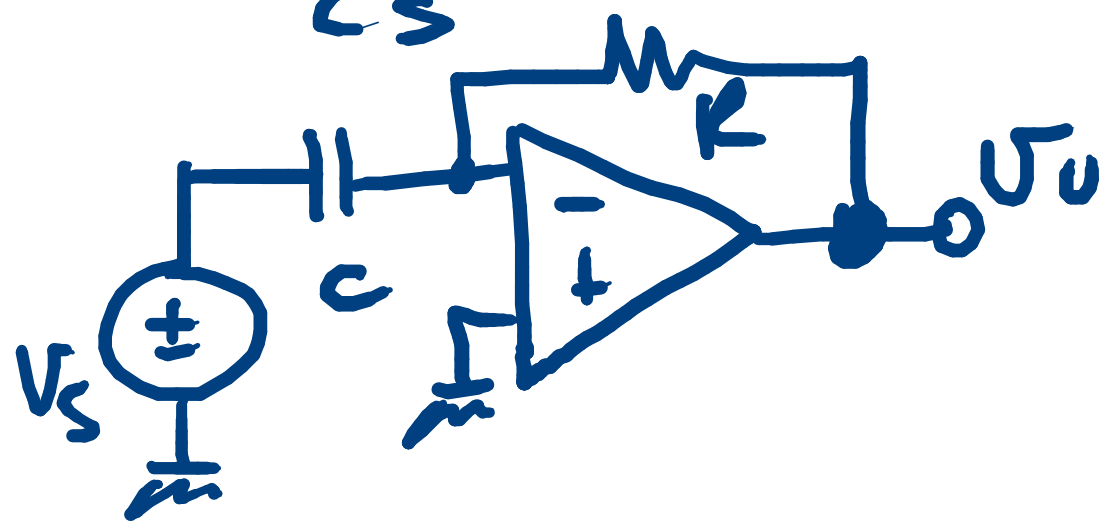
$$Z_1 = \frac{1}{Cs} \quad Z_2 = R \Rightarrow V_U = -Rcs V_S$$



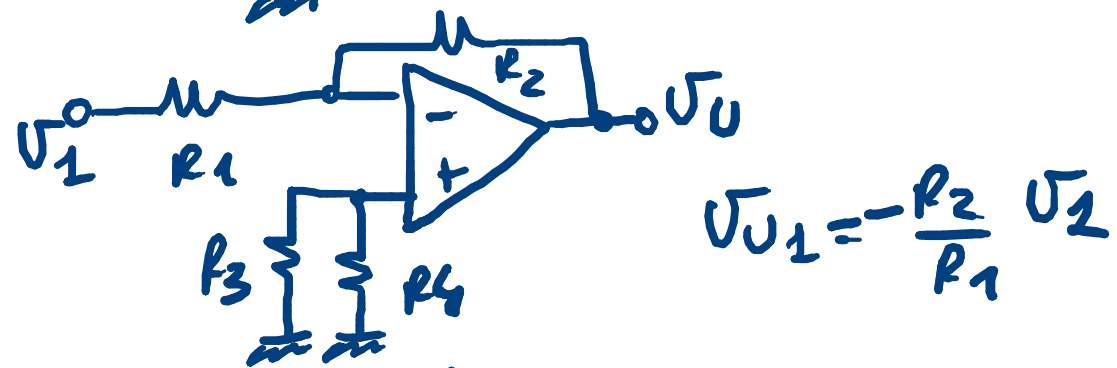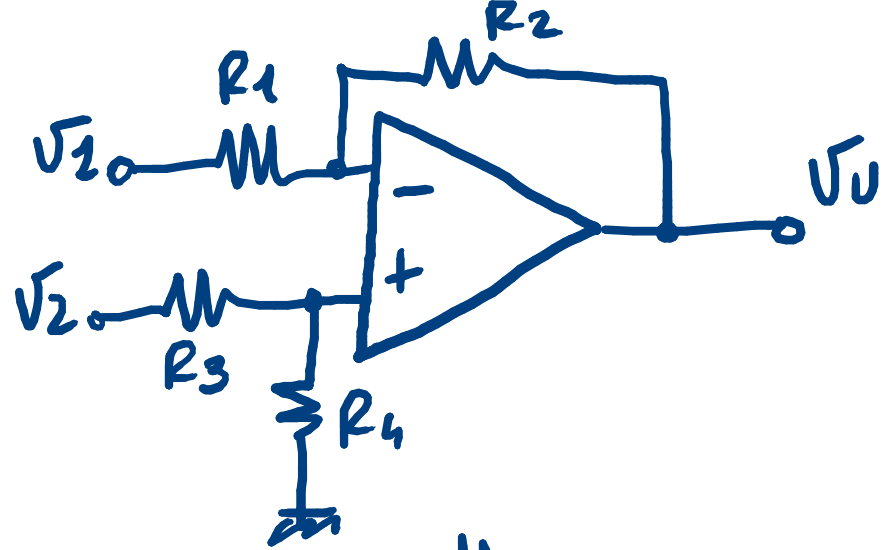

$$V_{U1} = -\frac{R_2}{R_1} V_2$$

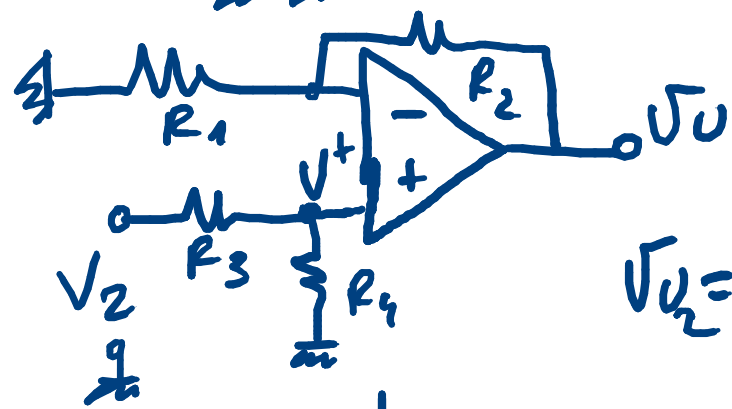

$$V_{U2} = \left(1 + \frac{R_2}{R_1}\right) V^+$$

$$V^+ = \frac{R_4}{R_3 + R_4} V_2$$

$$V_{U2} = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) V_2$$

$$V_U = V_{U1} + V_{U2} = -\frac{R_2}{R_1} V_1 + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) V_2$$



$$V_U = A_1 V_1 + A_2 V_2$$

$$V_U = A_d (V_1 - V_2)$$

$$V_U = -\frac{R_2}{R_1} V_1 + \frac{R_4/R_3}{1 + R_4/R_3} \left(1 + \frac{R_2}{R_1}\right) V_2$$

$$\frac{R_2}{R_1} = R_4/R_3$$

$$V_U = -\frac{R_2}{R_1} (V_1 - V_2)$$

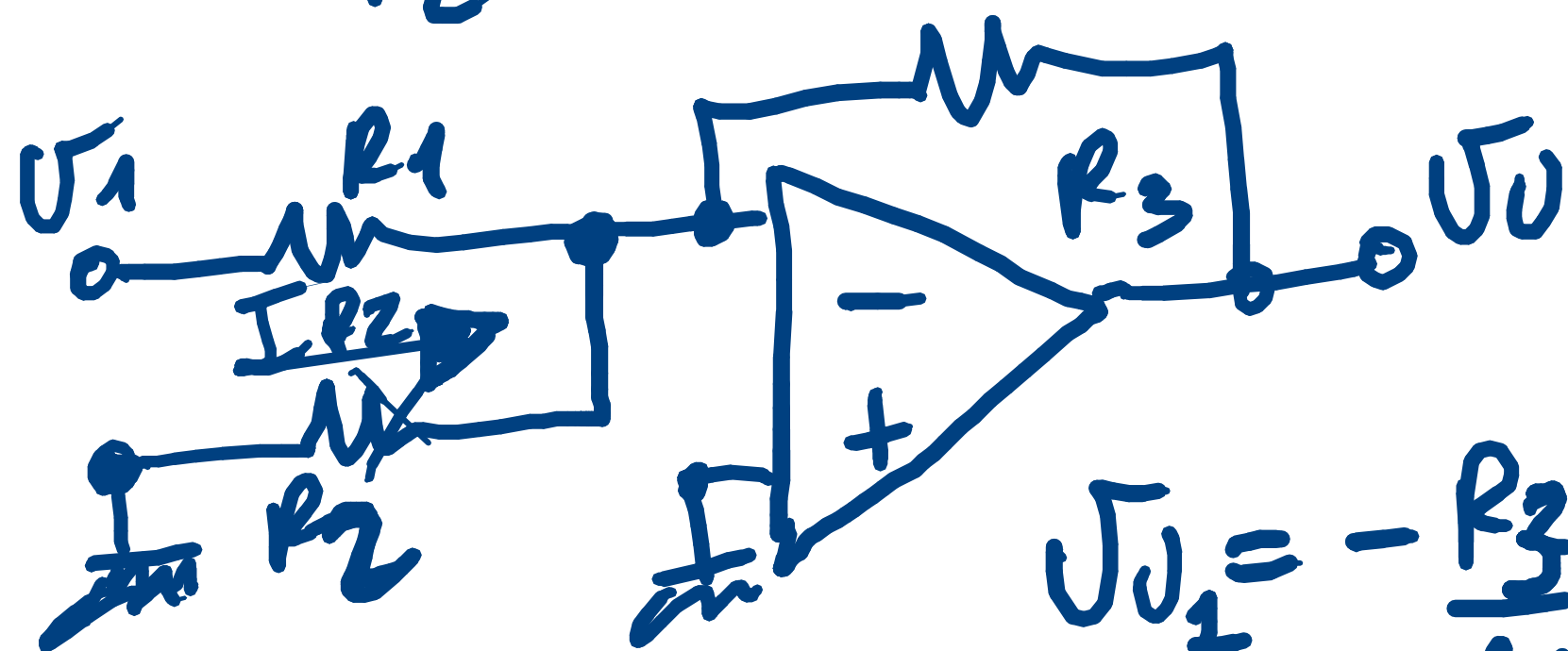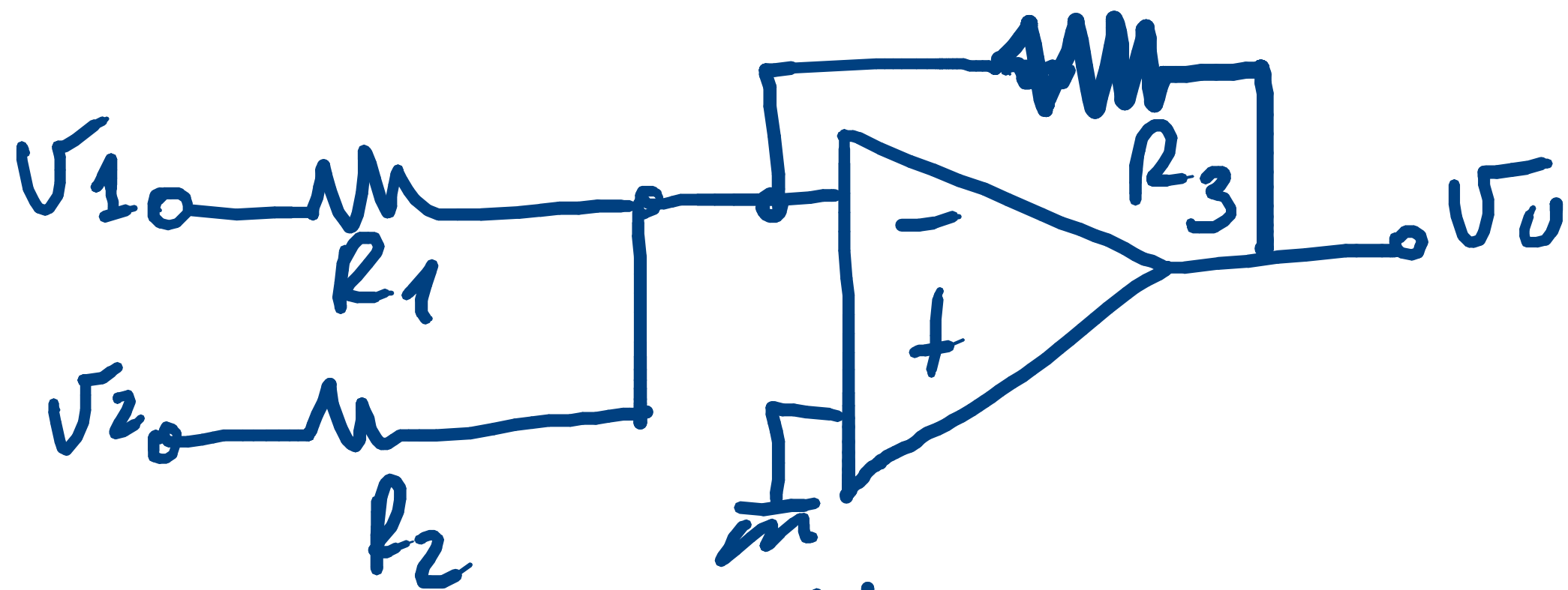

$$V_{U_1} = -\frac{R_3}{R_1} V_1$$

$$V_{U_2} = -\frac{R_3}{R_2} V_2$$

$$V_U = V_{U_1} + V_{U_2} = -\frac{R_3}{R_1} V_1 - \frac{R_3}{R_2} V_2$$