




Avoo nel circuito di sopra senza C2?

$$V_U = -g_m R_D V_{GS}$$

$$V_{GS} = V_G - V_S = \frac{V_{IN}}{1 + g_m R_S}$$

$$V_U = \frac{-g_m R_D}{1 + g_m R_S} V_{IN} \quad A_{vol}_{C_2} = \frac{-g_m R_D}{1 + g_m R_S}$$

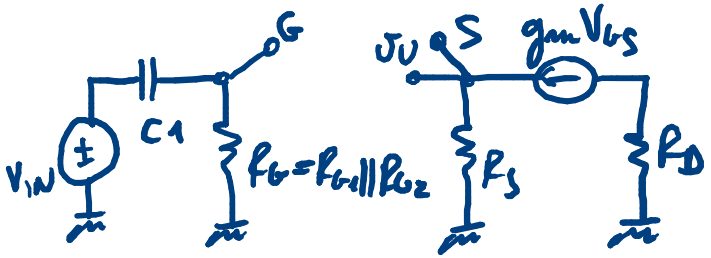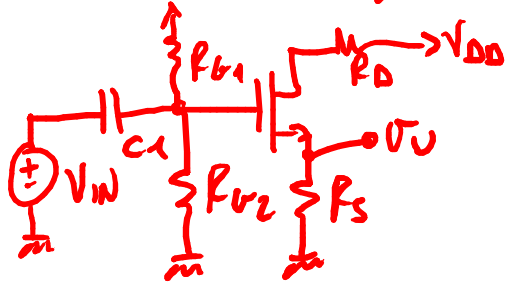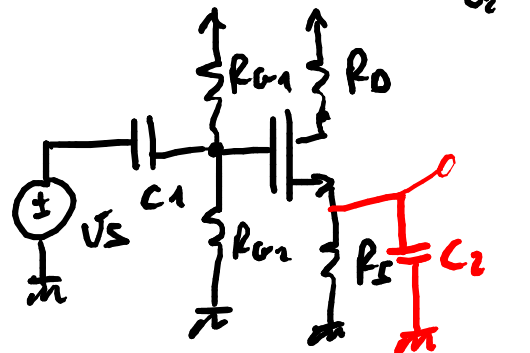
Se $g_m R_S \gg 1 \Rightarrow A_{vol}_{C_2} \approx -\frac{R_D}{R_S}$




$$V_U = g_m R_S V_{GS}$$

Per $S \rightarrow +\infty \quad V_{GS} = \frac{V_{IN}}{1 + g_m R_S}$
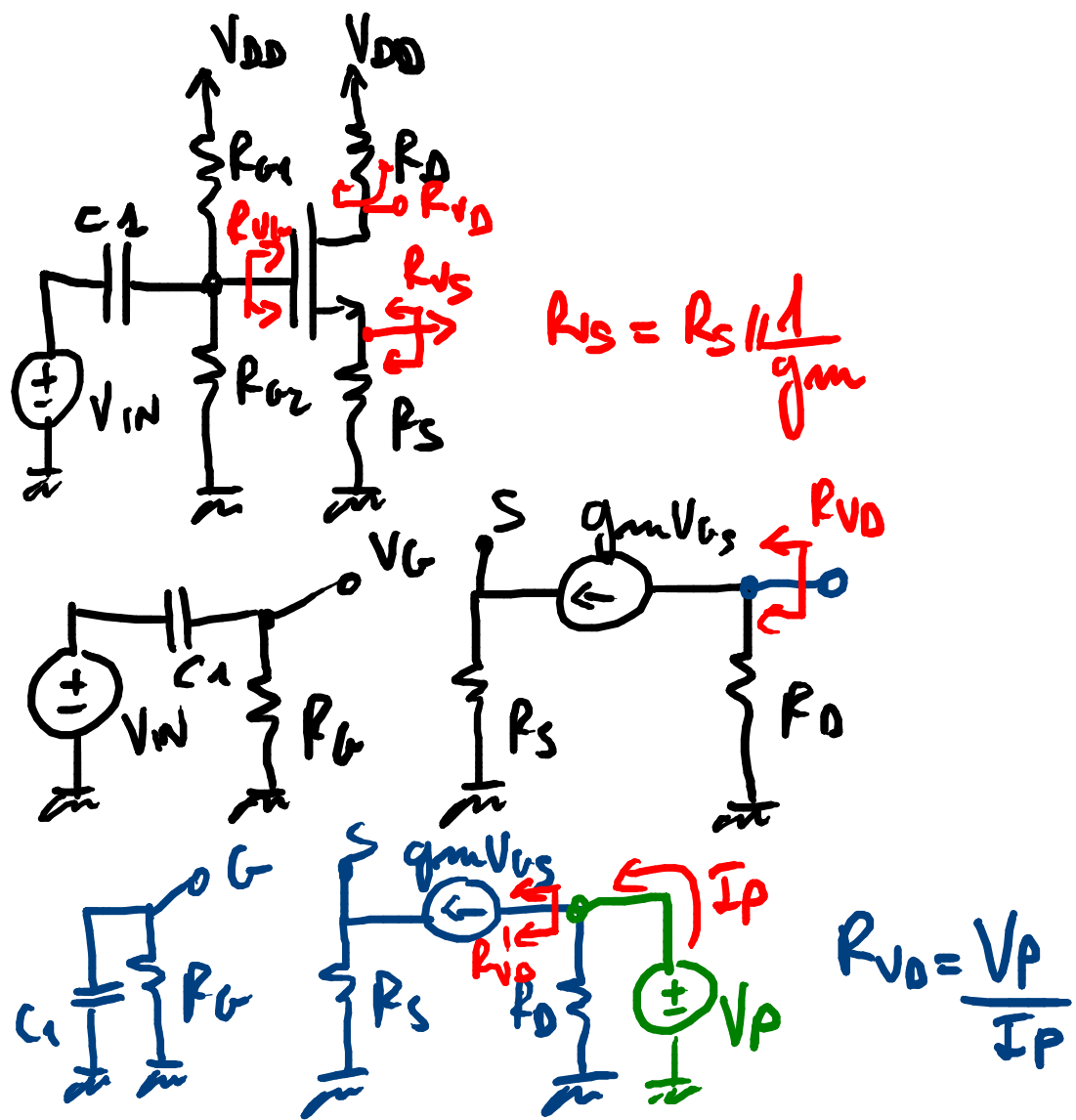
$$V_U = \frac{g_m R_S}{1 + g_m R_S} V_{IN} \quad \frac{V_U}{V_{IN}} = \frac{g_m R_S}{1 + g_m R_S} \xrightarrow{g_m R_S \gg 1} 1$$




$R_{O} = R_D // R_{O}'$

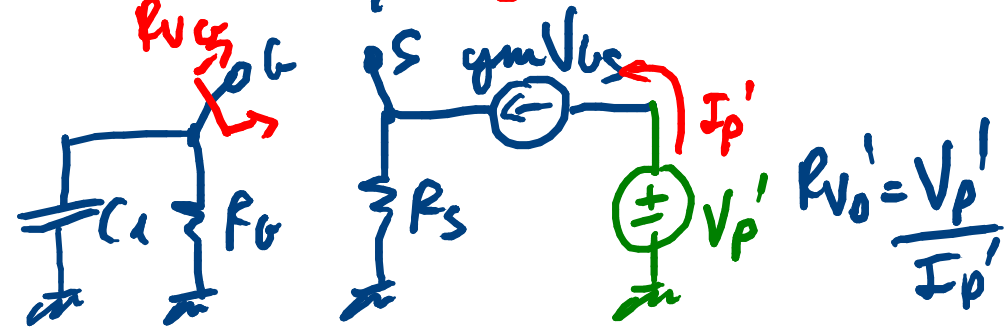


$I_P' = g_m V_{GS} = g_m (-V_S)$ where $V_G = 0V$

$V_S = g_m (-V_S) \cdot R_S \rightarrow V_S = 0 \rightarrow I_P' \rightarrow 0$

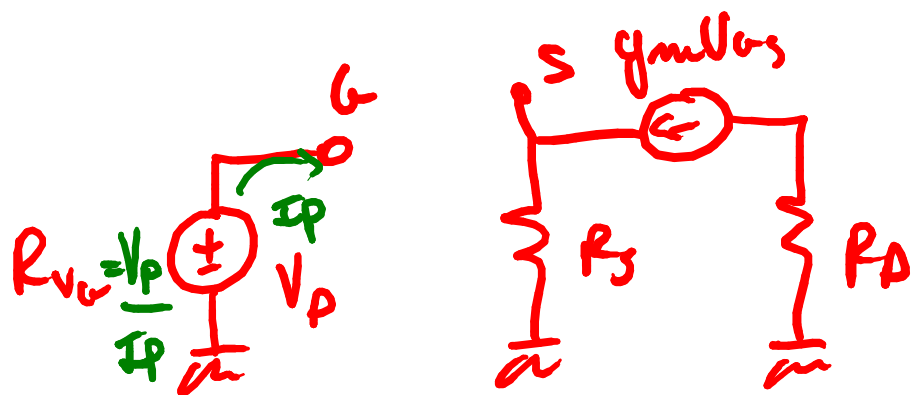$R_{O}' \rightarrow \infty$ $R_{O} = R_D$




$R_{VC} \rightarrow \infty$

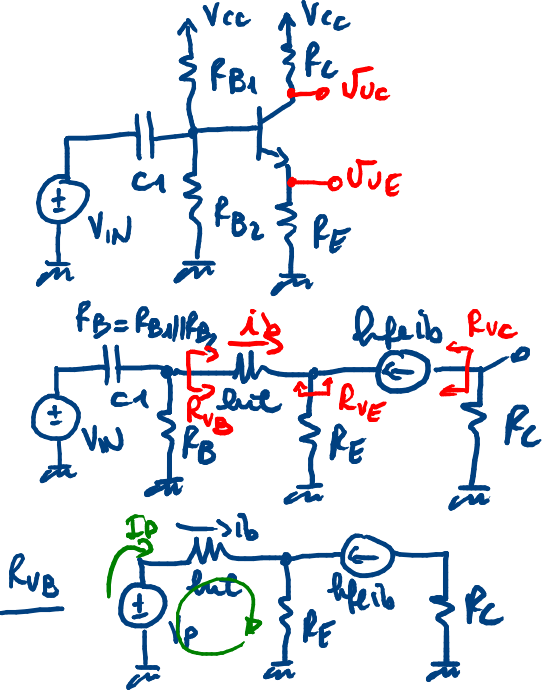


$$R_{vB} = \frac{V_P}{I_P} \quad I_P = i_b$$

$$V_P = h_{ie} i_b + R_E (h_{fe} + 1) i_b$$
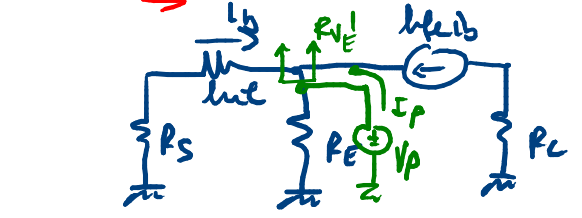
$$V_P = [h_{ie} + R_E (h_{fe} + 1)] I_P \Rightarrow R_{vB} = \frac{V_P}{I_P} = h_{ie} + R_E (h_{fe} + 1)$$


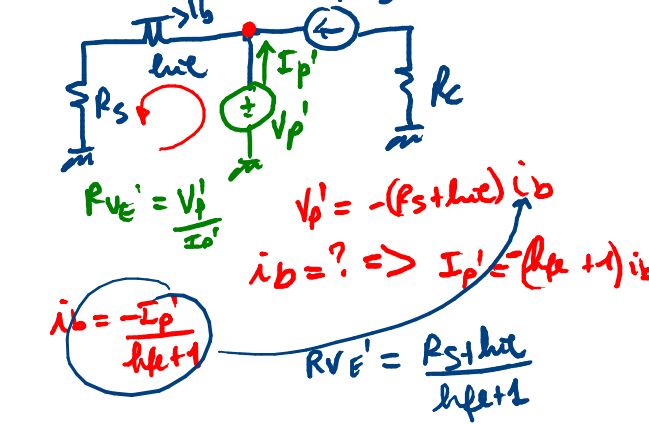
$$R_{vE} = \frac{V_P}{I_P} = R_E \parallel R_{vE}'$$




$$V_P' = -(R_S + h_{ie}) i_b$$

$$i_b = ? \Rightarrow I_P' = -(h_{fe} + 1) i_b$$

$$i_b = \frac{-I_P'}{h_{fe} + 1}$$
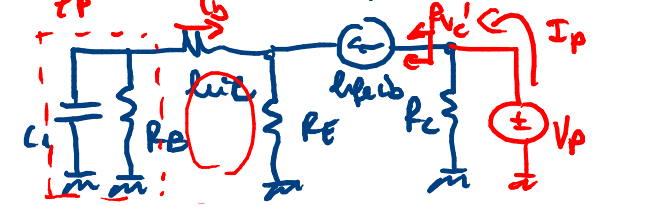
$$R_{vE}' = \frac{V_P'}{I_P'} = \frac{R_S + h_{ie}}{h_{fe} + 1}$$




$$R_{vC} = R_C \parallel R_{vC}' \quad R_{vC}' \rightarrow +\infty$$

$$R_{vC}' \Rightarrow (Z_p + h_{ie}) i_b + R_E (h_{fe} + 1) i_b = 0$$




$$I_P' = h_{fe} i_b \Rightarrow R_{vC}' \rightarrow +\infty$$

$$R_{vC} = R_C$$

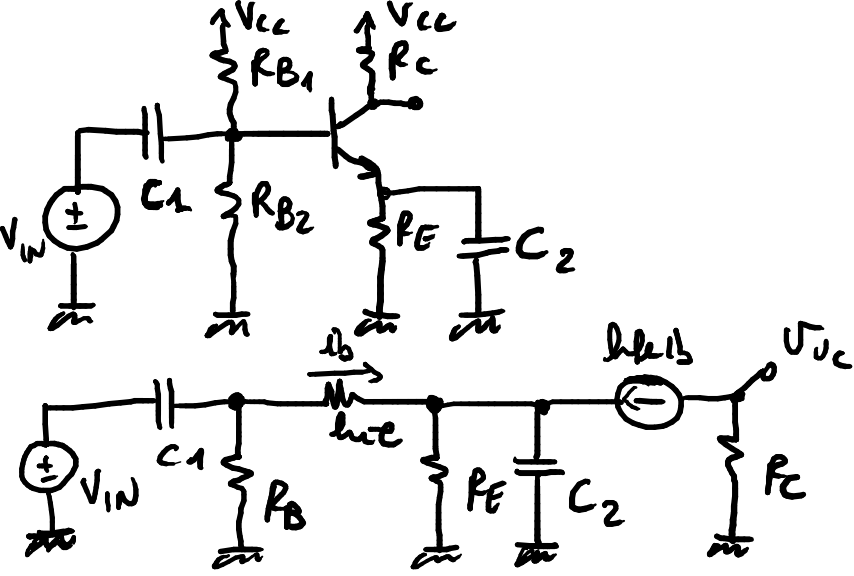

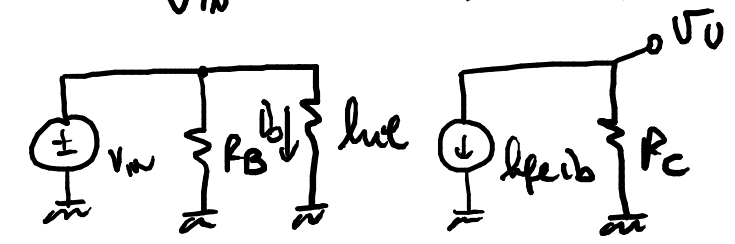
$$A_V(s) = \frac{V_{Uc}}{V_{IN}} = \frac{A_{V0}S(S+\omega_0)}{(S+\omega_{p1})(S+\omega_{p2})}$$




$$V_U = -h_{fe}i_b R_C \quad i_b = \frac{V_{IN}}{h_{ie}}$$
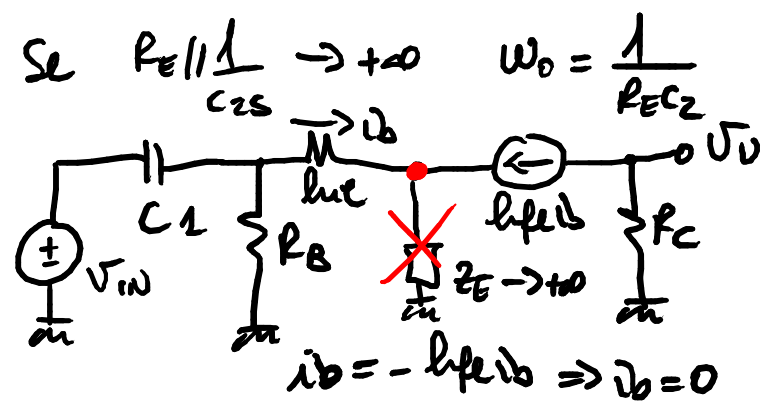
$$\frac{V_U}{V_{IN}} = A_{V0} = -\frac{h_{fe} R_C}{h_{ie}}$$



$$V_U = -R_C h_{fe} i_b \Rightarrow V_U(\omega_0 = \frac{1}{R_E C_2}) \rightarrow 0$$

ω_0 é uma zero

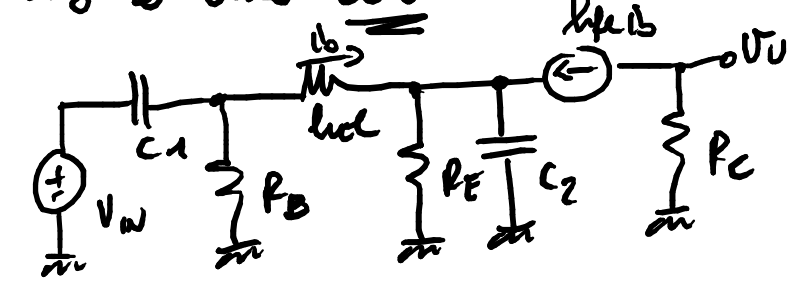


$$\omega_{p2} \gg \omega_{p1}$$


$$\omega_{p1} = \frac{1}{C_1 h_{ie}^0} \quad \omega_{p2} = \frac{1}{C_2 R_{V_{C2}}}$$

$$R_{V_{C1}} = R_B \parallel [h_{ie} + R_E(h_{fe} + 1)]$$
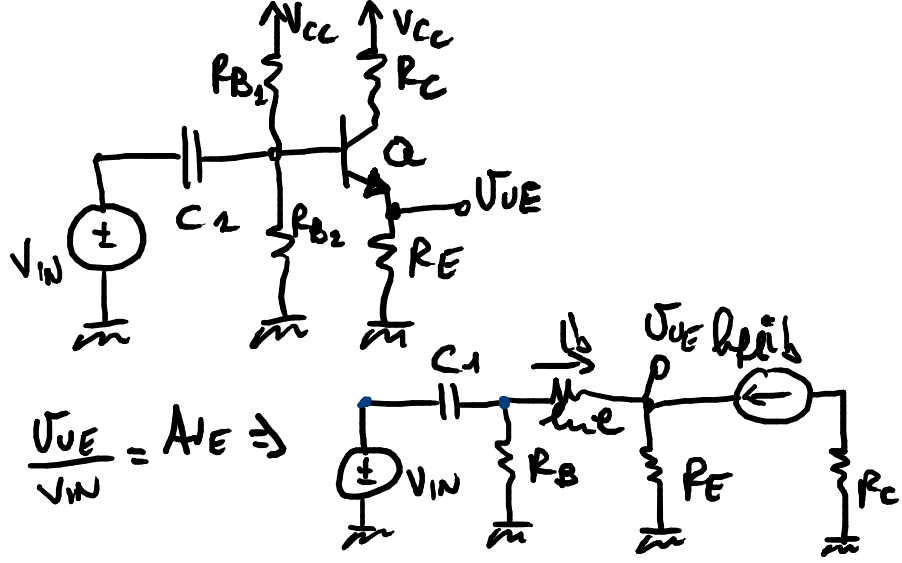
$$R_{V_{C2}}^0 = R_E \parallel \left[\frac{h_{ie}}{h_{fe} + 1} \right]$$


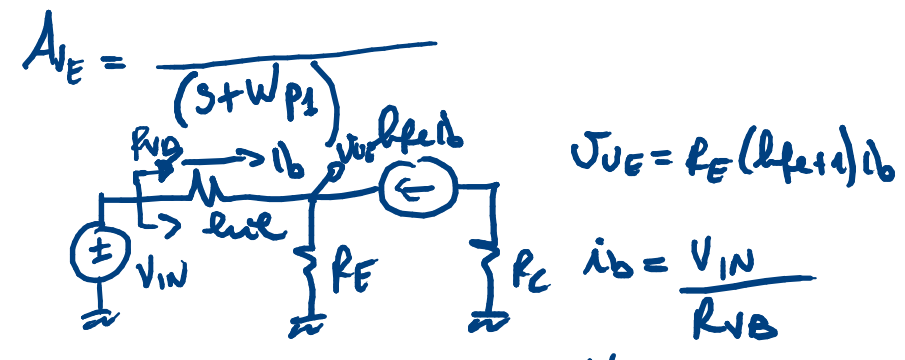
$$\frac{V_{UE}}{V_{IN}} = A_{VE} \Rightarrow$$




$$V_{UE} = R_E (\beta + 1) i_b$$

$$i_b = \frac{V_{IN}}{R_{VB}}$$

$$A_{V\infty} = \frac{V_{UE}}{V_{IN}} = \frac{R_E (\beta + 1)}{R_{VB} + R_E (\beta + 1)}$$



$$R_E (\beta + 1) \gg R_{VB} \Rightarrow A_{V\infty} \rightarrow 1$$
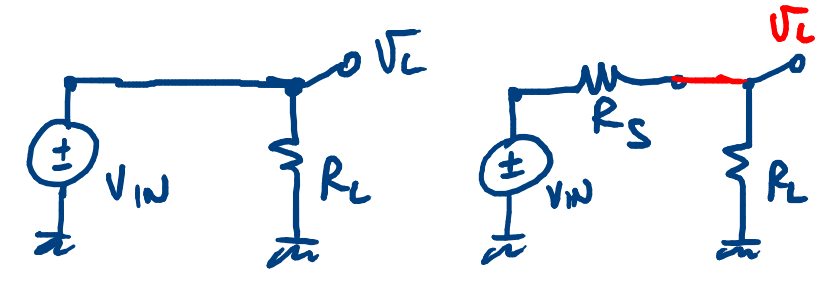
$$A_{VE} = \frac{A_{V\infty} S}{(S + \omega_p 1)}$$



$$V_L \neq V_{IN} \quad V_L = \frac{R_L}{R_L + R_S} V_{IN}$$
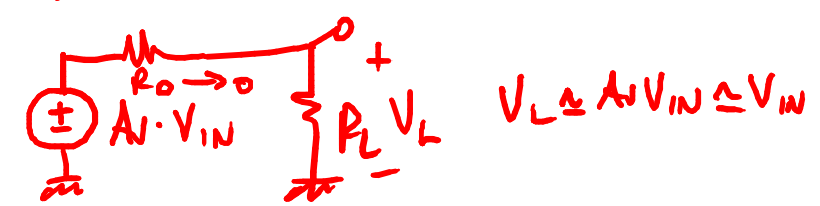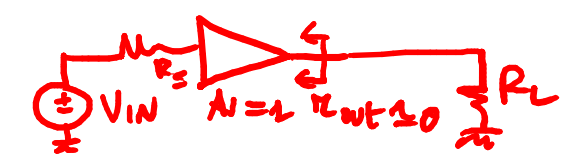
$$R_L \gg R_S \Rightarrow V_L \approx V_{IN}$$



$$V_L = \frac{R_L}{R_L + R_O} A V_{IN} \quad \left\{ \begin{array}{l} A \rightarrow \infty \\ R_O \rightarrow 0 \end{array} \right. \Rightarrow V_L \rightarrow V_{IN}$$