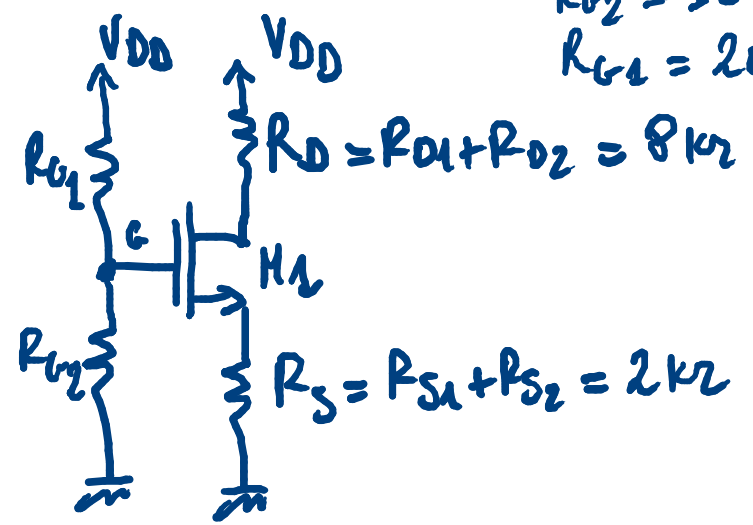


- $C_2 = 1 \text{ nF}$
- $C_3 = 1 \text{ nF}$
- $C_1 = 1 \mu\text{F}$
- $K = \mu\text{m Cox} \frac{W}{L} = 2 \text{ mA} / \sqrt{2}$
- $V_T = 1 \text{ V}$
- $V_{DD} = 12 \text{ V}$
- $R_{S1} = R_{S2} = 1 \text{ k}\Omega$
- $R_{D1} = R_{D2} = 4 \text{ k}\Omega$
- $R_{G2} = 10 \text{ k}\Omega$
- $R_{G1} = 20 \text{ k}\Omega$



$M_1$  i n s a t u r a t i o n  $\Rightarrow I_{D_S} = \frac{k}{2} (V_{G_S} - V_T)^2$

- $V_{G_S} \geq V_T$
- $V_{D_S} \geq V_{G_S} - V_T$

$$V_G = \frac{R_{G2}}{R_{G1} + R_{G2}} V_{DD}$$

$$V_G = V_{G_S} + R_S I_{D_S}$$

$$V_G = V_{G_S} + \frac{R_S k}{2} (V_{G_S} - V_T)^2$$

$$\frac{R_S k}{2} V_{G_S}^2 + (1 - R_S k) V_{G_S} + \frac{R_S k}{2} V_T^2 - V_G = 0$$


$$2 V_{G_S}^2 - 3 V_{G_S} - 2 = 0$$

$$V_{G_S} = \begin{cases} 2 \text{ V} \\ -0,5 \text{ V} \end{cases} \Rightarrow I_{D_S} = 1 \text{ mA}$$

$$V_{D_S} = V_D - V_S = \underbrace{V_{DD} - R_D I_{D_S}}_{V_D} - \underbrace{R_S I_{D_S}}_{V_S} = 2 \text{ V}$$

$$V_{D_S} = 4 \text{ V} \geq V_{G_S} - V_T = 1 \text{ V} \quad \text{OK saturation}$$


$$g_m = 2 \text{ mS}$$

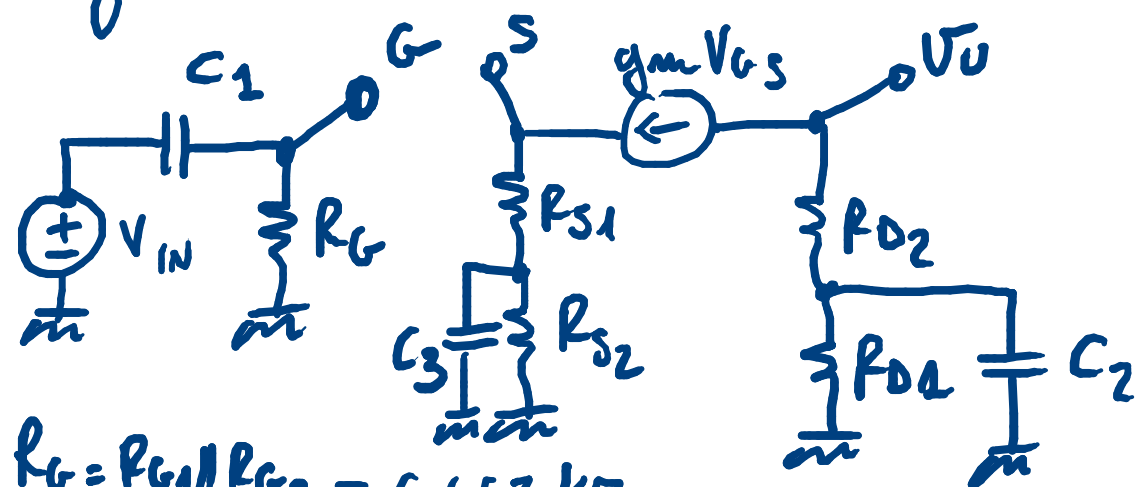

$$R_G = R_{G1} \parallel R_{G2} = 6,667 \text{ k}\Omega$$

$$A_V(s) = \frac{V_O}{V_{IN}} = \frac{A_{V0} s (s + \omega_{01})(s + \omega_{02})}{(s + \omega_{p1})(s + \omega_{p2})(s + \omega_{p3})}$$

Set  $s \rightarrow +\infty$

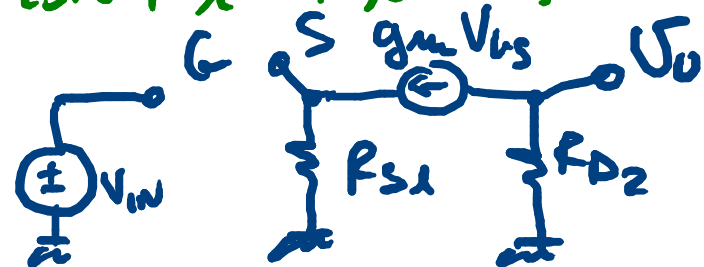

$$A_{V0} = \frac{-g_m R_{D2}}{1 + g_m R_{S1}} \rightarrow 0$$

$$\omega_{p1} = \frac{1}{R_{G1} C_1} = \frac{1}{C_1 R_G}$$

$$\omega_{p2} = \frac{1}{R_{Vc2} C_2} = \frac{1}{C_2 R_{D2}}$$

$$R_{Vc2} = R_{D1} \parallel [R_{D2} + R_{V_{DRAIN}}] \quad R_{V_{DRAIN}} \rightarrow +\infty$$

e quindi  $R_{Vc2} = R_{D1}$


$$\omega_{p3} = \frac{1}{C_3 R_{Vc3}} \quad R_{Vc3} = R_{S2} \parallel [R_{S1} + R_{V_{SOURCE}}]$$

$$R_{V_{SOURCE}} = \frac{1}{g_m}$$

$$R_{Vc3} = R_{S2} \parallel \left[ R_{S1} + \frac{1}{g_m} \right]$$

$$\omega_{01} = \frac{1}{C_3 R_{S2}}$$


$\rightarrow$

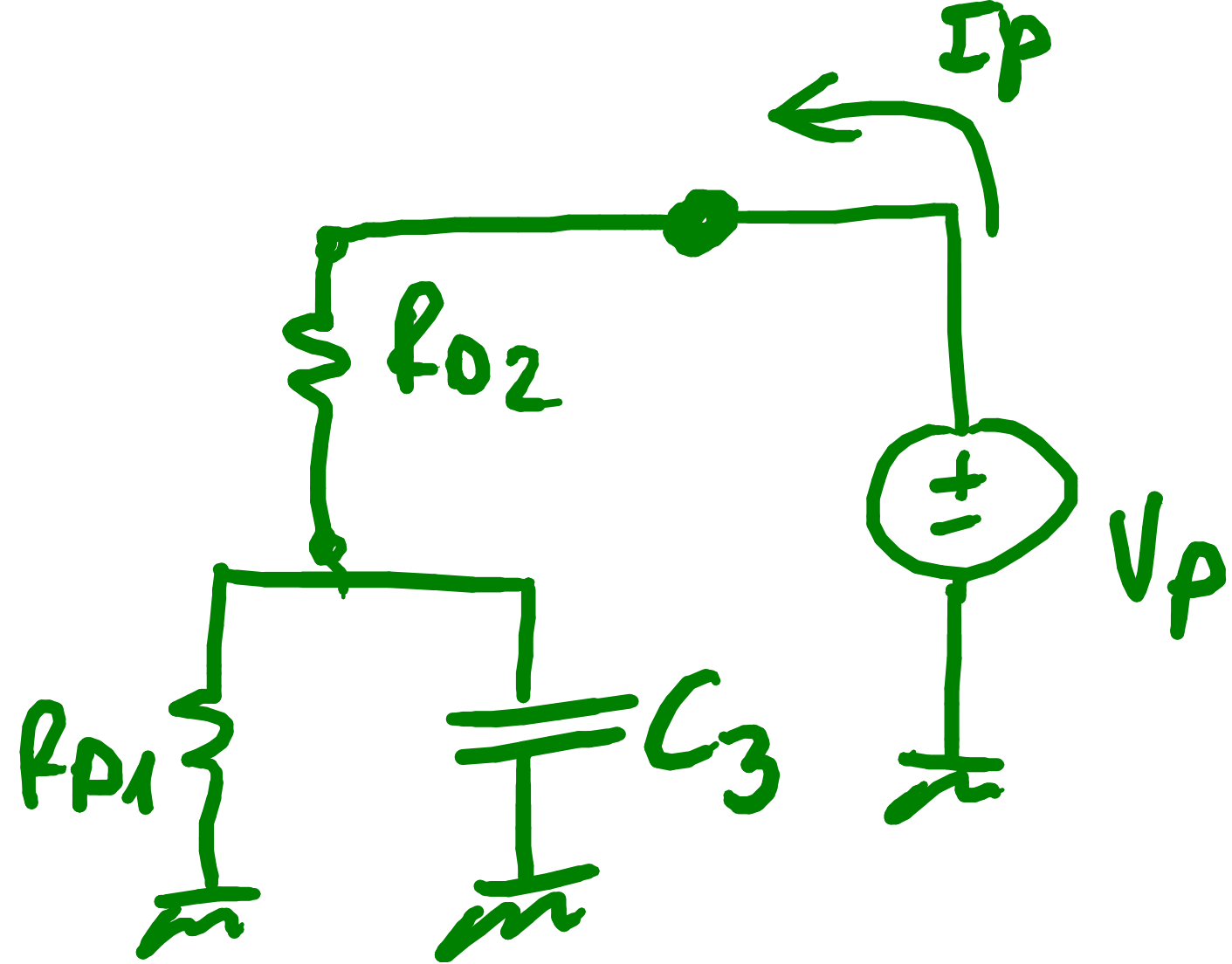

$$\frac{V_p}{I_p} = Z_{\text{ant}} = R_{02} + R_{01} \parallel \frac{1}{C_3 s} = 0$$



$$Z_{\text{out}} = \frac{V_p}{I_p}$$

$$Y_{\text{out}} = \frac{I_p}{V_p}$$

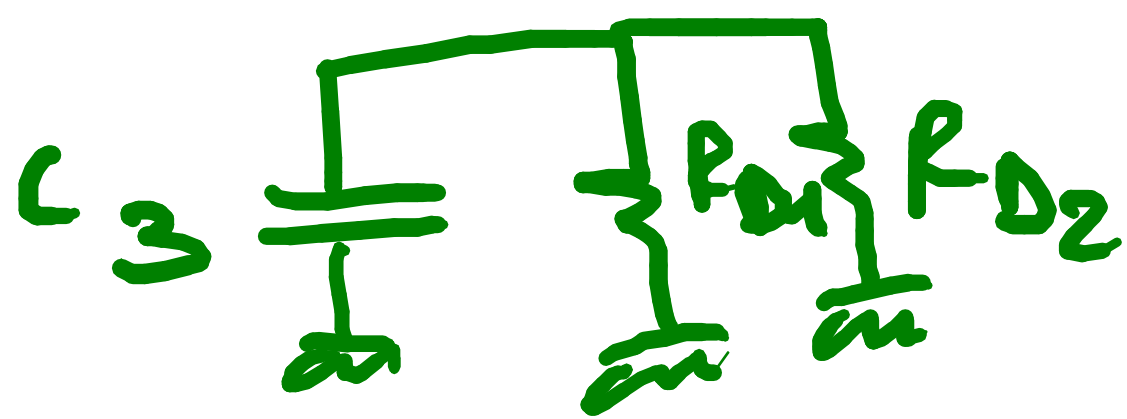

$$\omega_p = \frac{1}{C_3 R_{01} R_{02}} = \frac{1}{C_3 R_{01} R_{02}}$$

$$\omega_{02} = \omega_p$$

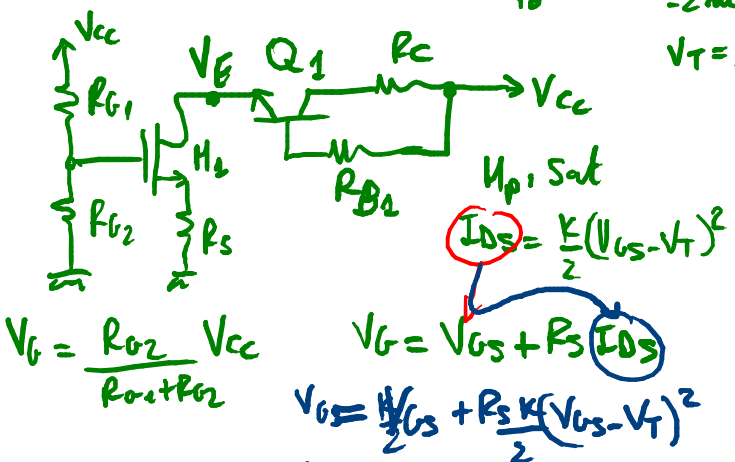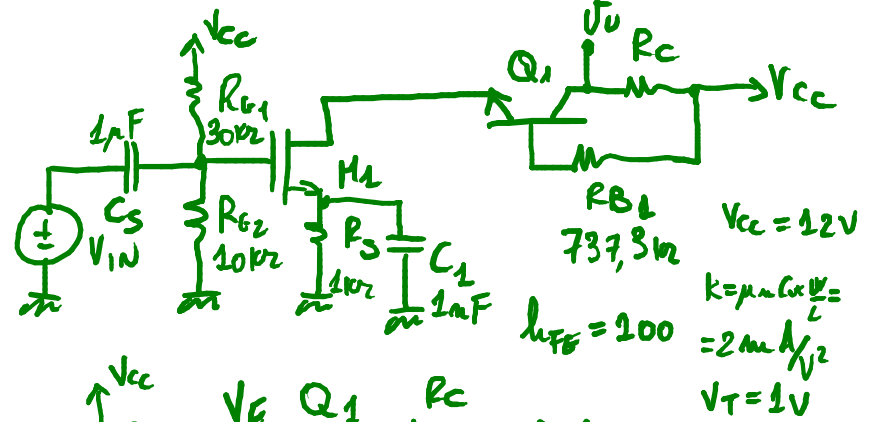

$$V_G = \frac{R_{G2}}{R_{G1} + R_{G2}} V_{CC}$$

$$V_G = V_{GS} + R_S I_{DS}$$

$$V_{GS} = \frac{1}{2} (V_{GS} + R_S K (V_{GS} - V_T)^2)$$

$$V_{GS} = \begin{cases} \frac{2V}{3} \\ -1V \end{cases} \quad V_{GS} \geq V_T \Rightarrow I_{DS} = 1mA$$

$$I_{DS} = I_E = (h_{FE} + 1) I_B \quad I_B = \frac{I_{DS}}{h_{FE} + 1} = 9,904 \mu A$$

$$I_C = h_{FE} I_B = 990,1 \mu A$$


$$V_E = V_D = V_{CC} - R_{B1} I_B - V_{BEON} = 4V$$

$$V_{DS} = V_D - V_S = 3V \geq V_{GS} - V_T = 1V \quad \text{OK sat. H}_1$$

$$V_{CE} \geq V_{CEsat} = 0,1V$$

$$V_C - V_E = V_{CC} - R_C I_C - V_E = 3,05V \geq V_{CEsat}$$

OK Zona Attiva  
Diretta per Q1

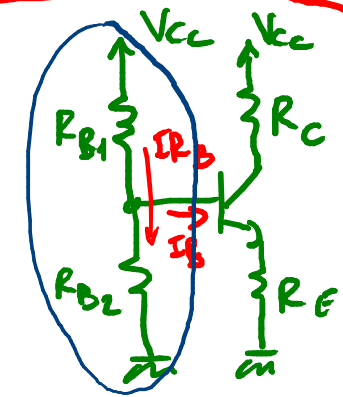

$h_{FE}$  Nota

Se  $I_{PB} \gg I_B$  Hp. PP

$$V_B = \frac{R_{B2}}{R_{B1} + R_{B2}} V_{CC}$$


$$I_{PB} = \frac{V_{CC}}{R_{B1} + R_{B2}}$$

$$R_{th} = R_{B1} \parallel R_{B2}$$

$$V_{th} = \frac{R_{B2}}{R_{B1} + R_{B2}} V_{CC}$$

$$V_{th} = R_{th} I_B + V_{BEON} + R_E (h_{FE} + 1) I_B$$
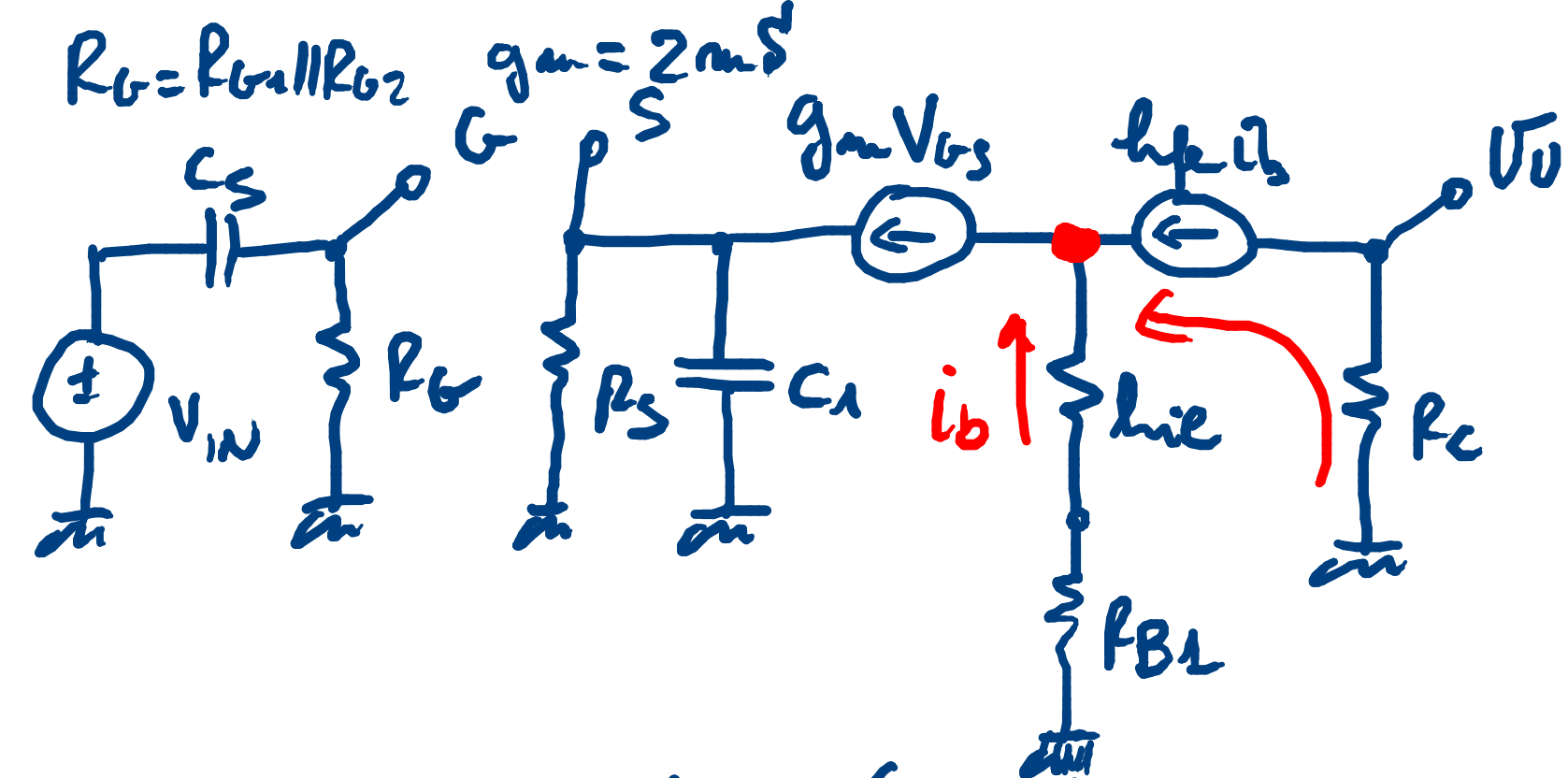
$$\frac{V_{th} - V_{BEON}}{R_{th} + R_E (h_{FE} + 1)} = I_B$$



$$A_U(s) = \frac{V_U(s)}{V_{IN}(s)} = \frac{A_{U0} S(s + \omega_0)}{(s + \omega_{p1})(s + \omega_{p2})}$$

for  $s \rightarrow +\infty$       $V_U = -R_C h_{fe} i_b$

$V_G = V_{IN} \wedge V_S = 0 \Rightarrow V_{GS} = V_{IN}$

$g_m V_{GS} = (h_{fe} + 1) i_b \Rightarrow i_b = \frac{g_m V_{GS}}{h_{fe} + 1}$

$V_U = - \frac{R_C h_{fe} g_m V_{IN}}{h_{fe} + 1}$


$\underbrace{\hspace{10em}}_{h_{fe} + 1}$

$A_{U0} = -9,967$

$\omega_0 = \frac{1}{C_1 R_S} = 1 \text{ Mrad/s}$


$\omega_{p1} = \frac{1}{C_S R_G} = 133,3 \text{ rad/s}$

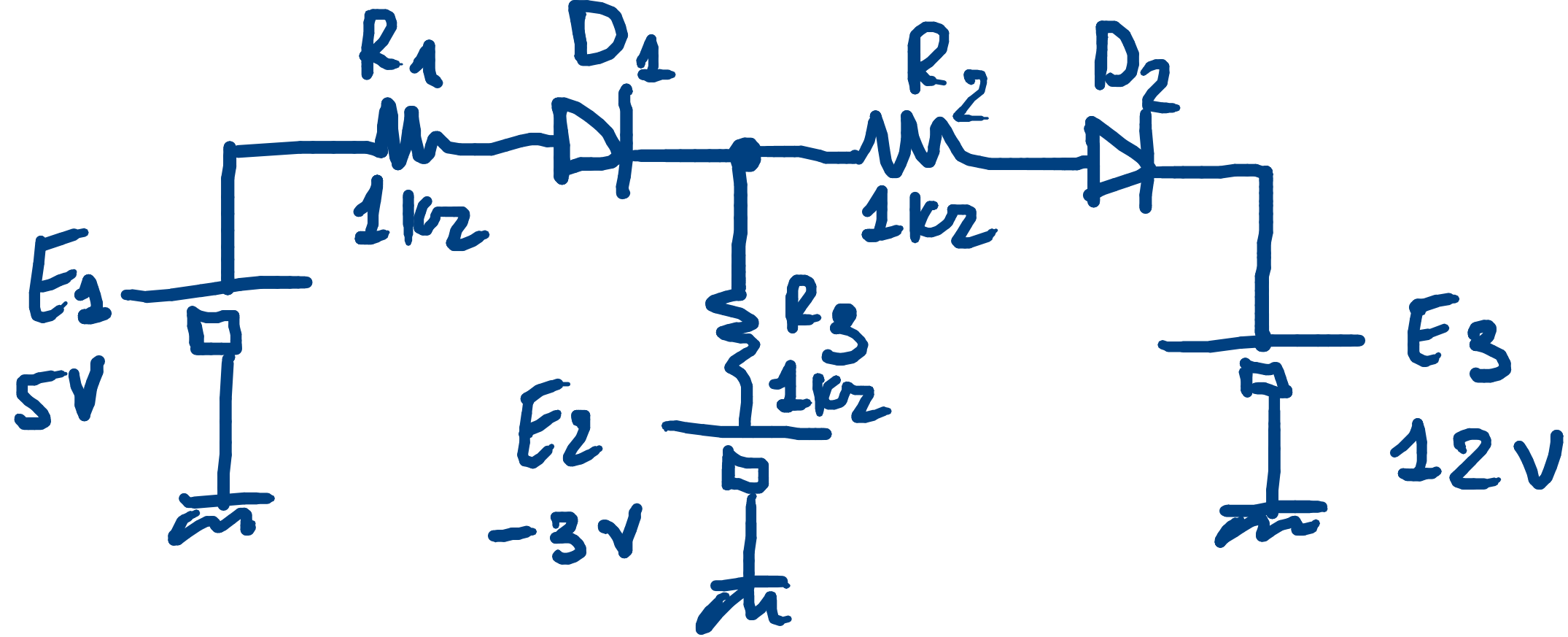$\omega_{p2} = \frac{1}{C_1 R_{V_S}} = 3 \text{ Mrad/s}$       $R_{V_S} = R_S \parallel \frac{1}{g_m}$



$D_2$ : OFF

$D_1$ : ON

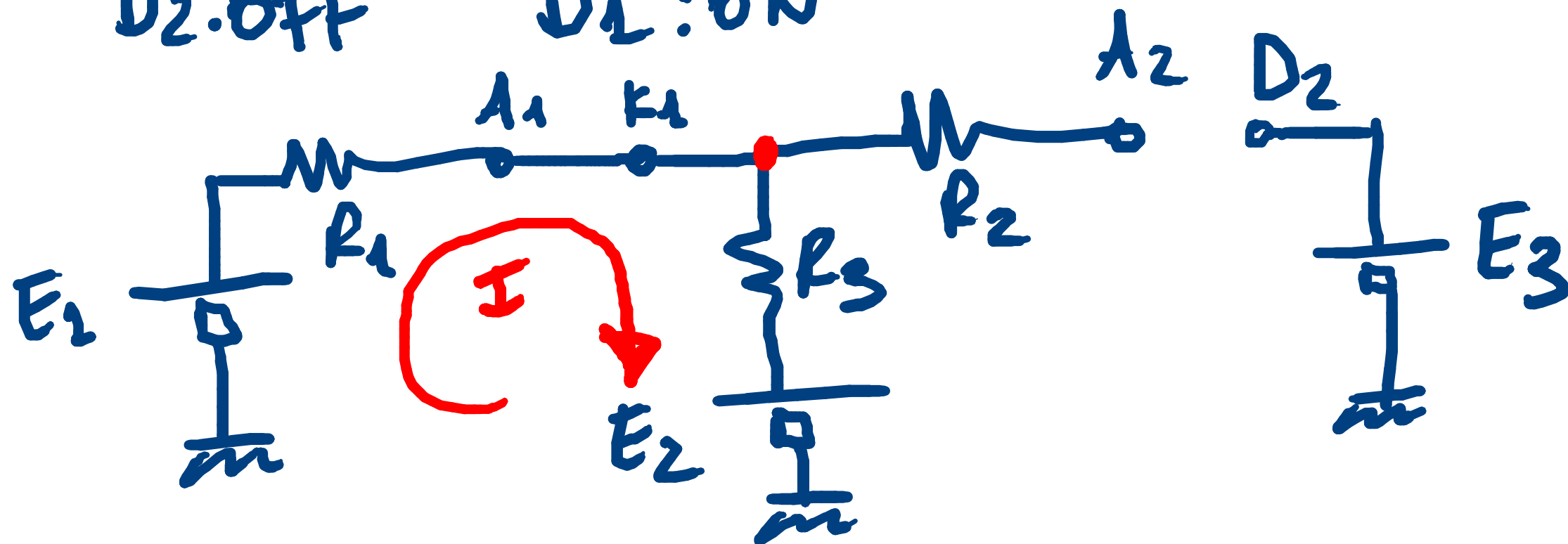

$$I = \frac{E_1 - E_2}{R_1 + R_2} = 4 \mu A$$

$$V_{A_2 D_2} < 0$$

$$V_{D_2} = 12V$$

$$V_{A_2} = E_2 + R_3 I = 1V$$

$$V_{A_2 D_2} = -11V$$